

Fundamentals of Electronic Circuits and Systems I

Resistive Circuits

Milin Zhang



Dept of EE, Tsinghua University




Outlines

- Linear resistor & Ohm's law
- Power & energy
- KVL/KCL
- Equivalent circuit

Review: a simple circuit

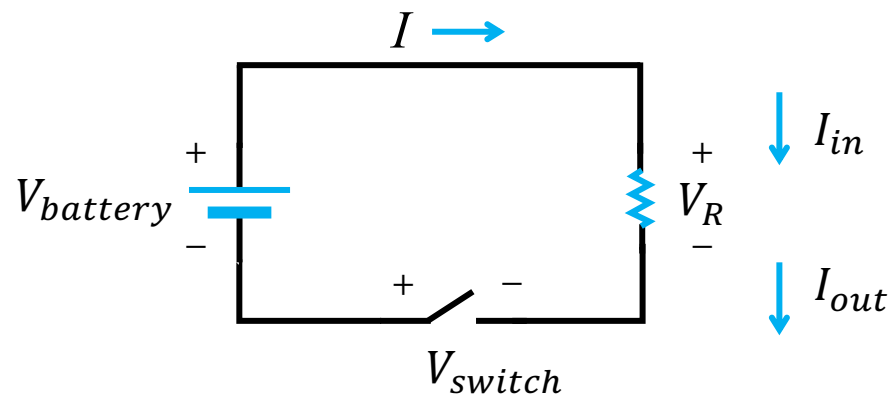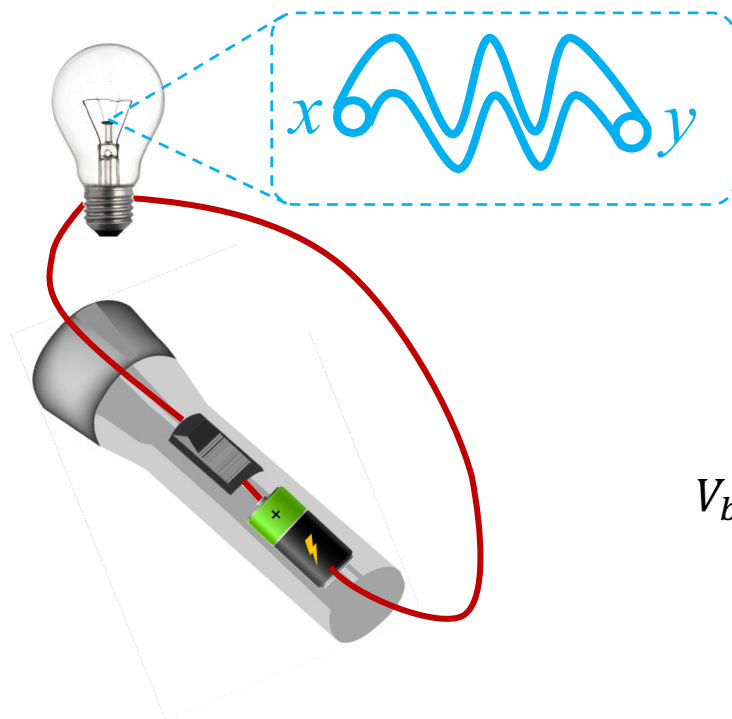

Resistance & Conductance

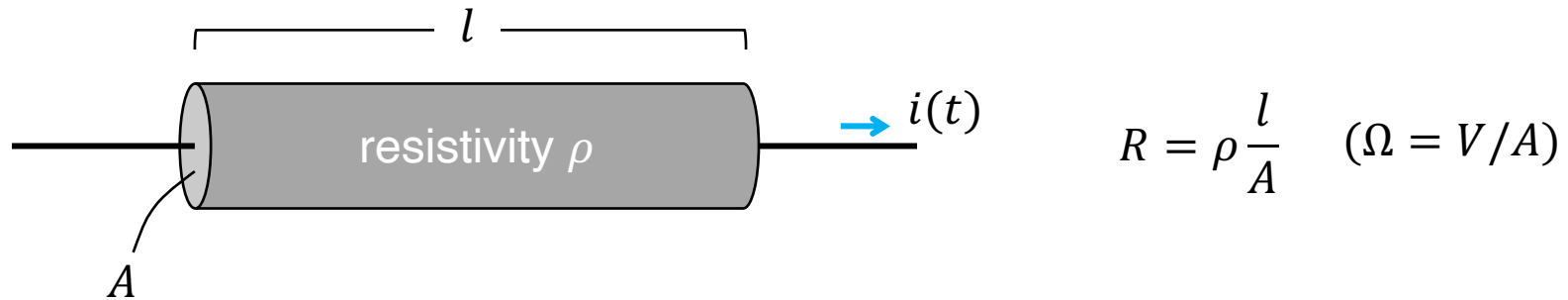

Resistance, R , represents the ability to resist flow of electric current

Conductance, $G = \frac{1}{R}$ ($S = A/V$)

* Resistivity of some common materials

Graphene	$1 \times 10^{-8} \Omega \cdot m$	Aluminum	$2.82 \times 10^{-8} \Omega \cdot m$
Silver	$1.59 \times 10^{-8} \Omega \cdot m$	Iron	$9.71 \times 10^{-8} \Omega \cdot m$
Copper	$1.68 \times 10^{-8} \Omega \cdot m$	Platinum	$1.06 \times 10^{-7} \Omega \cdot m$
Gold	$2.44 \times 10^{-8} \Omega \cdot m$	Titanium	$4.20 \times 10^{-7} \Omega \cdot m$

What is a resistor?

Resistors are passive electrical components that reduce the flow of electrical current in a circuit.



Axial resistor



Surface Mount
Devices (SMD)
resistor



Metal Electrode
Leadless Face
(MELF) resistor

Resistor properties

- **Resistance**

- represents the ability to resist flow of electric current

- **Resistor noise**

- Thermal noise: main contributor to resistor noise
- Current noise: declines when frequency is increased


- **Temperature coefficient of resistance (TCR)**

- Relationship between resistance and temperature
- Measured in $ppm/^\circ C$


- **Power rating**

- Maximum energy a resistor can dissipate without damaging or altering the properties

Color code for axial resistors


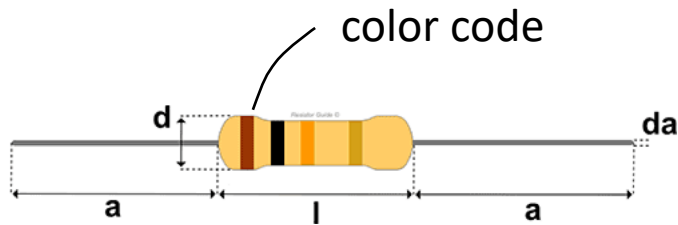


d	l	power
1.8 ± 0.3	3.0 ± 0.3	1/8
2.5 ± 0.3	6.5 ± 0.5	1/4
3.2 ± 0.3	8.5 ± 0.5	1/2
5 ± 0.3	11 ± 1	1

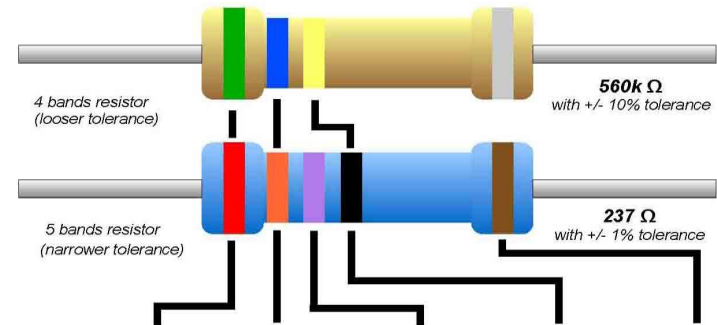

Color	1 st Band	2 nd Band	3 rd Band	Multiplier	Tolerance
Black	0	0	0	x 1 Ω	
Brown	1	1	1	x 10 Ω	+/- 1%
Red	2	2	2	x 100 Ω	+/- 2%
Orange	3	3	3	x 1K Ω	
Yellow	4	4	4	x 10K Ω	
Green	5	5	5	x 100K Ω	+/- 5%
Blue	6	6	6	x 1M Ω	+/- .25%
Violet	7	7	7	x 10M Ω	+/- .1%
Grey	8	8	8		+/- .05%
White	9	9	9		
Gold				x .1 Ω	+/- 5%
Silver				x .01 Ω	+/- 10%

SMD resistors

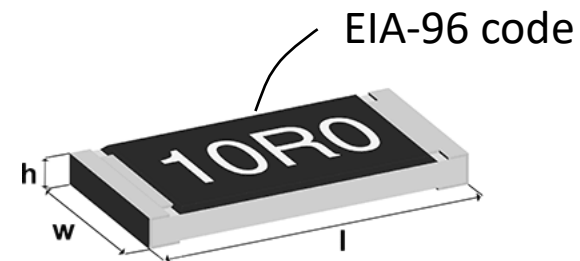
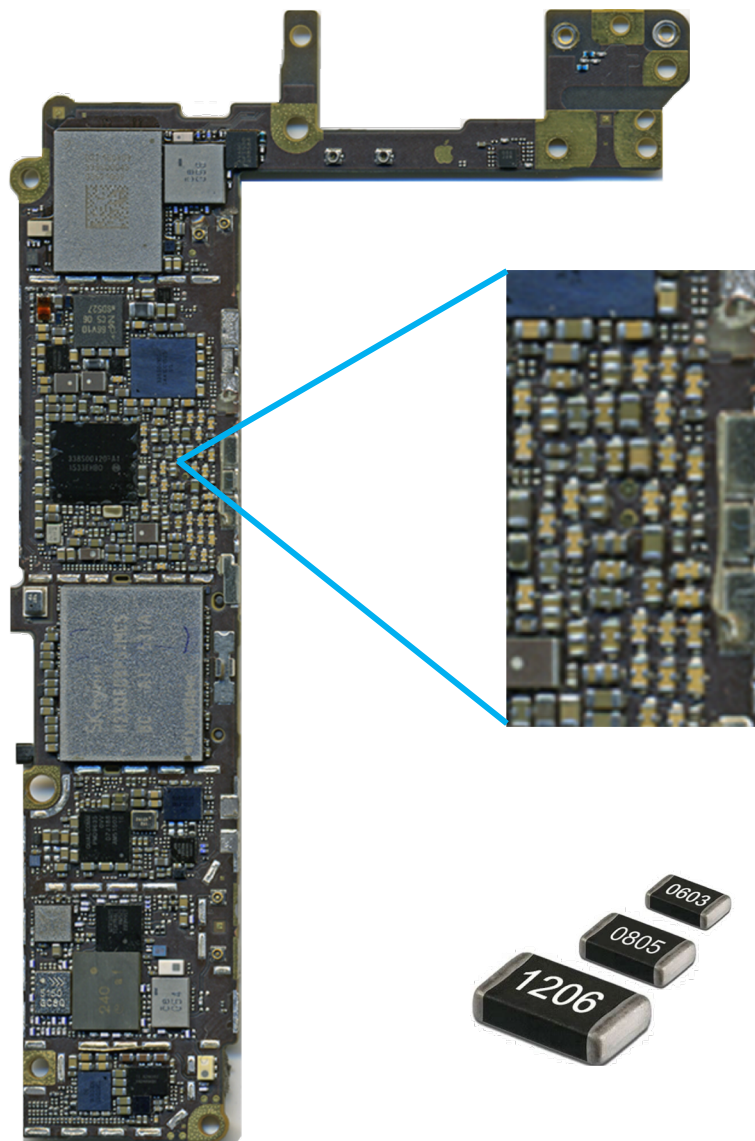


Size code	Size / mils	power
0201	20 x 10	1/20
0402	40 x 20	1/16
0603	60 x 30	1/10
0805	80 x 50	1/8
1206	120 x 60	1/4
2010	200 x 100	3/4
2512	250 x 120	1

SMD = Surface mounted device

“Resistors” are useful



Force sensitive resistor

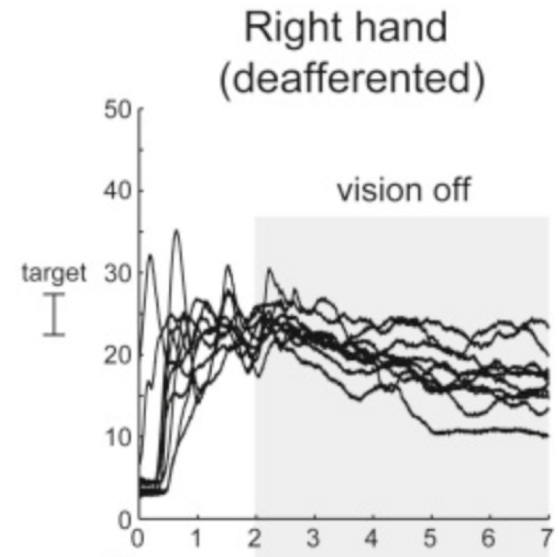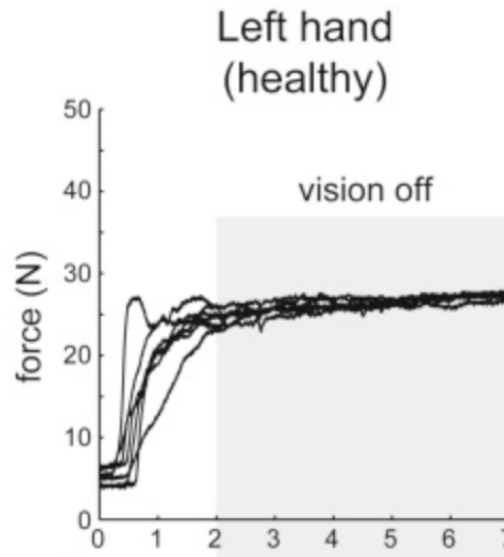

[Cortex 2016]

“Resistors” are useful

Photo resistor

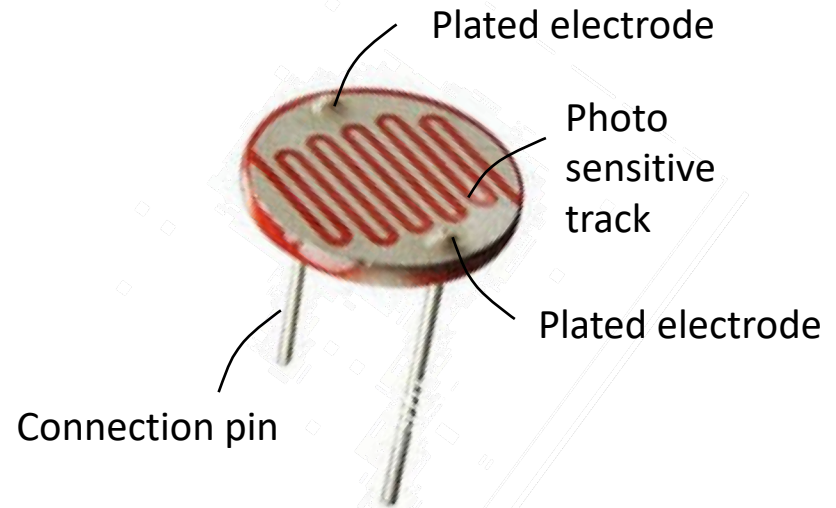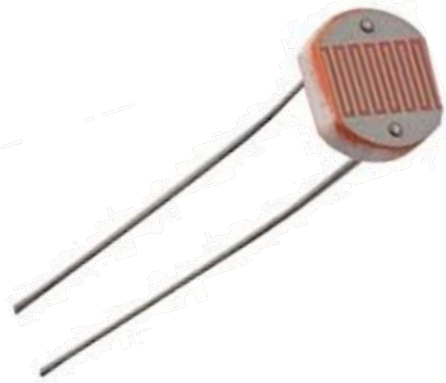

Symbol



- Light dependent resistor (LDR)
- Sensitivity varies with the light wavelength

“Resistors” are useful

Thermistor



- Thermistor is temperature sensitive resistor
- Positive temperature coefficient (PTC)
thermistor : resistance increases as the temperature increases
- Negative temperature coefficient (NTC)
thermistor : resistance decreases as the temperature increases

Symbol

NTC



PTC




Outlines

- Linear resistor & Ohm's law
 - Resistance & conductance
 - **Ohm's law**


Ohm's Law

Ohm's law states that the voltage across a resistance is directly proportional to the current flowing through it.

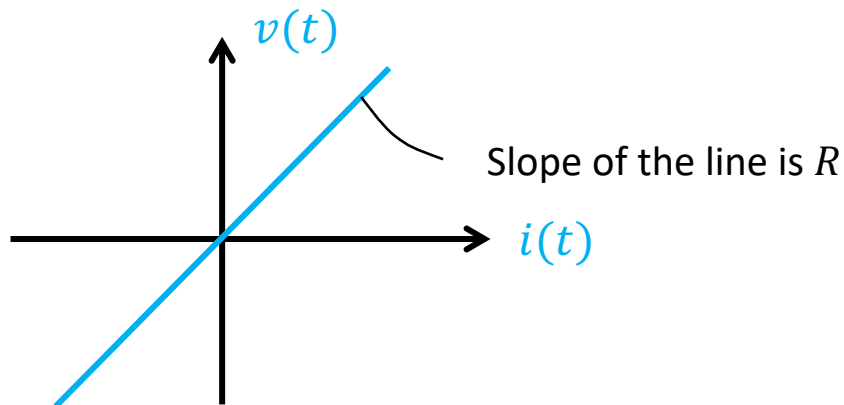Mathematical relationship of Ohm's law: $v(t) = Ri(t)$



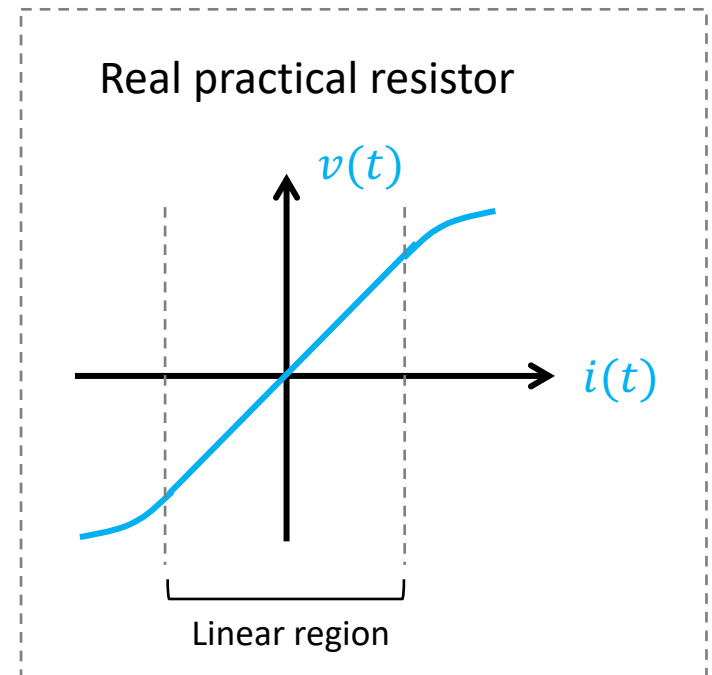- The resistance measured in ohm (Ω)
- The resistance is the constant of proportionality between the voltage and the current




Open Circuit & Short Circuit

▪ **Open circuit:** no path for current flow

➡ $R = \infty$

▪ **Short circuit:** no voltage drop

➡ $R = 0$

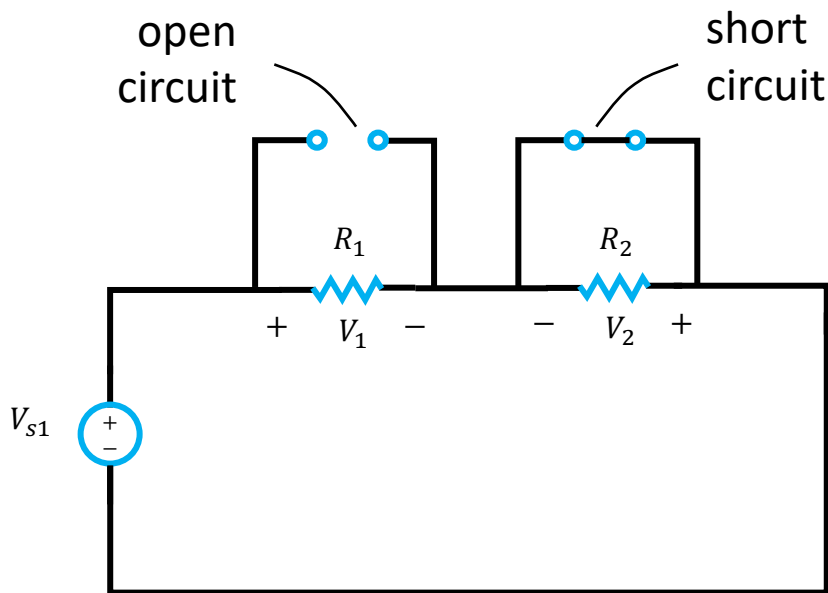

open switch = open circuit



closed switch = short circuit




*Note:

- open/short circuit is the basis for modeling a switch behavior.
- No perfect switches

Example 1

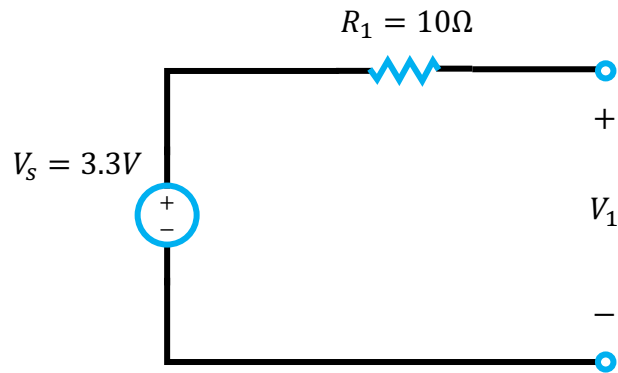
QUESTION: Find the voltage at V_1 in the circuit below:



ANSWER: $V_1 = 3.3V$

? How much current flows through R_1

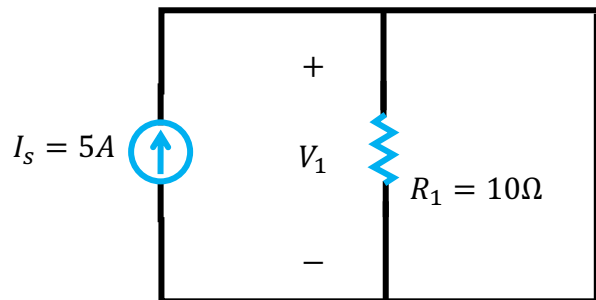QUESTION: Find the voltage across the resistor V_1 in the circuit below:



ANSWER: $V_1 = 0V$


? What is the voltage difference across I_s

Outlines

- Linear resistor & Ohm's law
 - Resistance & conductance
 - Ohm's law
 - Open circuit & short circuit
- **Power & energy**

Power

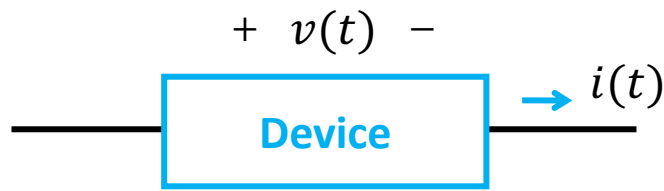The **POWER** delivered to or supplied by a device is the product of the voltage and the current




- Instantaneous power

$$p(t) = v(t)i(t)$$

- Average power
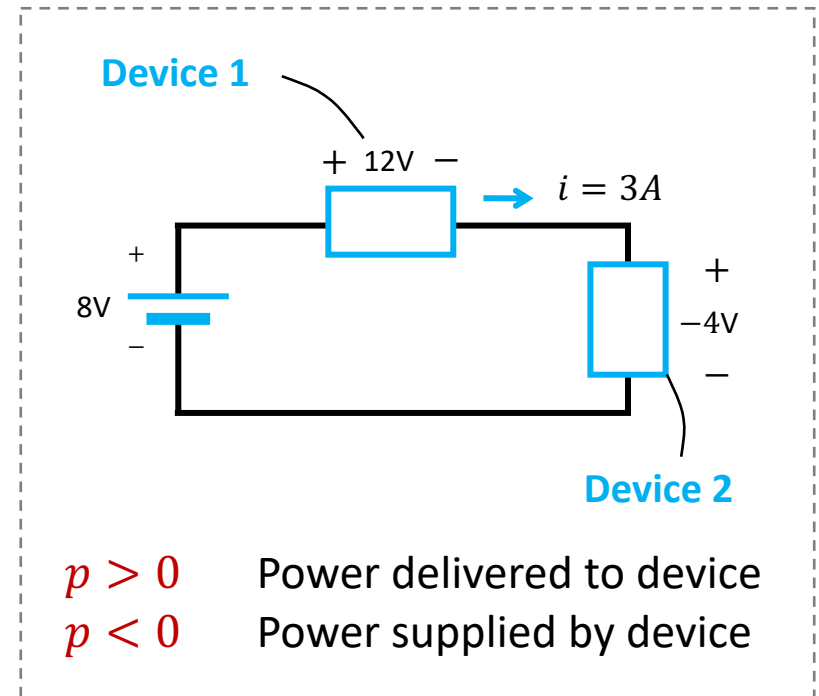
$$\bar{P} = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$



*Note: The average value of any periodic waveform can be computed by integrating the function over a complete period and dividing this result by the period

Power in dB

Decibel (dB) is a unitless measurement for expressing ratios

- For power $10 \log_{10} \frac{P}{1W} \rightarrow \text{dB}$

$$10 \log_{10} \frac{P}{1mW} \rightarrow \text{dBm}$$

- For voltage $20 \log_{10} \frac{v}{1V} \rightarrow \text{dBV}$

$$20 \log_{10} \frac{v}{1mV} \rightarrow \text{dBmV}$$

Example 2

QUESTION: Assume the load of a transceiver is $R_L = 50\Omega$. The voltage measured at the output point is V_o dBV. Find the output power in dBm

The output power

$$\begin{aligned} P_{out} &= \frac{V_{out}^2}{R_L} \\ &= 10 \log_{10} \frac{P_{out}}{1mW} \text{ dBm} \\ &= 10 \log_{10} \frac{V_{out}^2}{R_L} \frac{1}{1mW} \text{ dBm} \\ &= \left(10 \log_{10} \frac{1}{R_L \times 1mW} + 20 \log_{10} V_{out} \right) \text{ dBm} \\ &= \mathbf{(13 + V_o \text{ dBV}) \text{ dBm}} \end{aligned}$$

Energy & Effective I/V

If a constant amount of power P is delivered over an interval T the **ENERGY** w supplied is

$$w = \int_0^T p(t) dt$$

EFFECTIVE VALUE is found by first determining the **square of the current/voltage**, then computing the **average or mean value**


$$v_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt}$$

$$i_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

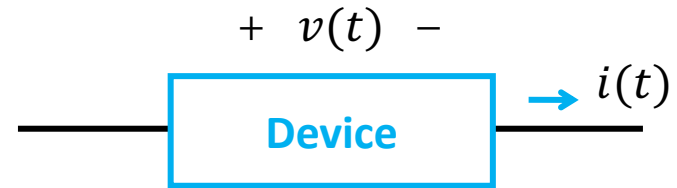Example 3

Given the voltage $v(t) = V_P \cos(\omega t + \varphi_V)$

Given the current $i(t) = I_P \cos(\omega t + \varphi_I)$




- Instantaneous power $p(t) = v(t)i(t) = V_P \cos(\omega t + \varphi_V) I_P \cos(\omega t + \varphi_I)$
$$= \frac{1}{2} V_P I_P \cos(\varphi_V - \varphi_I) + \frac{1}{2} V_P I_P \cos(2\omega t + \varphi_V + \varphi_I)$$
- Average power $\bar{P} = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$
$$= \frac{1}{T} \int_{t_0}^{t_0+T} \left(\frac{1}{2} V_P I_P \cos(\varphi_V - \varphi_I) + \frac{1}{2} V_P I_P \cos(2\omega t + \varphi_V + \varphi_I) \right) dt$$
$$= \frac{1}{2} V_P I_P \cos(\varphi_V - \varphi_I) = \frac{V_P}{\sqrt{2}} \frac{I_P}{\sqrt{2}} \cos(\varphi_V - \varphi_I)$$

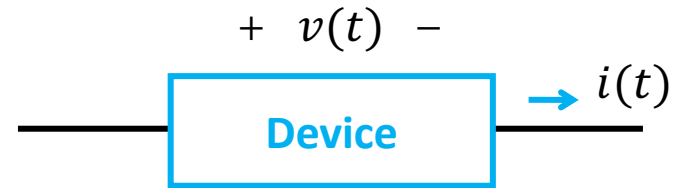Example 3

Given the voltage $v(t) = V_P \cos(\omega t + \varphi_V)$

Given the current $i(t) = I_P \cos(\omega t + \varphi_I)$




- Instantaneous power
$$p(t) = \frac{1}{2} V_P I_P \cos(\varphi_V - \varphi_I) + \frac{1}{2} V_P I_P \cos(2\omega t + \varphi_V + \varphi_I)$$

- Average power
$$\bar{P} = \frac{V_P}{\sqrt{2}} \frac{I_P}{\sqrt{2}} \cos(\varphi_V - \varphi_I) = v_{rms} i_{rms} \cos(\varphi_V - \varphi_I)$$

- Effective voltage
$$v_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} = \frac{V_P}{\sqrt{2}}$$

- Effective current
$$i_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt} = \frac{I_P}{\sqrt{2}}$$

Maximum Power Transfer

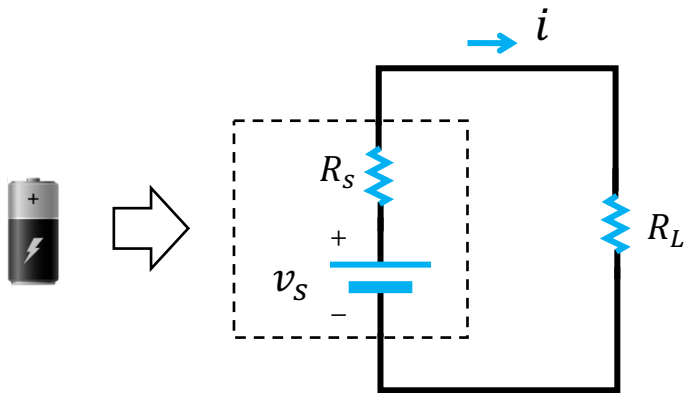

Practical voltage source

- Voltage of R_L

$$v_{R_L} = v_s - iR_s$$

- Power at the load R_L

$$P_L = v_{R_L} i = (v_s - iR_s) i = -R_s \left(i^2 - \frac{v_s}{R_s} i \right) = -R_s \left(i - \frac{1}{2} \frac{v_s}{R_s} \right)^2 + \frac{1}{4} \frac{v_s^2}{R_s}$$
$$\leq \frac{1}{4} \frac{v_{s,rms}^2}{R_s}$$

The maximum power being absorbed by the load

- When $R_s = R_L$ $P_L = P_{L,max} = \frac{1}{4} \frac{v_{s,rms}^2}{R_s}$

Outlines

- Linear resistor & Ohm's law
 - Resistance & conductance
 - Ohm's law
 - Open circuit & short circuit
- Power & energy
 - Definition of power
 - Power in dB
 - Definition of energy
 - Effective current/voltage
 - Maximum power transfer
- KVL/KCL

Review: Lumped Matter Discipline (LMD)

- The rate of change of magnetic flux linked with any portion of the circuit must be zero for all time.

$$\oint E \cdot dl = -\frac{\partial \Phi_B}{\partial t} = 0$$

- The rate of change of the charge at any node in the circuit must be zero for all time. A node is any point in the circuit at which two or more element terminals are connected using wires.

$$\int_{S_x} J \cdot dS - \int_{S_y} J \cdot dS = \frac{\partial q}{\partial t} = 0$$

- The signal timescales must be much larger than the propagation delay of electromagnetic waves through the circuit.

LMD:

The fundamental of circuit and system theory


Kirchhoff's Voltage Law (KVL)

- The rate of change of magnetic flux linked with any portion of the circuit must be zero for all time.

$$\oint E \cdot dl = -\frac{\partial \Phi_B}{\partial t} = 0 \quad \Rightarrow \quad \sum_{n=1}^N v_n = 0$$

KVL: Sum of voltages around a closed path is zero

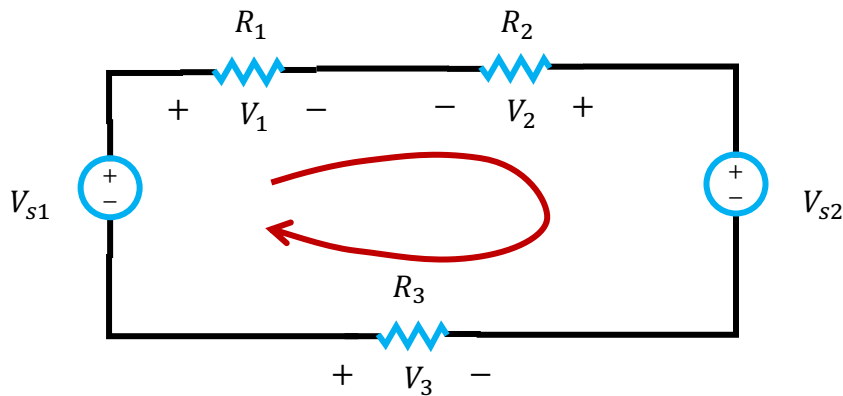Sum of voltage drops = Sum of voltage rises



* Note

- Add up the voltages in a systematic clockwise movement around the loop
- Assign a positive sign to the voltage across an element if the (+) side of that voltage is encountered first, and assign a negative sign if the (-) side is encountered first


$$V_{s1} - V_1 + V_2 - V_{s2} + V_3 = 0$$

Kirchhoff's Current Law (KCL)

- The rate of change of the charge at any node in the circuit must be zero for all time. A node is any point in the circuit at which two or more element terminals are connected using wires.

$$\int_{S_x} J \cdot dS - \int_{S_y} J \cdot dS = \frac{\partial q}{\partial t} = 0 \quad \Rightarrow \quad \sum_{n=1}^N i_n = 0$$

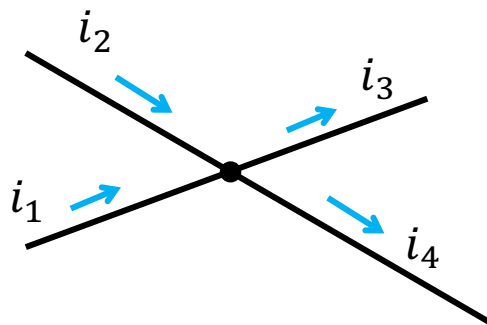KCL: Sum of currents entering a node is zero





$$i_1 + i_2 - i_3 - i_4 = 0$$

* Note: sign convention in Engineering

- Assign a positive sign to current entering a node
- Assign a negative sign to current entering a node

Example 4: power source connection

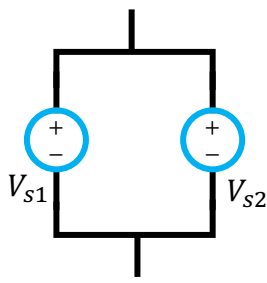
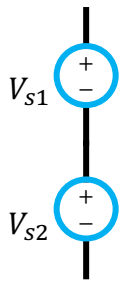
QUESTION: Find if the connection of the circuit is right or wrong



If $V_{s1} = V_{s2}$




If $V_{s1} \neq V_{s2}$

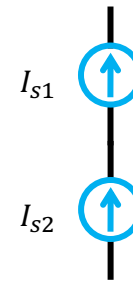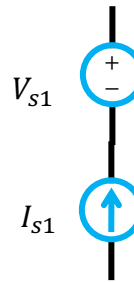

If $I_{s1} = I_{s2}$




If $I_{s1} \neq I_{s2}$

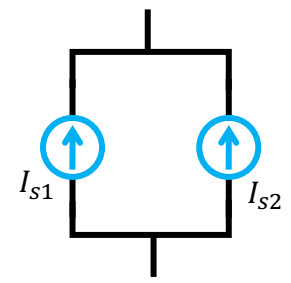

Example 5: Ballast resistor

QUESTION: Find if the resistance of R_1

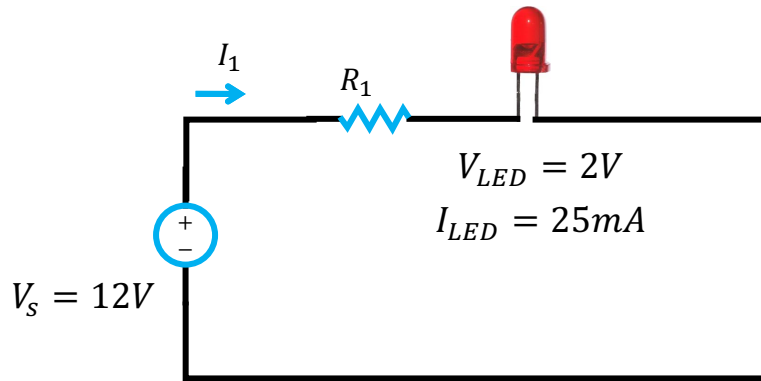

A ballast resistor is used to limit the current through a device, and to prevent that it burns

- According to KVL

$$V_S - V_{R_1} - V_{LED} = 0$$


$$\rightarrow V_{R_1} = 10V$$

- According to Ohm's law

$$R_1 = \frac{V_{R_1}}{I_{LED}} = 40\Omega$$

Example 6

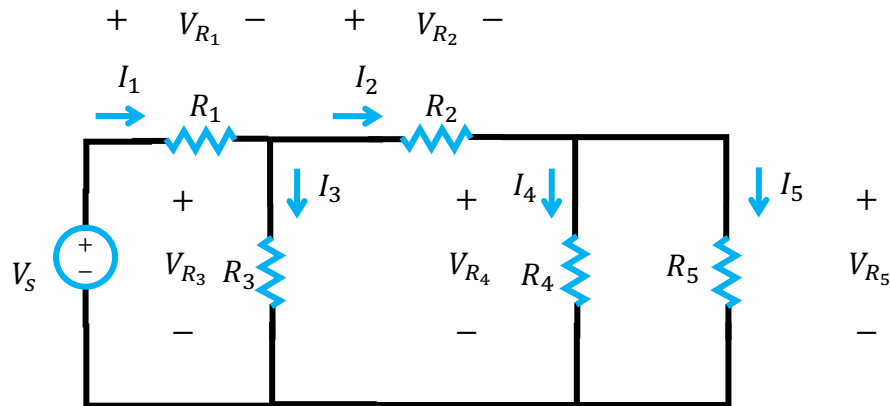QUESTION: Find the output current of the voltage source




Step 1 define i and v

Step 2 According to Ohm's law

$$\left\{ \begin{array}{l} V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \end{array} \right.$$

Example 6

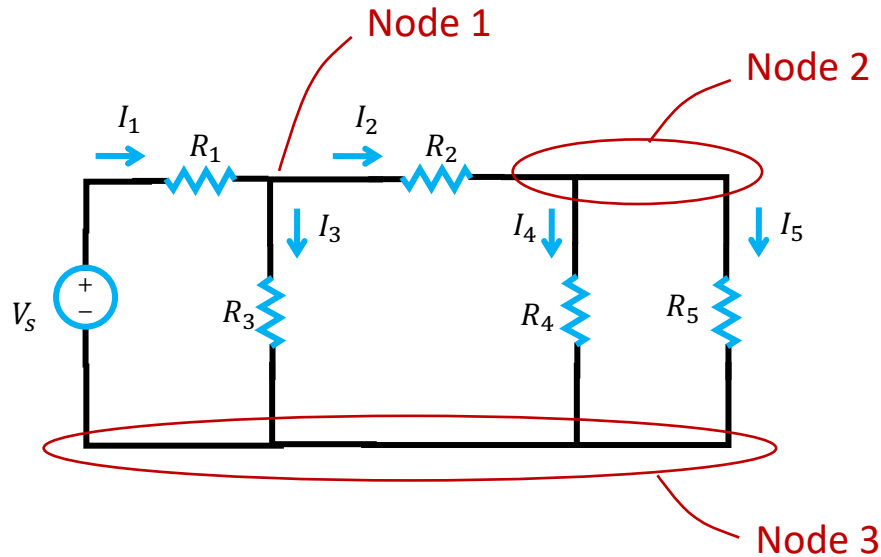QUESTION: Find the output current of the voltage source



Step1 define i and v

Step 2 According to Ohm's law

$$\left\{ \begin{array}{l} V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \end{array} \right.$$


Step 3 Check the nodes

- According to KCL

$$\left\{ \begin{array}{l} I_1 - I_2 - I_3 = 0 \\ I_2 - I_4 - I_5 = 0 \\ I_1 - I_3 - I_4 - I_5 = 0 \end{array} \right.$$

Example 6

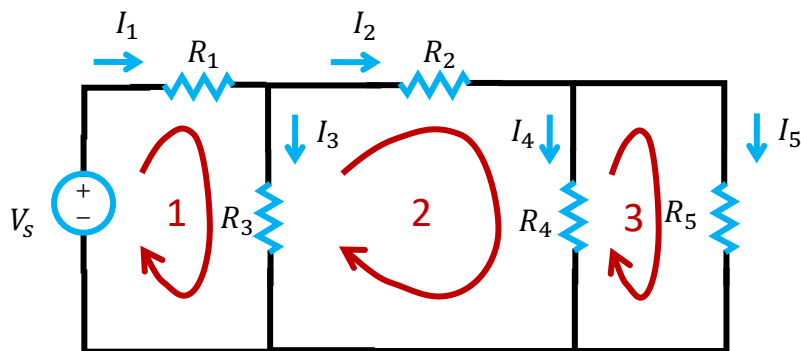QUESTION: Find the output current of the voltage source



Step 1 define i and v

Step 2 According to Ohm's law

$$\left\{ \begin{array}{l} V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \\ V_{R_1} = I_1 R_1 \end{array} \right.$$

Step 3 Check the nodes

Step 4 Check the loops

▪ According to KCL

$$\left\{ \begin{array}{l} I_1 - I_2 - I_3 = 0 \\ I_2 - I_4 - I_5 = 0 \\ I_1 - I_3 - I_4 - I_5 = 0 \end{array} \right.$$

▪ According to KVL

$$\left\{ \begin{array}{l} V_s - V_{R_1} - V_{R_3} = 0 \\ V_{R_3} - V_{R_2} - V_{R_4} = 0 \\ V_{R_4} - V_{R_5} = 0 \end{array} \right.$$


Example 6

$$\begin{bmatrix}
 1 & -1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & -1 & -1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 1 & 0 & 1 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & -1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & -1 \\
 R_s & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 \\
 0 & R_2 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\
 0 & 0 & R_3 & 0 & 0 & 0 & 0 & -1 & 0 & 0 \\
 0 & 0 & 0 & R_4 & 0 & 0 & 0 & 0 & -1 & 0 \\
 0 & 0 & 0 & 0 & R_L & 0 & 0 & 0 & 0 & -1
 \end{bmatrix}
 \begin{bmatrix}
 I_1 \\
 I_2 \\
 I_3 \\
 I_4 \\
 I_L \\
 V_{R_s} \\
 V_{R_2} \\
 V_{R_3} \\
 V_{R_4} \\
 V_{R_L}
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 1 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{bmatrix}
 V_s$$

Very friendly to numerical calculation !

Example 6

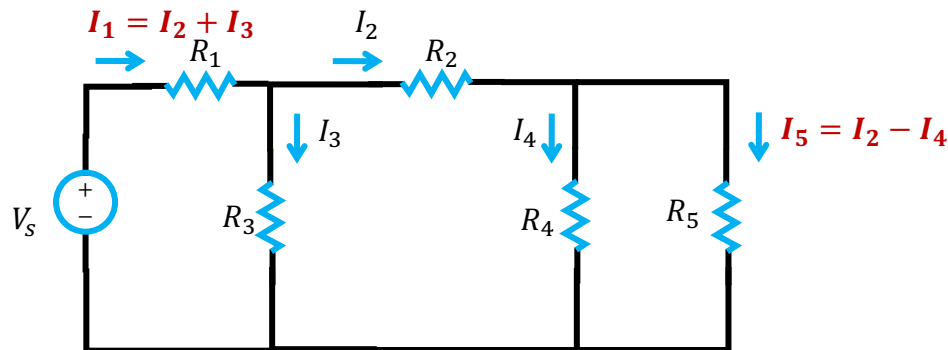QUESTION: Find the output current of the voltage source



■ According to KVL

$$\begin{cases} V_S - V_{R_1} - V_{R_3} = 0 \\ V_{R_3} - V_{R_2} - V_{R_4} = 0 \\ V_{R_4} - V_{R_5} = 0 \end{cases}$$




$$\begin{cases} V_S - (I_2 + I_3)R_1 - I_3R_3 = 0 \\ I_3R_3 - I_2R_2 - I_4R_4 = 0 \\ I_4R_4 - (I_2 - I_4)R_5 = 0 \end{cases}$$

$$\begin{bmatrix} R_1 & R_1 & R_3 \\ -R_2 & R_3 & -R_4 \\ -R_5 & 0 & R_4 + R_5 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} V_S \\ 0 \\ 0 \end{bmatrix}$$

3 equations in 3 unknowns

Example 7

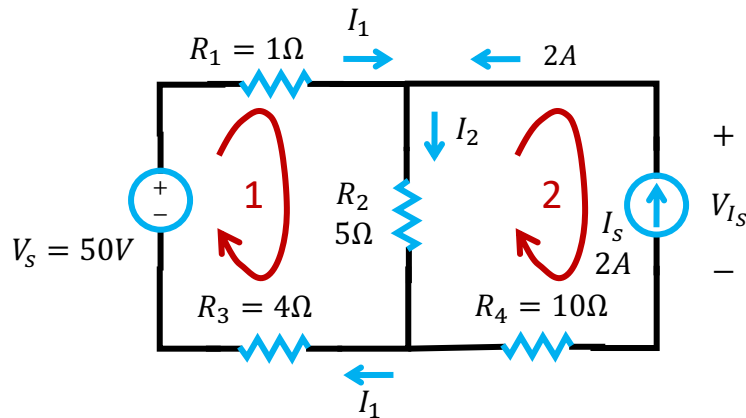QUESTION: Find the output current of the voltage source



$$\begin{cases} 50 - I_1 - 5I_2 - 4I_1 = 0 \\ -V_{I_S} + 5I_2 + 10 \times 2 = 0 \\ I_1 + 2 = I_2 \end{cases}$$

3 equations in 3 unknowns

- According to KVL

$$\begin{cases} V_S - V_{R_1} - V_{R_2} - V_{R_3} = 0 \\ -V_{I_S} + V_{R_2} + V_{R_4} = 0 \end{cases}$$



$$\begin{cases} 50 - I_1 - 5I_2 - 4I_1 = 0 \\ -V_{I_S} + 5I_2 + 10 \times 2 = 0 \end{cases}$$

- According to KCL


$$I_1 + 2 = I_2$$

Outlines

- Linear resistor & Ohm's law
 - Resistance & conductance
 - Ohm's law
 - Open circuit & short circuit
- Power & energy
 - Definition of power
 - Power in dB
 - Definition of energy
 - Effective current/voltage
 - Maximum power transfer
- KVL/KCL
- **Equivalent circuit**

Resistors in series

VOLTAGE DIVIDER

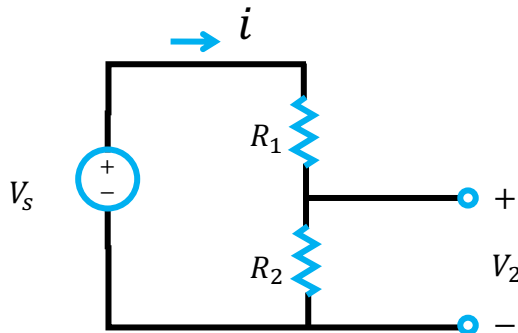

According to KVL $V_s = iR_1 + iR_2$

$$\rightarrow i = \frac{V_s}{R_1 + R_2}$$

$$V_2 = iR_2 = \frac{R_2}{R_1 + R_2} V_s$$

Voltage divided over resistors


- **Equivalent resistance, R_{eq} , (series) is sum of resistances**
- **Voltage difference across a single resistance of resistors in series**

$$R_{eq} = \sum_{i=1}^N R_i$$

$$V_i = \frac{R_i}{R_{eq}} V_s$$

Example 8

QUESTION: Find the output voltage on R_L

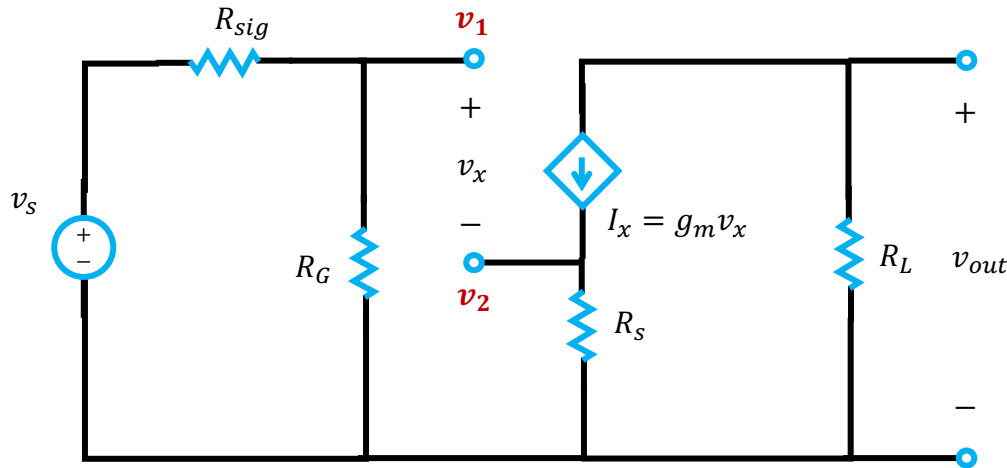

- According to the rule of voltage divided over resistors

$$v_1 = \frac{R_G}{R_{sig} + R_G} v_s$$


- According to Ohm's law $v_2 = R_s I_x$

$$= R_s g_m v_x = R_s g_m (v_1 - v_2) \quad \blacktriangleright \quad v_2 = \frac{1}{1 + g_m R_s} v_1$$

- According to Ohm's law, the voltage on R_L

$$v_{out} = -g_m v_x R_L$$

Resistors in parallel

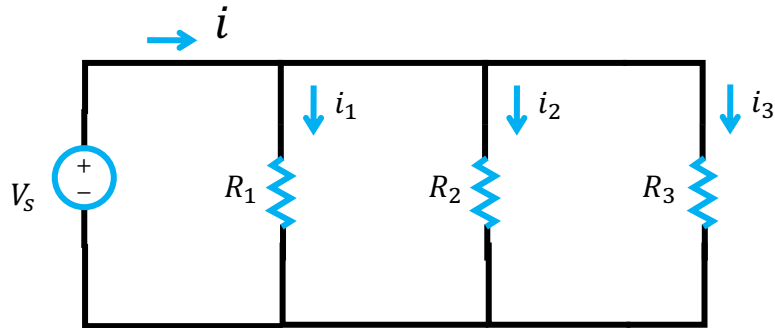

According to KCL




$$\begin{aligned} i &= i_1 + i_2 + i_3 = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \frac{V_s}{R_3} \\ &= \frac{V_s}{R_{eq}} \end{aligned}$$

- **Equivalent resistance, R_{eq} , (series) is sum of resistances**
- **Current flowing through a single resistance of resistors in parallel**

$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$

$$i_i = \frac{R_{eq}}{R_i} i_s$$

Equivalent circuits

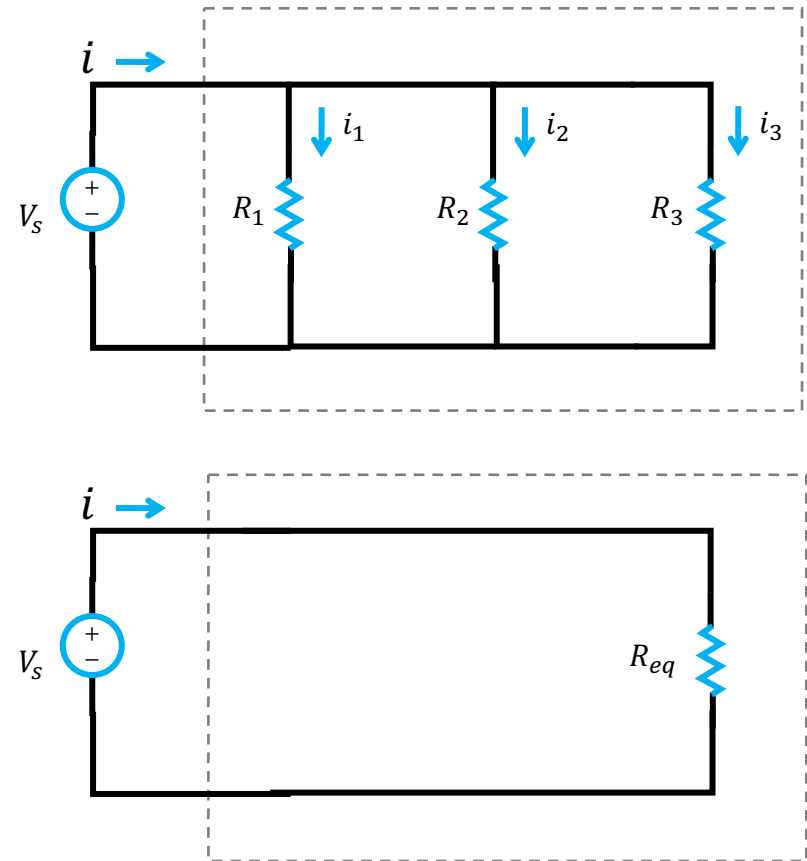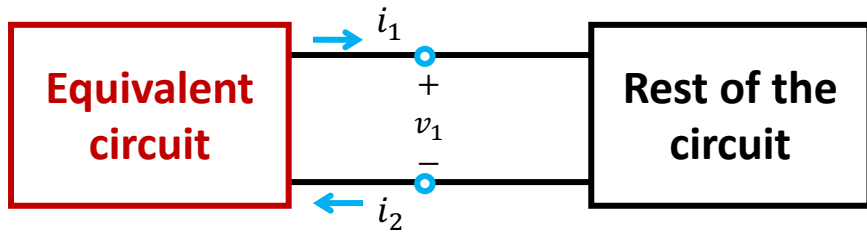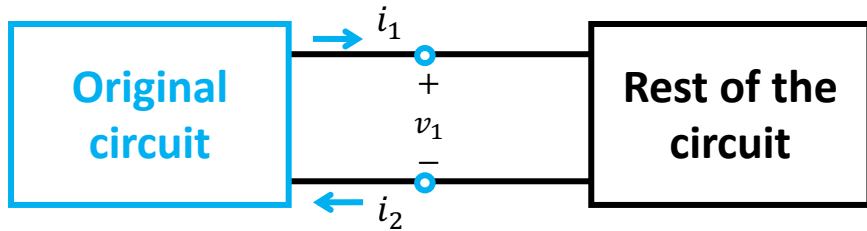


- If the current & voltage at nodes are identical, the circuits are considered “equivalent”
- Identifying equivalent circuits simplifies analysis

Example 9

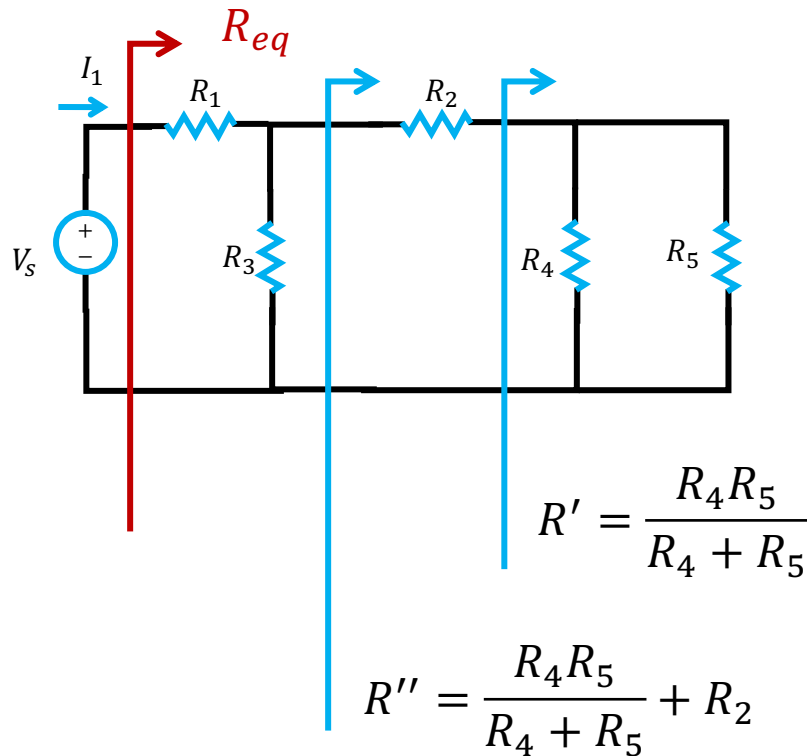QUESTION: Find the value of the equivalent resistance, R_{eq}

Find the output current of the voltage source





ANSWER:

$$R_{eq} = \frac{R_3 R''}{R_3 + R''} + R_1$$

$$I_1 = \frac{V_s}{R_{eq}}$$

Source Transformation

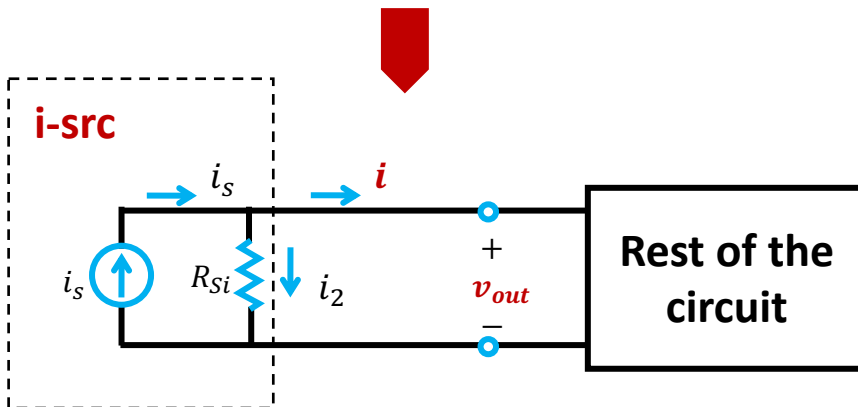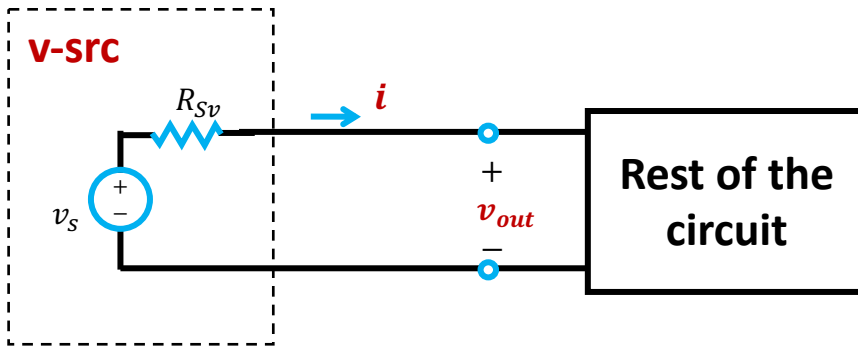The goal of source transformation is to turn a voltage source into current source, and vice-versa



- For the v-src, according to KVL

$$-v_s + iR_{Sv} + v_{out} = 0$$

- For the i-src, according to KCL





$$\begin{cases} i_s = i + i_2 \\ i_2 = \frac{v_{out}}{R_{Si}} \end{cases}$$

- If $R_{Sv} = R_{Si} = R_S$

$$v_s = i_s R_S$$

Example 10

QUESTION: Find the current of R_5

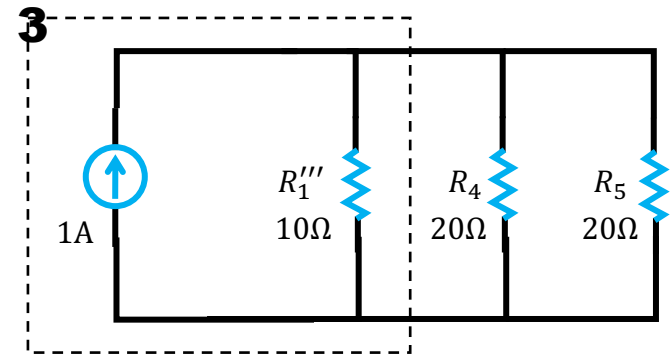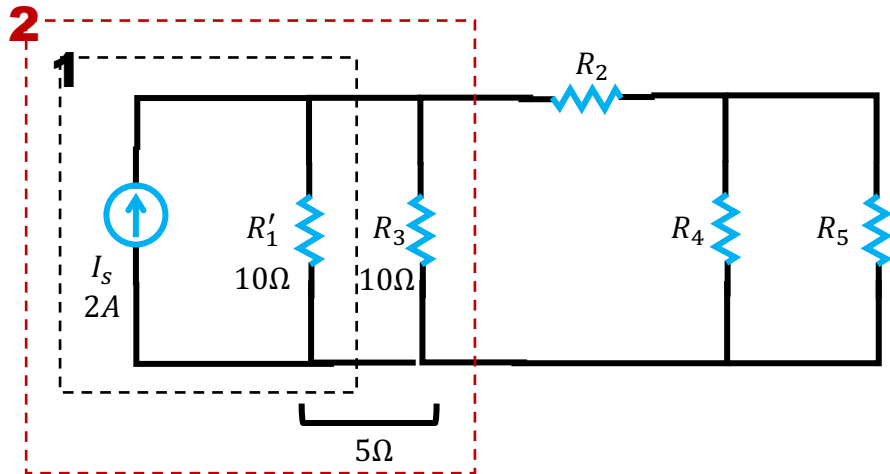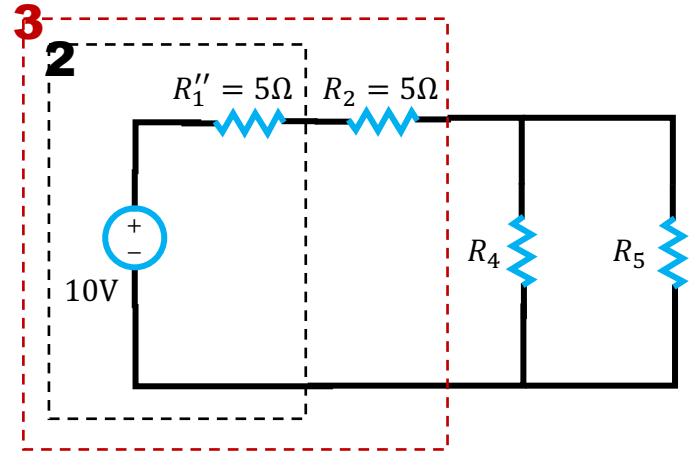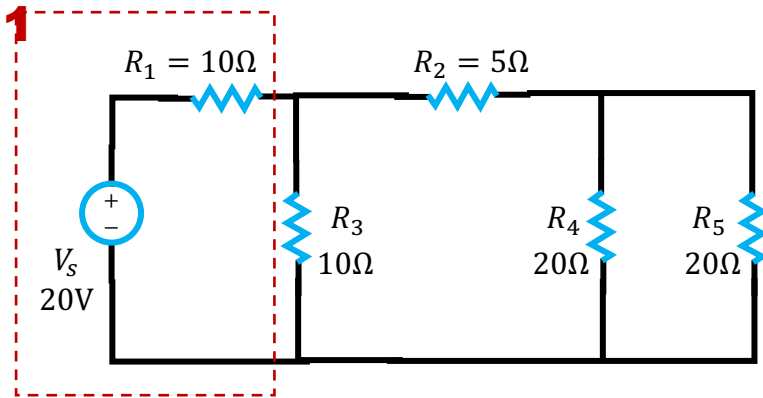

ANSWER: $I_{R_5} = 0.25A$

? Shall we calculate the output current of V_s using this method

Outlines

- Linear resistor & Ohm's law
 - Resistance & conductance
 - Ohm's law
 - Open circuit & short circuit
- Power & energy
 - Definition of power
 - Power in dB
 - Definition of energy
 - Effective current/voltage
 - Maximum power transfer
- KVL/KCL
- Equivalent circuit
 - Resistors in series/parallel
 - Source transformation

Reading tasks & learning goals

■ Reading tasks

- Basic Engineering Circuit Analysis (10th edition)
 - Chapter 2.1 – 2.6, 2.8, 2.10
 - Chapter 9.1, 9.2, 9.4, 9.5

■ Learning goals

- Be able to use **Ohm's law** for circuit analysis
- Be able to calculate **power/energy/effective V/I** of a circuit
- Be able to use **KVL/KCL** for circuit analysis
- Know how to combine **resistors in series/parallel**
- Know how to do **source transformation**
- Be able to analysis circuit containing **dependent sources**