

Fundamentals of Electronic Circuits and Systems I

# AC Steady-State Analysis

Milin Zhang



Dept of EE, Tsinghua University



# Recall

- How to analyze 1<sup>st</sup>/2<sup>nd</sup> order circuit in time domain?
  - Write the circuit equation according to KVL/KCL
  - Solve the differential equation
    - Step 1a: Find the **particular integral solution**  $v_p(t)$
    - Step 1b: substitute  $v_p(t)$  to the equation to solve the unknown
    - Step 2a: find the **homogeneous equation**
    - Step 2b: find the **complementary solution**  $v_c(t)$  to the homogeneous equation
    - Step 3a: find the initial voltage/current values
    - Step 3b: substitute the initials to the full solution to solve the unknown
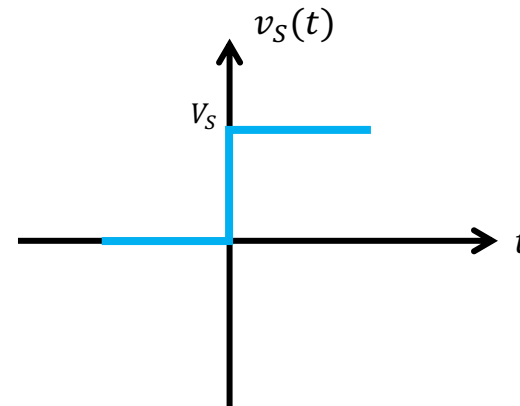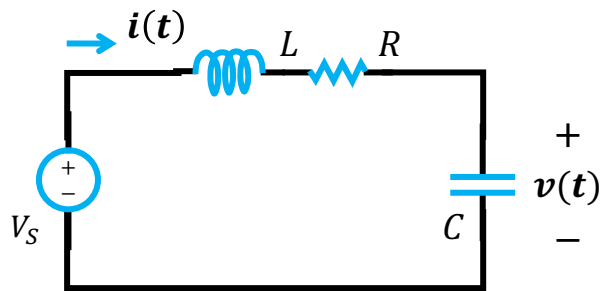
# Recall: Particular integral solution to step forcing func.



- Circuit equations according to KVL/KCL

$$\frac{d^2 v(t)}{dt^2} + \frac{R}{L} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = \frac{V_S}{LC}$$

- Particular integral solution


$$v_p(t) = V_S$$




# Outlines

- Response to different forcing function


# More forcing functions

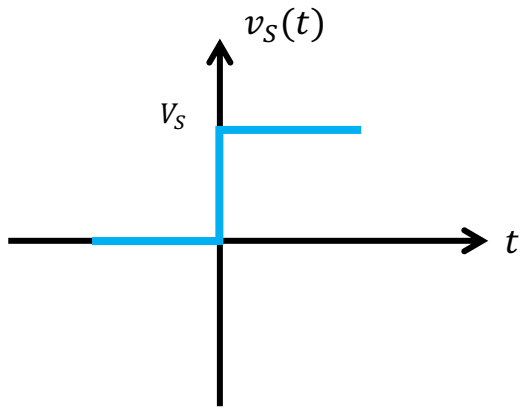

Step function

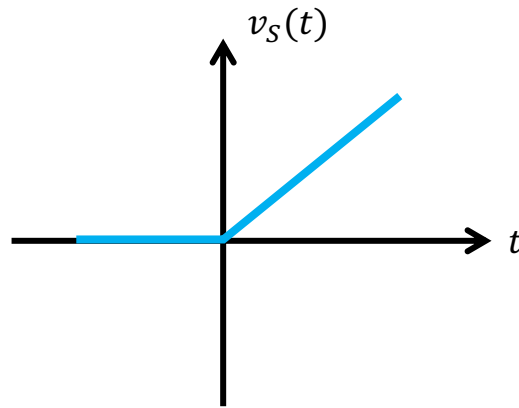

Ramp function

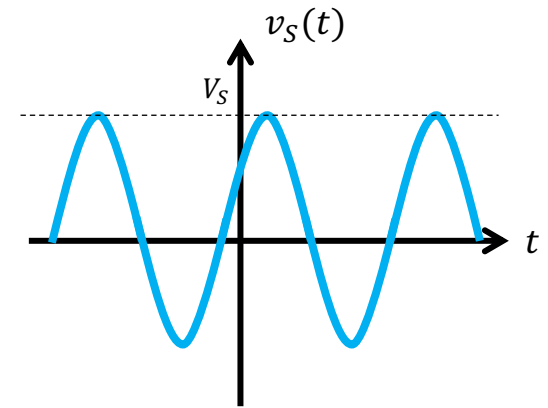


Sinusoidal function

Assume  $x_p(t) = K$

# Example 1: ramp forcing function

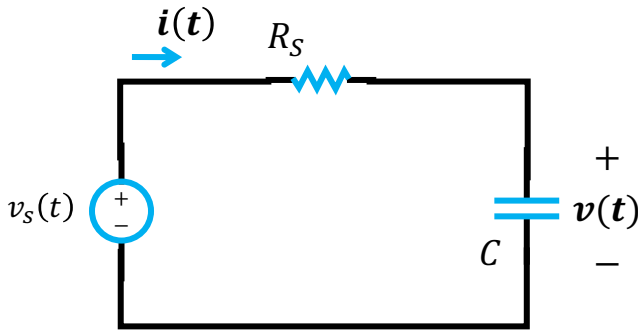
**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.



- According to KVL


$$i_R R + v(t) = v_S(t)$$
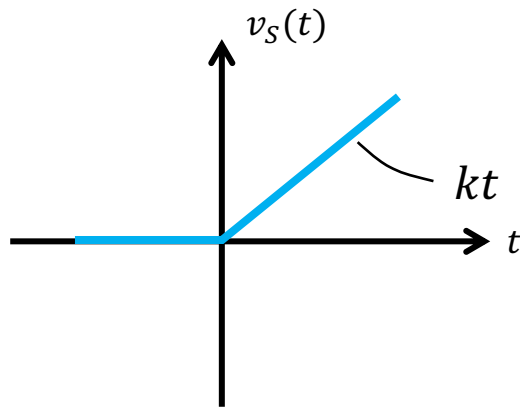
$$\rightarrow \frac{d}{dt} v(t) + \frac{1}{RC} v(t) = \frac{1}{RC} kt$$



# Example 1: ramp forcing function

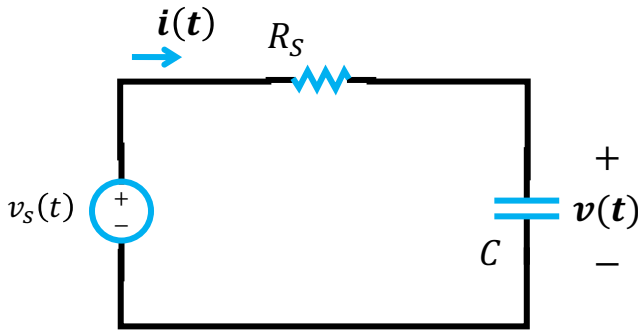**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.



$$\frac{d}{dt}v(t) + \frac{1}{RC}v(t) = \frac{1}{RC}kt$$

- Step 1a: find the **particular integral solution  $v_p(t)$**


$$\text{Assume } v_p(t) = pt + q$$

- Step 1b: substitute  $v_p(t)$  to the equation

$$p + \frac{pt + q}{RC} = \frac{1}{RC}kt$$


$$\rightarrow pt + (RCp + q) = kt$$

$$\rightarrow p = k, q = -RCk$$

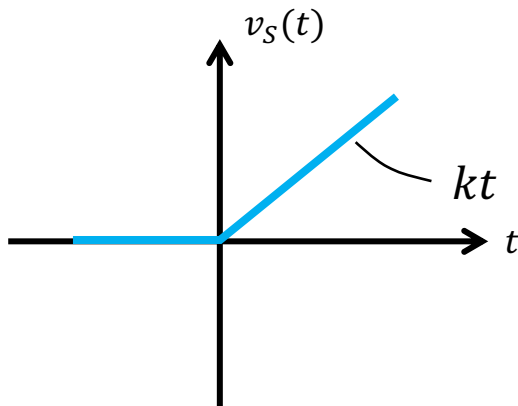

# Example 1: ramp forcing function

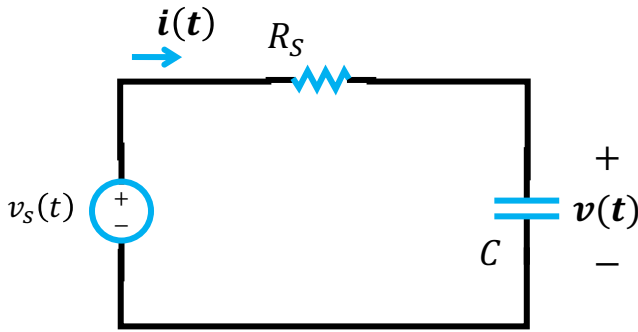**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.




$$\frac{d}{dt}v(t) + \frac{1}{RC}v(t) = \frac{1}{RC}kt$$

- Step 1: find the **particular integral solution**  $v_p(t)$

$$v_p(t) = kt - RCq$$

- Step 2: find the **complementary solution**  $v_c(t)$

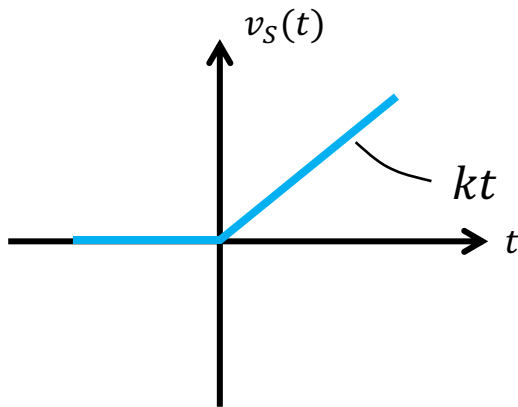
$$v_c(t) = K_2 e^{-a_1 t} \quad \text{where } a_1 = \frac{1}{RC}$$





# Example 1: ramp forcing function

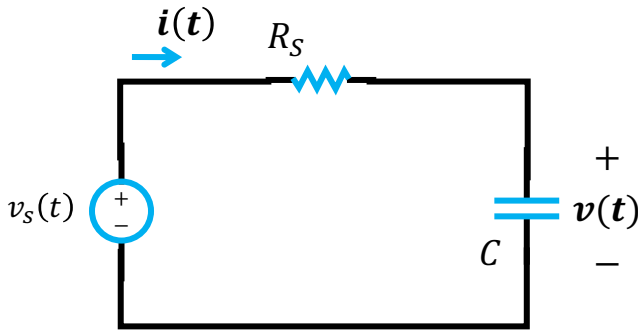**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.



$$\frac{d}{dt}v(t) + \frac{1}{RC}v(t) = \frac{1}{RC}kt$$

- Full solution


$$v(t) = kt - RCk + K_2e^{-a_1t} \quad \text{where } a_1 = \frac{1}{RC}$$

- Step 3a: find the value of  $v(t)$  at one instant of time

$$v(0) = 0$$


- Step 3b: substitute  $v(0) = 0$  to  $v(t)$

$$\rightarrow K_2 = RCk$$

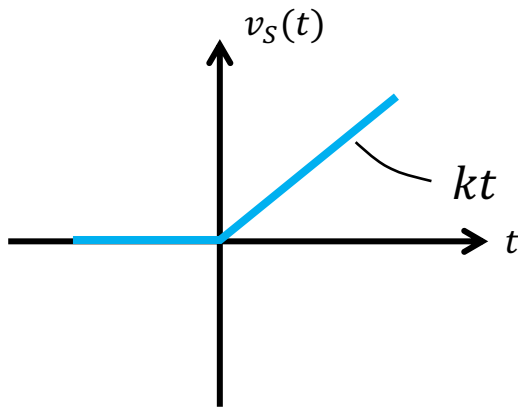



# Example 1: ramp forcing function

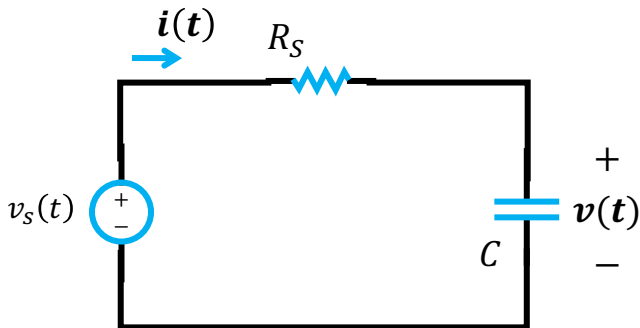**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.




$$\frac{d}{dt}v(t) + \frac{1}{RC}v(t) = \frac{1}{RC}kt$$

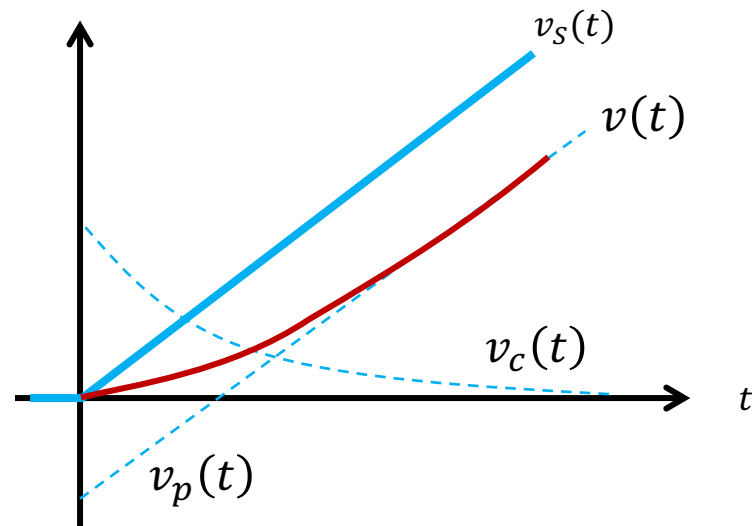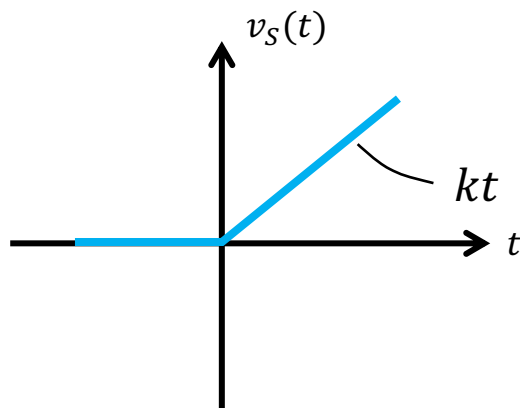Solution  $v(t) = kt - RCk + RCke^{-\frac{1}{RC}t}$





# Example 1: ramp forcing function

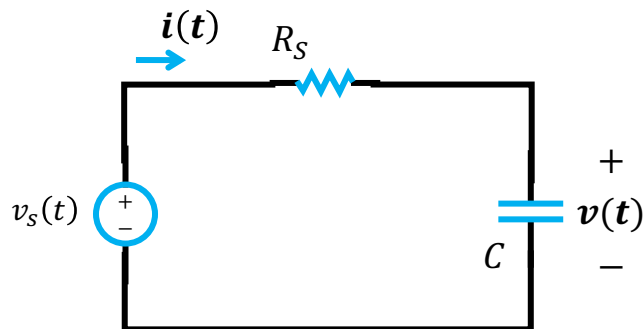
**QUESTION:** Assume there is no charge on the capacitor  $C$  at  $t = -\infty$ . Find the voltage response to the ramping forcing function.



What if  $v(0) \neq 0$  ?

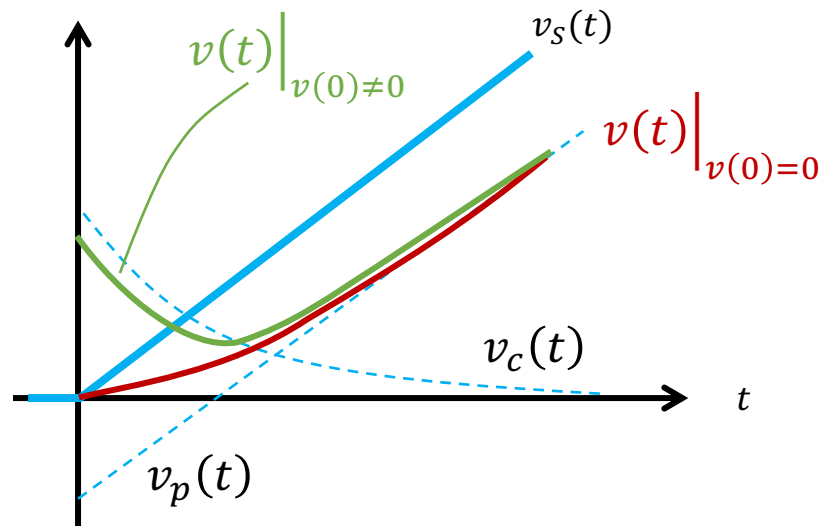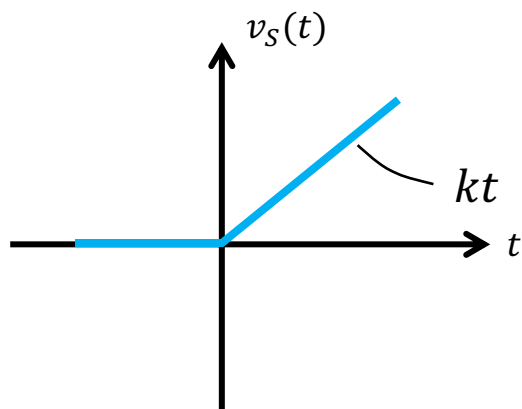


# More forcing functions

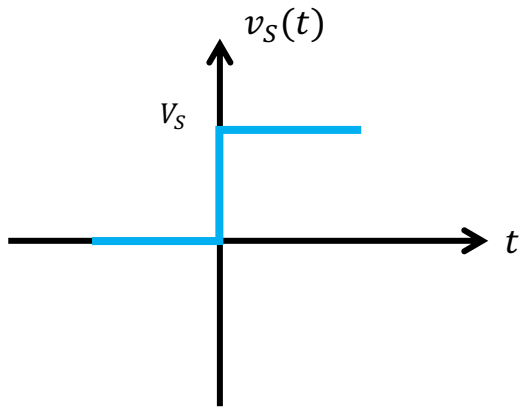


Step function

Assume  $x_p(t) = K$

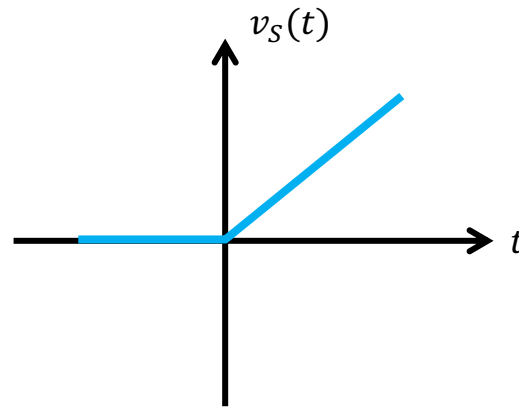

Ramp function



Assume  $x_p(t) = pt + q$

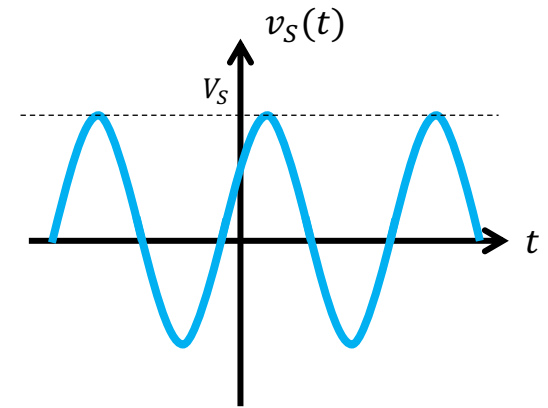

Sinusoidal function

# Example 2: Sinusoidal forcing function

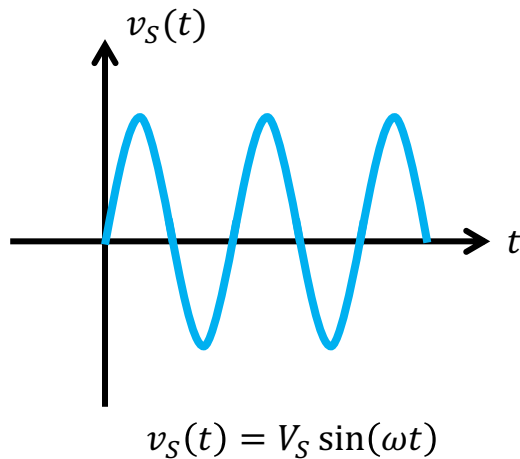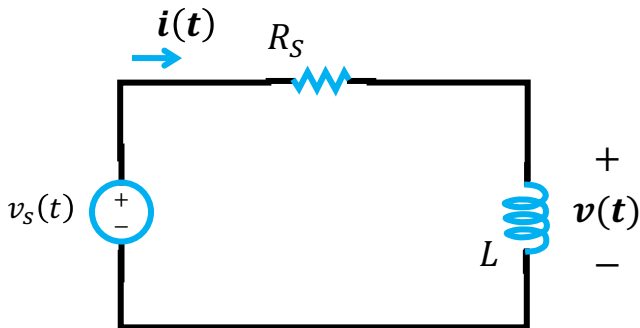**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



- According to KVL


$$i(t)R + v_L(t) = v_S(t)$$

$$\rightarrow i(t)R + L \frac{d}{dt} i(t) = v_S(t)$$

$$\rightarrow \frac{d}{dt} i(t) + \frac{R}{L} i(t) = \frac{1}{L} v_S(t)$$

# Example 2: Sinusoidal forcing function

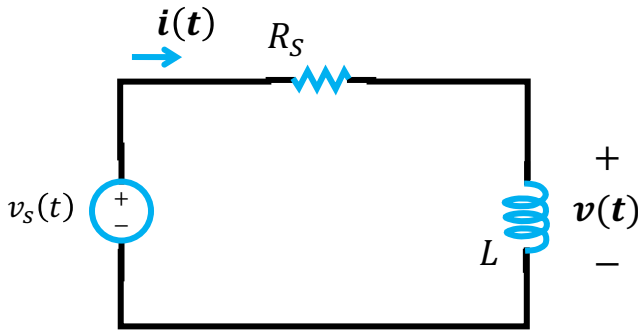**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



$$\frac{d}{dt}i(t) + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$


- Step 1a: find the **particular integral solution**  $i_p(t)$

$$\text{Assume } i_p(t) = K_1 \cos(\omega t) + K_2 \sin(\omega t)$$

- Step 1b: substitute  $i_p(t)$  to the equation



$$V_S \sin(\omega t) = K_1 R \cos(\omega t) + K_2 R \sin(\omega t) + L\omega K_2 \cos(\omega t) - L\omega K_1 \sin(\omega t)$$
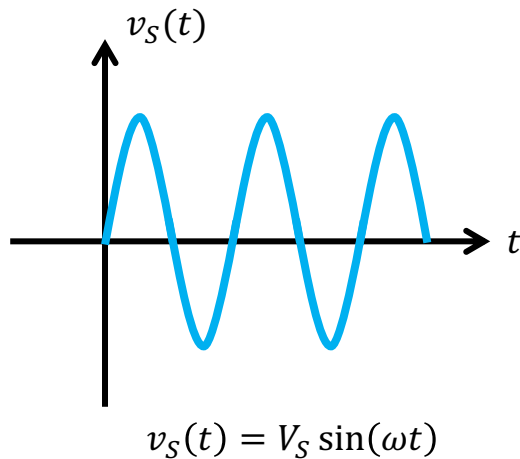
$$\rightarrow \begin{cases} V_S = K_2 R - L\omega K_1 \\ 0 = K_1 R + L\omega K_2 \end{cases} \rightarrow \begin{cases} K_1 = V_S \frac{-\omega L}{R^2 + \omega^2 L^2} \\ K_2 = V_S \frac{R}{R^2 + \omega^2 L^2} \end{cases}$$



# Example 2: Sinusoidal forcing function

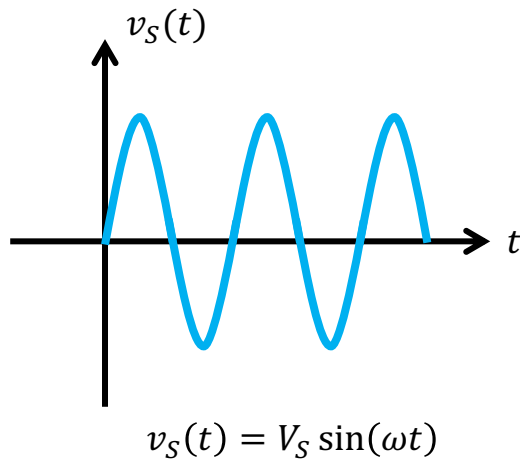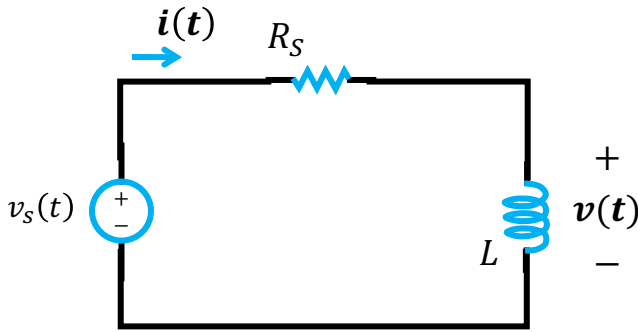**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



$$\frac{d}{dt}i(t) + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$

- Step 1: find the **particular integral solution**  $i_p(t)$

$$i_p(t) = K_1 \cos(\omega t) + K_2 \sin(\omega t)$$


$$\text{where } \begin{cases} K_1 = V_S \frac{-\omega L}{R^2 + \omega^2 L^2} \\ K_2 = V_S \frac{R}{R^2 + \omega^2 L^2} \end{cases}$$

- Step 2: find the **complementary solution**  $i_c(t)$

$$i_c(t) = K_3 e^{-\frac{R}{L}t}$$

# Example 2: Sinusoidal forcing function

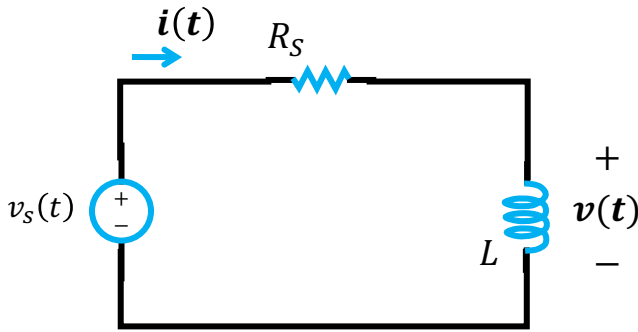**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



$$\frac{d}{dt}i(t) + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$

- Full solution


$$i(t) = K_1 \cos(\omega t) + K_2 \sin(\omega t) + K_3 e^{-\frac{R}{L}t}$$

- Step 3a: find the value of  $i(t)$  at one instant of time

$$i(0) = 0$$

- Step 3b: substitute  $i(0) = 0$  to  $i(t)$

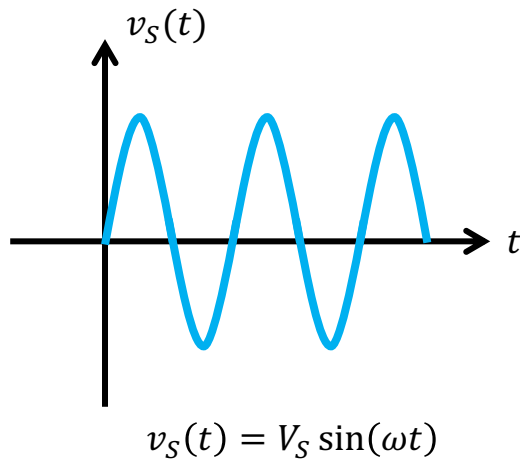
$$\rightarrow K_3 = \frac{\omega L V_S}{R^2 + \omega^2 L^2}$$







# Example 2: Sinusoidal forcing function

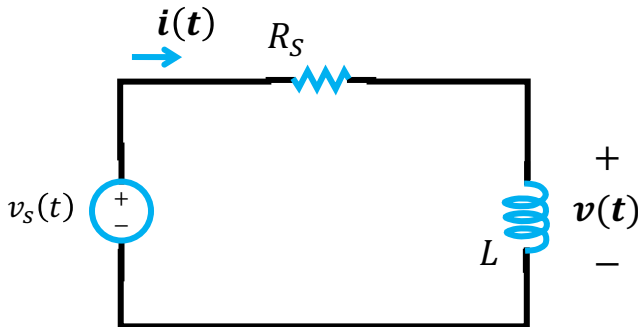**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



$$\frac{d}{dt}i(t) + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$

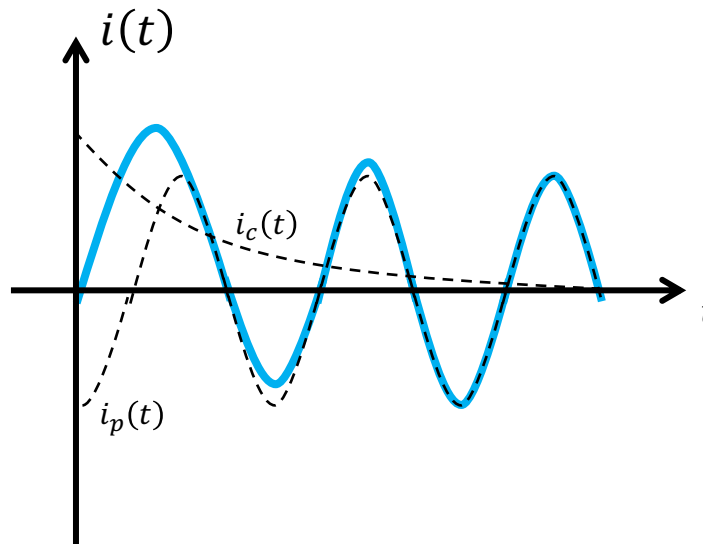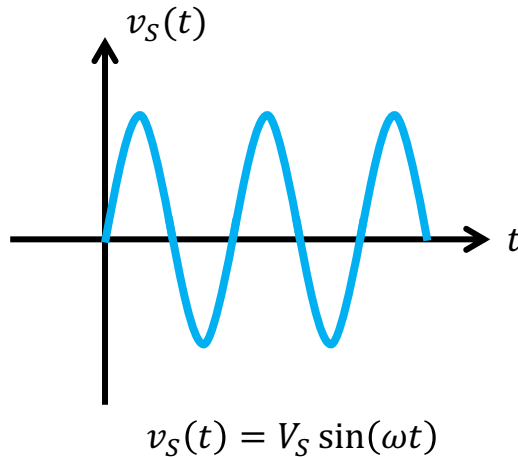
Solution  $i(t) = K_1 \cos(\omega t) + K_2 \sin(\omega t) + K_3 e^{-\frac{R}{L}t}$



where


$$\begin{cases} K_1 = V_S \frac{-\omega L}{R^2 + \omega^2 L^2} \\ K_2 = V_S \frac{R}{R^2 + \omega^2 L^2} \\ K_3 = V_S \frac{\omega L}{R^2 + \omega^2 L^2} \end{cases}$$

# More forcing functions

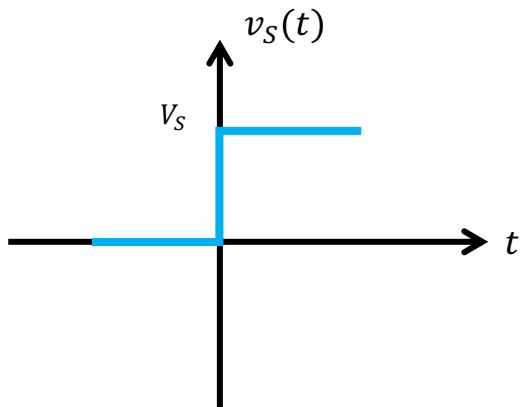


Step function

Assume  $x_p(t) = K$

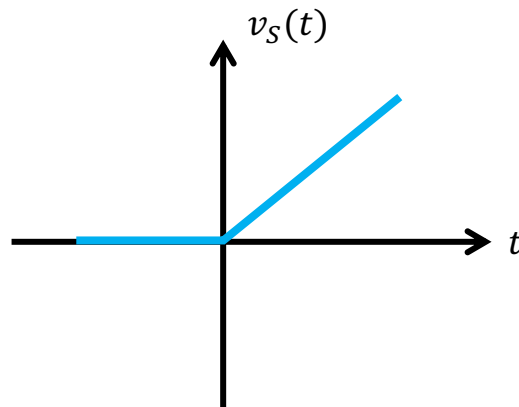

Ramp function

Assume  $x_p(t) = pt + q$

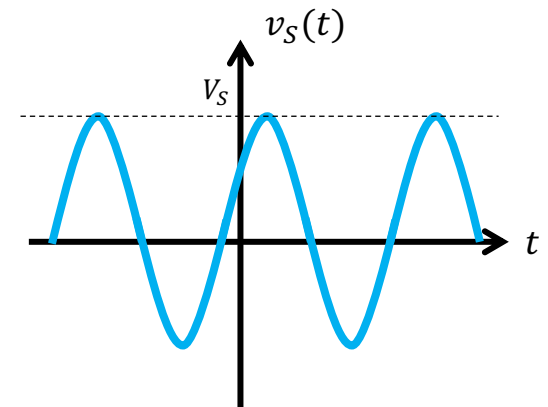



Sinusoidal function

Assume  $x_p(t) = K_1 \sin(\omega t) + K_2 \cos(\omega t)$

# Outlines

- Response to different forcing function
  - Ramping forcing function
  - Sinusoidal forcing function
- **Complex forcing function**

# Resistors with a sin. forcing func.

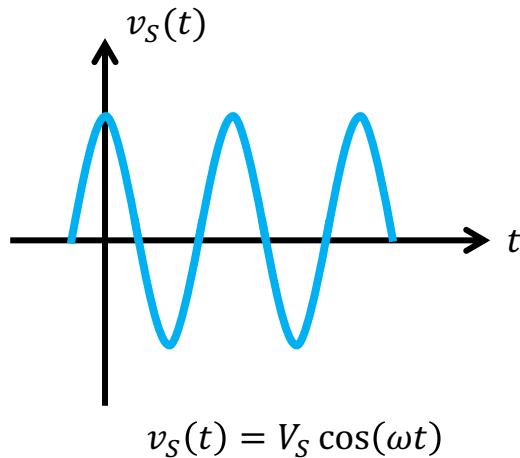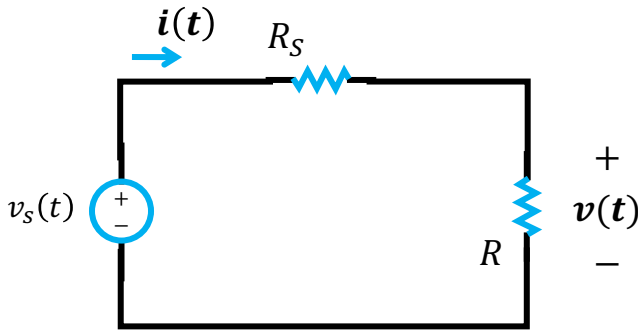

With  $v_{s1}(t) = V_S \cos(\omega t)$

- According to KVL


$$v(t) = \frac{R}{R + R_S} v_{s1}(t) = \frac{R V_S}{R + R_S} \cos(\omega t)$$

With  $v_{s2}(t) = j V_S \sin(\omega t)$

- According to KVL

$$v(t) = \frac{R}{R + R_S} v_{s2}(t) = j \frac{R V_S}{R + R_S} \sin(\omega t)$$

# Resistors with a sin. forcing func.

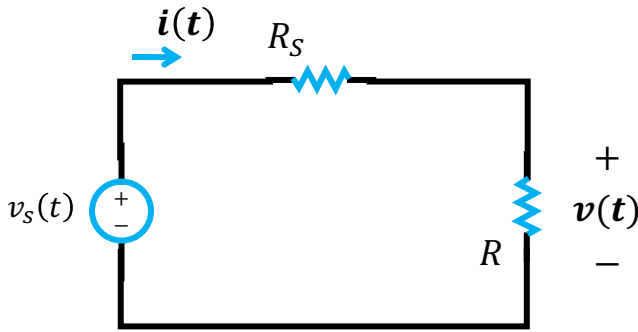


What if  $v_s(t) = V_S \cos(\omega t) + jV_S \sin(\omega t)$  ?

- According to KVL

$$v(t) = \frac{R}{R + R_S} v_s(t)$$


$$= \frac{R}{R + R_S} (V_S \cos(\omega t) + jV_S \sin(\omega t))$$

# Resistors with a sin. forcing func.

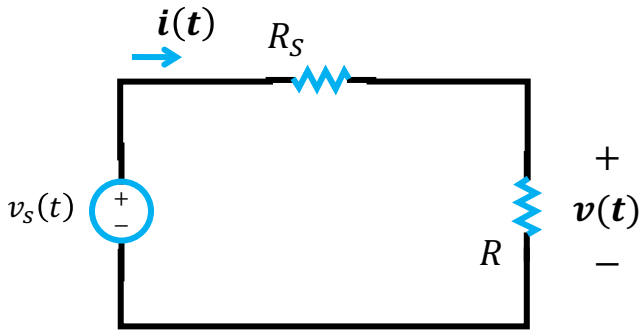


What if  $v_s(t) = V_S \cos(\omega t) + jV_S \sin(\omega t)$  ?

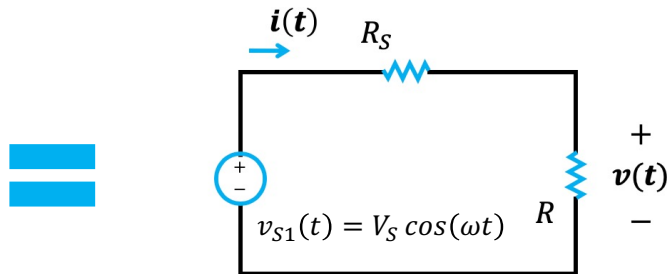Solution: 
$$v(t) = \frac{R}{R + R_S} (V_S \cos(\omega t) + jV_S \sin(\omega t))$$


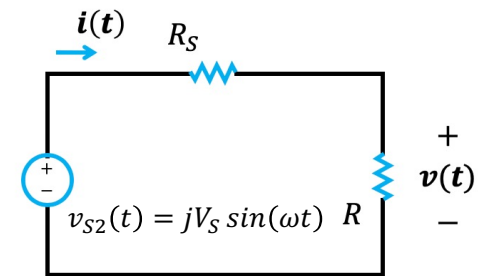
$$v(t) = \frac{RV_S}{R + R_S} \cos(\omega t)$$



$$v(t) = j \frac{RV_S}{R + R_S} \sin(\omega t)$$

# Recall: Euler's eq. & Complex num.

**Phasor representation:**  $A \cos(\omega t + \theta) = |z| \angle \theta$


**Euler's equation:**  $e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$

- Real part  $\Re[e^{j\omega t}] = \cos(\omega t)$
- imaginary part  $\Im[e^{j\omega t}] = \sin(\omega t)$


## Complex numbers

- Rectangular coordinates  $z = x + jy$
- Polar coordinates  $z = |z|e^{j\theta}$

Where 
$$\begin{cases} |z| = \sqrt{x^2 + y^2} \\ \theta = \tan^{-1}\left(\frac{y}{x}\right) \end{cases}$$

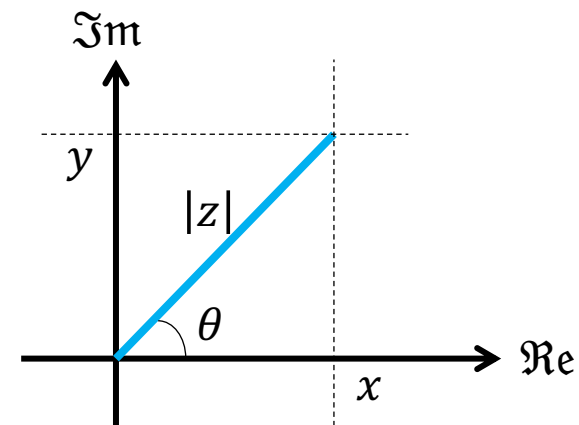

# Complex forcing function

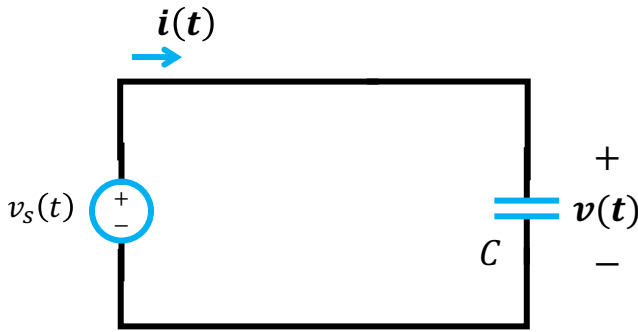

- If a complex function is applied to the capacitor


$$v_s(t) = V_S e^{j\omega t}$$

- According to the  $i - v$  relationship of capacitor

$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ &= C \frac{d}{dt} (V_S e^{j\omega t}) \\ &= j\omega C V_S e^{j\omega t} \end{aligned}$$



# Complex forcing function

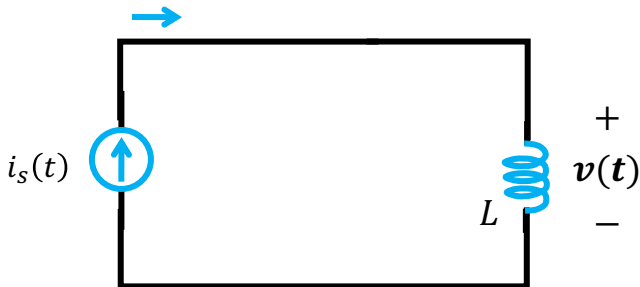


- If a complex function is applied to the inductor

$$i_s(t) = I_s e^{j\omega t}$$

- According to the  $i - v$  relationship of inductor

$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= L \frac{d}{dt} (I_s e^{j\omega t}) \\ &= j\omega L I_s e^{j\omega t} \end{aligned}$$


# Complex forcing func. on passive dev.

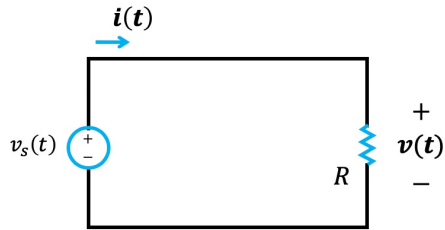

$$v(t) = V_S e^{j\omega t}$$

$$i(t) = \frac{V_S}{R} e^{j\omega t}$$

$$\frac{v(t)}{i(t)} = R$$

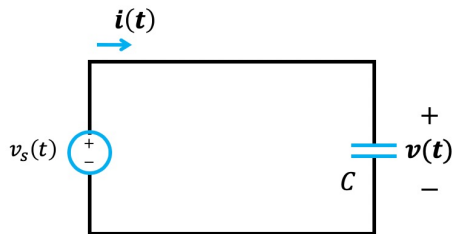

$$v(t) = V_S e^{j\omega t}$$

$$i(t) = j\omega C V_S e^{j\omega t}$$

$$\frac{v(t)}{i(t)} = \frac{1}{j\omega C}$$






$$i(t) = I_S e^{j\omega t}$$

$$v(t) = j\omega L I_S e^{j\omega t}$$



$$\frac{v(t)}{i(t)} = j\omega L$$

# Impedance

Impedance,  $Z$ ,  
is defined as the ratio of the phasor voltage to the phasor current

			
$i$ - $v$ relation	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
$v$ - $i$ relation	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
<b>Impedance</b>	<b><math>R</math></b>	<b><math>\frac{1}{j\omega C}</math></b>	<b><math>j\omega L</math></b>

# Series connection

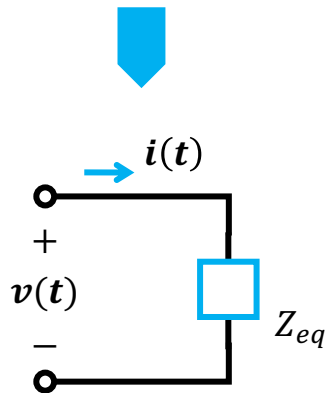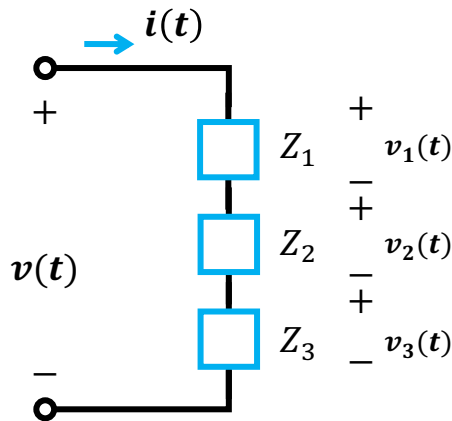

According to KVL

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$

According  $i$ - $v$  relationship


$$\begin{aligned} v(t) &= i(t)Z_1 + i(t)Z_2 + i(t)Z_3 \\ &= i(t)(Z_1 + Z_2 + Z_3) \end{aligned}$$

For the equivalent circuit

$$v(t) = i(t)Z_{eq}$$

$$\Rightarrow Z_{eq} = Z_1 + Z_2 + Z_3$$

# Parallel connection

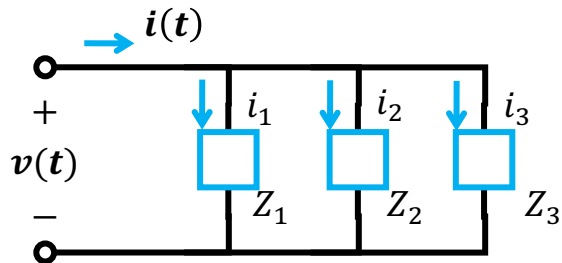

According to  $i$ - $v$  relationship


$$v(t) = i_1(t)Z_1 = i_2(t)Z_2 = i_3(t)Z_3$$

$$v(t) = i(t)Z_{eq}$$

According to KVL

$$v(t) = Z_{eq}(i_1(t) + i_2(t) + i_3(t))$$

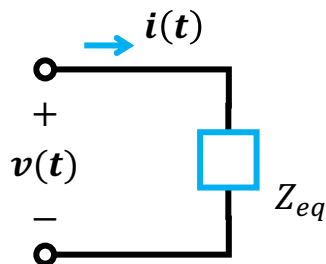
$$= Z_{eq} \left( \frac{v(t)}{Z_1} + \frac{v(t)}{Z_2} + \frac{v(t)}{Z_3} \right)$$



$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

# Capacitive & Inductive

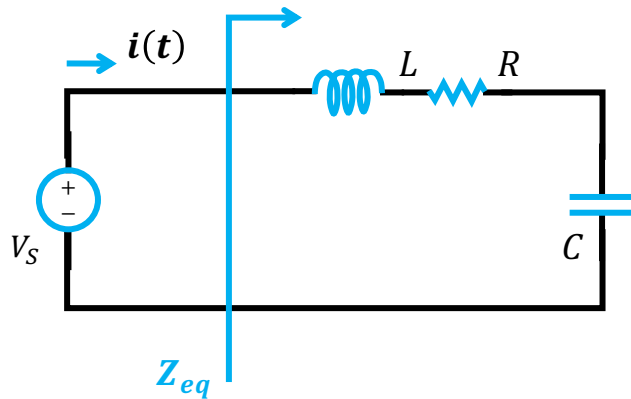**QUESTION:** Find the value of the equivalent impedance,  $Z_{eq}$




$$Z_{eq} = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

- if  $\omega L - \frac{1}{\omega C} > 0$  the reactance is inductive
- if  $\omega L - \frac{1}{\omega C} < 0$  the reactance is capacitive

# Example 4: mesh-current with imp.

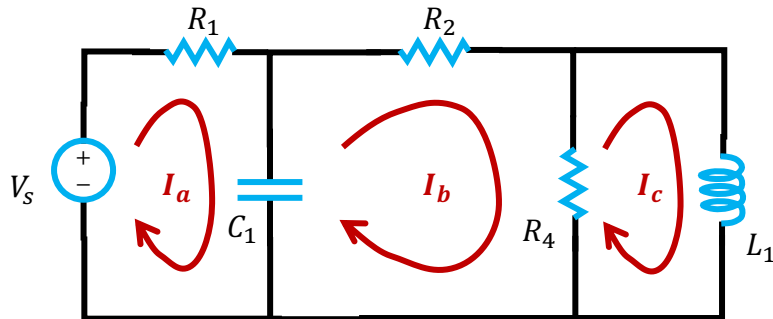**QUESTION:** Find the output current of the voltage source




- According to KVL

$$\begin{cases} -V_s + I_a R_1 + (I_a - I_b) \frac{1}{j\omega C} = 0 \\ (I_b - I_a) \frac{1}{j\omega C} + I_b R_2 + (I_b - I_c) R_4 = 0 \\ (I_c - I_b) R_4 + j\omega L I_c = 0 \end{cases}$$

# Example 4: mesh-current with imp.

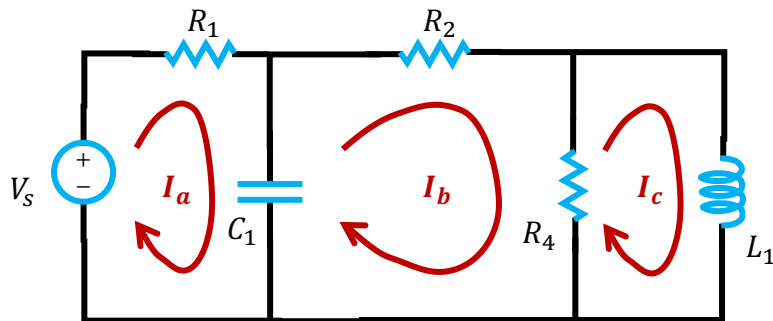**QUESTION:** Find the output current of the voltage source




- According to KVL **3 equations in 3 unknowns**

$$\left\{ \begin{array}{l} I_a \left( R_1 + \frac{1}{j\omega C} \right) - I_b \frac{1}{j\omega C} = V_s \\ -I_a \frac{1}{j\omega C} + I_b \left( \frac{1}{j\omega C} + R_2 + R_4 \right) - I_c R_4 = 0 \\ -I_b R_4 + I_c (R_4 + j\omega L) = 0 \end{array} \right.$$



# Example 5: Superposition with imp.

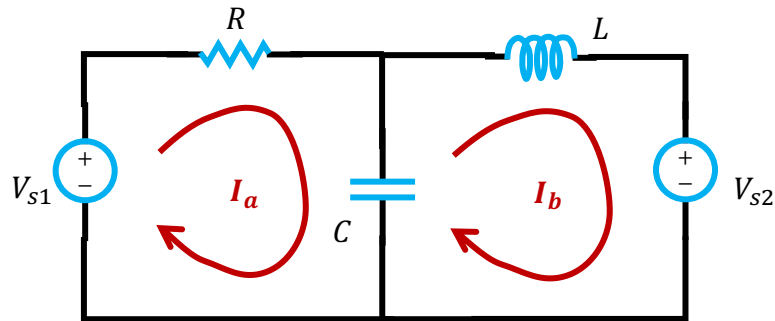**QUESTION:** Find the voltage on the capacitor  $C$



$$\begin{cases} I_a = \frac{\frac{1}{j\omega C} V_{s1} + \left(R + \frac{1}{j\omega C}\right) V_{s2}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}} \\ I_b = \frac{j\left(\omega L - \frac{1}{\omega C}\right) V_{s1} + \frac{1}{j\omega C} V_{s2}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}} \end{cases}$$


- According to KVL

$$\begin{cases} -V_{s1} + RI_a + \frac{1}{j\omega C} (I_a - I_b) = 0 \\ \frac{1}{j\omega C} (I_b - I_a) + j\omega LI_b - V_{s2} = 0 \end{cases}$$



$$V_C = \frac{1}{j\omega C} (I_a - I_b) = \frac{\frac{L}{C} V_{s1} - \frac{R}{j\omega C} V_{s2}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}}$$


# Example 5: Superposition with imp.

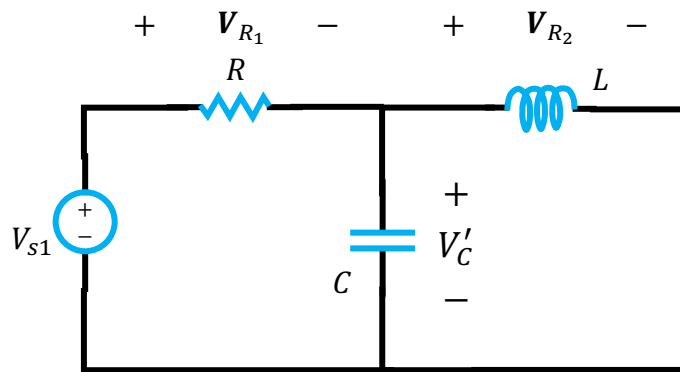

- According to voltage division

$$V'_C = \frac{j\omega L \parallel \frac{1}{j\omega C}}{R + j\omega L \parallel \frac{1}{j\omega C}} V_{s1}$$
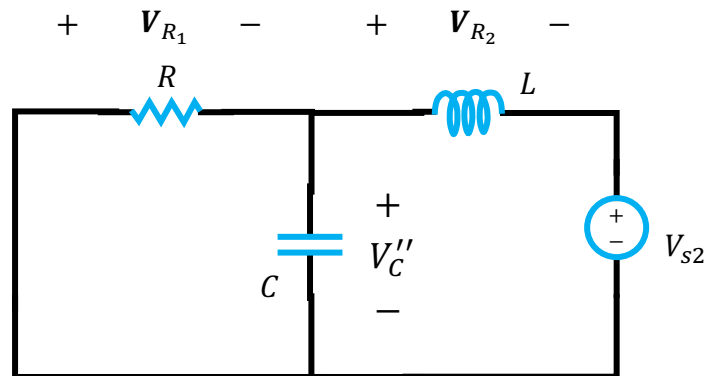
$$= \frac{\frac{L}{C}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}} V_{s1}$$




$$V''_C = -\frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}} V_{s2}$$

$$= -\frac{\frac{R}{j\omega C}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}} V_{s2}$$


# Example 5: Superposition with imp.

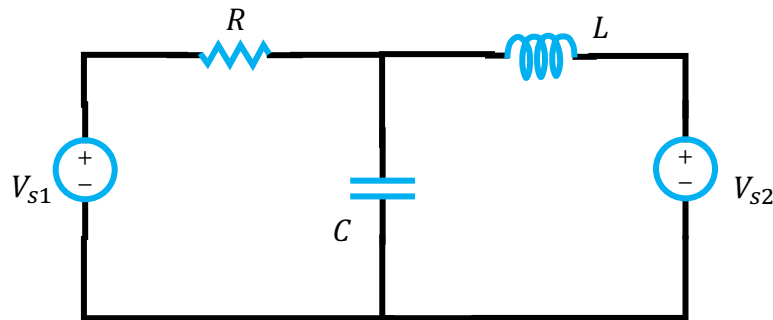QUESTION: Find the voltage on the capacitor  $C$




$$V_C = \frac{\frac{L}{C}V_{s1} - \frac{R}{j\omega C}V_{s2}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}}$$

=

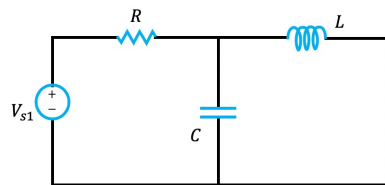

$$V'_C = \frac{\frac{L}{C}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}}V_{s1}$$

+

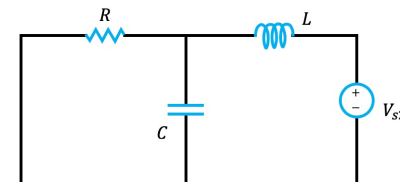


$$V''_C = -\frac{\frac{R}{j\omega C}}{j\omega LR + \frac{R}{j\omega C} + \frac{L}{C}}V_{s2}$$

**The superposition property works for ALL LINEAR circuit**

# Example 6: Thévenin equivalency with imp.

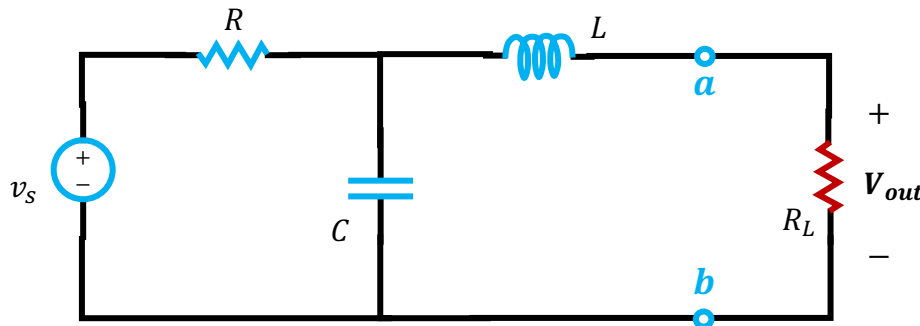**QUESTION:** Find the Thévenin equivalent circuit of the network at the terminals a & b



## Thévenin's theorem


LINEAR two-terminal circuit can be replaced by an equivalent circuit composed of a voltage source and a series impedance

## Norton's theorem

LINEAR two-terminal circuit can be replaced by an equivalent circuit composed of a current source and a parallel impedance

# Example 6: Thévenin equivalency with imp.

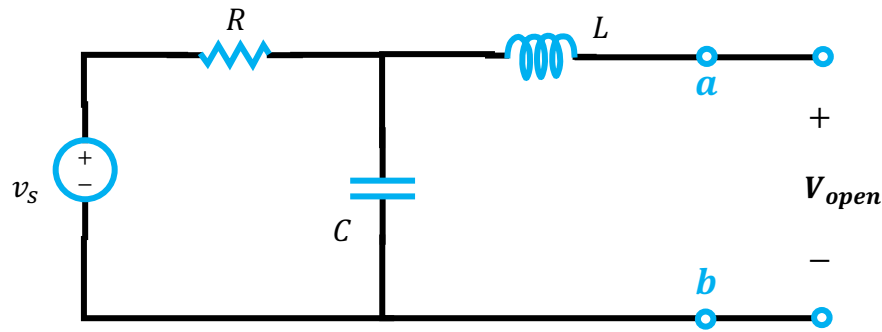**QUESTION:** Find the Thévenin equivalent circuit of the network at the terminals a & b



- Step 1: remove the load
- Step 2: find  $V_{open}$

- According to voltage division


$$V_{open} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} v_s = \frac{1}{1 + j\omega CR} v_s$$



$V_{TH}$

# Example 6: Thévenin equivalency with imp.

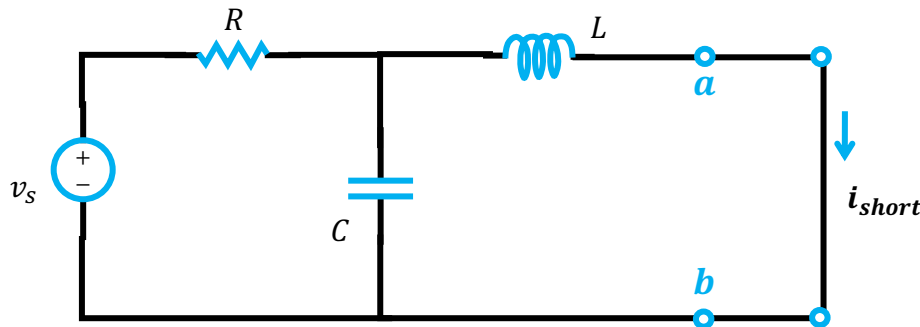**QUESTION:** Find the Thévenin equivalent circuit of the network at the terminals a & b



- Step 1: remove the load
- Step 2: find  $V_{open}$
- Step 3: find  $i_{short}$

- According to Ohm's law



$$i_{open} = \frac{v_s}{R + \frac{1}{j\omega C} \parallel j\omega L} \cdot \frac{1}{\frac{1}{j\omega C} + j\omega L}$$

$$= \frac{v_s}{R + j\omega L - \omega^2 LC}$$

$$\parallel$$
$$i_N$$


# Example 6: Thévenin equivalency with imp.

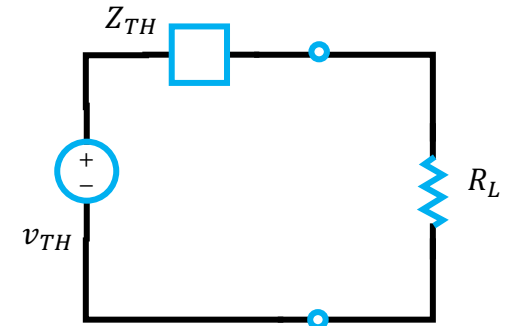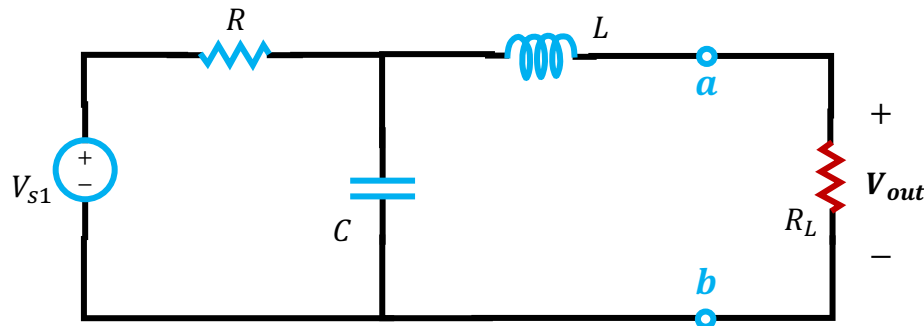**QUESTION:** Find the Thévenin equivalent circuit of the network at the terminals a & b




- Step 1: remove the load
- Step 2: find  $V_{open} = v_{TH}$
- Step 3: find  $i_{short} = i_N$
- Step 4: find  $Z_{TH}$
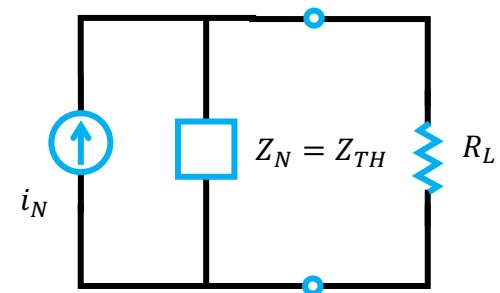
$$Z_{TH} = \frac{v_{TH}}{i_N} = \frac{R + j\omega L - \omega^2 LC}{1 + j\omega CR}$$



# Example 7

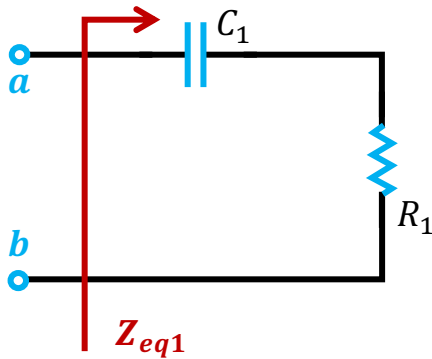**QUESTION:** Find the value of  $\omega$  and  $C_2$ , which makes the two circuit equivalent to each other




- The equivalent impedance of the upper circuit

$$Z_{eq1} = R_1 + \frac{1}{j\omega C_1}$$

- The equivalent admittance of the lower circuit
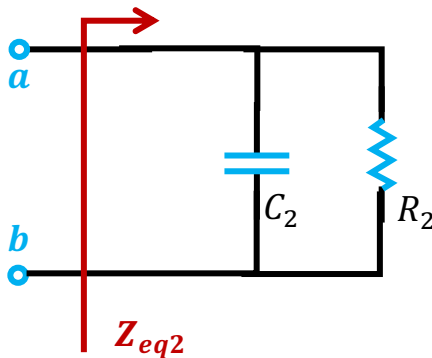
$$G_{eq2} = \frac{1}{R_2} + j\omega C_2$$




$$Z_{eq1} = \frac{1}{G_{eq2}} \quad \text{when} \quad \begin{cases} \Re[Z_{eq1}] = \Re\left[\frac{1}{G_{eq2}}\right] \\ \Im[Z_{eq1}] = \Im\left[\frac{1}{G_{eq2}}\right] \end{cases}$$




# Example 7

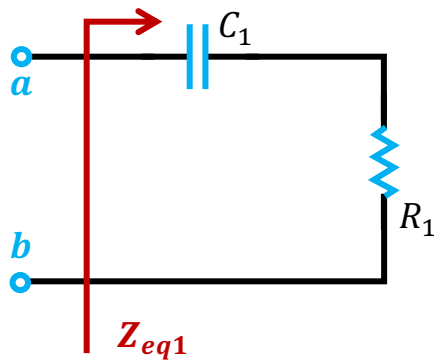**QUESTION:** Find the value of  $R_2$  and  $C_2$ , which makes the two circuit equivalent to each other



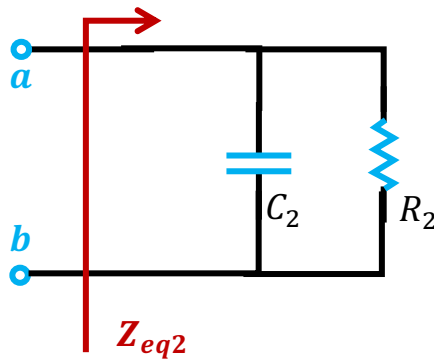
$$G_{eq1} = \frac{1}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1 + j\frac{1}{\omega C_1}}{R_1^2 + \omega^2 C_1^2}$$
$$= \frac{R_1 \omega^2 C_1^2}{R_1^2 + \omega^2 C_1^2} + j \frac{\omega C_1}{R_1^2 + \omega^2 C_1^2}$$



$$G_{eq2} = \frac{1}{R_2} + j\omega C_2$$
$$\Rightarrow \begin{cases} R_2 = \frac{R_1^2 + \omega^2 C_1^2}{R_1 \omega^2 C_1^2} \\ C_2 = \frac{C_1}{R_1^2 + \omega^2 C_1^2} \end{cases}$$

# Example 8

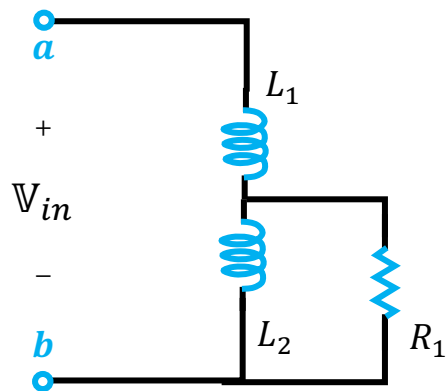
**QUESTION:** Find the value of  $R_2$ , which makes the power dissipated by  $R_2$  is approximately equivalent to the dissipated by  $R_1$ , when the load resistance  $R_1$  is very high



- According to KVL

$$V_{R_1} = V_{in} \frac{R_1 || Z_{L_2}}{Z_{L_1} + R_1 || Z_{L_2}}$$
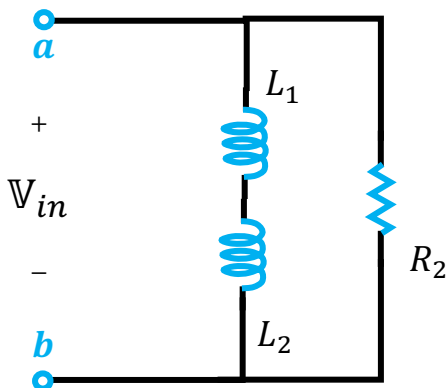
$$\xrightarrow{R_1 \gg \omega L_2} V_{in} \frac{Z_{L_2}}{Z_{L_1} + Z_{L_2}} = V_{in} \frac{L_2}{L_1 + L_2}$$



- the power dissipated by  $R_1$  and  $R_2$

$$\begin{cases} P_{R_1} = \frac{V_{R_1}^2}{R_1} \\ P_{R_2} = \frac{V_{in}^2}{R_2} \end{cases}$$




$$R_2 = \frac{R_1}{p^2}$$

$$\text{where } p = \frac{L_2}{L_1 + L_2}$$

# Example 9

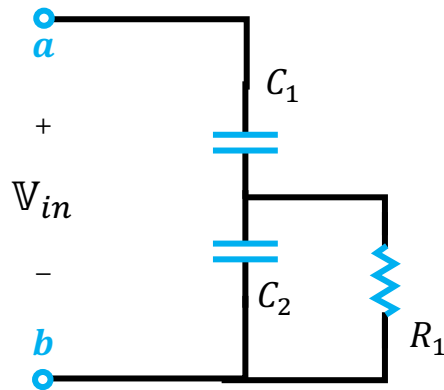
**QUESTION:** Find the value of  $R_2$ , which makes the power dissipated by  $R_2$  is approximately equivalent to the dissipated by  $R_1$ , when the load resistance  $R_1$  is very high



- According to KVL

$$\mathbb{V}_{R_1} = \mathbb{V}_{in} \frac{R_1 \parallel Z_{C_2}}{Z_{C_1} + R_1 \parallel Z_{C_2}}$$
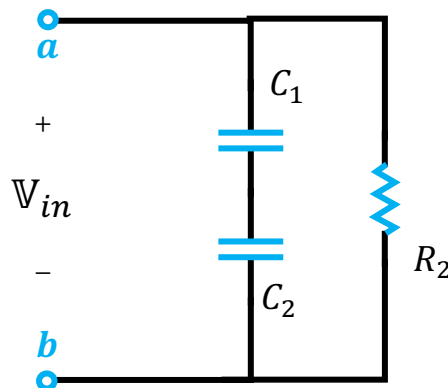
$$\xrightarrow{R_1 \gg \frac{1}{\omega C_2}} \mathbb{V}_{in} \frac{Z_{C_2}}{Z_{C_1} + Z_{C_2}} = \mathbb{V}_{in} \frac{C_1}{C_1 + C_2}$$






- the power dissipated by  $R_1$  and  $R_2$

$$\begin{cases} P_{R_1} = \frac{\mathbb{V}_{R_1}^2}{R_1} \\ P_{R_2} = \frac{\mathbb{V}_{in}^2}{R_2} \end{cases} \quad \rightarrow \quad R_2 = \frac{R_1}{p^2}$$

where  $p = \frac{C_1}{C_1 + C_2}$




# Outlines

- Response to different forcing function
  - Ramping forcing function
  - Sinusoidal forcing function
- Complex forcing function
  - Impedance & admittance
  - KVL&KCL / Superposition / Equivalency

			
<i>i-v</i> relation	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
<i>v-i</i> relation	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
<b>Impedance</b>	<b><math>R</math></b>	<b><math>\frac{1}{j\omega C}</math></b>	<b><math>j\omega L</math></b>

# Outlines


- Response to different forcing function
  - Ramping forcing function
  - Sinusoidal forcing function
- Complex forcing function
  - Impedance & admittance
  - KVL&KCL / Superposition / Equivalency

			
<i>i-v</i> relation	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
<i>v-i</i> relation	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
<b>Impedance</b>	<b><math>R</math></b>	<b><math>\frac{1}{j\omega C}</math></b>	<b><math>j\omega L</math></b>

## ■ AC steady-state analysis

# Example 10

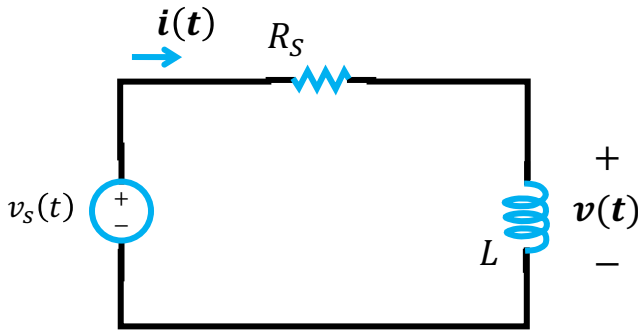**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to a complex forcing function  $v_S = V_S e^{j\omega t}$ .



## METHODS 1

- According to KVL

$$\frac{d}{dt} i(t) + \frac{R}{L} i(t) = \frac{1}{L} v_S(t)$$

- The current through  $L$  must be in the form of


$$i_S(t) = I_S e^{j(\omega t + \varphi)}$$

- Substitute  $i_S(t)$  to the equation

$$\frac{d}{dt} (I_S e^{j(\omega t + \varphi)}) + \frac{R}{L} I_S e^{j(\omega t + \varphi)} = \frac{1}{L} V_S e^{j\omega t}$$

# Example 10

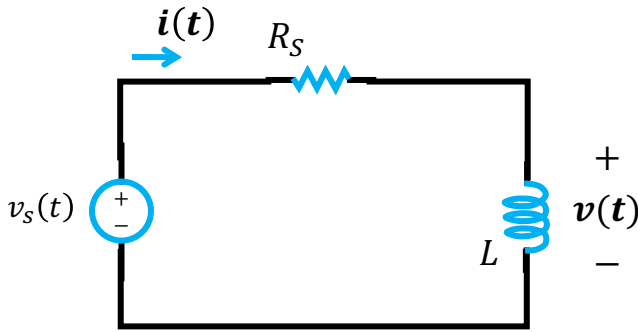**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to a complex forcing function  $v_S = V_S e^{j\omega t}$ .



$$j\omega I_S e^{j(\omega t + \varphi)} + \frac{R}{L} I_S e^{j(\omega t + \varphi)} = \frac{1}{L} V_S e^{j\omega t}$$


$$j\omega I_S e^{j\varphi} + \frac{R}{L} I_S e^{j\varphi} = \frac{1}{L} V_S$$

$$I_S e^{j\varphi} = \frac{V_S}{R + j\omega L}$$

$$\blacktriangleright \begin{cases} I_S = \frac{V_S}{\sqrt{R^2 + \omega^2 L^2}} \\ \varphi = -\tan^{-1} \frac{\omega L}{R} \end{cases}$$

# Example 10

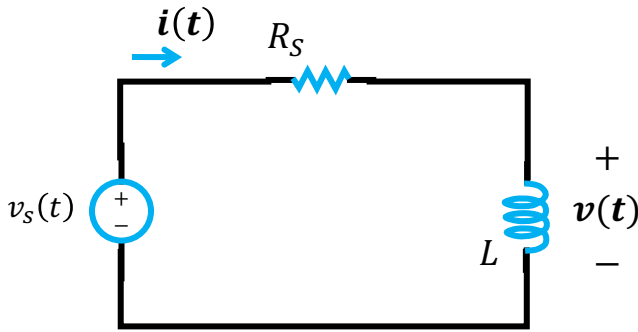**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to a complex forcing function  $\mathbb{V}_S = V_S e^{j\omega t}$ .



$$i_S(t) = I_S e^{j(\omega t + \varphi)}$$

$$= I_S \cos(\omega t + \varphi) + j I_S \sin(\omega t + \varphi)$$

$$\Re[i_S(t)] = I_S \cos(\omega t + \varphi)$$

$$\begin{cases} I_S = \frac{V_S}{\sqrt{R^2 + \omega^2 L^2}} \\ \varphi = -\tan^{-1} \frac{\omega L}{R} \end{cases}$$

$$= I_S (\cos \omega t \cos \varphi + \sin \omega t \sin \varphi)$$


$$= K_1 \cos(\omega t) + K_2 \sin(\omega t)$$

$$\text{where } \begin{cases} K_1 = V_S \frac{R}{R^2 + \omega^2 L^2} \\ K_2 = V_S \frac{-\omega L}{R^2 + \omega^2 L^2} \end{cases}$$



# Example 10

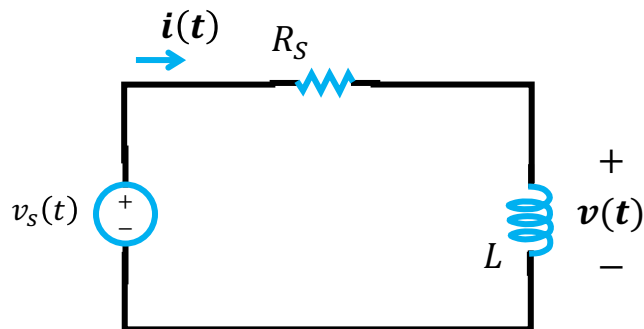**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to a complex forcing function  $\mathbb{V}_S = V_S e^{j\omega t}$ .



## METHODS 2

- Consider the impedance circuit
- According to KVL

$$\mathbb{V}_S = R\mathbb{I}_S + j\omega L\mathbb{I}_S \quad \blacktriangleright \quad \mathbb{I}_S = \frac{\mathbb{V}_S}{R + j\omega L}$$

- The real part of  $\mathbb{I}_S$

$$\Re[\mathbb{I}_S] = \frac{V_S}{R^2 + \omega^2 L^2} [R \cos(\omega t) + \omega L \sin(\omega t)]$$



$$\Re[i_S(t)]$$


Solution from the differential equation

$$i_S(t) = I_S e^{j(\omega t + \varphi)}$$

$$\left\{ \begin{array}{l} I_S = \frac{V_S}{\sqrt{R^2 + \omega^2 L^2}} \\ \varphi = -\tan^{-1} \frac{\omega L}{R} \end{array} \right.$$



# Recall: Sinusoidal forcing function

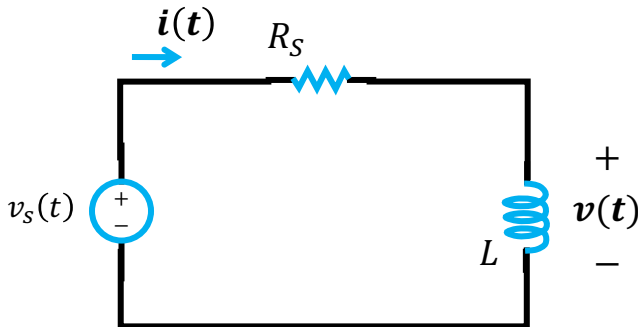**QUESTION:** Assume there is no charge on the inductor  $L$  at  $t = -\infty$ . Find the voltage response to the sinusoidal forcing function.



$$\frac{d}{dt}i(t) + \frac{R}{L}i(t) = \frac{1}{L}v_s(t)$$

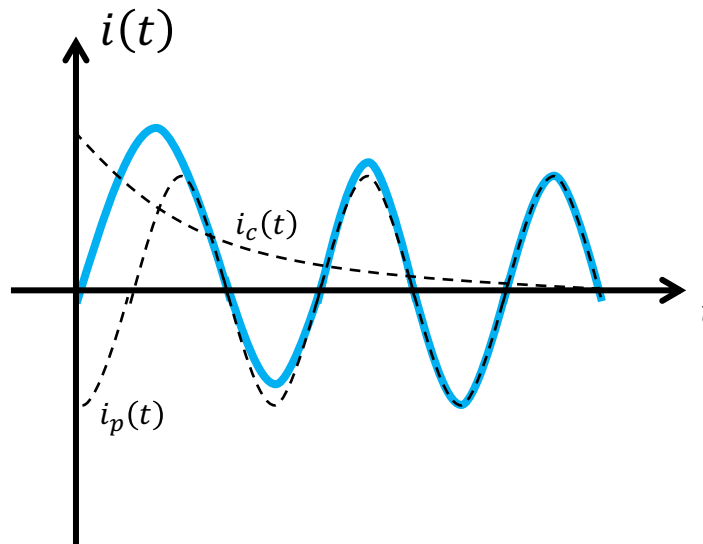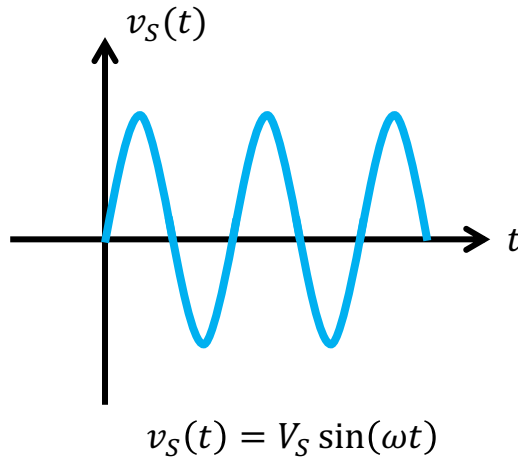Solution  $i(t) = K_1 \cos(\omega t) + K_2 \sin(\omega t) + K_3 e^{-\frac{R}{L}t}$




where

$$\begin{cases} K_1 = V_S \frac{-\omega L}{R^2 + \omega^2 L^2} \\ K_2 = V_S \frac{R}{R^2 + \omega^2 L^2} \\ K_3 = V_S \frac{\omega L}{R^2 + \omega^2 L^2} \end{cases}$$


# Circuit analysis in TIME domain

**Method can be applied to ALL circuit**

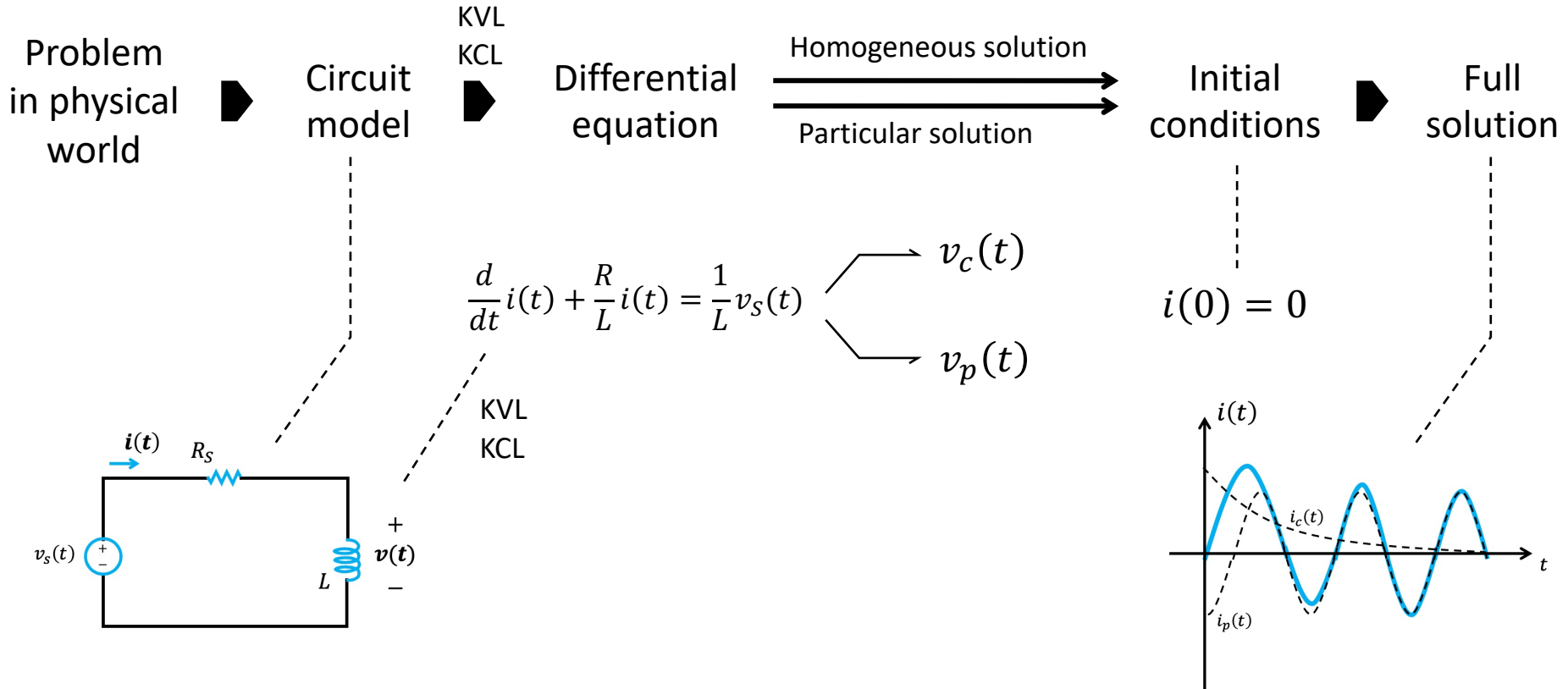

# Circuit analysis in TIME domain

## Method for ALL circuit

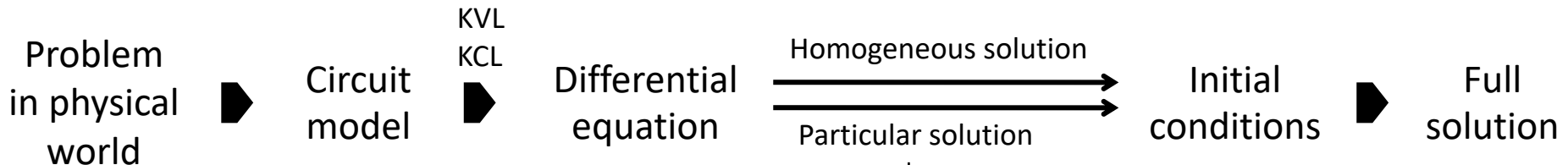


## Method ONLY for LINEAR circuit



$\Re[*]$

$$\Re[\mathbb{I}_S] = \frac{V_S}{R^2 + \omega^2 L^2} [R \cos(\omega t) - \omega L \sin(\omega t)]$$
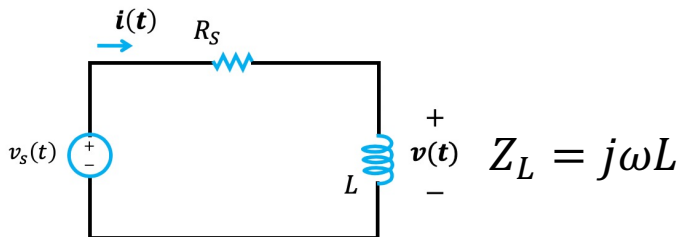
$$V_S = R\mathbb{I}_S + j\omega L\mathbb{I}_S$$






# Outlines

- Response to different forcing function

- Ramping forcing function
- Sinusoidal forcing function

- Complex forcing function

- Impedance & admittance
- KVL&KCL / Superposition / Equivalency

			
<i>i-v</i> relation	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
<i>v-i</i> relation	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
<b>Impedance</b>	<b><math>R</math></b>	<b><math>\frac{1}{j\omega C}</math></b>	<b><math>j\omega L</math></b>

- AC steady-state analysis


- Impedance circuit analysis for steady-state solution in LINEAR circuit

- Complex Power analysis**
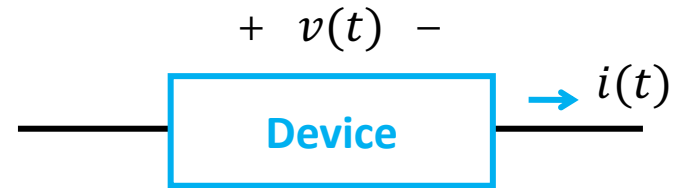
# Recall: Inst./Avg. power & eff. v/i

Given the voltage  $v(t) = V_P \cos(\omega t + \varphi_V)$

Given the current  $i(t) = I_P \cos(\omega t + \varphi_I)$




- Instantaneous power  $p(t) = \frac{1}{2} V_P I_P \cos(\varphi_V - \varphi_I) + \frac{1}{2} V_P I_P \cos(2\omega t + \varphi_V + \varphi_I)$

- Average power  $\bar{P} = \frac{V_P}{\sqrt{2}} \frac{I_P}{\sqrt{2}} \cos(\varphi_V - \varphi_I) = v_{rms} i_{rms} \cos(\varphi_V - \varphi_I)$

- Effective voltage  $v_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} = \frac{V_P}{\sqrt{2}}$

- Effective current  $i_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt} = \frac{I_P}{\sqrt{2}}$

# Complex power

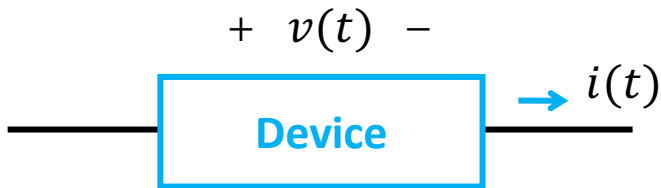

$$\text{Given } v(t) = V_s \cos(\omega t + \varphi_V) \quad \rightarrow \quad V_s \angle \varphi_V \quad \rightarrow \quad \mathbb{V} = V_s e^{j\varphi_V}$$

$$\text{Given } i(t) = I_s \cos(\omega t + \varphi_I) \quad \rightarrow \quad I_s \angle \varphi_I \quad \rightarrow \quad \mathbb{I} = I_s e^{j\varphi_I}$$

**DEFINE COMPLEX POWER**       $\mathbb{S} = \frac{1}{2} \mathbb{V} \mathbb{I}^*$

$$\mathbb{S} = \frac{1}{2} \mathbb{V} \mathbb{I}^* = \frac{1}{2} (V_s e^{j\varphi_V}) (I_s e^{-j\varphi_I}) = \frac{1}{2} V_s I_s e^{j(\varphi_V - \varphi_I)}$$

$$= \frac{1}{2} V_s I_s [\cos(\varphi_V - \varphi_I) + j \sin(\varphi_V - \varphi_I)]$$

# Complex power

$$S = \underbrace{\frac{1}{2} V_s I_s \cos(\varphi_V - \varphi_I)}_{\text{Average power } \bar{P}} + j \underbrace{\frac{1}{2} V_s I_s \sin(\varphi_V - \varphi_I)}_{\text{Reactive power } Q}$$

**Average power  $\bar{P}$  + Reactive power  $Q$  = COMPLEX POWER  $S$**

- **Average power**       $\bar{P} = \Re\{S\} = V_{rms} I_{rms} \cos(\varphi_V - \varphi_I) = I_{rms}^2 R \cos(\varphi_V - \varphi_I)$   
(unit: watt/W)
- **Reactive power**       $Q = \Im\{S\} = V_{rms} I_{rms} \sin(\varphi_V - \varphi_I) = I_{rms}^2 X \sin(\varphi_V - \varphi_I)$   
(unit: Volt-Ampere Reactive/VAR)
- **COMPLEX POWER**       $S = \bar{P} + jQ$   
(unit: Volt-Amp/VA)



# Complex power


- **COMPLEX POWER**  $\mathbf{S} = \bar{P} + jQ$

$$\bar{P} = \Re\{\mathbf{S}\} = V_{rms}I_{rms} \cos(\varphi_V - \varphi_I)$$

$$Q = \Im\{\mathbf{S}\} = jV_{rms}I_{rms} \sin(\varphi_V - \varphi_I)$$

- Define **power factor**  $pf = \frac{P}{V_{rms}I_{rms}} = \cos(\varphi_V - \varphi_I)$
- Define **power angle**  $\tan(\varphi_V - \varphi_I) = \frac{Q}{P}$

# Recall: Max. Power Trans. in DC Circ.

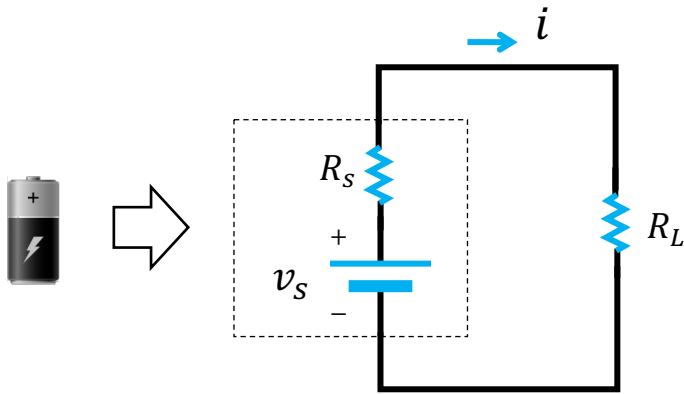

## Practical voltage source

- Voltage of  $R_L$

$$v_{R_L} = v_s - iR_s$$


- Power at the load  $R_L$

$$P_L = v_{R_L} i = (v_s - iR_s) i = -R_s \left( i^2 - \frac{v_s}{R_s} i \right) = -R_s \left( i - \frac{1}{2} \frac{v_s}{R_s} \right)^2 + \frac{1}{4} \frac{v_s^2}{R_s}$$
$$\leq \frac{1}{4} \frac{v_{s,rms}^2}{R_s}$$

**The maximum power being absorbed by the load**

- When  $R_s = R_L$   $P_L = P_{L,max} = \frac{1}{4} \frac{v_{s,rms}^2}{R_s}$

# Maximum Average Power Transfer

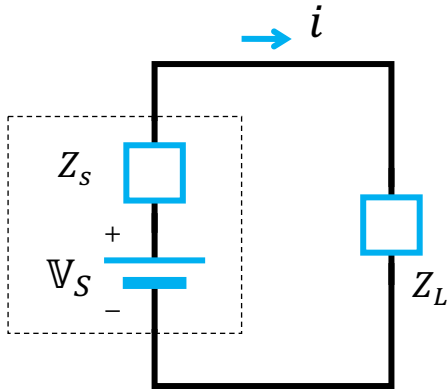

Assume

$$\mathbb{V}_S = V_S \angle \theta_{v_S}$$

$$Z_S = R_S + jX_S$$

$$Z_L = R_L + jX_L$$

- The current through  $Z_L$  is  $\mathbb{I}_L = I_L \angle \theta_{i_L}$

$$\mathbb{I}_L = \frac{\mathbb{V}_S}{Z_S + Z_L} = \frac{\mathbb{V}_S}{(R_S + jX_S) + (R_L + jX_L)}$$


$$\rightarrow I_L = \frac{V_S}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}}$$

- The voltage on  $Z_L$  is  $\mathbb{V}_L = V_L \angle \theta_{v_L}$

$$\mathbb{V}_L = \frac{\mathbb{V}_S Z_L}{Z_S + Z_L} = \frac{\mathbb{V}_S (R_L + jX_L)}{(R_S + jX_S) + (R_L + jX_L)}$$

$$\rightarrow V_L = \frac{V_S \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}}$$

# Maximum Average Power Transfer

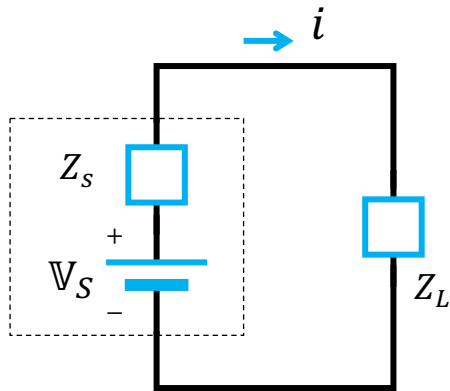

$$\begin{cases} I_L = \frac{V_S}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}} \\ V_L = \frac{V_S \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}} \end{cases}$$

- The average power at the load  $Z_L$

$$P_L = V_{rms} I_{rms} \cos(\theta_{v_L} - \theta_{i_L}) \quad \text{where} \quad \theta_{v_L} - \theta_{i_L} = \cos^{-1} \left( \frac{R_L}{\sqrt{R_L^2 + X_L^2}} \right)$$

$$= \frac{V_{rms}^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \leq \frac{V_{rms}^2 R_L}{(R_S + R_L)^2} \leq \frac{1}{4} \frac{V_{rms}^2}{R_S}$$

- when  $\begin{cases} R_S = R_L \\ X_S = -X_L \end{cases} \rightarrow Z_S = Z_L^* \quad P_{L,max} = \frac{1}{4} \frac{V_{rms}^2}{R_S}$

# Outlines

- Response to different forcing function

- Ramping forcing function
- Sinusoidal forcing function

- Complex forcing function




- Impedance & admittance
- KVL&KCL / Superposition / Equivalency

- AC steady-state analysis

- Impedance circuit analysis for steady-state solution in LINEAR circuit

- Complex Power analysis

- Definition of complex power/average power/reactive power
- Maximum average power transfer

			
<i>i-v</i> relation	$i = \frac{v}{R}$	$i(t) = C \frac{dv(t)}{dt}$	$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$
<i>v-i</i> relation	$v = iR$	$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$	$v(t) = L \frac{di(t)}{dt}$
<b>Impedance</b>	<b><math>R</math></b>	<b><math>\frac{1}{j\omega C}</math></b>	<b><math>j\omega L</math></b>

# Reading tasks & learning goals

- Reading tasks
  - Basic Engineering Circuit Analysis, 10<sup>th</sup> edition
    - Chapter 8.1-8.8 & 9.1-9.6
- Learning goals
  - Know how to solve response with **ramp/sin. forcing functions**
  - Understand the basic characteristics of sinusoidal functions
  - Know how to calculate **impedance/admittance**
  - Know how to perform **AC steady-state analysis**
  - Know how to calculate **real power/reactive power/complex power/power factor** in AC circuits
  - Be able to calculate the **maximum average power transfer** for a load in an AC circuit