

Fundamentals of Electronic Circuits and Systems II

# *pn* Junction & Diodes

Milin Zhang

Dept of EE, Tsinghua University

# Outline

- Introduction to semiconductors
- Diodes

# Semiconductor material

**SEMICONDUCTORS** are materials whose conductivity lies between that of conductors and insulators


Single-element semiconductors

1																	18									
H 1.01																	He 4.00									
2	3	4											5	6	7	8	9	10								
Li 6.94	Be 9.01											B 10.81	C 12.01	N 14.01	O 16.00	F 19.00	Ne 20.18									
11	12	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18									
Na 22.99	Mg 24.31											Al 26.98	Si 28.09	P 30.97	S 32.06	Cl 35.45	Ar 39.95									
19	20	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36									
K 39.10	Ca 40.08	Sc 44.96	Ti 47.88	V 50.94	Cr 51.99	Mn 54.94	Fe 55.85	Co 58.93	Ni 58.69	Cu 63.55	Zn 65.38	Ga 69.72	Ge 72.63	As 74.92	Se 78.97	Br 79.90	Kr 83.80									
37	38	39	40	41	42	43	44	45	46	47	48	49	50	51	52	53	54									
Rb 85.47	Sr 87.62	Y 88.91	Zr 91.22	Nb 92.91	Mo 95.95	Tc 98.91	Ru 101.07	Rh 102.91	Pd 106.42	Ag 107.87	Cd 112.41	In 114.82	Sn 118.71	Sb 121.76	Te 127.6	I 126.90	Xe 131.29									
55	56	57-71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86									
Cs 132.91	Ba 137.33											Hf 178.49	Ta 180.95	W 183.85	Re 186.21	Os 190.23	Ir 192.22	Pt 195.08	Au 196.97	Hg 200.59	Tl 204.38	Pb 207.20	Bi 208.98	Po [208.9]	At 209.98	Rn 222.02
87	88	89-103	104	105	106	107	108	109	110	111	112	113	114	115	116	117	118									
Fr 223.02	Ra 226.03											Rf [261]	Db [262]	Sg [266]	Bh [264]	Hs [269]	Mt [278]	Ds [281]	Rg [280]	Cn [285]	Nh [286]	Fl [289]	Mc [289]	Lv [293]	Ts [294]	Og [294]
57	58	59	60	61	62	63	64	65	66	67	68	69	70	71												
La 138.91	Ce 140.12	Pr 140.91	Nd 144.24	Pm 144.91	Sm 150.36	Eu 151.96	Gd 157.25	Tb 158.93	Dy 162.50	Ho 164.93	Er 167.26	Tm 168.93	Yb 173.06	Lu 174.97												
89	90	91	92	93	94	95	96	97	98	99	100	101	102	103												
Ac 227.03	Th 232.04	Pa 231.04	U 238.03	Np 237.05	Pu 244.06	Am 243.06	Cm 247.07	Bk 247.07	Cf 251.08	Es [254]	Fm 257.10	Md 258.10	No 259.10	Lr [262]												

# Silicon crystal


@0K

all bonds are intact & no free electrons

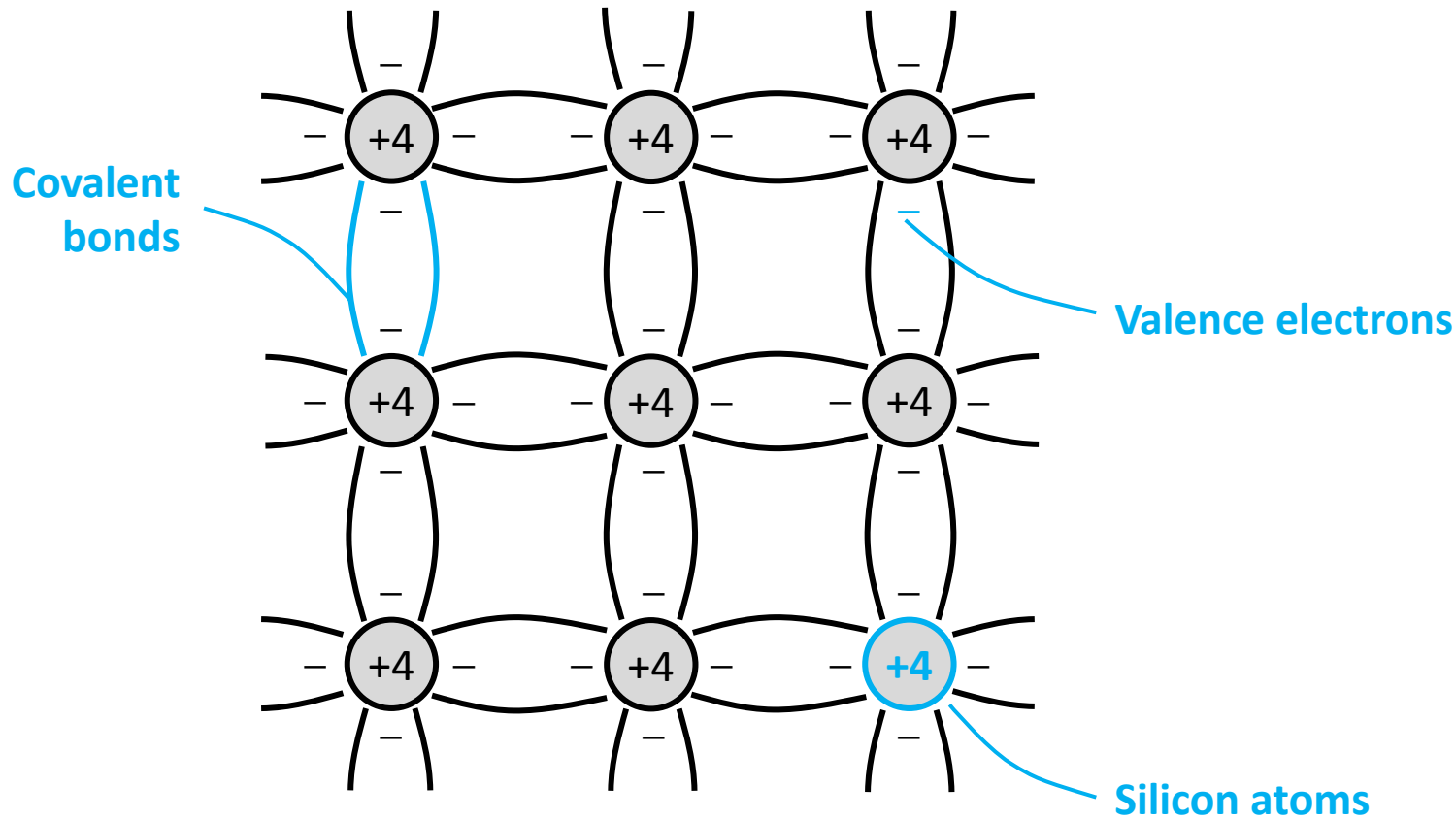


# Silicon crystal

@room temperature

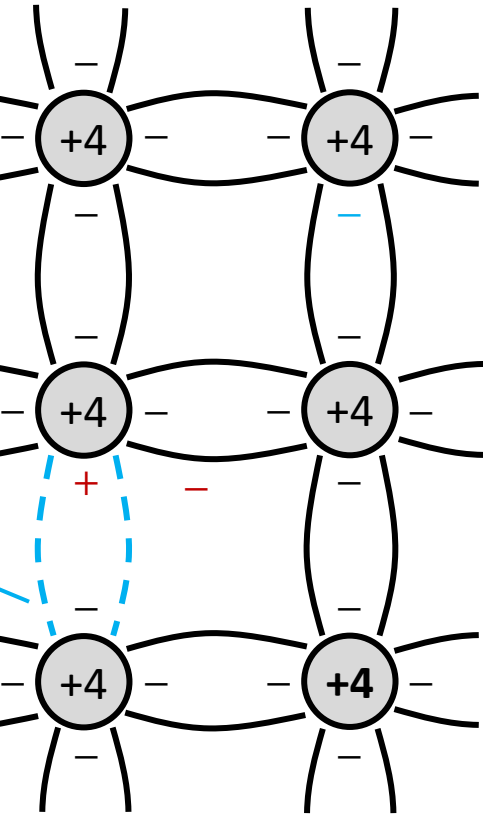


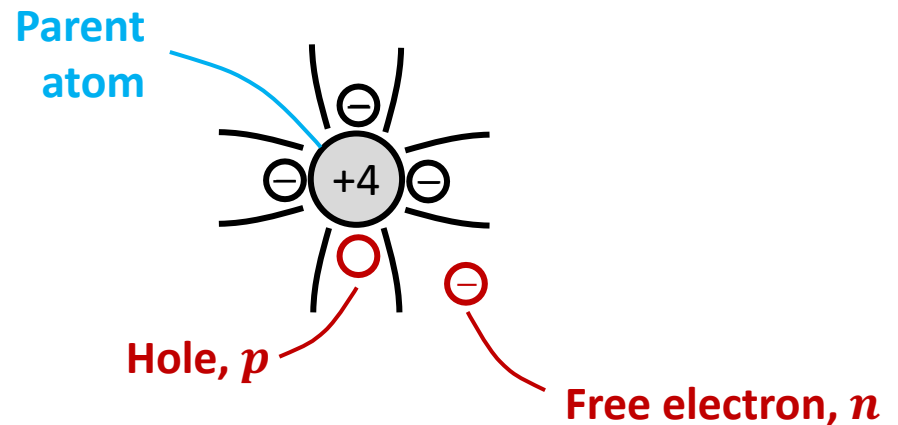- **free electron** wanders away from its parent atom
- A net positive charge left at the parent atom
- A “**hole**” left at the parent atom





# Silicon crystal

@room temperature

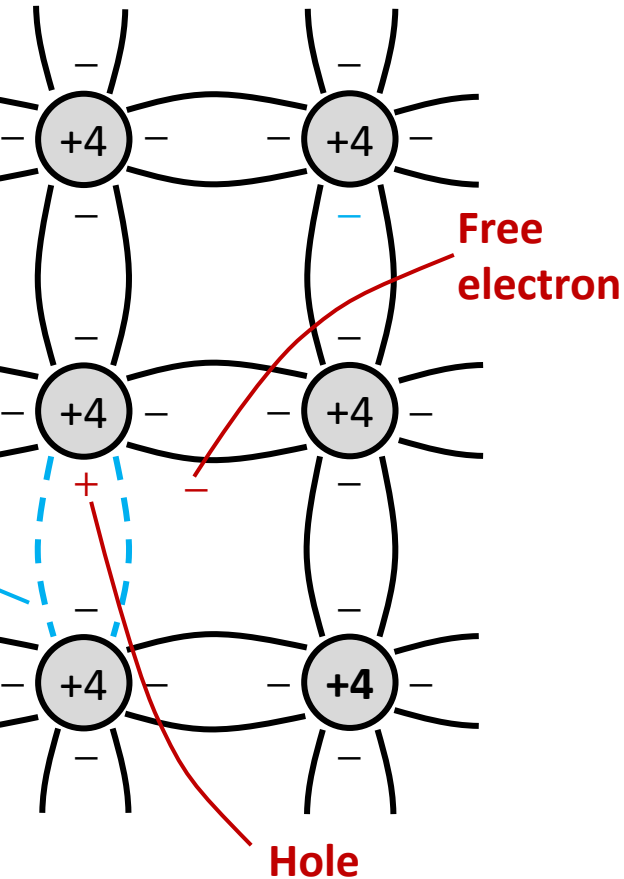


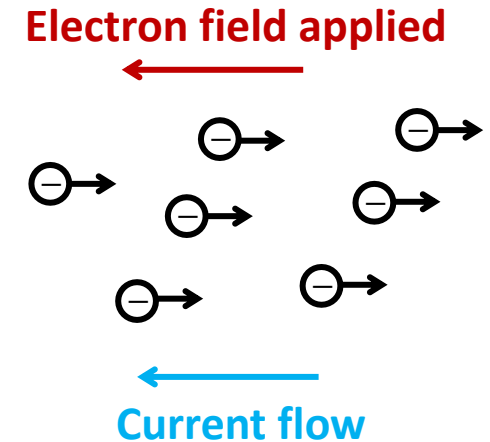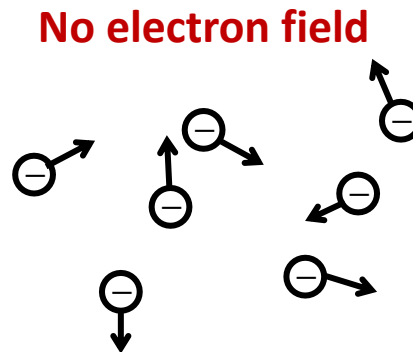- free electron wanders away from its parent atom
- A net positive charge left at the parent atom
- A “hole” left at the parent atom
- **Current** generated when an **electric field** applied





# Silicon crystal

@room temperature

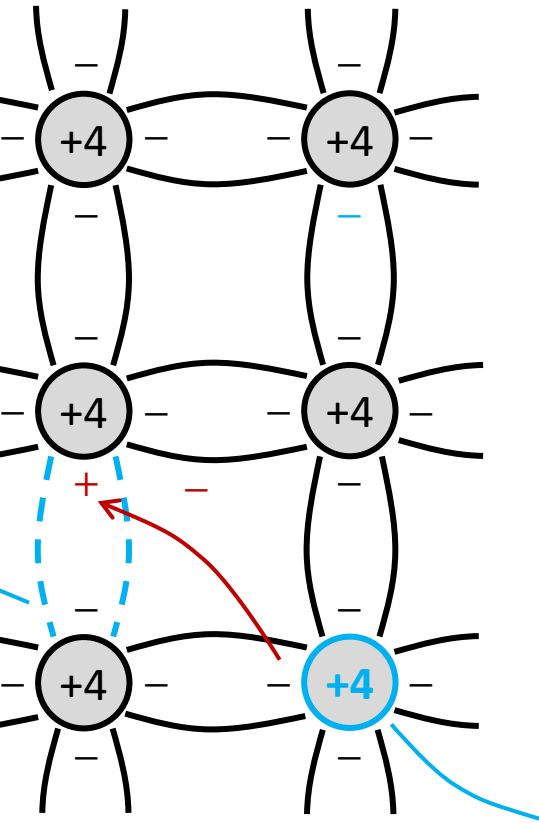

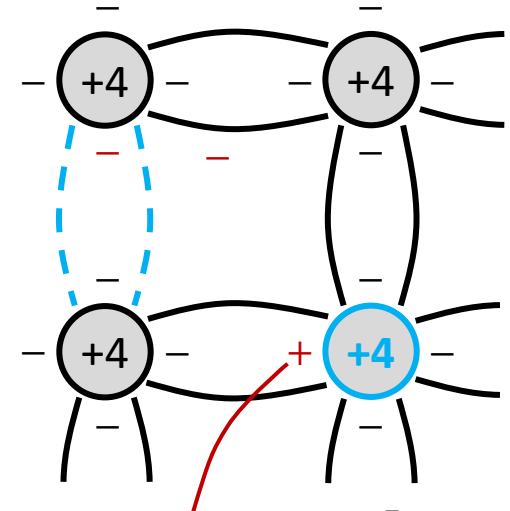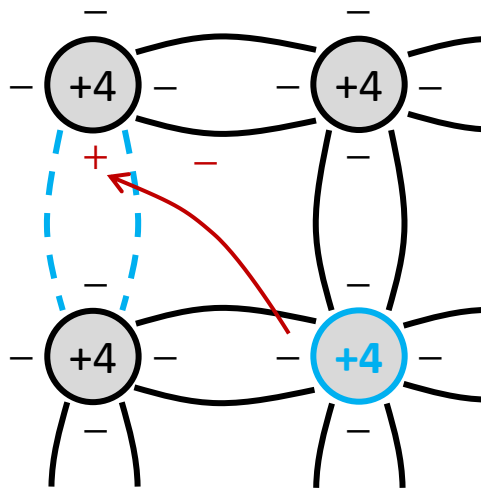
- free electron wanders away from its parent atom
- A net positive charge left at the parent atom
- A “hole” left at the parent atom
- Current generated when an electric field applied
- Electron from neighboring atom may fill up the hole, but generating a new hole – **RECOMBINATION**



**A new hole**

# Silicon crystal

@room temperature

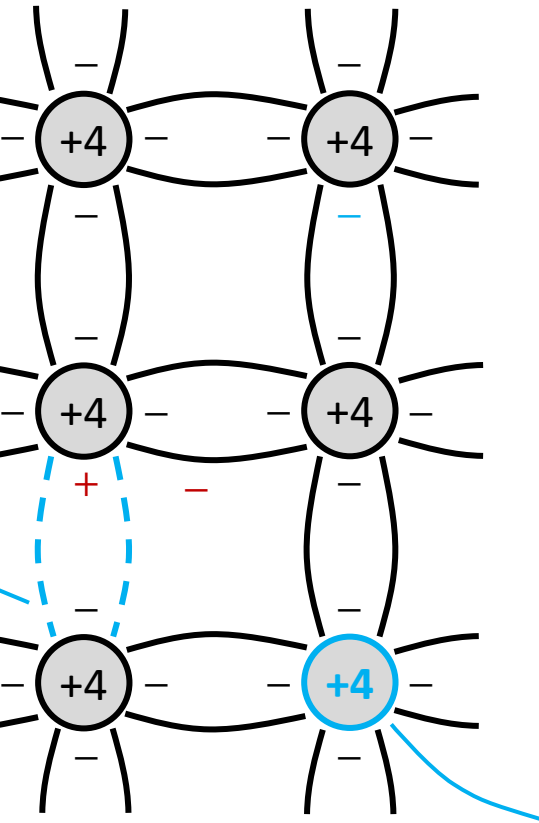


- free electron wanders away from its parent atom
- A net positive charge left at the parent atom
- A “hole” left at the parent atom
- Current generated when an electric field applied
- Electron from neighboring atom may fill up the hole, but generating a new hole - RECOMBINATION
- **Charge of a hole =  $-$ charge of an electron**



# Silicon crystal
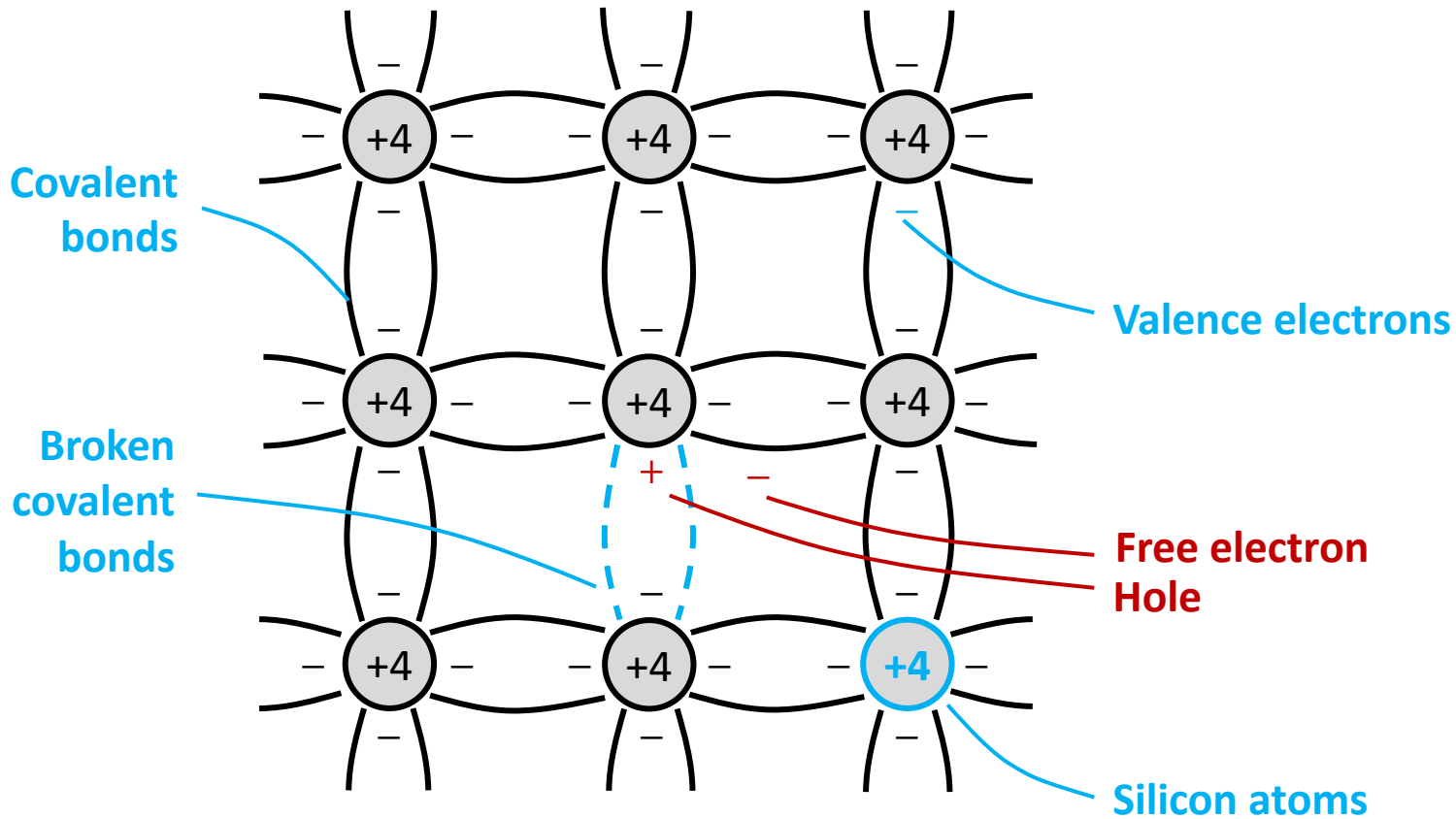
## 2 carriers in semiconductor: free electron & hole




# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - **Doped semiconductors**
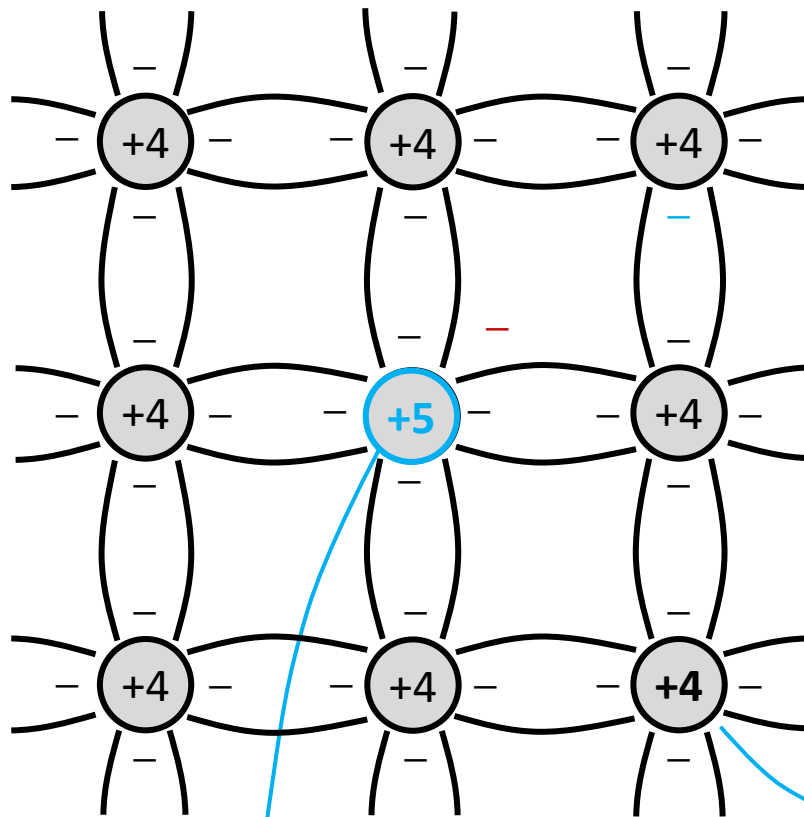
# Doped semiconductors

A key issue of nature silicon crystal:

The **concentrations** of carriers are **too low** to conduct appreciable current



Impurity atom

Silicon atoms


Solution: **DOPING**

- Introduce **impurity atoms**
- To increase concentration of  $n$ , doping element with a **valence of 5**, e.g.  $P$   
→  **$n$  type doped silicon**
- Each phosphorus atom **donates** a free electron  
the  $P$  atom → **DONOR**
- For the  **$n$  type doped silicon**  
**Majority** charge carriers – electrons  
**Minority** charge carriers - holes
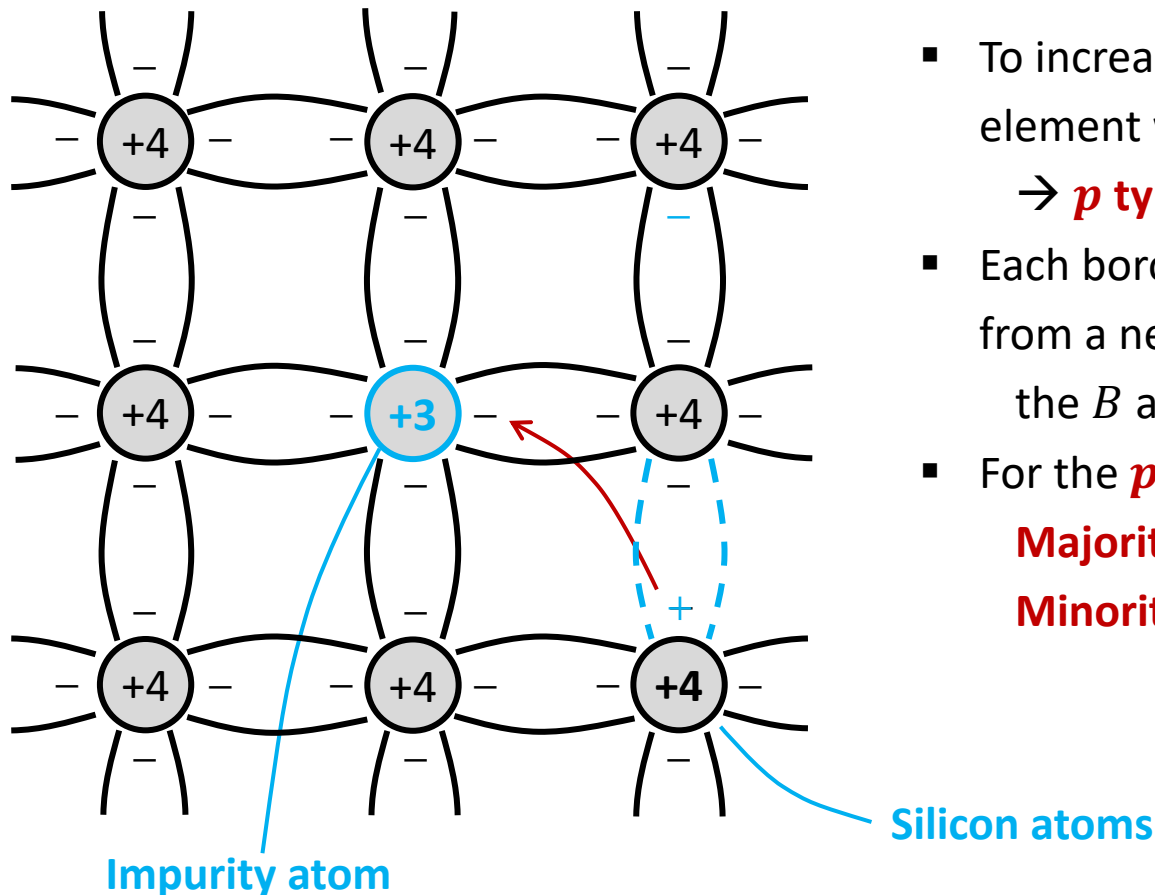
# Doped semiconductors

A key issue of nature silicon crystal:

The **concentrations** of carriers are **too low** to conduct appreciable current





- To increase concentration of  $p$ , doping element with a **valence of 3**, e.g.  $B$   
→  **$p$  type doped silicon**
- Each boron atom **accepts** an electron from a neighboring atom  
the  $B$  atom → **ACCEPTOR**
- For the  **$p$  type doped silicon**  
**Majority** charge carriers – holes  
**Minority** charge carriers - electrons

# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - **Current flow in semiconductor**

# Recall: where does current come from?

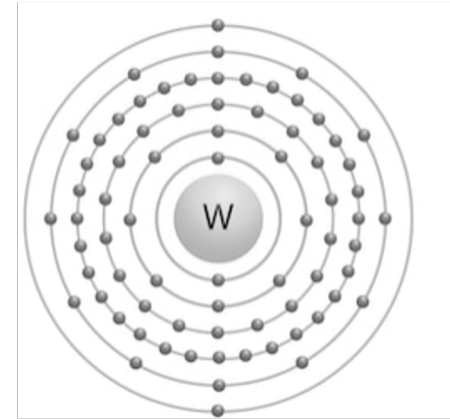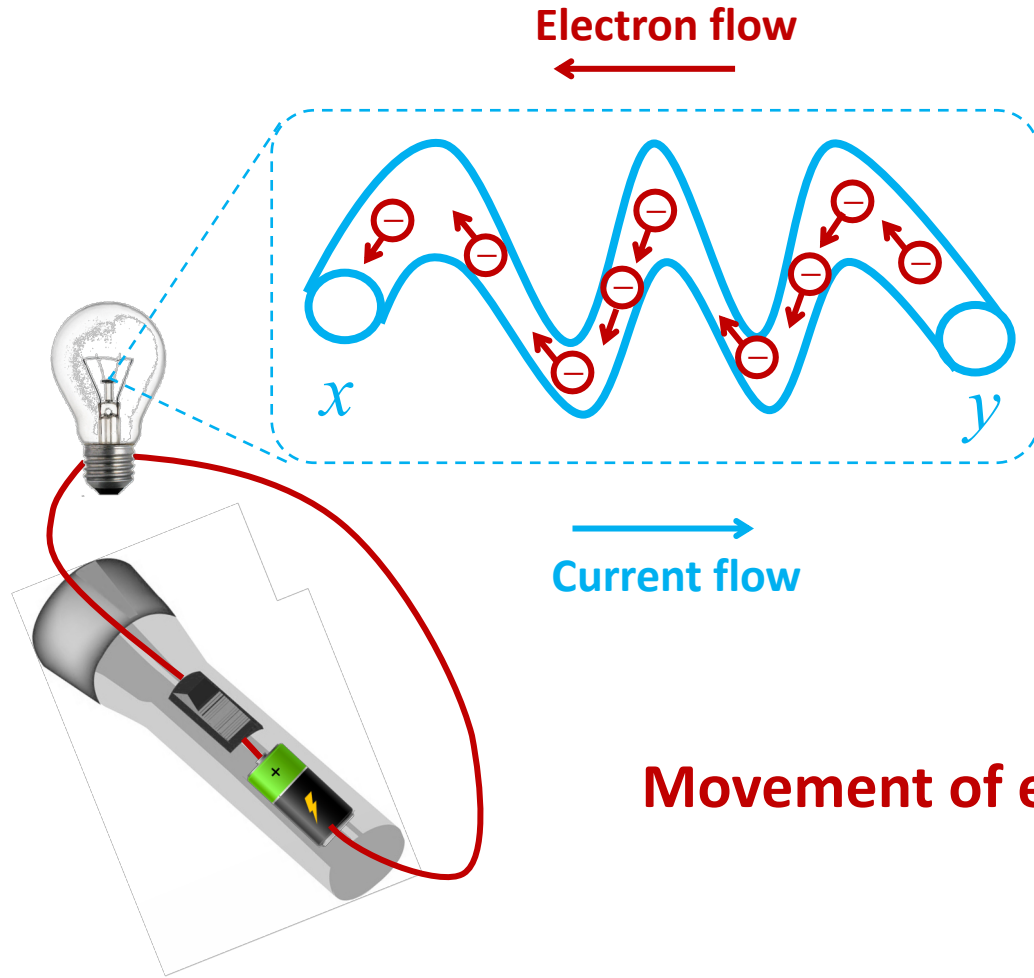

Tungsten


**Movement of electrons generates current**

# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**
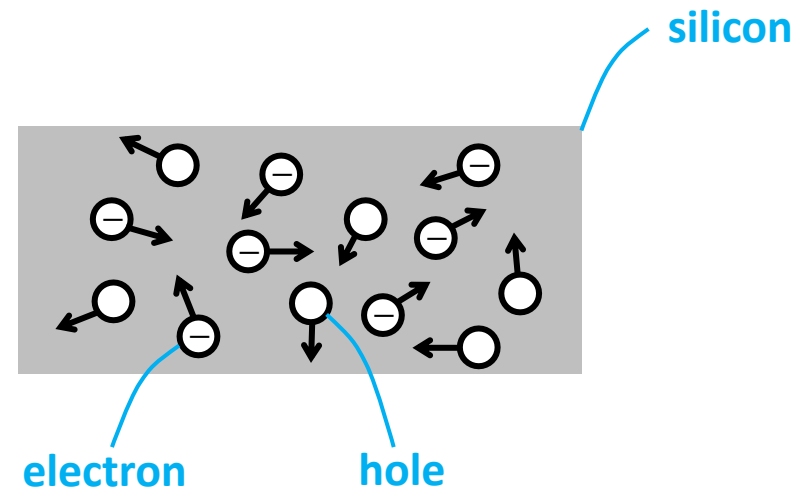
## Movement I – drift

- Free electrons and holes **randomly move** in a silicon
- An **electrical field  $E$**  is applied in a semiconductor




# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**
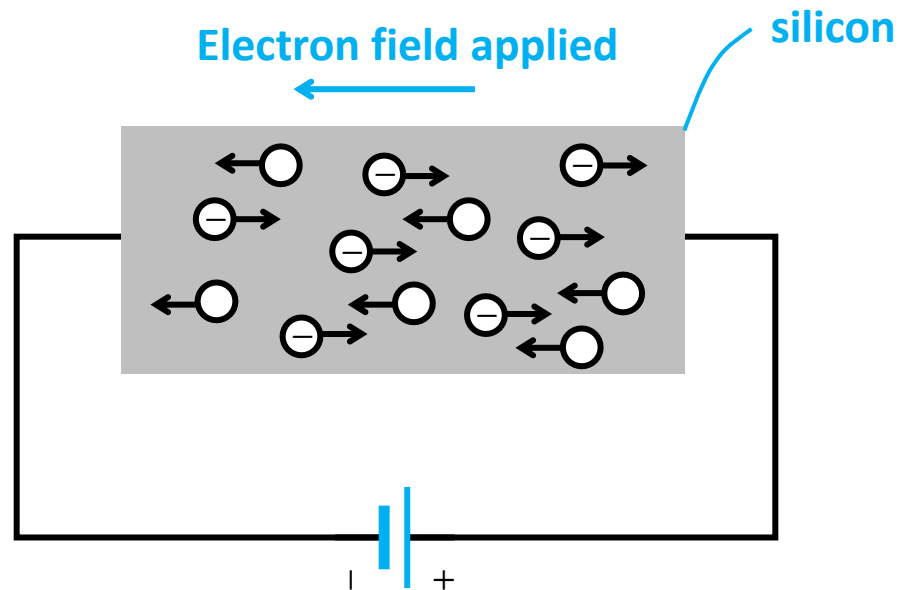
## Movement I – drift

- Free electrons and holes **randomly move** in a silicon
- An **electrical field  $E$**  is applied in a semiconductor
- Holes moves in the direction of  $E$
- Electrons moves in the opposite direction of  $E$





# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**

## Movement I – drift

- Current density of the holes

$$J_p = q p \mu_p E$$

hole concentration


hole mobility

- Current density of the electrons

$$J_n = q n \mu_n E$$

electron concentration

electron mobility

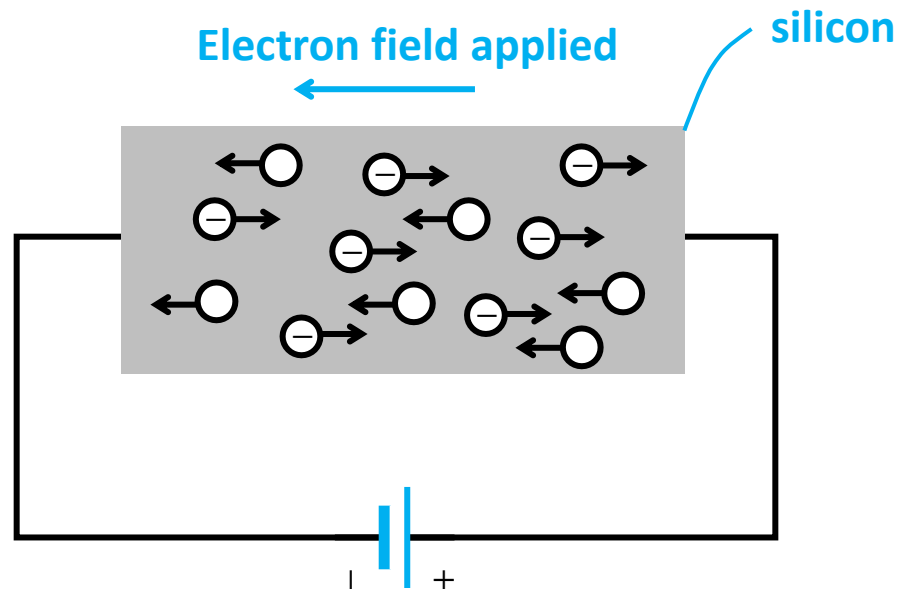

# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**

## Movement I – drift

- Current density of the holes

$$J_p = qp\mu_p E$$

- Current density of the electrons


$$J_n = qn\mu_n E$$

- Total drift current density

$$J = J_p + J_n = qp\mu_p E + qn\mu_n E$$

Since  $J = \sigma E$

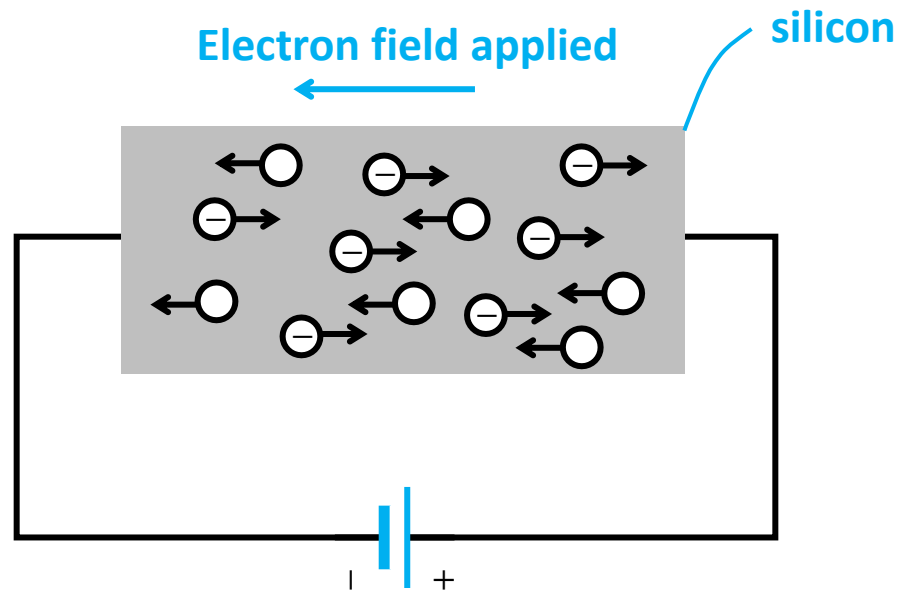- The conductivity  $\sigma = q(p\mu_p + n\mu_n)$



# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**

## Movement II – diffusion

- Why there is carrier diffusion? – carrier **density gradient**

- Current density of the holes

$$J_p = -qD_p \frac{dp(x)}{dx}$$

Diffusion constant of the holes

hole concentration gradient

- Current density of the electrons

$$J_n = -qD_n \frac{dn(x)}{dx}$$

Diffusion constant of the electron

electron concentration gradient



# The current flow in semiconductors

**Movement of carriers (electrons/holes) in semiconductors generates current**

**2 types of movement – DRIFT & DIFFUSION**

- Total drift current density  $J = J_p + J_n = qp\mu_p E + qn\mu_n E$
- Total diffusion current density  $J = -q \left( D_p \frac{dp(x)}{dx} + D_n \frac{dn(x)}{dx} \right)$
- A relationship between diffusion constant and mobility


$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T \quad \leftarrow \text{thermal voltage} \quad V_T = \frac{kT}{q}$$

# Outline


- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - **The *pn* junction**

# The two types doped silicon

*p* type doped silicon

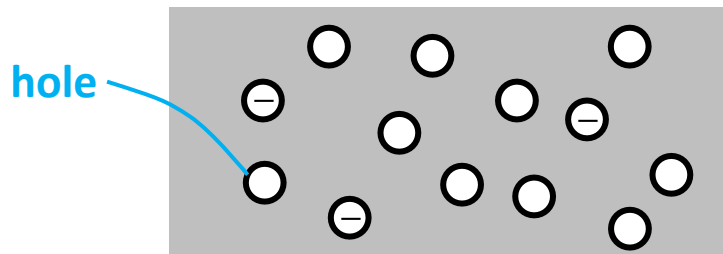

*n* type doped silicon

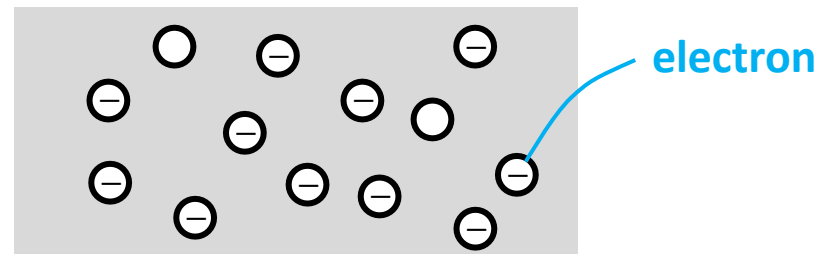

majority carrier

hole

electron


minority carrier

electron

hole

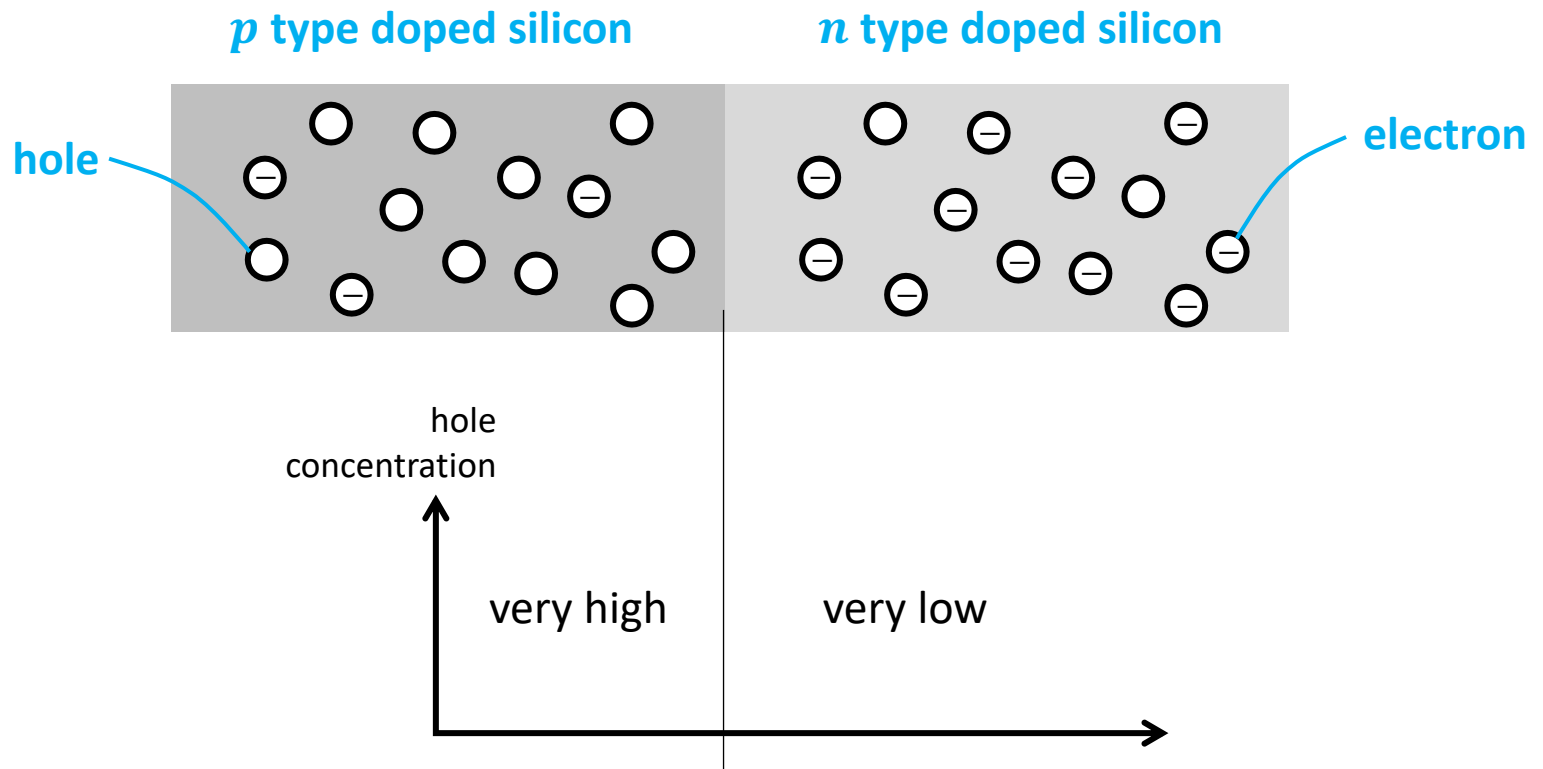
# The $pn$ junction

Step 1: a  $p$ -type & a  $n$ -type semiconductor brought into close contact with each other, a  **$pn$  junction** is generated


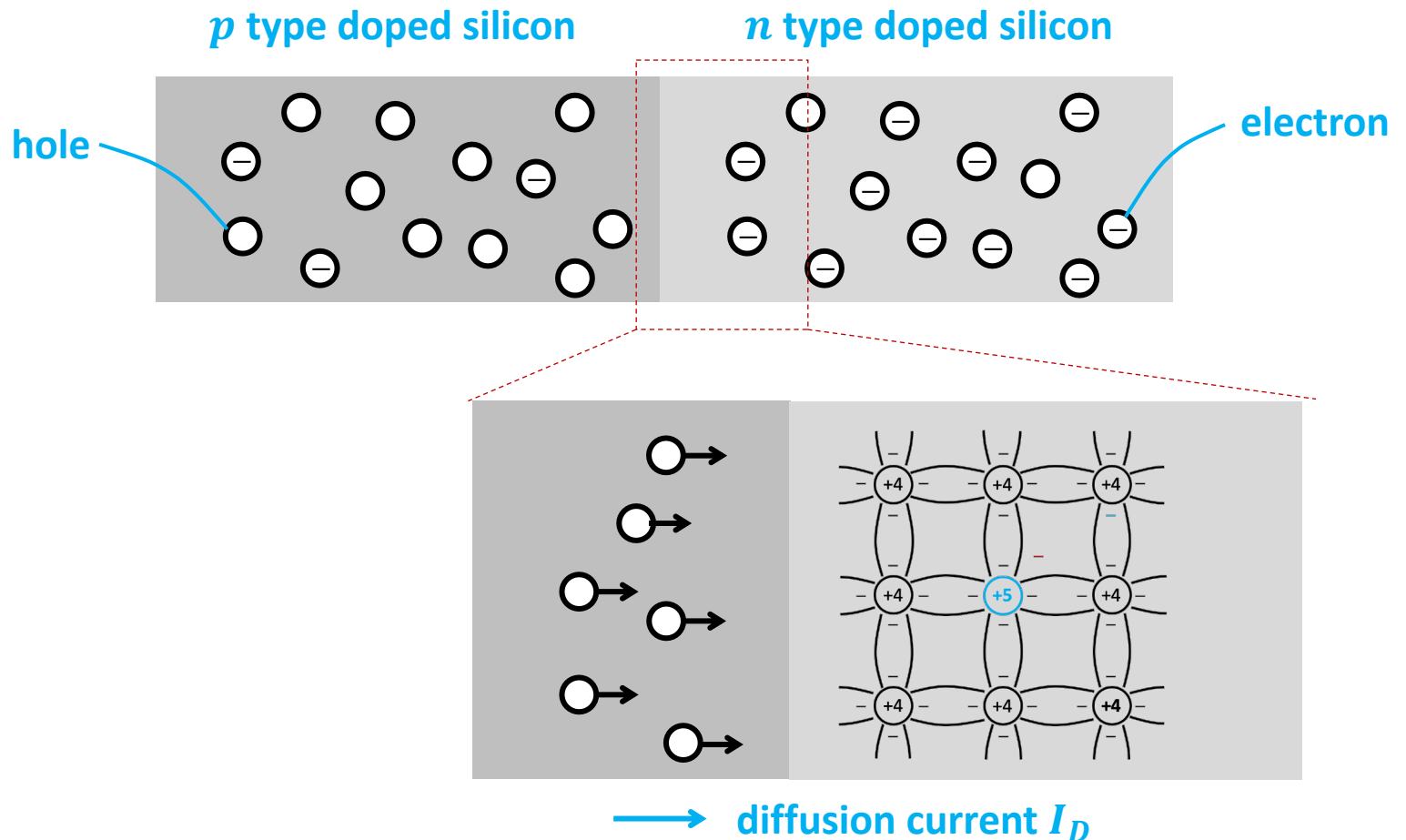
# The $pn$ junction


Step 2: diffusion current generated due to concentration gradient





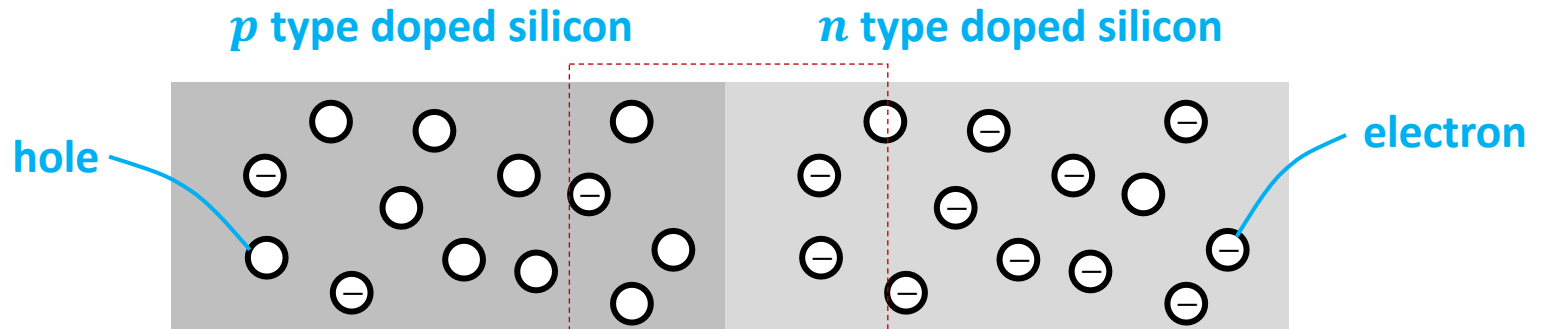
# The $pn$ junction

Step 3: the holes crossed the junction and recombine with the majority (electron) in the  $n$  type doped silicon


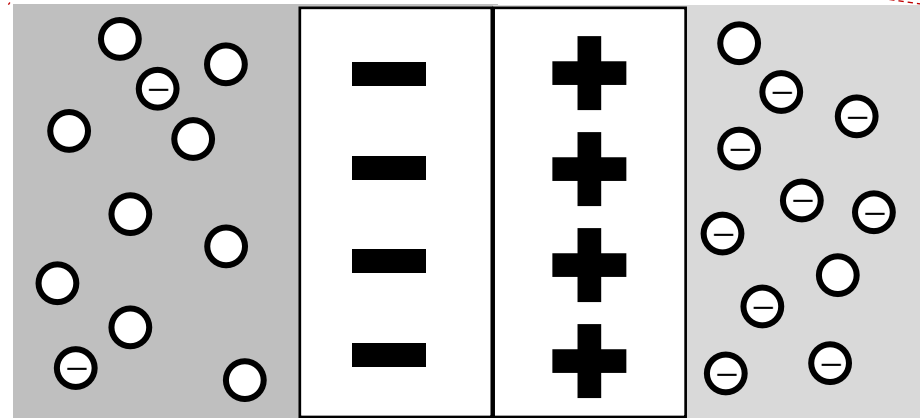
## Carrier-depletion region


- Exist in both sides
- Uncovered charges
- $n$  is more positive than  $p$
- Electronic field generated



**Depletion region**

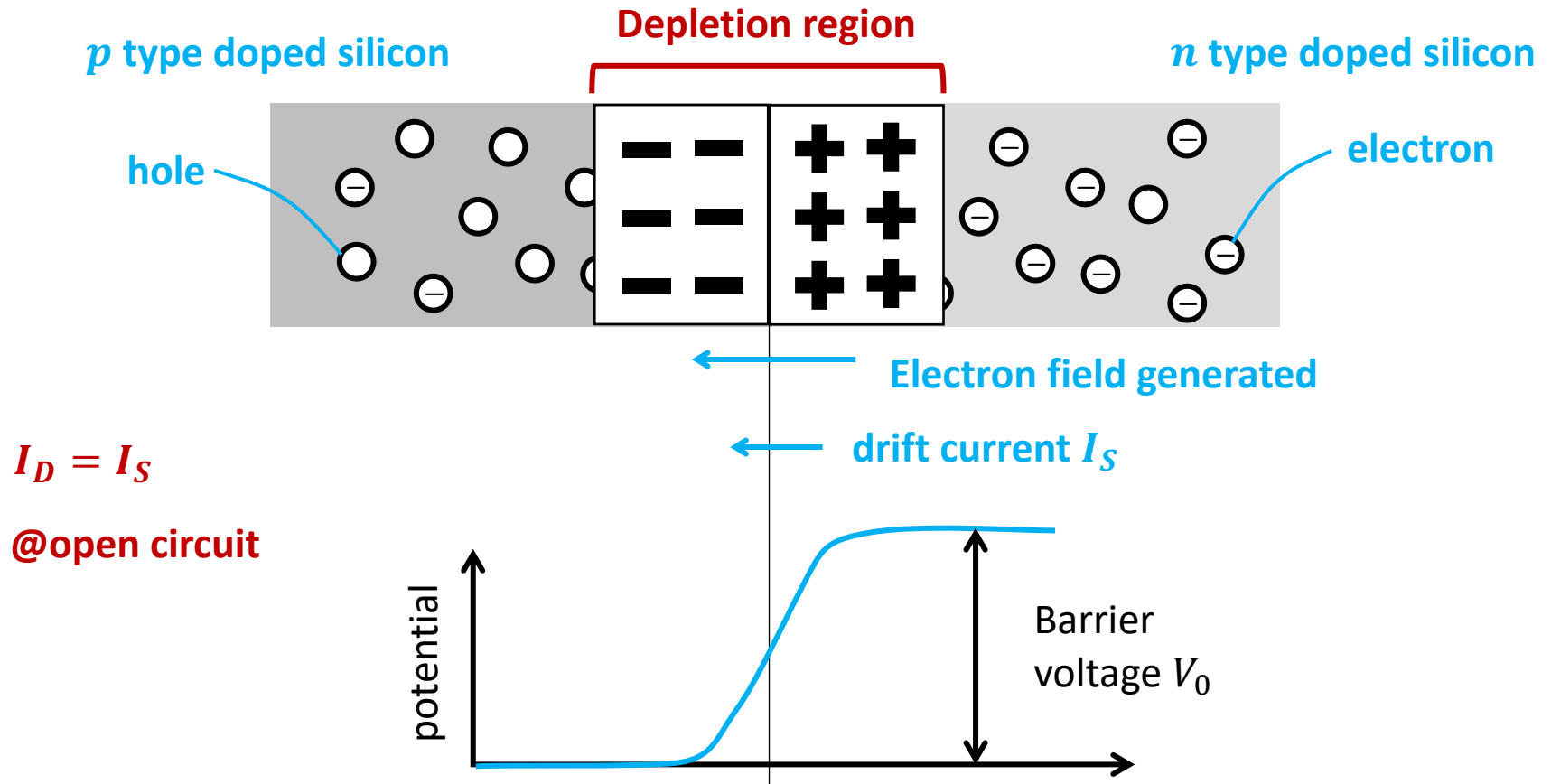
# The $pn$ junction

Step 4: an electronic field  $E$  is generated. Drift current is created due to minority carrier drift in this electronic field


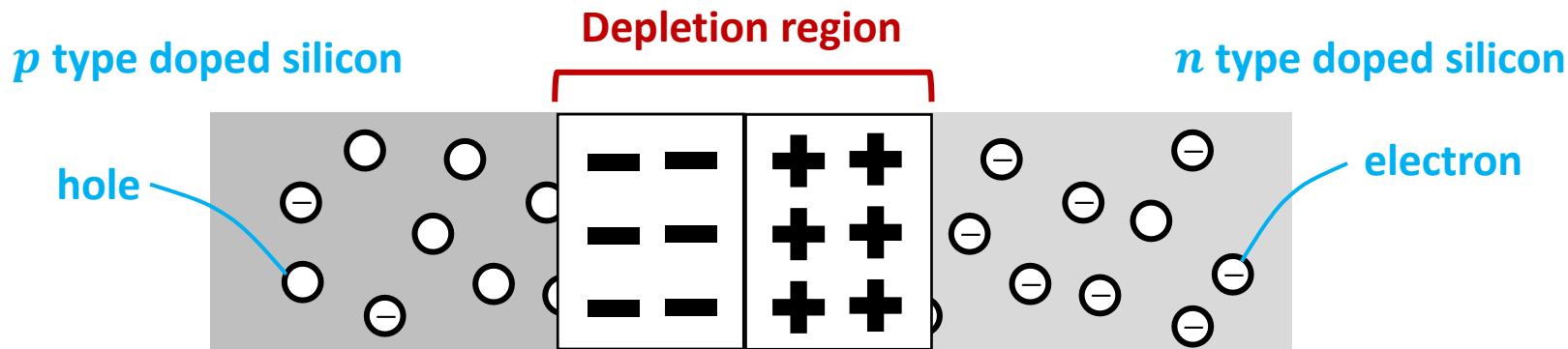
# The $pn$ junction

Step 4: an electronic field  $E$  is generated. Drift current is created due to minority carrier drift in this electronic field



Barrier voltage  $V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right)$

doping concentration of  $p$  side  
doping concentration of  $n$  side


thermal voltage  $V_T = \frac{kT}{q}$

The barrier voltage is known as the **junction build-in voltage**

# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - The *pn* junction
    - *pn* junction @open circuit
    - *pn* junction with applied voltage


# Recall: $pn$ junction @ open circuit

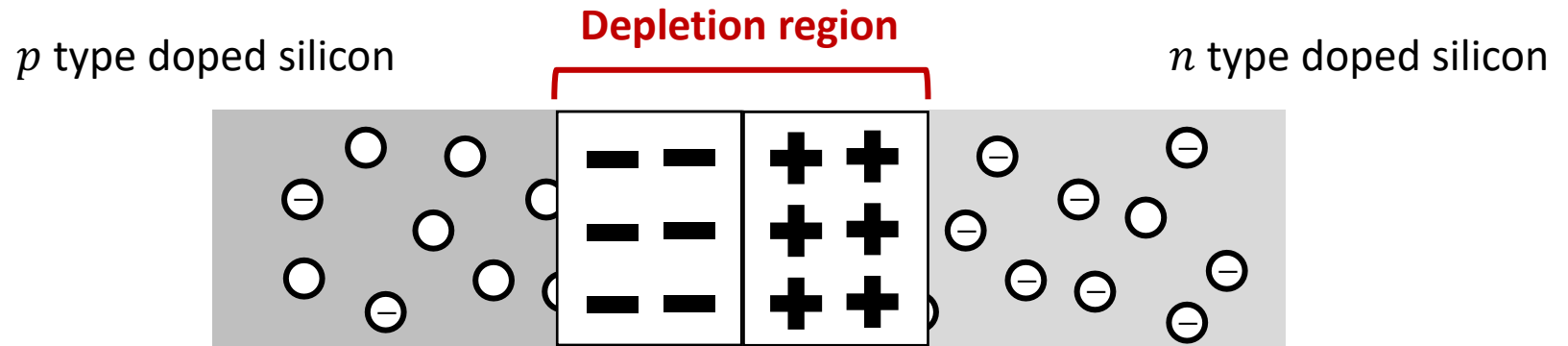


$n$  is more positive than  $p$  due to the depletion region

$I_D = I_S$  due to the barrier voltage

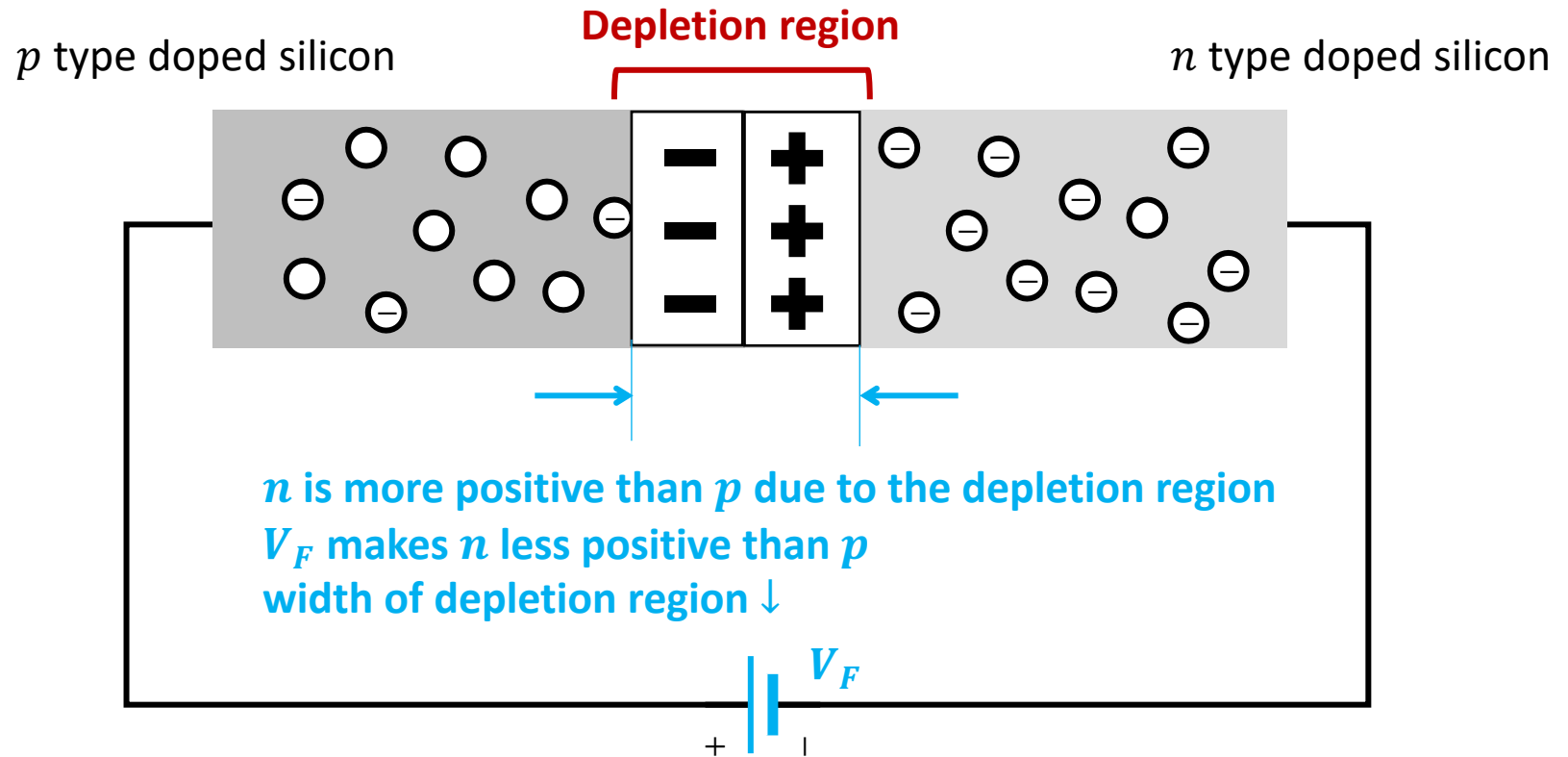
# $pn$ junction with forward-bias voltage


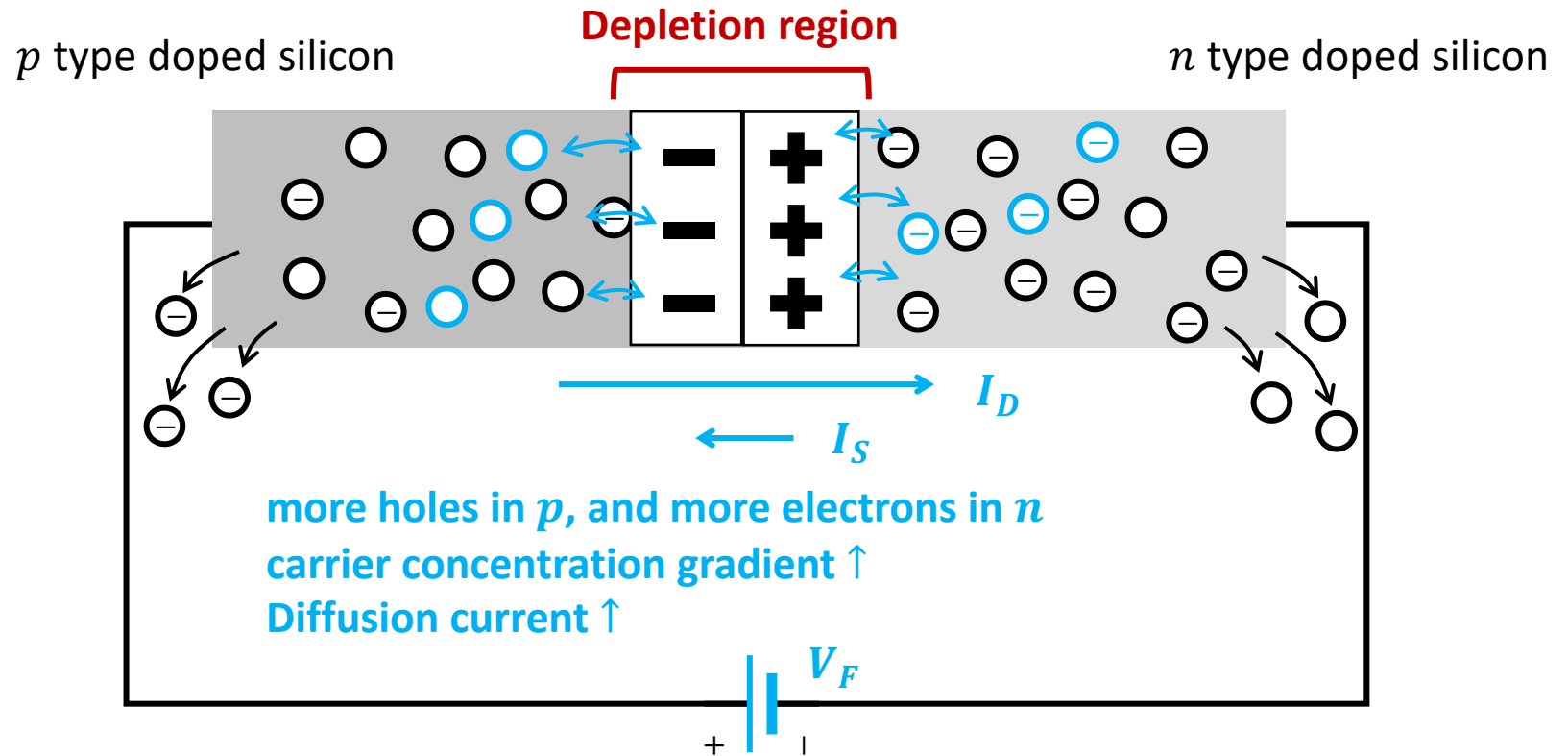
# *pn* junction with forward-bias voltage



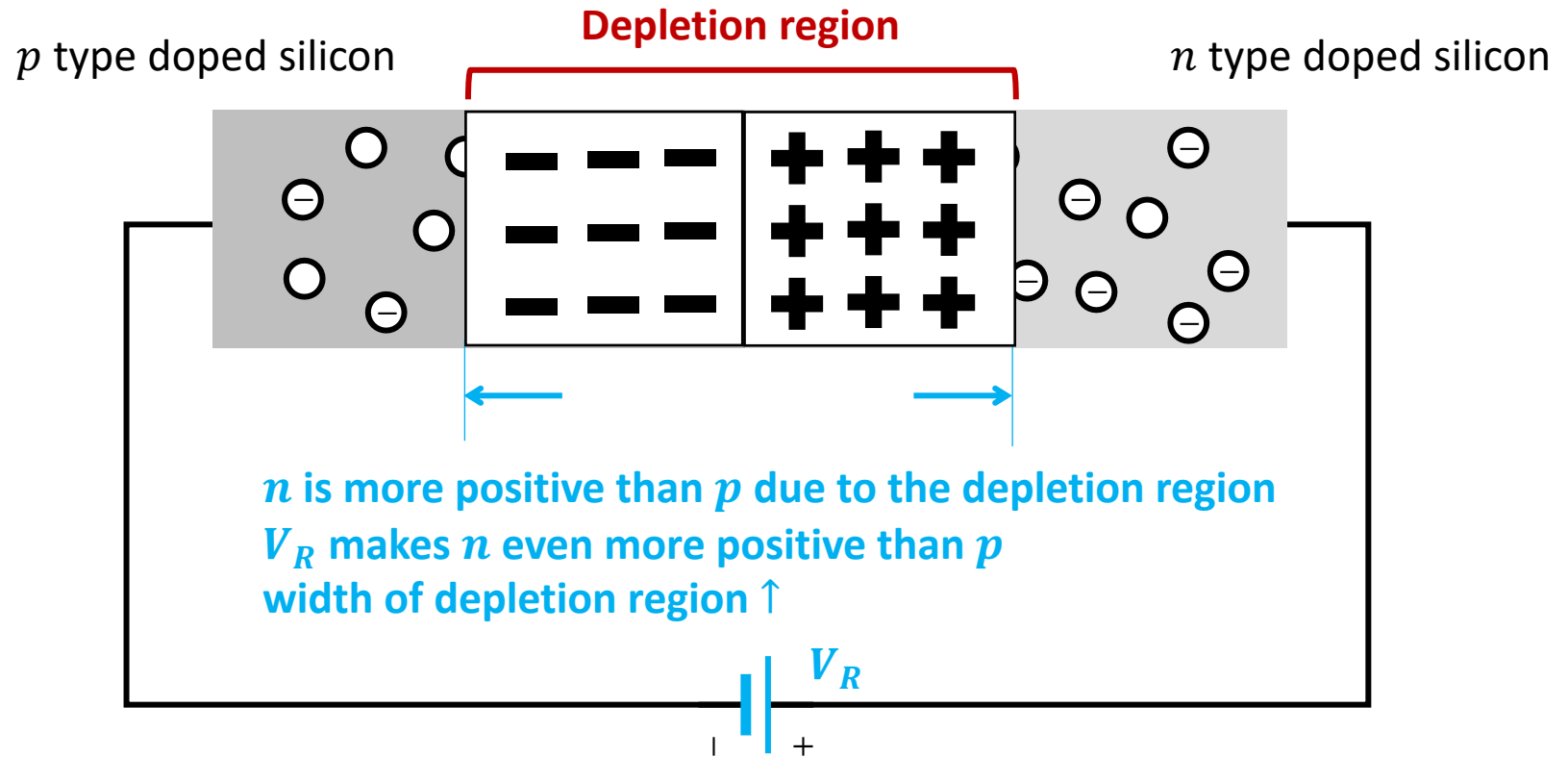
# *pn* junction with reverse-bias voltage





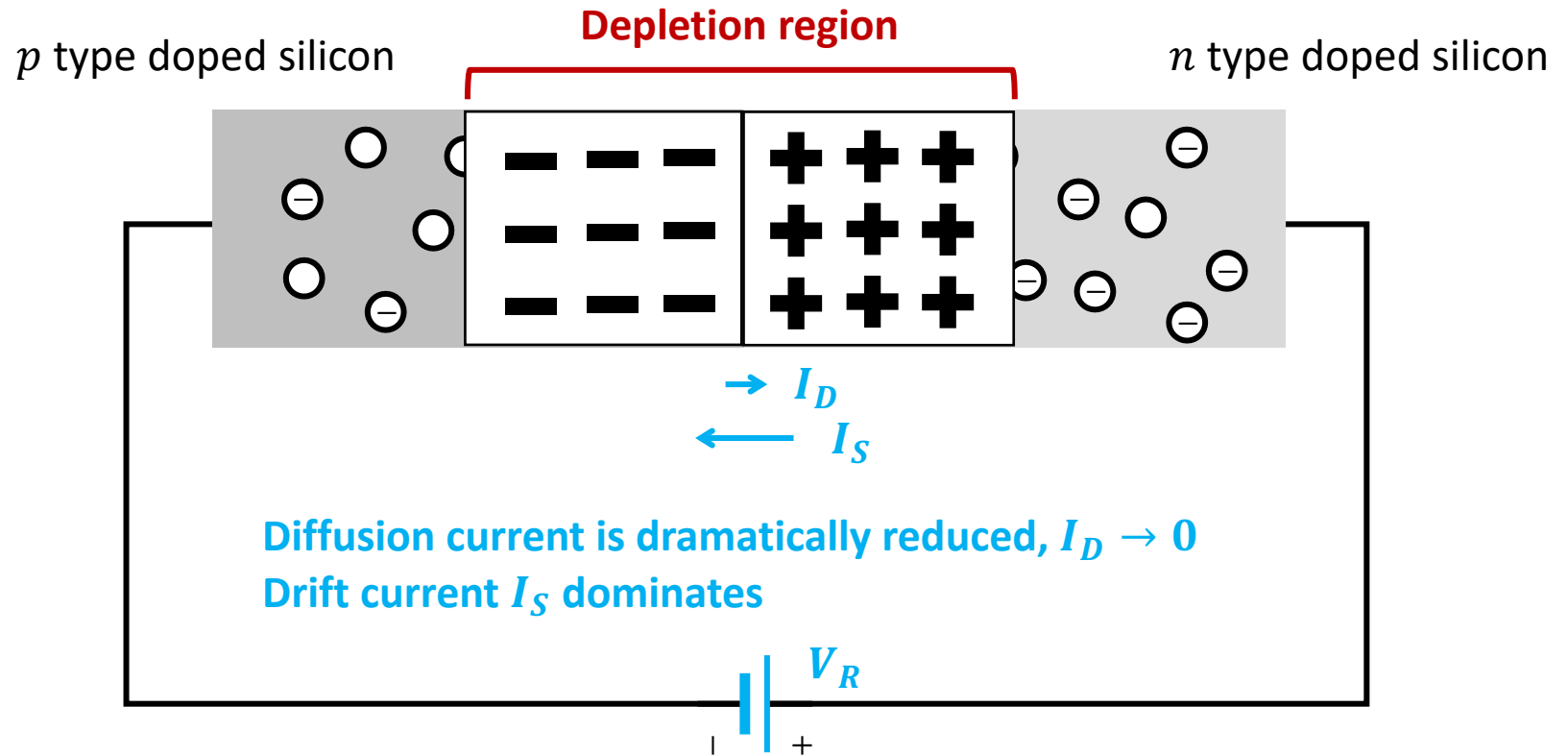
# *pn* junction with reverse-bias voltage


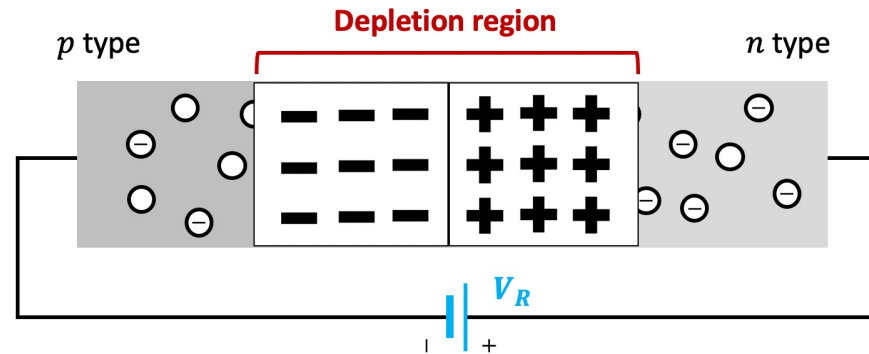
# Reverse breakdown

**JUNCTION BREAKDOWN** happens when the reverse voltage is very high




- **Zener effect**

- Reverse voltage is usually less than  $5V$
- Breaks covalent bonds & generates electron-hole pairs

- **Avalanche effect**

- Reverse voltage is usually  $> 7V$
- Breaks covalent bonds in atoms

# pn junction with applied voltage

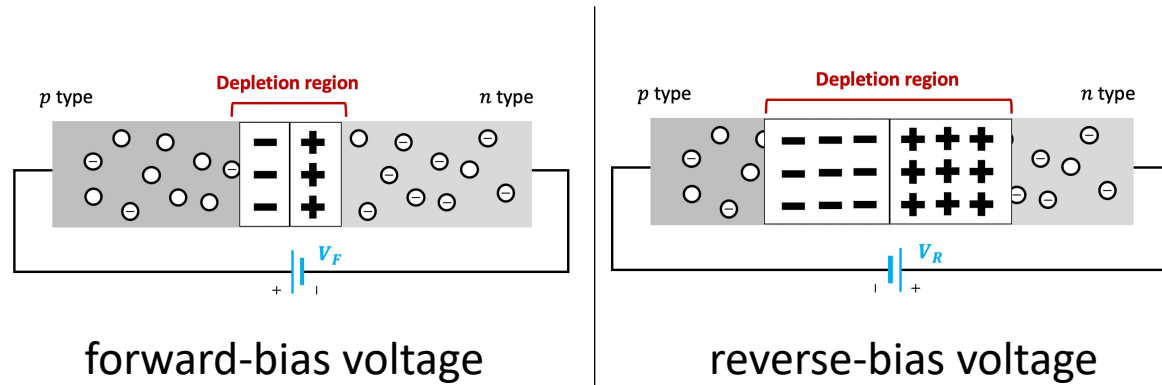


	forward-bias voltage	reverse-bias voltage
Depletion region width	↓	↑
Barrier voltage	↓	↑
current	$I = I_D - I_S$	$I = I_D - I_S \approx -I_S$


# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - The *pn* junction
    - *pn* junction @open circuit
    - *pn* junction with applied voltage
    - Reverse breakdown
- Diodes

# Junction diodes

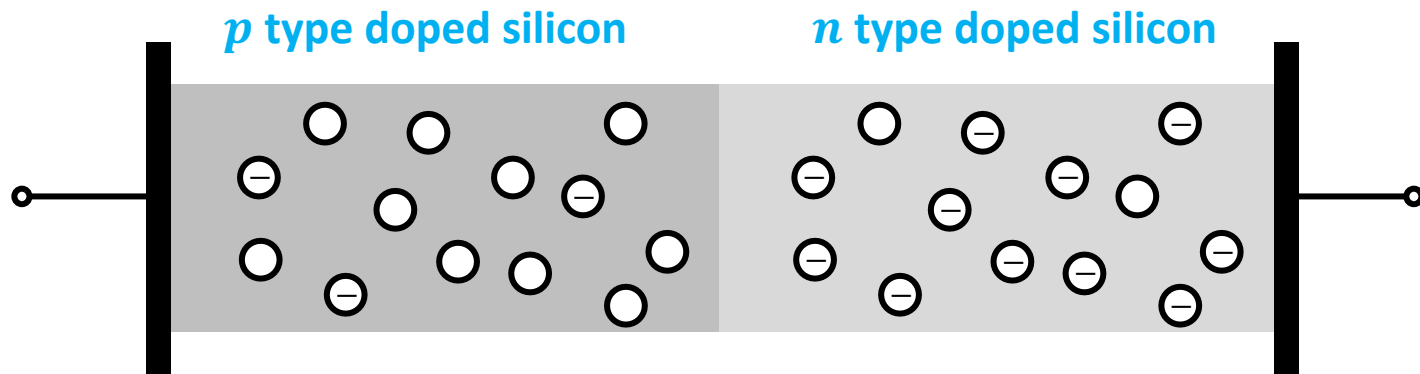

symbol

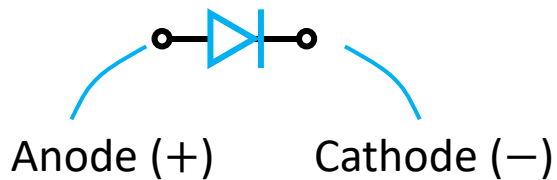


Diode


- A two-terminal device
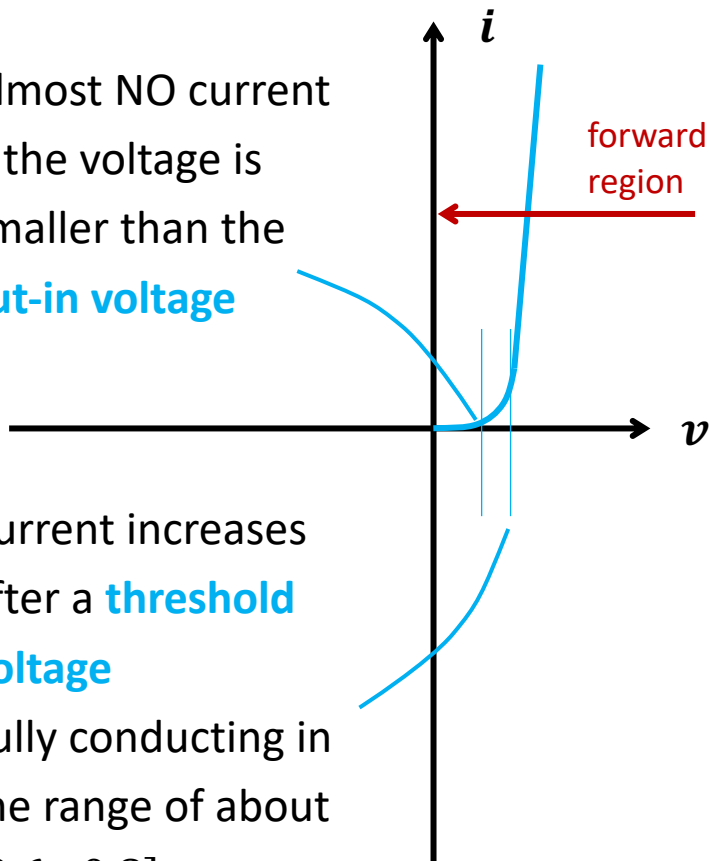
# $i - v$ characteristics of $pn$ junction

- Almost NO current if the voltage is smaller than the **cut-in voltage**
- Current increases after a **threshold voltage**
- Fully conducting in the range of about [0.6, 0.8]



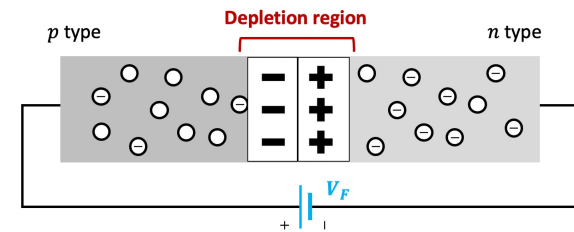Recall:  $pn$  junction with forward-bias voltage



- $n$  is more positive than  $p$  due to the depletion region
- $V_F$  makes  $n$  less positive than  $p$
- width of depletion region  $\downarrow$
- more holes in  $p$ , and more electrons in  $n$
- carrier concentration gradient  $\uparrow$
- Diffusion current  $\uparrow$

# $i - v$ characteristics of $pn$ junction

- Diode current in forward region


terminal voltage

$$i = I_S \left( e^{\frac{v}{V_T}} - 1 \right)$$


a constant  
@given temp.

Thermal voltage  
 $V_T = \frac{kT}{q}$

$$v = V_T \ln \frac{i}{I_S}$$

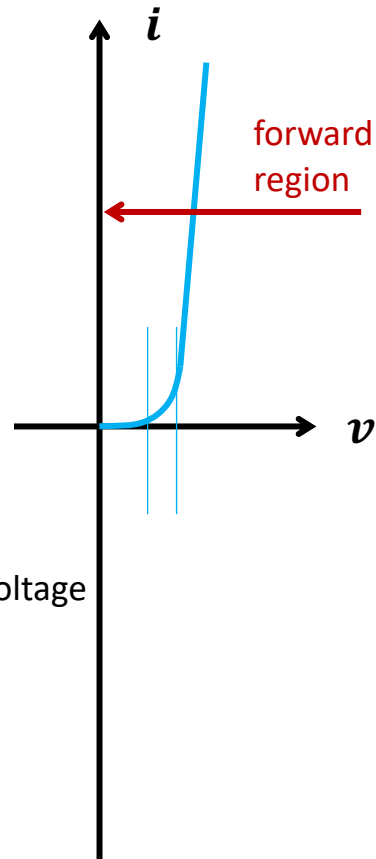

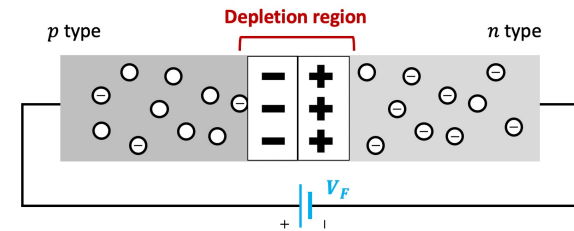
Recall:  $pn$  junction with forward-bias voltage



- $n$  is more positive than  $p$  due to the depletion region
- $V_F$  makes  $n$  less positive than  $p$
- width of depletion region  $\downarrow$
- more holes in  $p$ , and more electrons in  $n$
- carrier concentration gradient  $\uparrow$
- Diffusion current  $\uparrow$

# Example 1

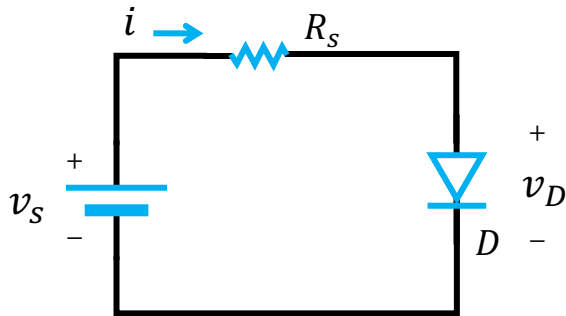**QUESTION:** Find the current through the resistor  $R_S$



$$\left[ \begin{array}{l} i - v \text{ characteristics} \\ \text{of the diode} \\ i = I_S \left( e^{\frac{v}{V_T}} - 1 \right) \\ v = V_T \ln \frac{i}{I_S} \end{array} \right]$$

- According to KVL

$$v_s = iR_s + v_D$$

- According to  $i - v$  characteristics of the diode


$$v_s = iR_s + V_T \ln \frac{i}{I_S}$$

**1 unknown in 1 equation**


**BUT WE CANNOT FIND AN ANALYTICAL SOLUTION**  
**NUMERICAL SOLUTION AVAILABLE IN 20230253**



# The constant-voltage-drop model

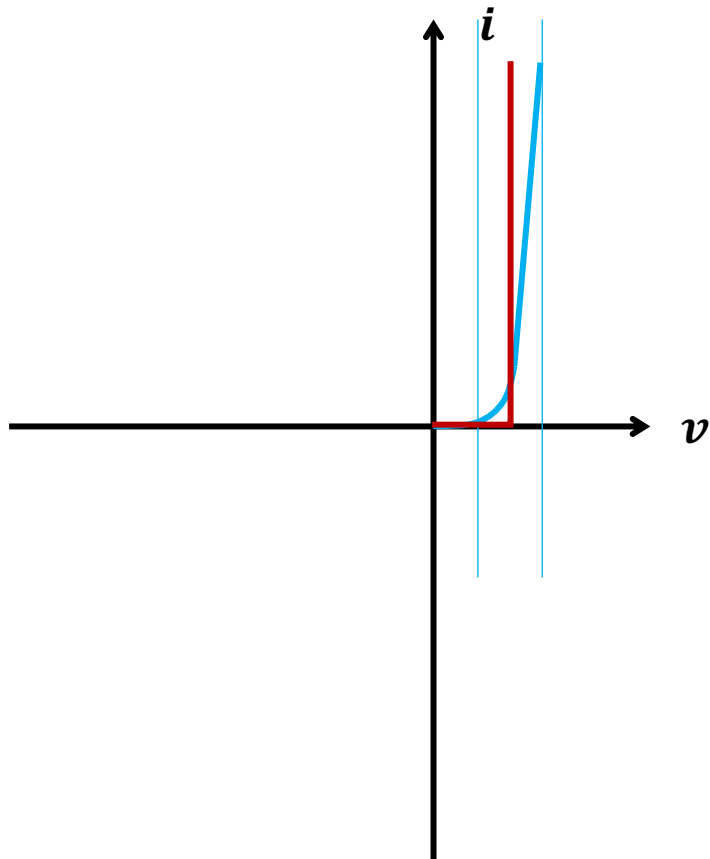

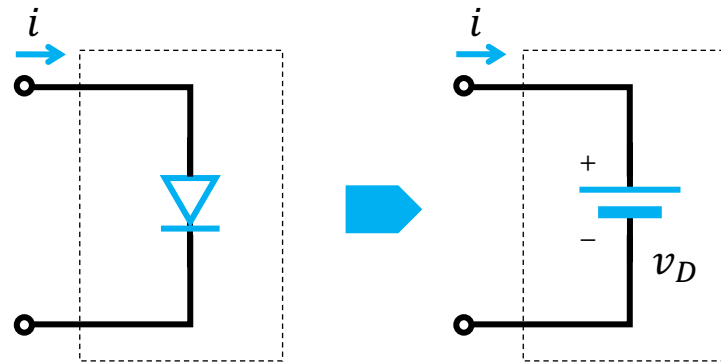- One of the most widely used diode **MODEL**
- Voltage drops in a narrow range, roughly [0.6, 0.8]
- A constant value of 0.7 is used




$$i > 0$$

$$v_D = 0.7V$$

# Example 1

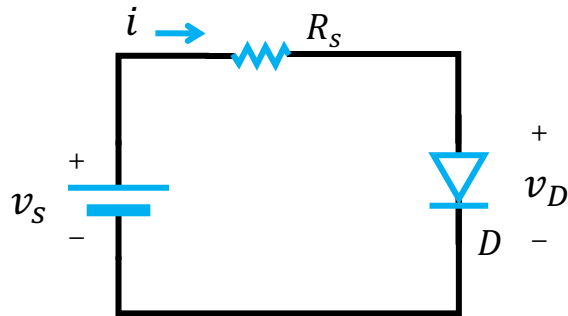**QUESTION:** Find the current through the resistor  $R_S$




- According to KVL

$$v_s = iR_S + v_D$$


- According to the constant-volt-drop model of diode

$$v_s = iR_S + 0.7$$
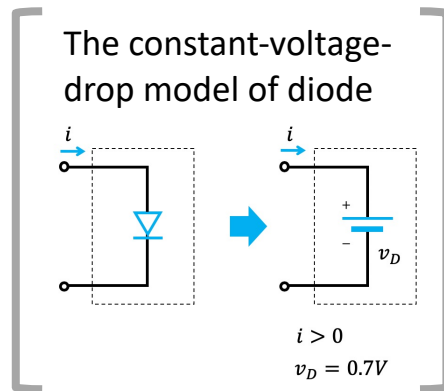
$$\Rightarrow i = \frac{v_s - 0.7}{R_S}$$



# The small-signal model

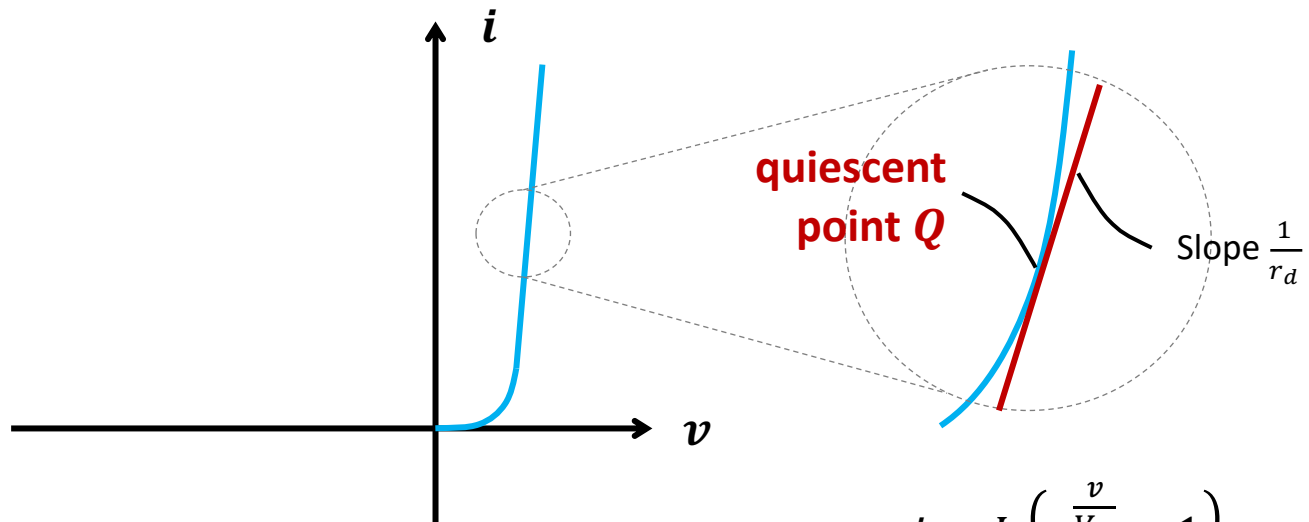

**The small-signal model works ONLY when the signal amplitude is close enough to the quiescent point**

$$i = I_S \left( e^{\frac{v}{V_T}} - 1 \right)$$


$$\left. \frac{\partial i}{\partial v} \right|_{@Q} = \frac{I_{@Q}}{V_T} = \frac{1}{r_d}$$



**Incremental resistance**

# Example 1

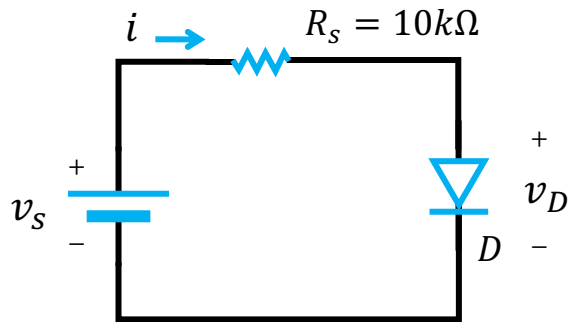**QUESTION:** Find the current through the resistor  $R_S$  with  $v_s = 10 + \sin(\omega t)$  (V)




- There are 2 parts in  $v_s$

$$v_s = \underbrace{10}_{\text{DC voltage}} + \underbrace{\sin(\omega t)}_{\text{AC voltage with a peak of 1V}} \text{ (V)}$$

**DC voltage**      **AC voltage with a peak of 1V**

# Example 1

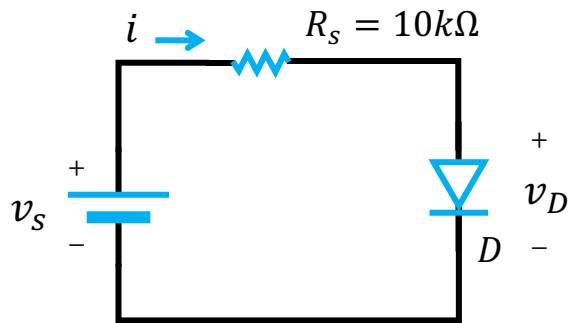
**QUESTION:** Find the current through the resistor  $R_S$  with  $v_s = 10 + \sin(\omega t)$  (V)



$$v_s = 10 + \sin(\omega t) \text{ (V)}$$



DC voltage

AC voltage  
with a peak  
of 1V

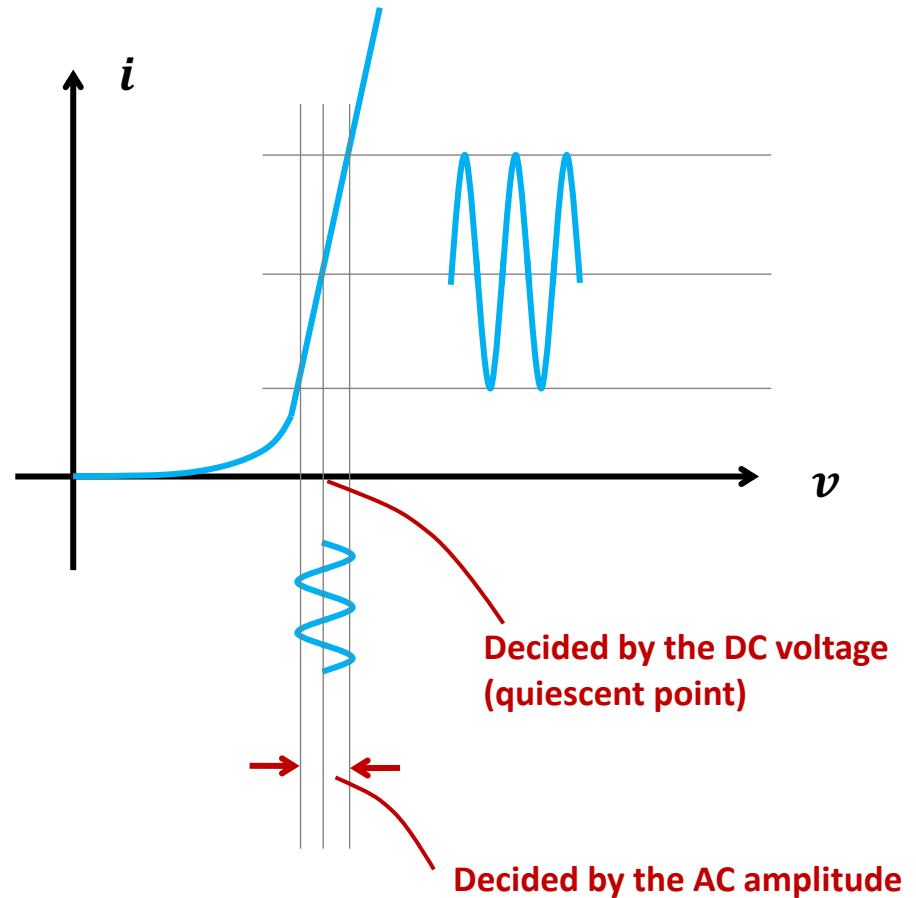

# Example 1

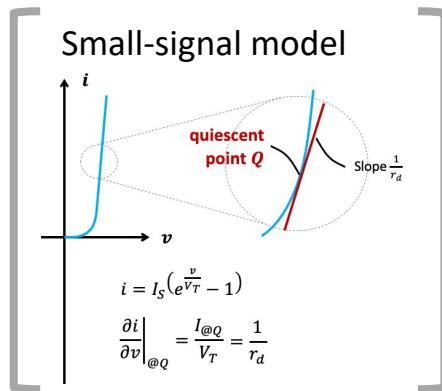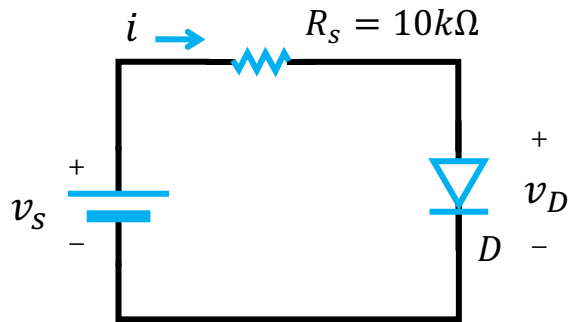**QUESTION:** Find the current through the resistor  $R_S$  with  $v_S = 10V + \sin(\omega t)$



- According to KVL

$$v_S = iR_S + v_D$$

- Find the quiescent point by assuming  $v_D|_{DC} = 0.7V$


$$I_D = \frac{v_S|_{DC} - 0.7}{R_S} = 0.93mA$$

$$r_d = \frac{V_T}{I_{@Q}} = 26.9\Omega$$

- According to KVL

$$v_D|_{AC} = \frac{r_d v_S|_{AC}}{R_S + r_d} = 2.68mV$$

# Example 1

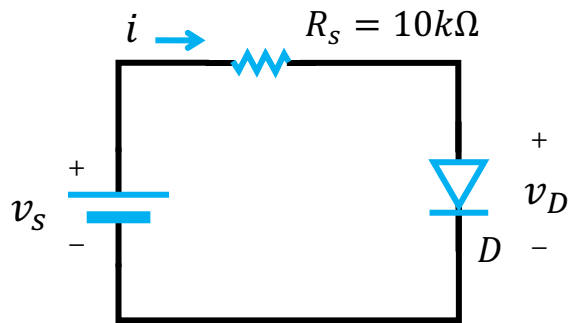


- Solution 1 – using  $i - v$  characteristics of the diode

$$v_s = iR_s + V_T \ln \frac{i}{I_S}$$

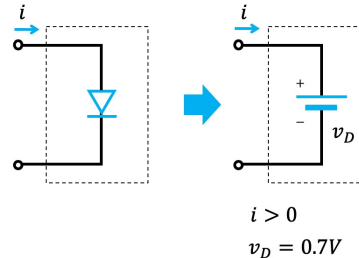
**BUT WE CANNOT FIND AN ANALYTICAL SOLUTION**

- Solution 2 – using constant-voltage-drop model



$$i = \frac{v_s - 0.7}{R_s}$$

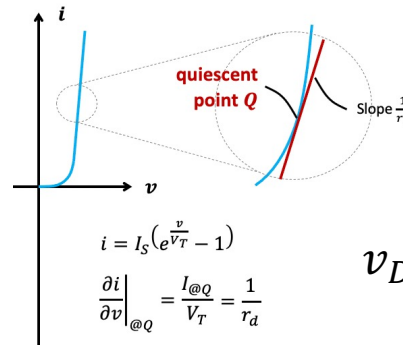- Solution 3 – using the small-signal model




$$i = I_S \left( e^{\frac{v}{V_T}} - 1 \right)$$

$$\left. \frac{\partial i}{\partial v} \right|_{@Q} = \frac{I_{@Q}}{V_T} = \frac{1}{r_d}$$

$$v_D \Big|_{AC} = \frac{r_d v_s \Big|_{AC}}{R_s + r_d} = 2.68mV$$

# Example 2

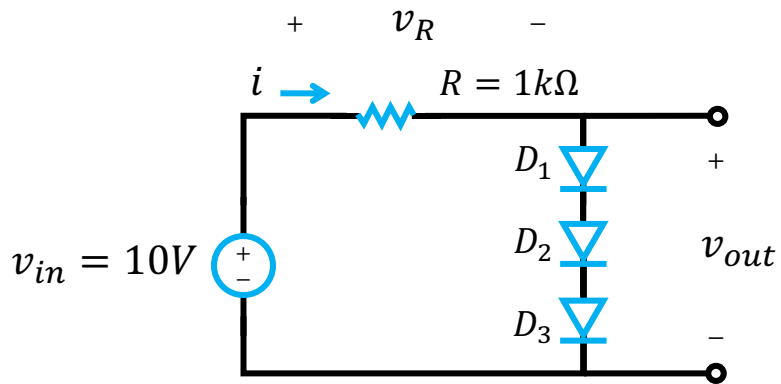**QUESTION:** Find the current through the resistor  $R$ . Use the constant-voltage-drop model.




- Use the constant-voltage-drop model

$$v_{out} = 0.7V \times 3 = 2.1V$$



- According to KVL
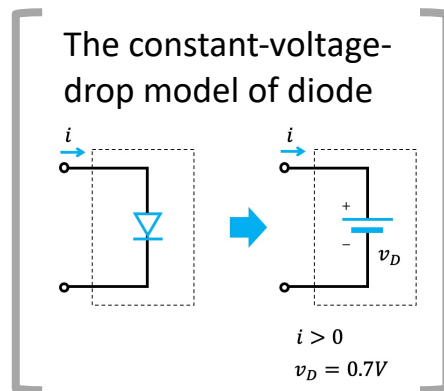
$$I_R = \frac{v_{in} - v_{out}}{R} = 7.9mA$$





# Junction diodes

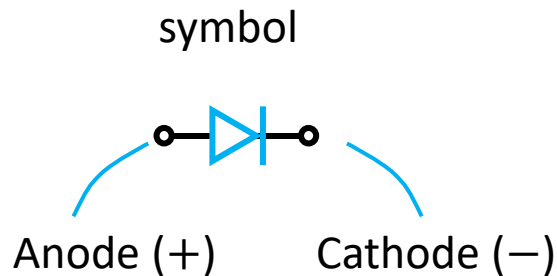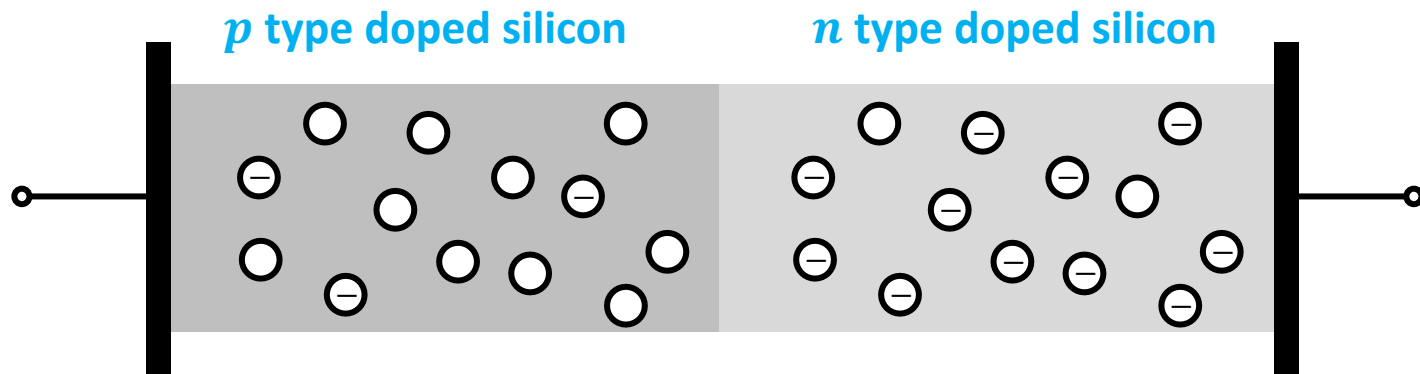

Diode

- A two-terminal device
- **Current flows from Anode to Cathode**


# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - The *pn* junction
    - *pn* junction @open circuit
    - *pn* junction with applied voltage
- Diodes
  - The forward region
  - **The reverse region**


# $i - v$ characteristics of $pn$ junction

- Very low current

$$i \approx -I_S$$

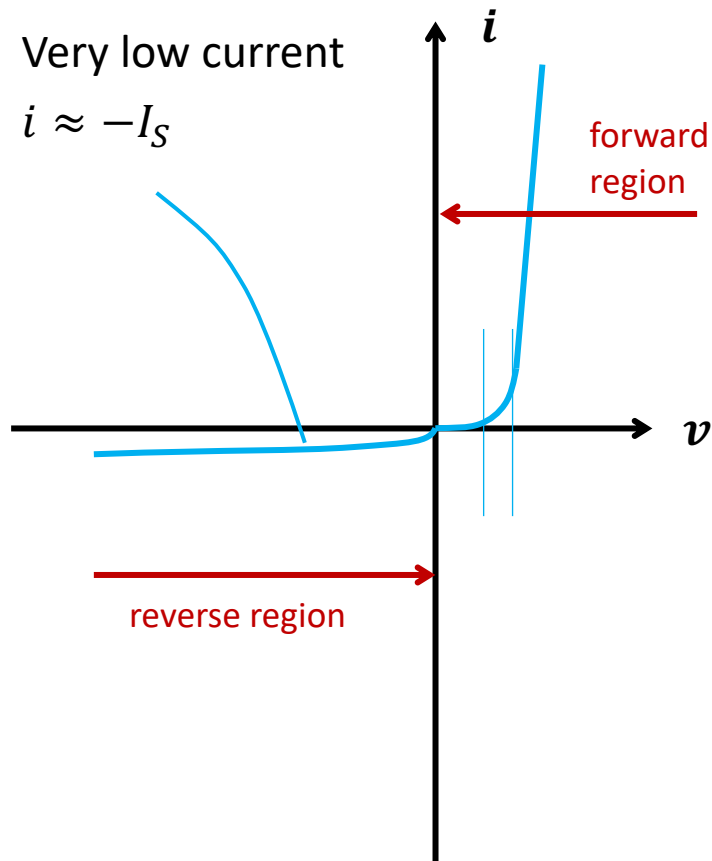

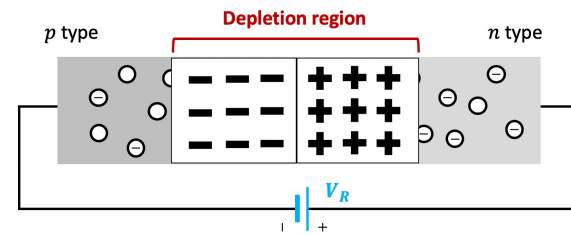Recall:  $pn$  junction with reverse-bias voltage




- $n$  is more positive than  $p$  due to the depletion region
- $V_F$  makes  $n$  even more positive than  $p$
- width of depletion region  $\uparrow$
- Diffusion current is dramatically reduced,  $I_D \rightarrow 0$
- Drift current  $I_S$  dominates


# The models of diode
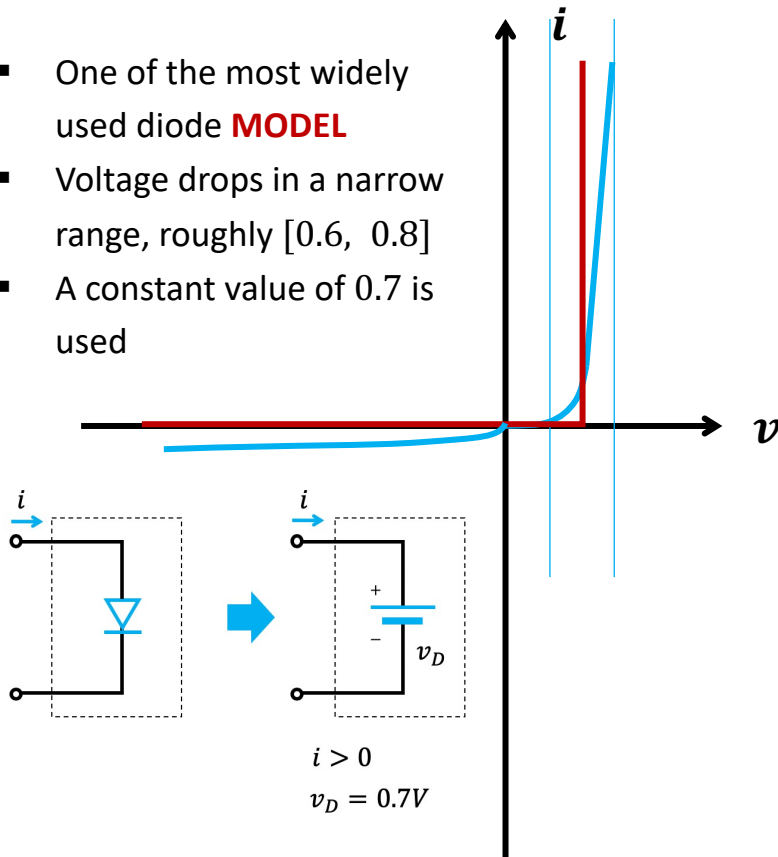
## CONSTANT-VOLTAGE-DROP MODEL

- One of the most widely used diode **MODEL**
- Voltage drops in a narrow range, roughly  $[0.6, 0.8]$
- A constant value of 0.7 is used




## More realistic model

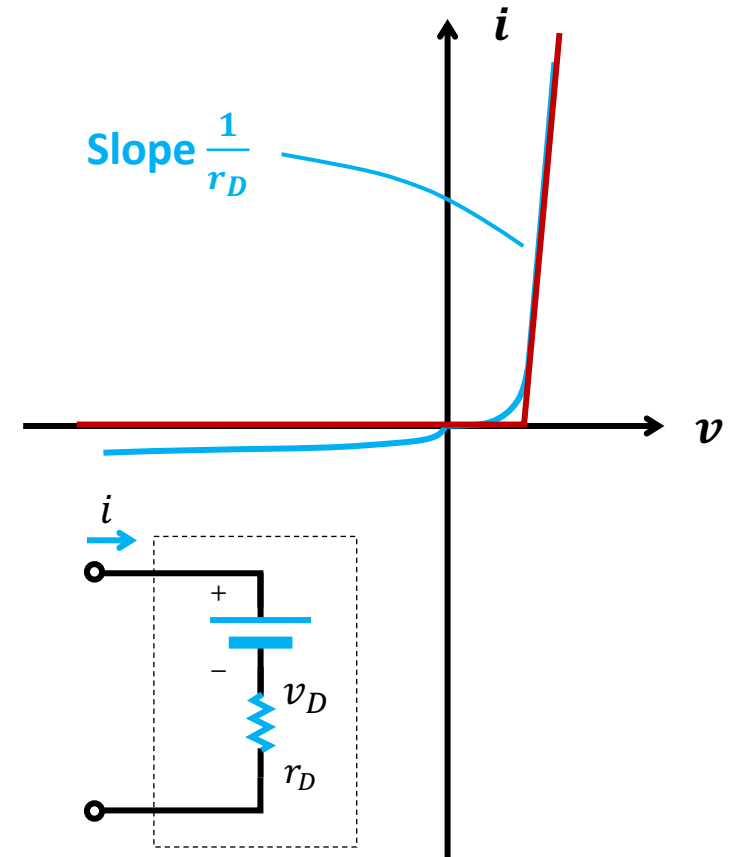

# Example 4: half-wave rectifier

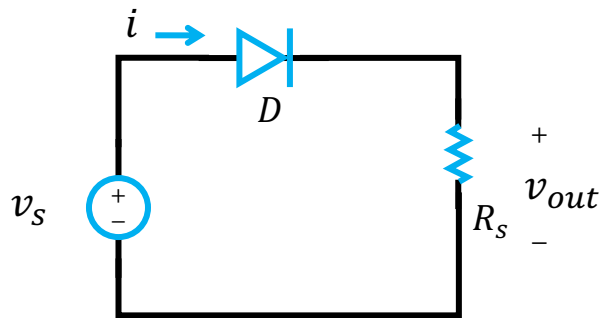**QUESTION:** Find the output voltage with the given input. The resistance of the diode must be considered




- When  $v_s < 0$   
The diode is reverse biased

$$i = 0 \quad v_{out} = 0$$


- When  $v_s > 0$

The diode is forward biased

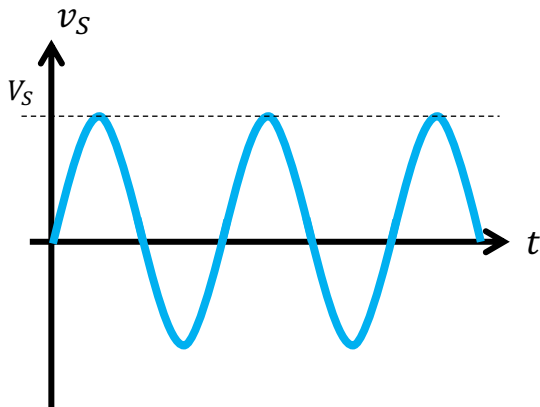

# Example 4: half-wave rectifier

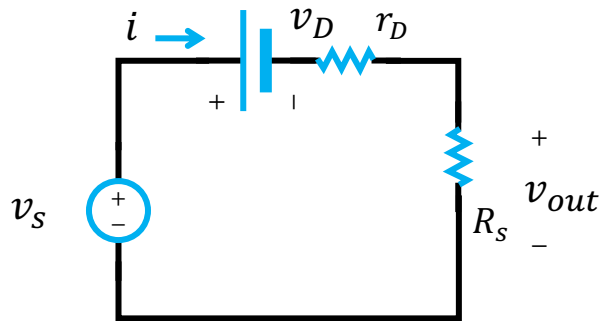**QUESTION:** Find the output voltage with the given input. The resistance of the diode must be considered



- When  $v_s < 0$

The diode is reverse biased


$$i = 0 \quad v_{out} = 0$$

- When  $v_s > 0$

The diode is forward biased


$$i = \frac{v_s - v_D}{r_D + R_s}$$

$$v_{out} = iR_s$$

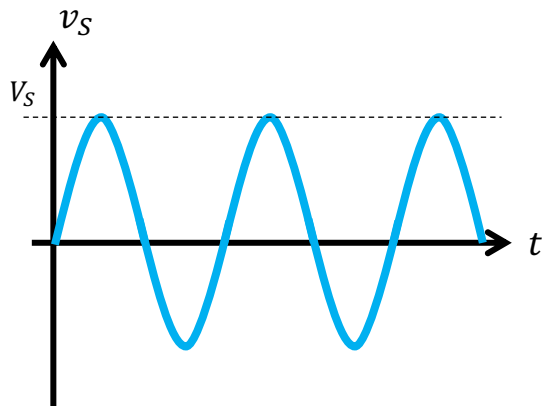


# Example 4: half-wave rectifier

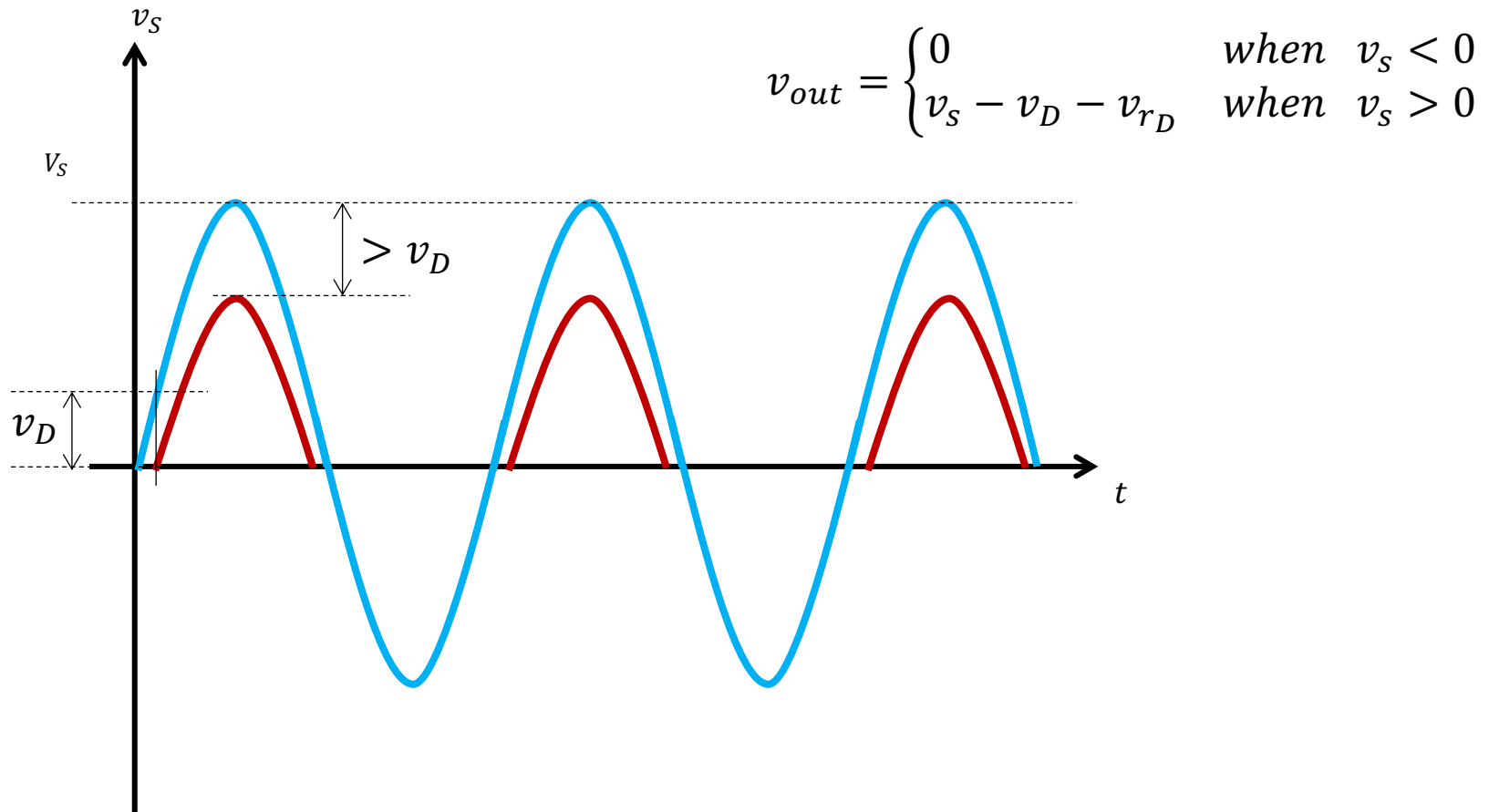**QUESTION:** Find the output voltage with the given input. The resistance of the diode must be considered



# Example 4: half-wave rectifier

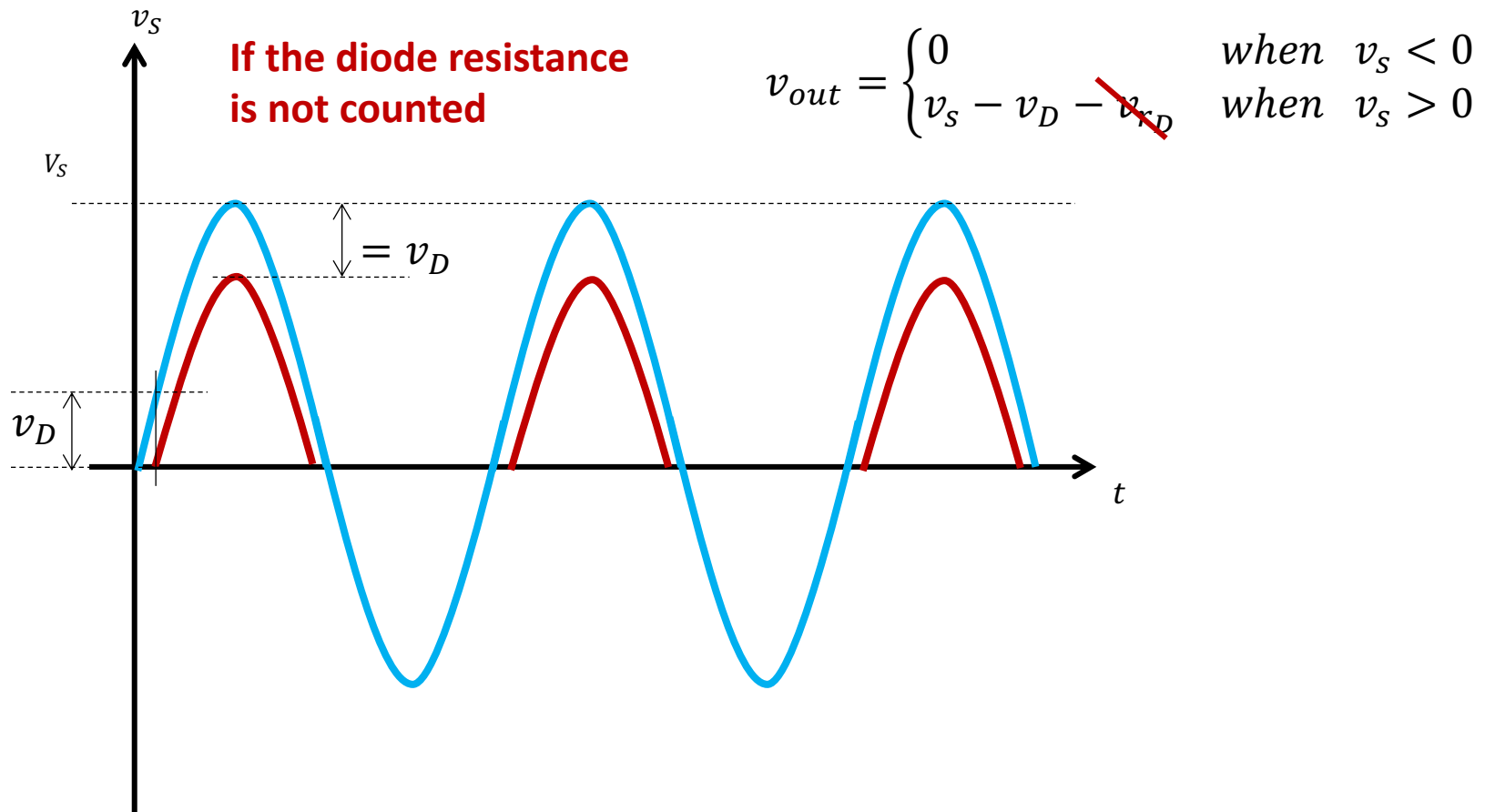**QUESTION:** Find the output voltage with the given input. The resistance of the diode must be considered







# The models of diode
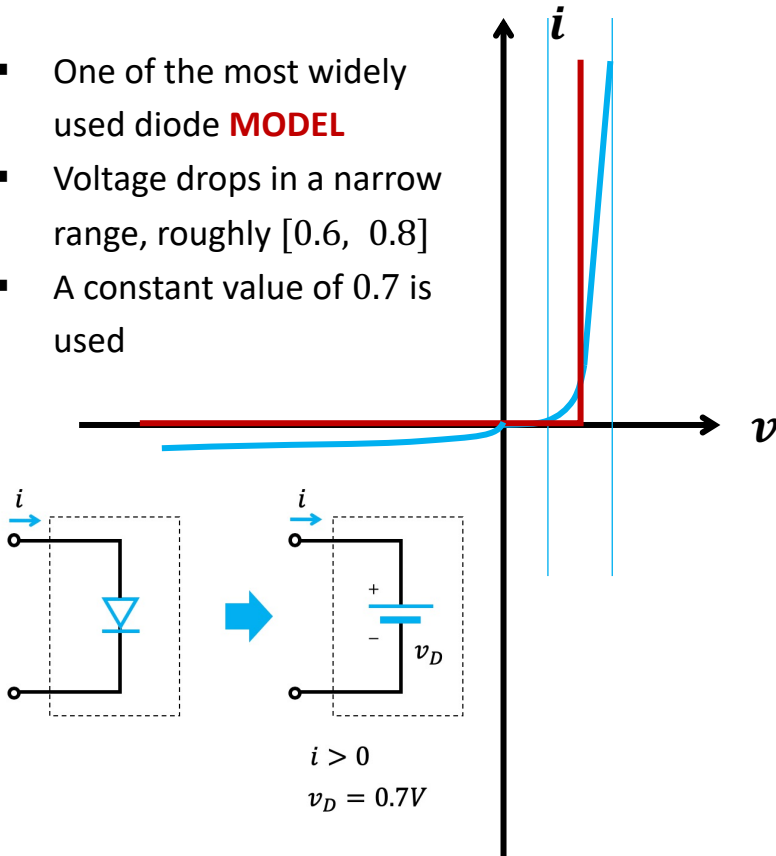
## CONSTANT-VOLTAGE-DROP MODEL


- One of the most widely used diode **MODEL**
- Voltage drops in a narrow range, roughly  $[0.6, 0.8]$
- A constant value of 0.7 is used



## IDEAL MODEL

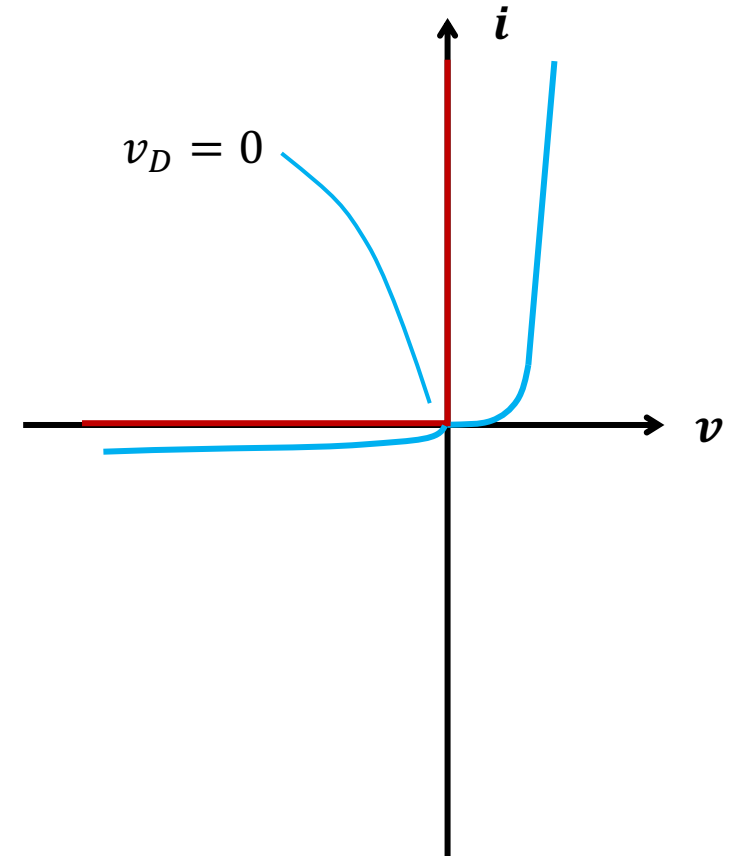


# The models of ideal diode

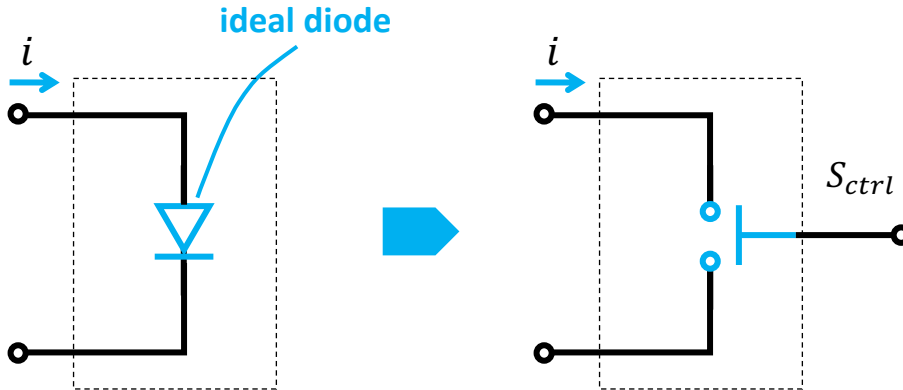

$$i = \begin{cases} > 0 & \text{if } S_{ctrl} > 0 \\ 0 & \text{if } S_{ctrl} < 0 \end{cases}$$

## IDEAL MODEL

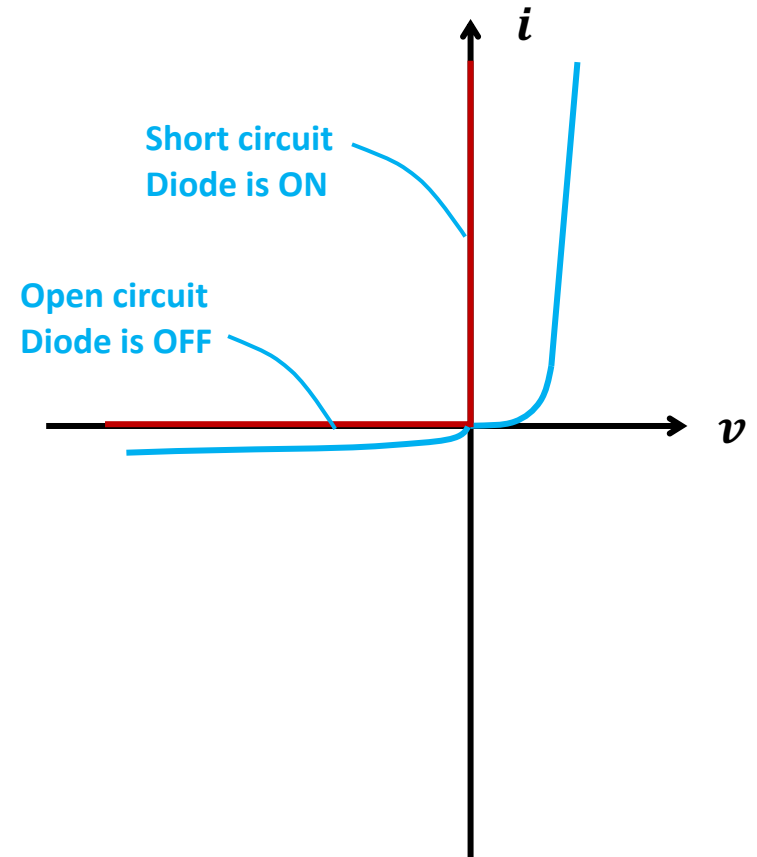


## Ideal Diode

- A two-terminal device
- Current **ONLY** flows from Anode to Cathode
- An electronic 1-way valve

# Example 3: ideal diode

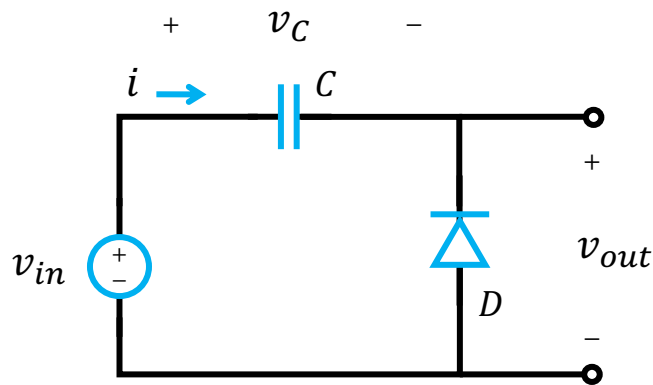
**QUESTION:** Find the output voltage with the given input. The diode is ideal



- When  $t \in [0, t_1)$



$D$  is forward-biased
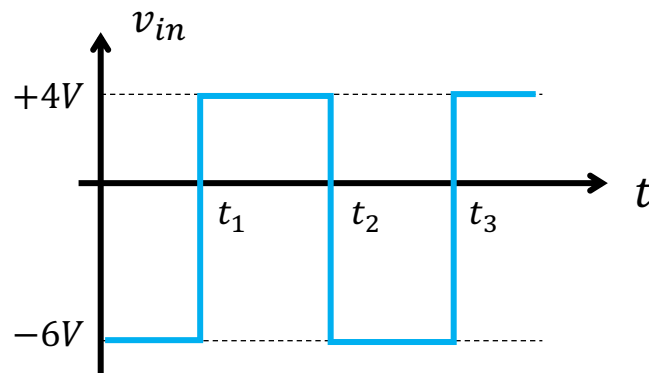
$$\rightarrow v_{out} = 0 \quad v_C = -6V$$



# Example 3: ideal diode

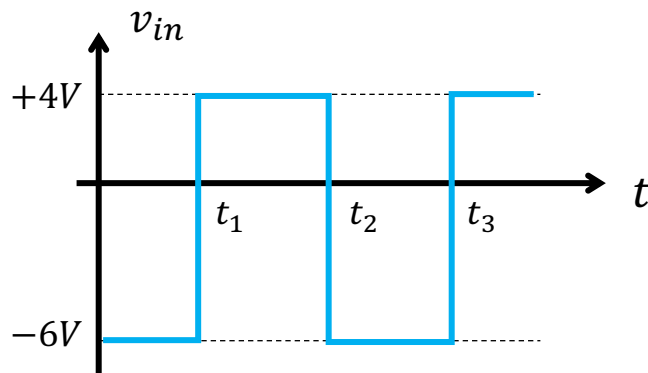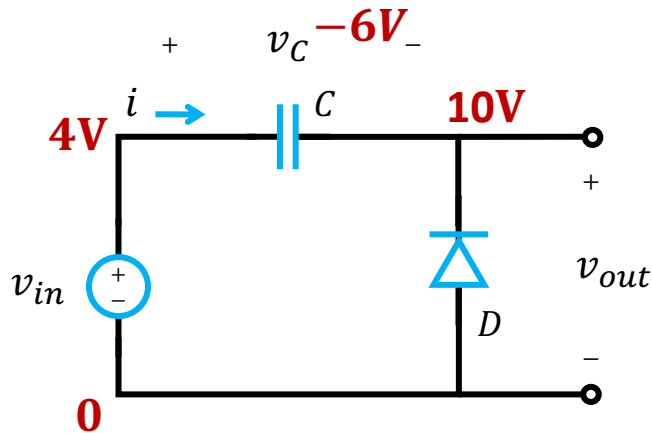**QUESTION:** Find the output voltage with the given input. The diode is ideal



- When  $t \in [0, t_1)$ 
  - $D$  is forward-biased
  - $\rightarrow v_{out} = 0 \quad v_C = -6V$
- When  $t = t_1^+$


Since voltage on capacitor CANNOT change abruptly

$$\rightarrow v_{out} = 10V \quad v_C = -6V$$

$D$  is reverse-biased

# Example 3: ideal diode

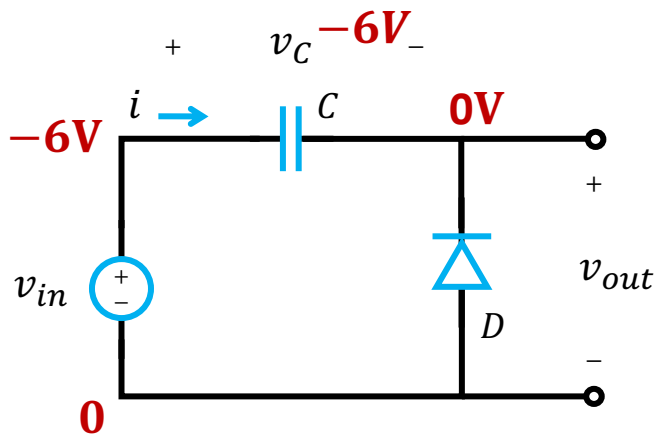**QUESTION:** Find the output voltage with the given input. The diode is ideal




- When  $t = t_2^+$

$D$  is forward-biased




Since voltage on capacitor CANNOT change abruptly
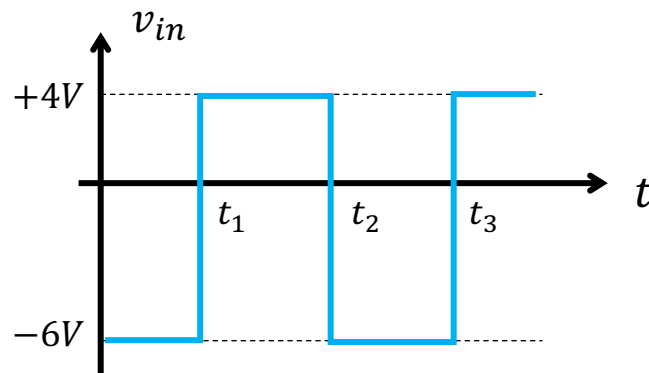
$$\rightarrow v_{out} = 0 \quad v_C = -6V$$




# Example 3: ideal diode

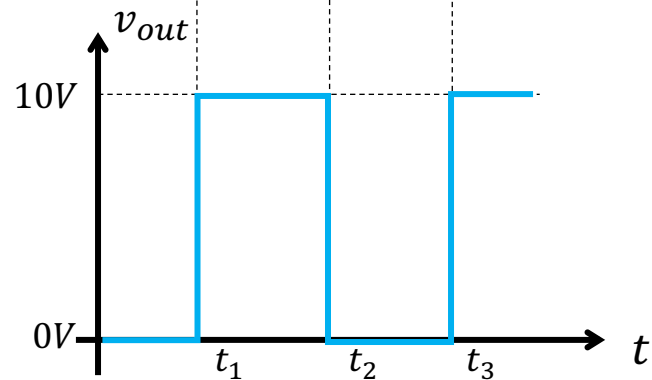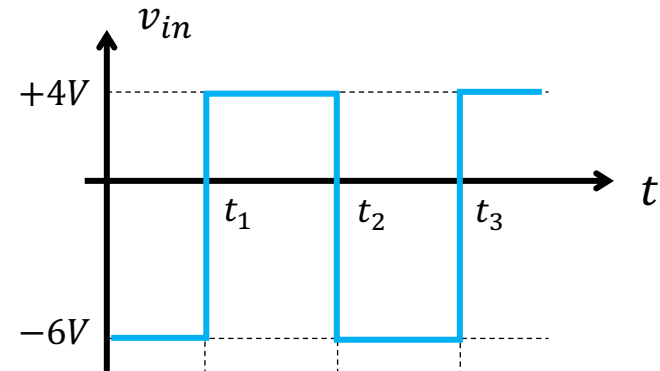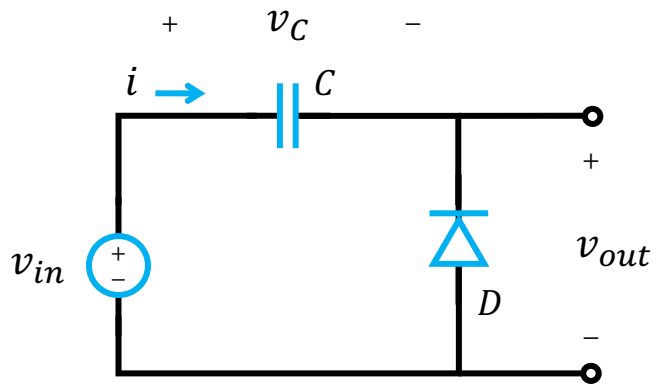**QUESTION:** Find the output voltage with the given input. The diode is ideal


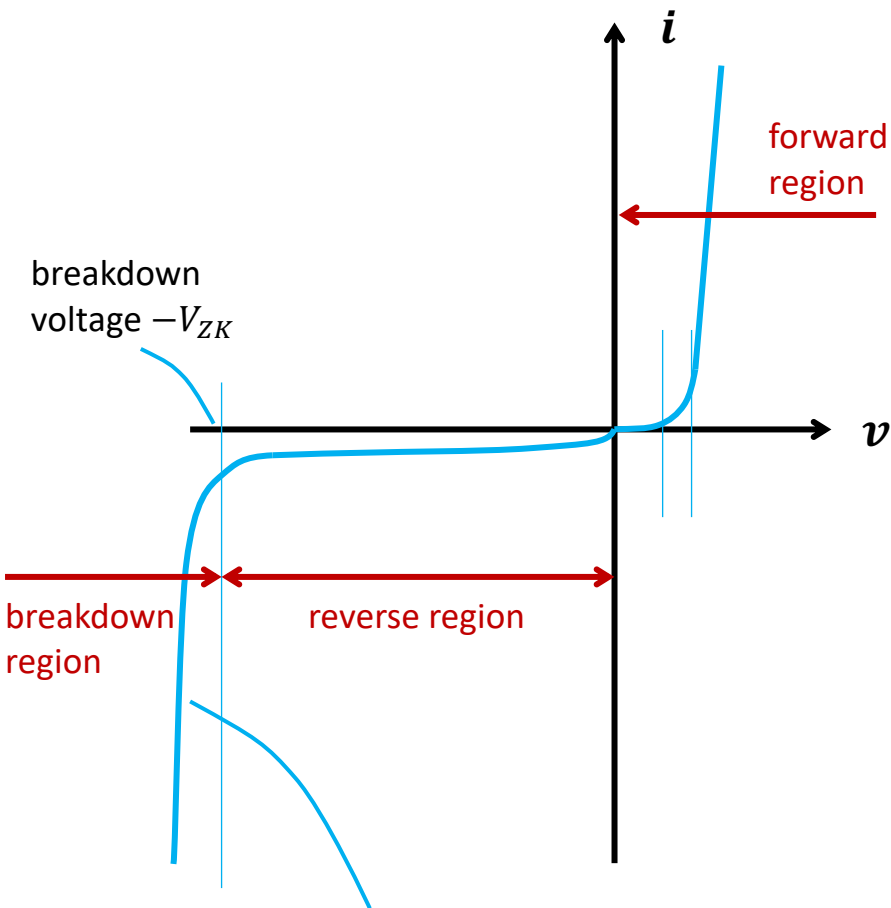
# $i - v$ characteristics of $pn$ junction



- Junction breakdown @  $V = - -V_{ZK}$
- Case 1 – **Zener effect**
  - Current generated by breaking the electron-hole pairs
- Case 2 – **Avalanche effect**
  - Current generated by breaking the covalent bonds in atoms


- Current increases rapidly
- Voltage drops very small

# Zener diode



symbol



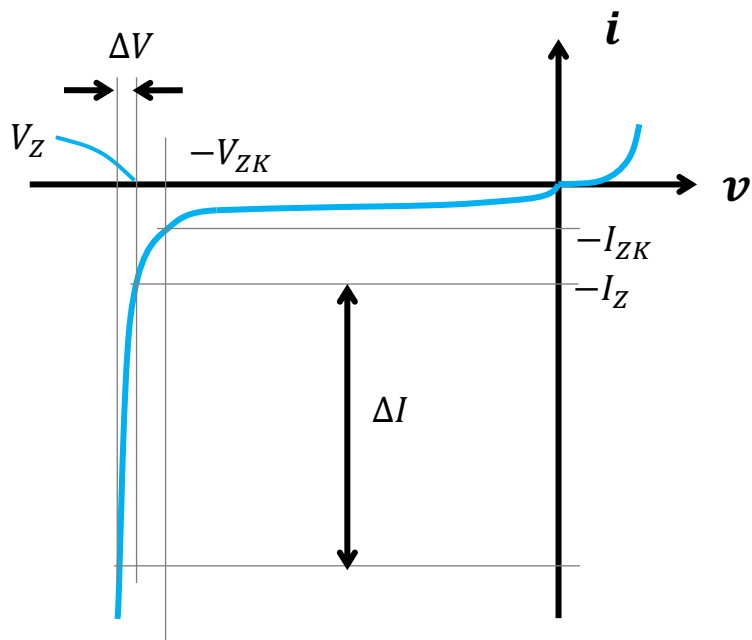**ZENER DIODE is special diodes manufactured to operate in the breakdown region**



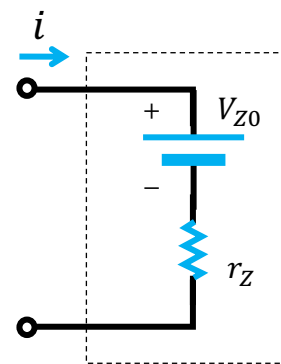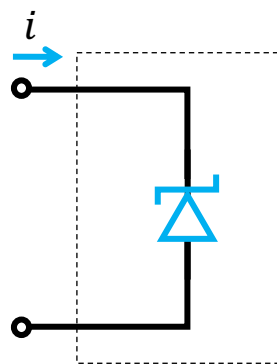Dynamic resistance  $r_Z = \frac{\Delta V}{\Delta I}$




Model for Zener diode

$$V_Z = V_{Z0} + I_Z r_Z$$



# Example 3: Zener diode

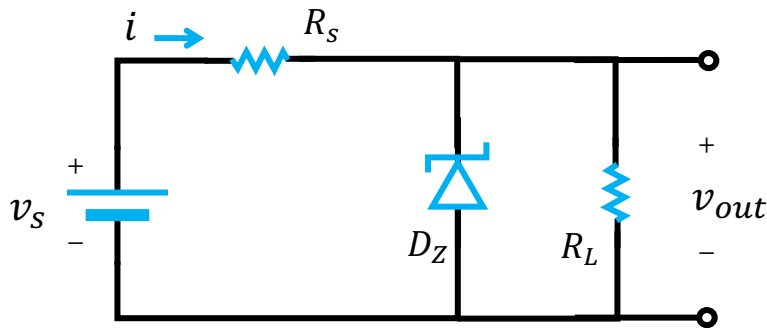
**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_Z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .



- For the Zener diode model, according to KVL


$$V_Z = V_{Z0} + I_Z r_Z$$

$$\rightarrow V_{Z0} = 6.7V$$

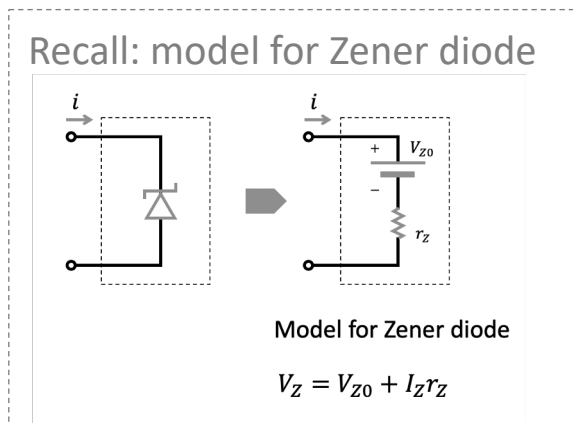

# Example 3: Zener diode

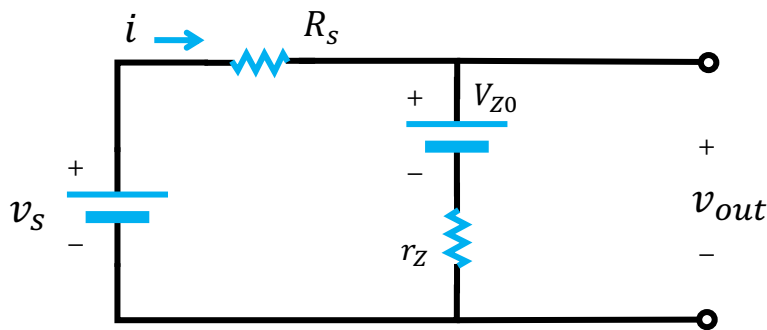**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_Z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .



- For the zener diode model, according to KVL

$$V_Z = V_{Z0} + I_Z r_Z$$

$$\rightarrow V_{Z0} = 6.7V$$


- If there is no load ( $R_L = \infty$ ), according to KVL

$$v_s = I_Z R_S + V_{Z0} + I_Z r_Z$$

$$\rightarrow I_Z = 6.35mA$$

$$v_{out} = V_{Z0} + I_Z r_Z = 6.83V$$

Recall: model for Zener diode

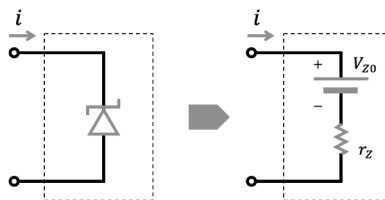


Model for Zener diode

$$V_Z = V_{Z0} + I_Z r_Z$$

# Example 3: Zener diode

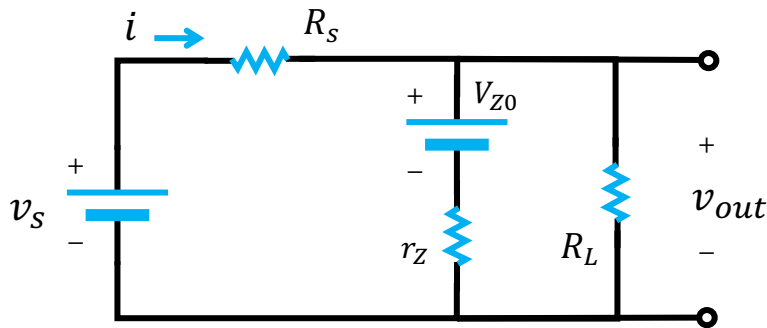**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_Z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .



- If  $R_L = 2k\Omega$ , since  $R_L \gg r_Z$ , approximately,


→  $i$  does not change

→  $i_{R_L} \uparrow$  compared to no load

→  $i_{r_Z} \downarrow$  compared to no load


$$i_{R_L} \approx \frac{V_Z}{R_L} = 3.4mA = -\Delta i_{r_Z}$$
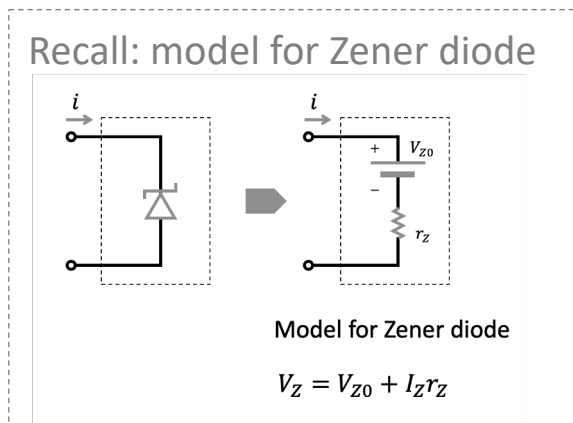
$$\Delta v_{out} \approx -\Delta i_{r_Z} r_Z = -68mV$$



# Example 3: Zener diode

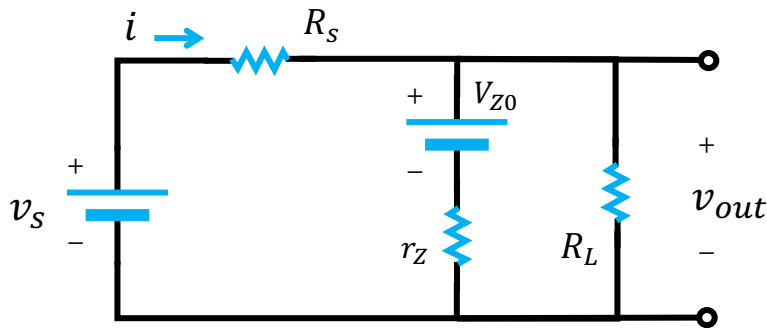**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_Z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .




- If  $R_L = 2k\Omega$ , more precisely, according to KCL

$$\frac{v_s - v_{out}}{R_S} = \frac{v_{out} - V_{Z0}}{r_Z} + \frac{v_{out}}{R_L}$$

$$\rightarrow v_{out} = 6.87V$$

$$\Delta v_{out} = -70mV$$

Recall: model for Zener diode

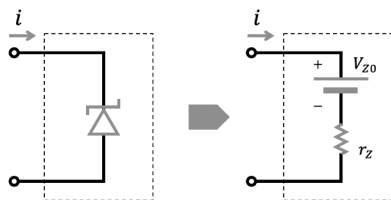


Model for Zener diode

$$V_Z = V_{Z0} + I_Z r_Z$$

# Example 3: Zener diode

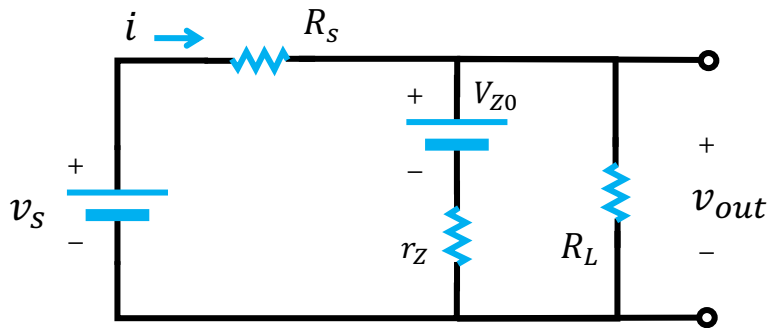**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .




- If  $R_L = 0.5k\Omega$ , if the zener diode is on

$$I_{R_L} \approx \frac{V_Z}{R_L} = 13.6mA > I_Z$$


**It's impossible**

Thus, the Zener diode is disabled

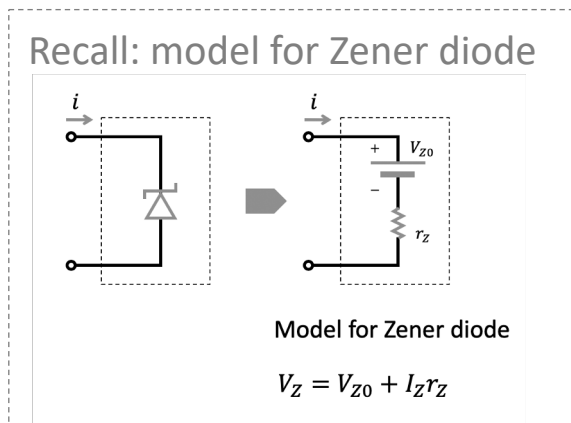

# Example 3: Zener diode

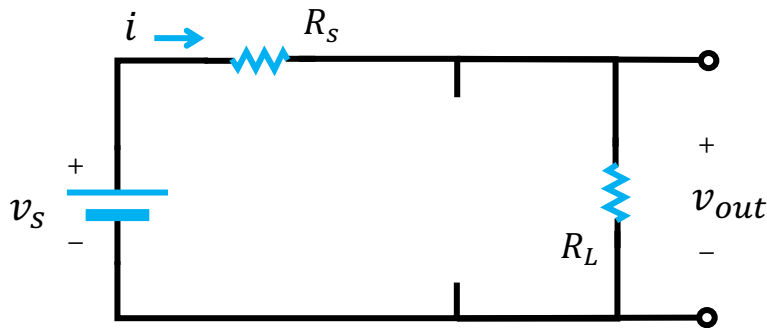**QUESTION:** the zener diode  $D_Z$  is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ ,  $r_Z = 20\Omega$ . The supply voltage  $v_s$  is nominally  $10V$  but can vary by  $\pm 1V$ .  $R_S = 0.5k\Omega$ . Find the output voltage with different load  $R_L = \infty, 2k\Omega$  or  $0.5k\Omega$ .



- If  $R_L = 0.5k\Omega$ , if the zener diode is on


$$I_{R_L} \approx \frac{V_Z}{R_L} = 13.6mA > I_Z$$

**It's impossible**



Thus, the Zener diode is disabled

- According to KVL

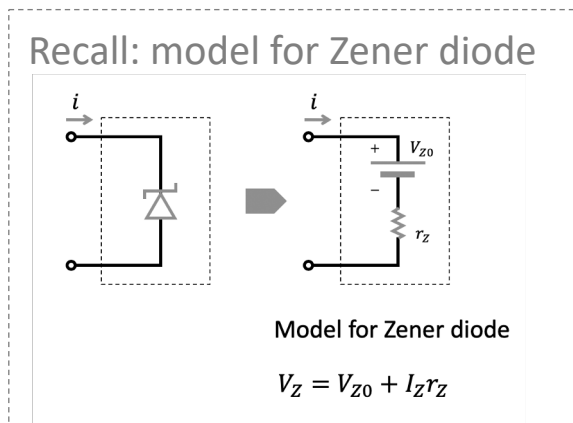
$$v_{out} = v_s \frac{R_L}{R_S + R_L} = 5V$$



# Summary: the $pn$ junction diode

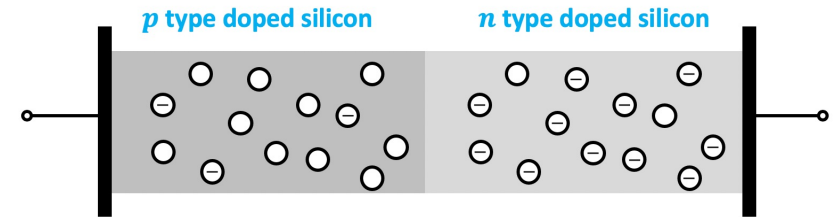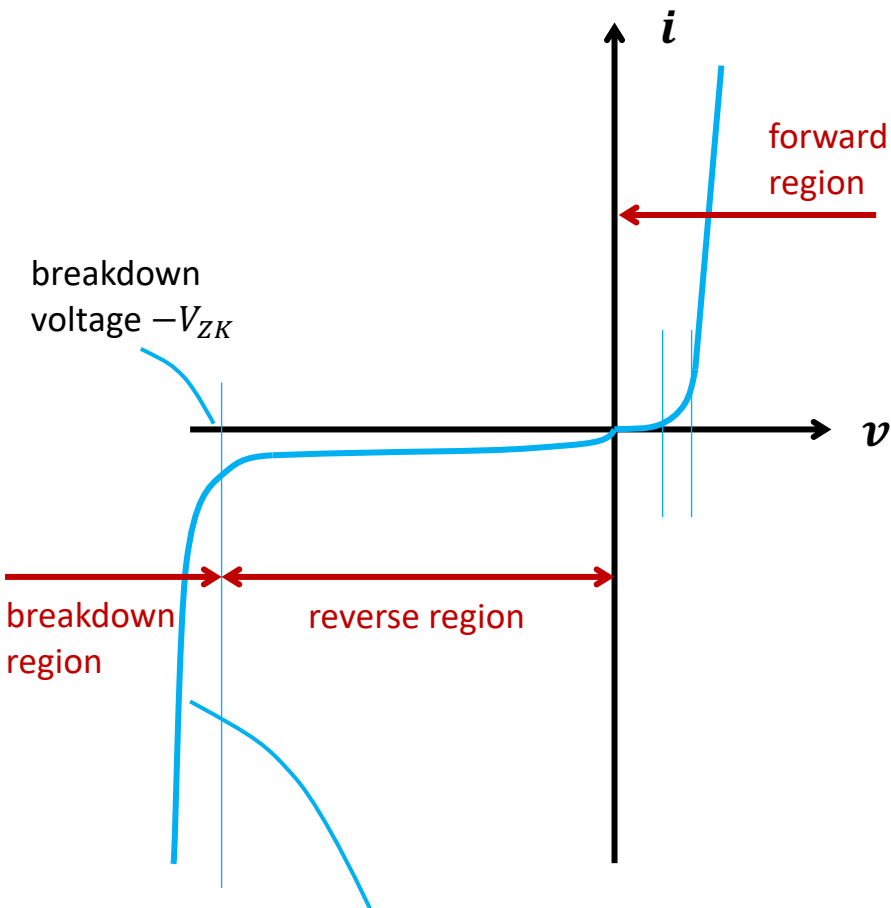


symbol

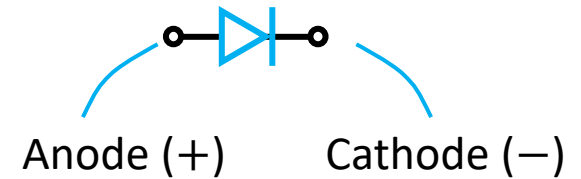

Diode

- A two-terminal device
- Current flows from Anode to Cathode

# Summary: the $pn$ junction diode

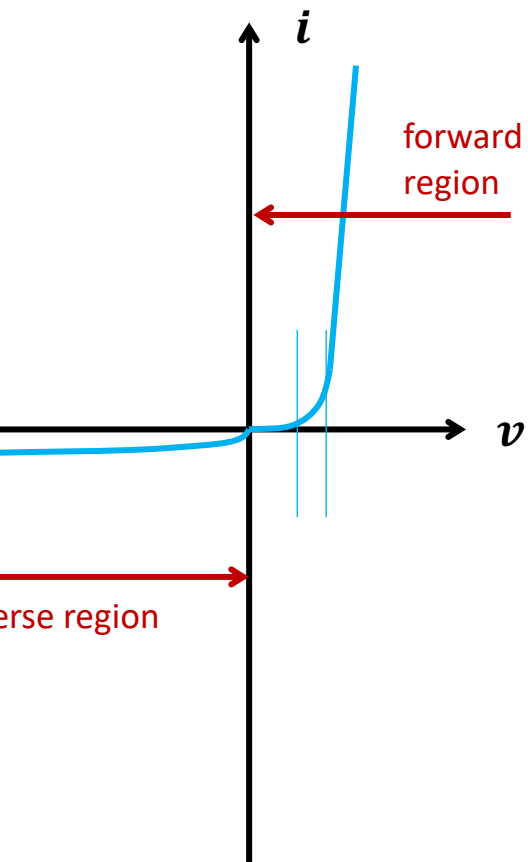

- In forward region

$$i = I_S \left( e^{\frac{v}{V_T}} - 1 \right)$$


Solution to circuit with diodes

→ KVL/KCL +  $i - v$  characteristics


→ Analytical solution **UNAVAILABLE**

## Alternative practical solutions – MODELLING


Small-signal model

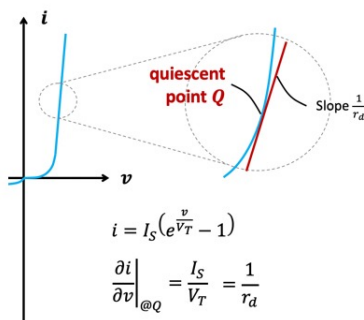

Constant-voltage drop model

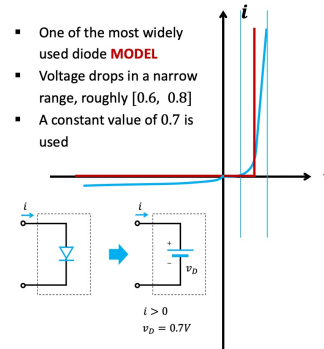

Ideal model

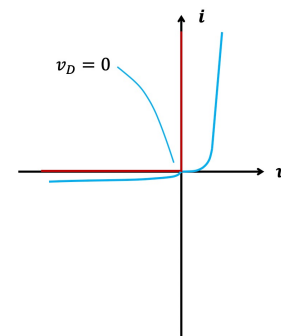




# Summary: the *pn* junction diode

- In reverse region


Modelling: no current pass through

Constant-voltage drop model

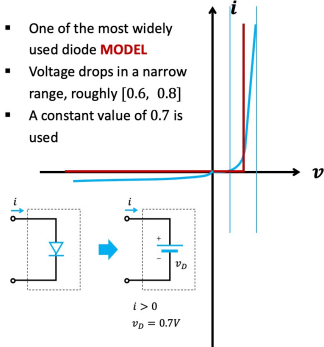
- One of the most widely used diode **MODEL**
- Voltage drops in a narrow range, roughly [0.6, 0.8]
- A constant value of 0.7 is used




Ideal model

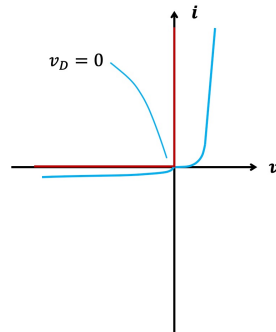

- In breakdown region

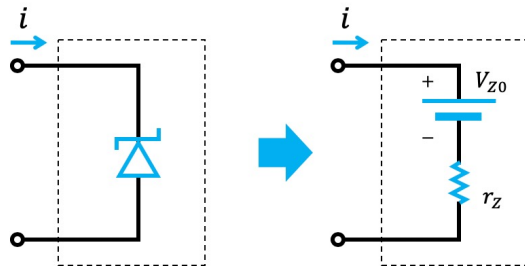

Model for Zener diode

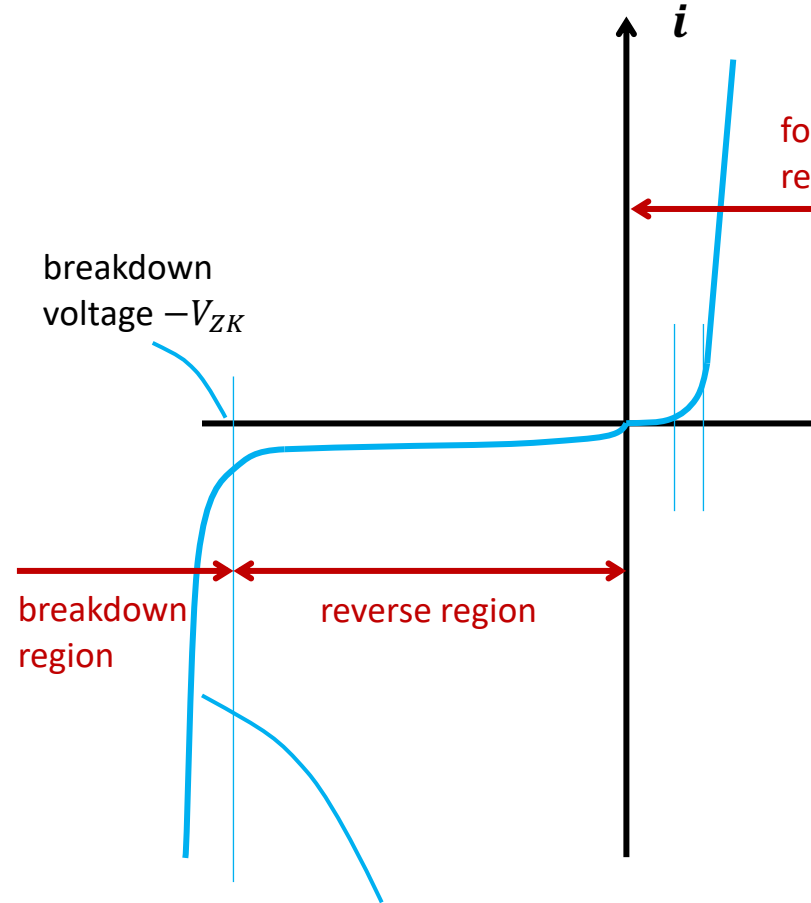


# Outline

- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - The *pn* junction
- Diodes
  - The  $i - v$  characteristics
  - The models: Constant-voltage-drop / ideal / Small-signal model
  - The 3 working regions: forward / reverse / reverse breakdown
  - **Applications of diodes**



# Example 5: full-wave rectifier

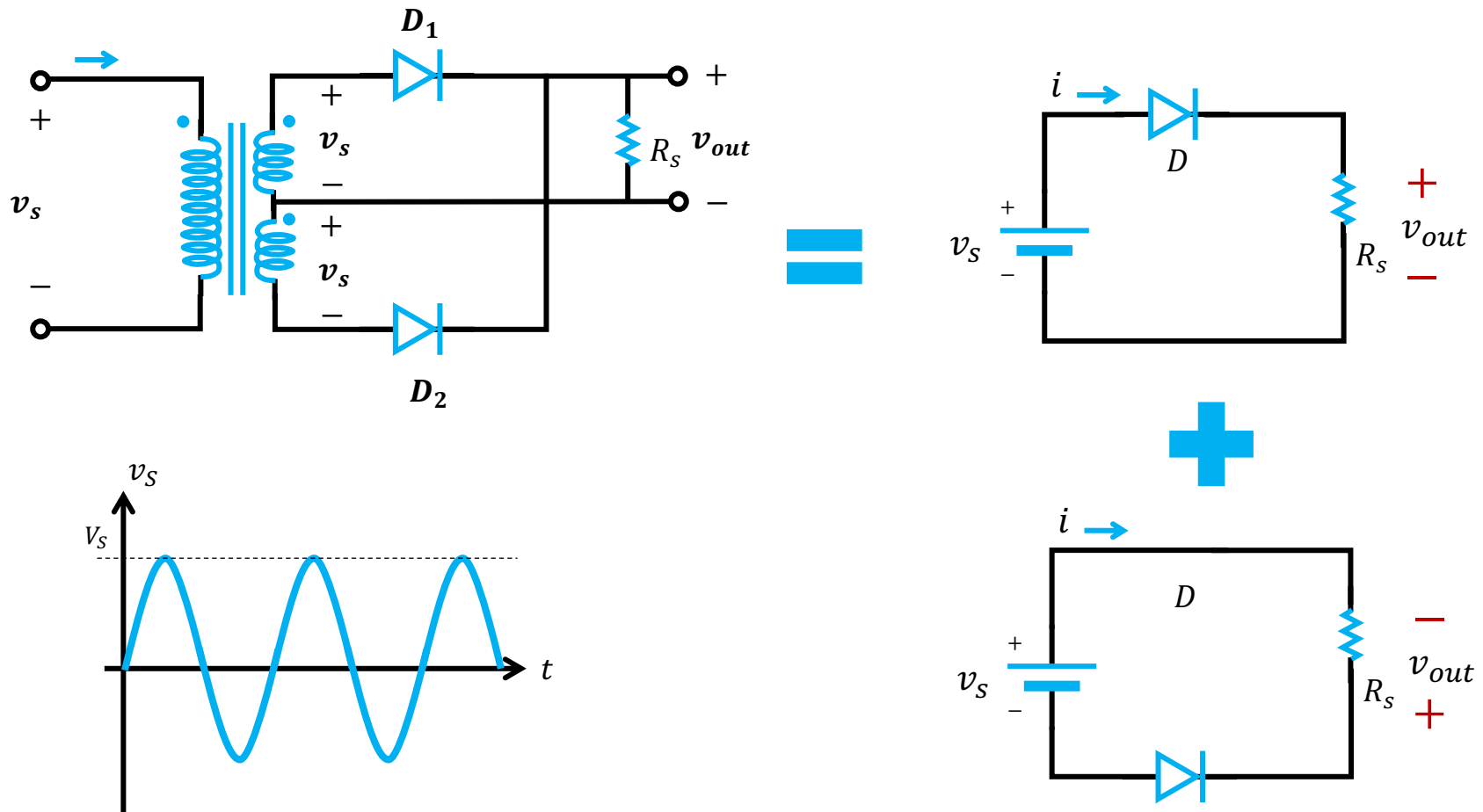QUESTION: Find the output voltage with the given input.



# Recall: half-wave rectifier

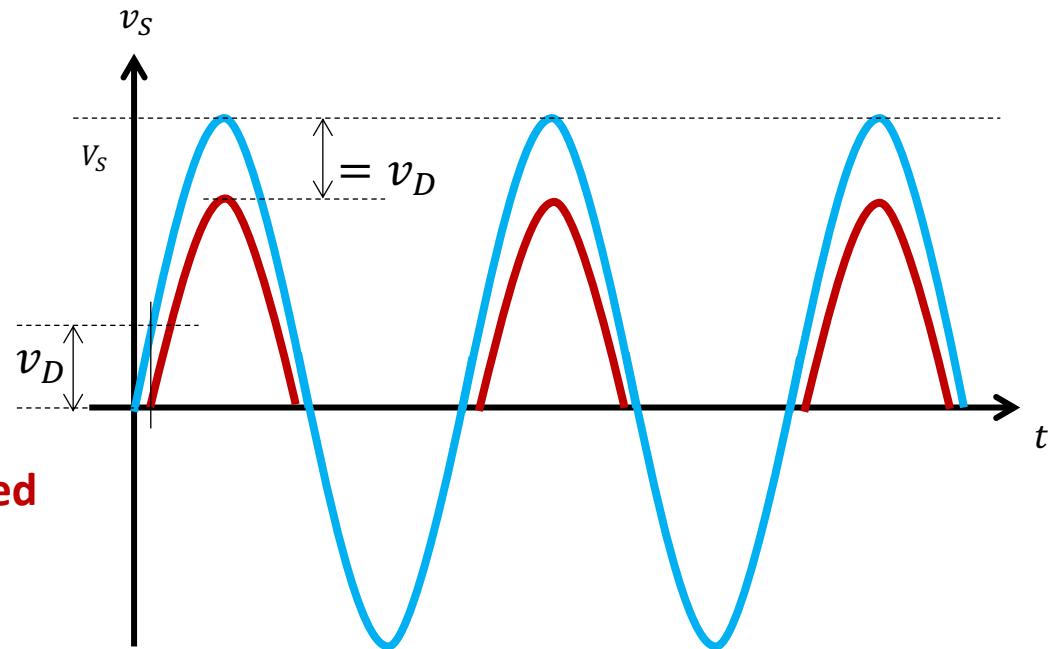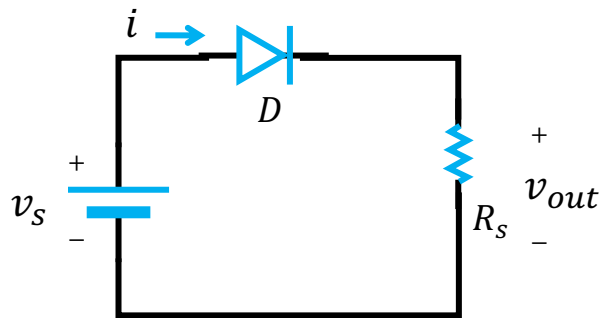**QUESTION:** Find the output voltage with the given input. The resistance of the diode must be considered




**If the diode resistance is not counted**

$$v_{out} = \begin{cases} 0 & \text{when } v_s < 0 \\ v_s - v_D & \text{when } v_s > 0 \end{cases}$$


# Example 5: full-wave rectifier

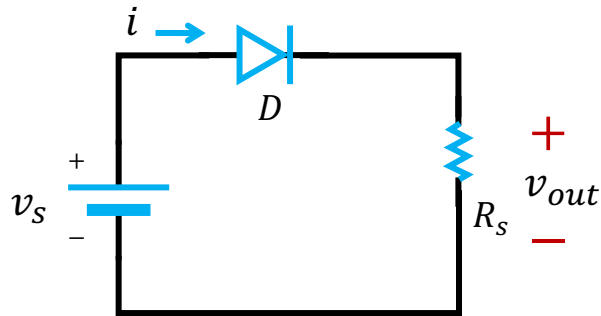**QUESTION:** Find the output voltage with the given input.



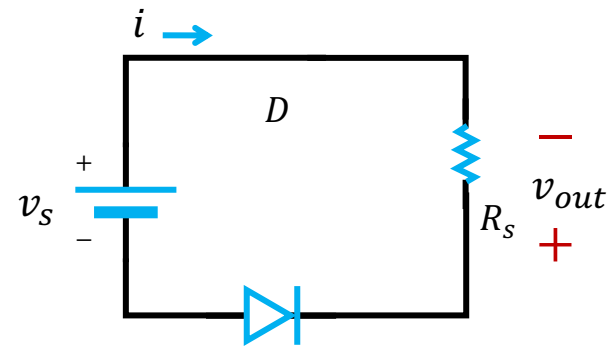**If the diode resistance is not counted**

$$v_{out} = \begin{cases} 0 & \text{when } v_s < 0 \\ v_s - v_D & \text{when } v_s > 0 \end{cases}$$




**If the diode resistance is not counted**

$$v_{out} = \begin{cases} -v_s - v_D & \text{when } v_s < 0 \\ 0 & \text{when } v_s > 0 \end{cases}$$

# Example 5: full-wave rectifier

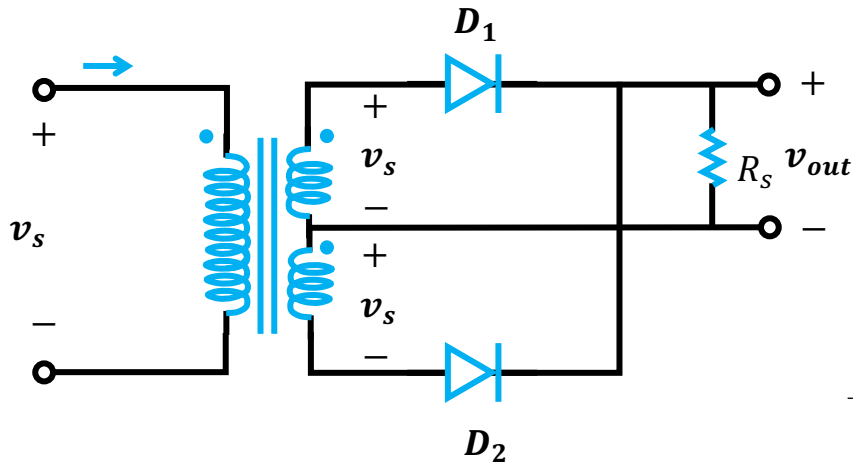
QUESTION: Find the output voltage with the given input.



Full-wave rectifier utilizes both halves of the input. It is more energetic and more useful.



If the diode resistance is not counted
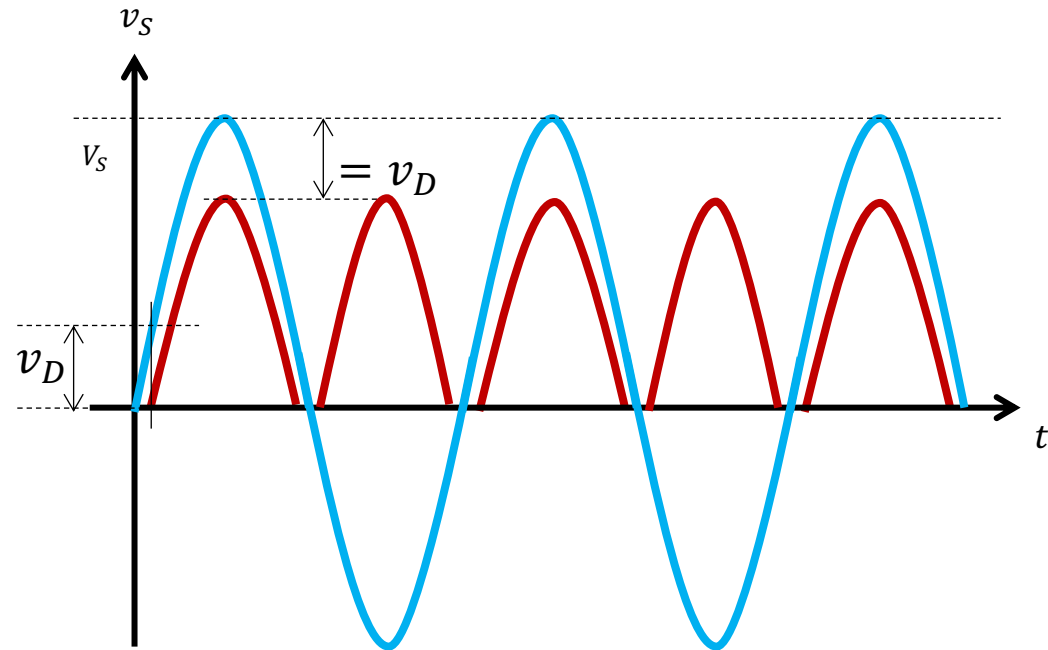
$$v_{out} = \begin{cases} -v_s - v_D & \text{when } v_s < 0 \\ v_s - v_D & \text{when } v_s > 0 \end{cases}$$



# Example 6: bridge rectifier

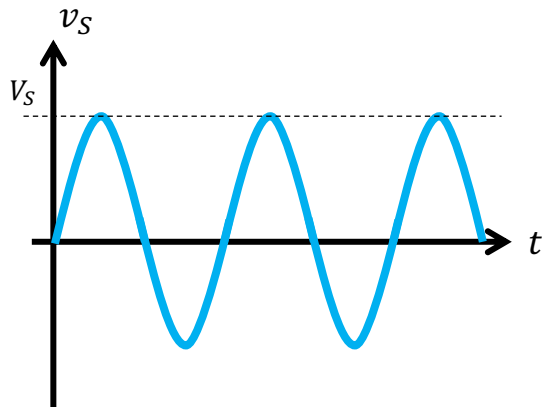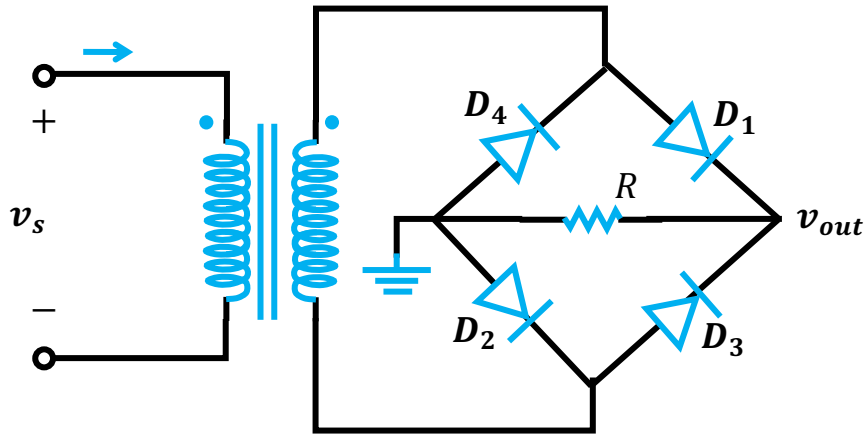**QUESTION:** Find the output voltage with the given input. The diodes are ideal.





- Each diode maybe ON/OFF
- How to solve it?
  - Step 1a: assume  $D_1$  is ON/OFF
  - Step 1b: assume  $D_2$  is ON/OFF
  - Step 1c: assume  $D_3$  is ON/OFF
  - Step 1d: assume  $D_4$  is ON/OFF

**A combination of 16 cases, a lot of work!!!**


**IS THERE A BETTER WAY?**

# Example 6: bridge rectifier

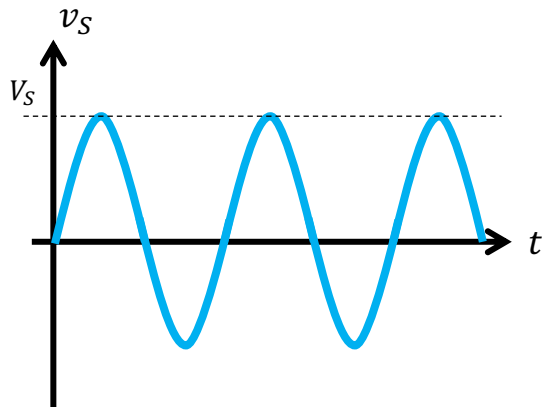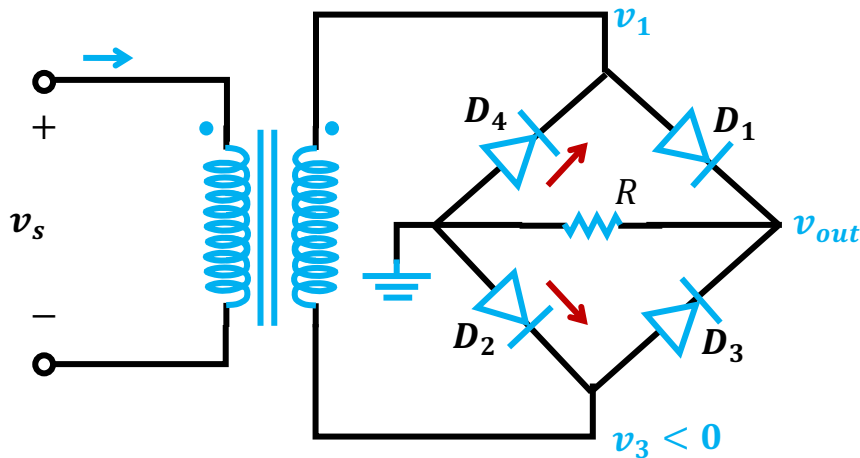**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




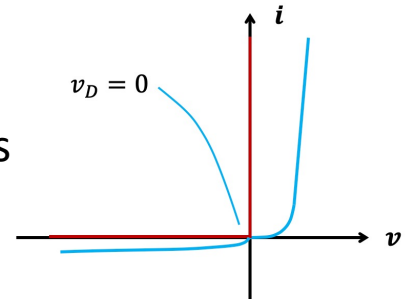
- Assume  $D_2$  is ON
- According to the  $i - v$  characteristics of ideal diode
  - $\rightarrow v_3 < 0$
- If  $D_4$  is also ON  $\rightarrow v_1 < 0$
- Only 1 possible path for current flow






# Example 6: bridge rectifier

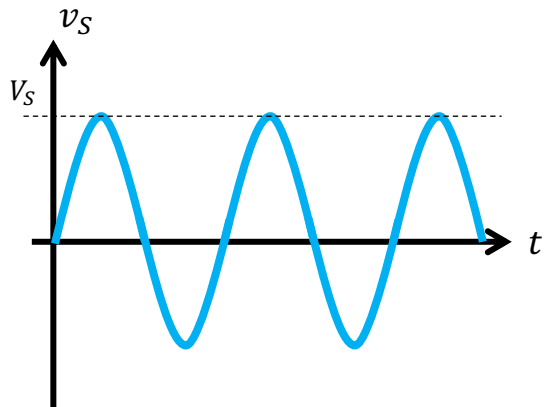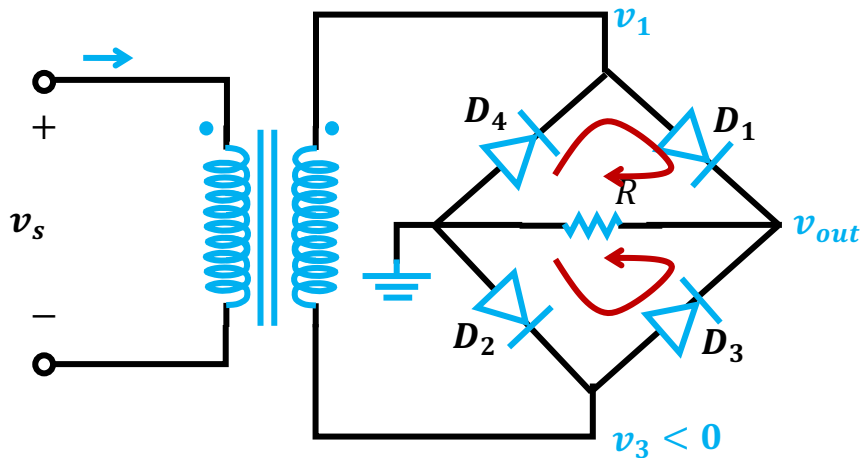**QUESTION:** Find the output voltage with the given input. The diodes are ideal.



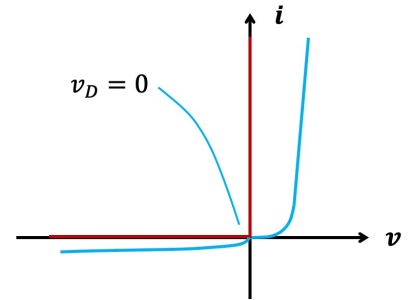- Assume  $D_2$  is ON
- According to the  $i - v$  relationship of ideal diode



$\rightarrow v_3 < 0$


- If  $D_4$  is also ON  $\rightarrow v_1 < 0$  **X**
- Only 1 possible path for current flow

requiring  $\begin{cases} D_1 \text{ is ON} \rightarrow v_{out} < 0 \\ v_{out} > 0 \end{cases}$


**IMPOSSIBLE**

# Example 6: bridge rectifier

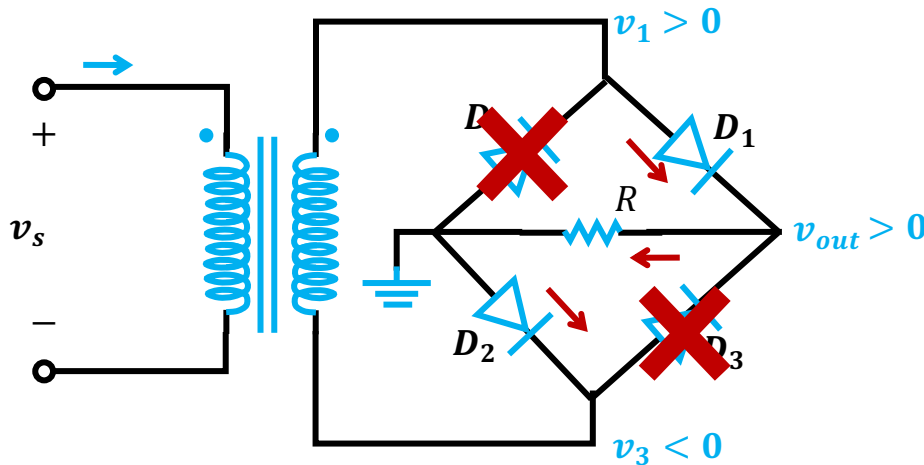**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




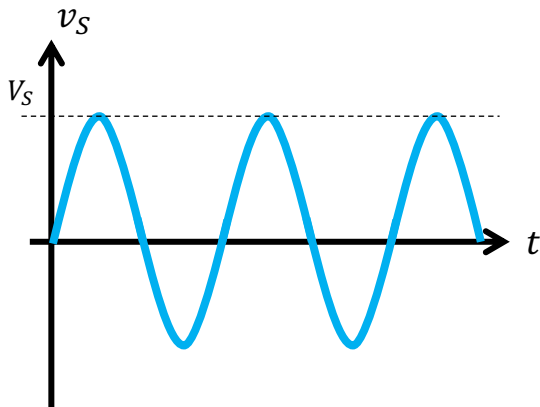- Assume  $D_2$  is ON
- According to the  $i - v$  relationship of ideal diode  $\rightarrow v_3 < 0$
- $D_4$  must be OFF  $\rightarrow v_1 > 0$
- According to KCL, current goes through  $R$   
 $\rightarrow v_{out} > 0$
- $D_3$  is OFF, since  $v_3 < v_{out}$
- According to KCL, current goes through  $D_1$   
 $\rightarrow v_1 > v_{out}$




# Example 6: bridge rectifier

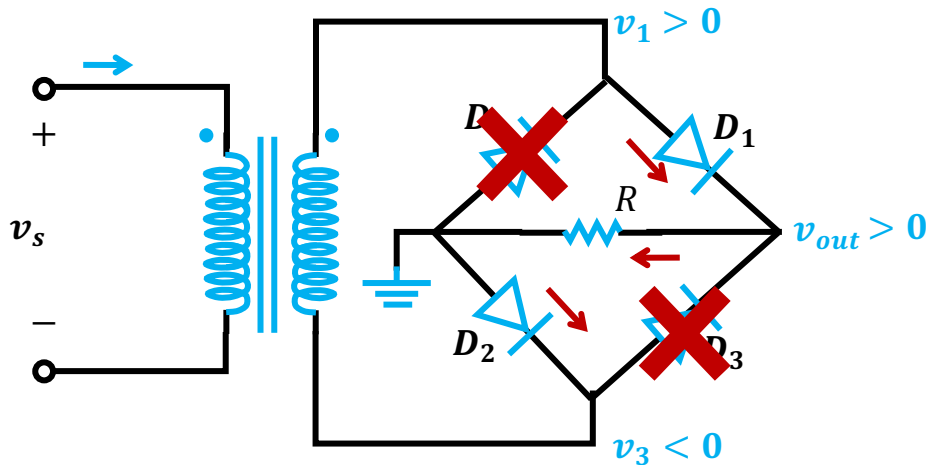**QUESTION:** Find the output voltage with the given input. The diodes are ideal.





- Assume  $D_2$  is ON
- $D_1$  must be ON
- $D_3$  must be OFF
- $D_4$  must be OFF
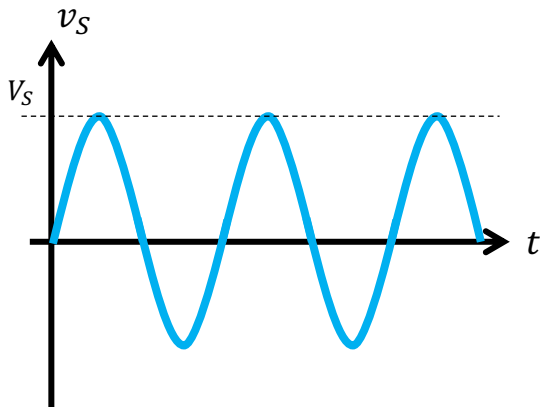
$$\left\{ \begin{array}{l} v_1 > v_{out} > 0 \\ v_3 < 0 \end{array} \right. \rightarrow \text{requiring } v_s > 0$$



# Example 6: bridge rectifier

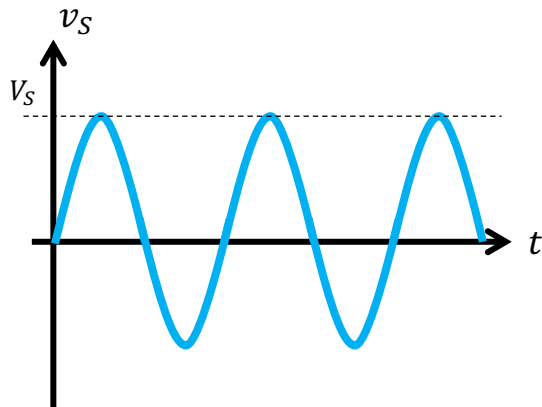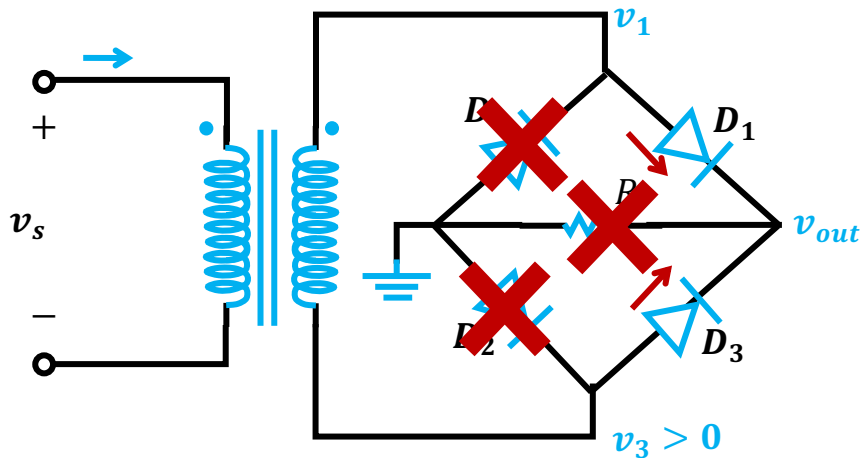**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




- Assume  $D_2$  is OFF
- According to the  $i - v$  characteristics of ideal diode  $\rightarrow v_3 > 0$
- If  $D_4$  is also OFF **X**
- According to KCL, no current through  $R$
- Only 1 possible path for current flow  
 $D_1$  and  $D_3$  must be ON at the same time


**Conflict of current flow direction!!!**

# Example 6: bridge rectifier

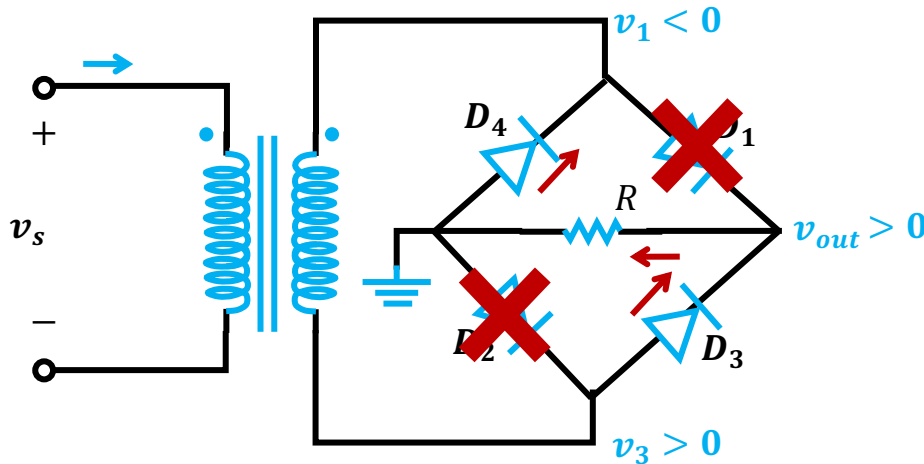**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




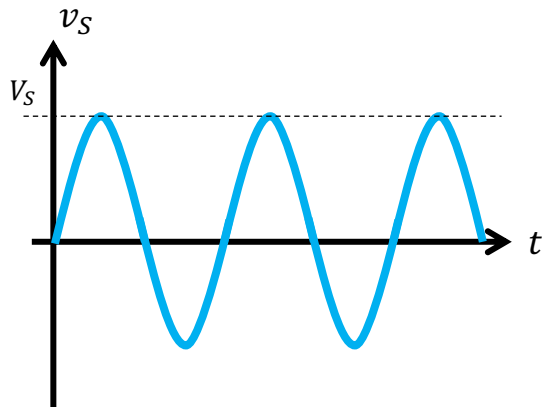- Assume  $D_2$  is OFF
- According to the  $i - v$  relationship of ideal diode  $\rightarrow v_3 > 0$
- $D_4$  must be ON  $\rightarrow v_1 < 0$
- According to KCL, current goes through  $R$   
 $\rightarrow v_{out} > 0$
- $D_1$  is OFF, since  $v_1 < v_{out}$
- According to KCL, current goes through  $D_4$   
 $\rightarrow v_3 > v_{out}$




# Example 6: bridge rectifier

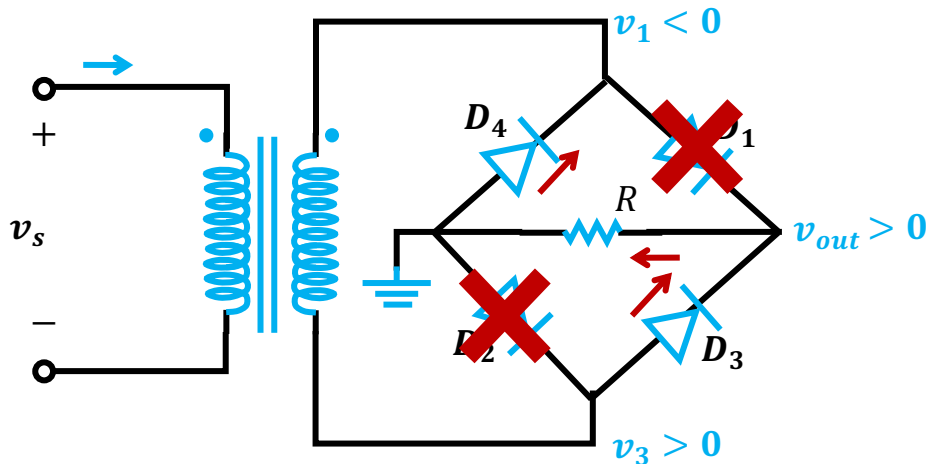**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




- Assume  $D_2$  is OFF
- $D_1$  must be OFF
- $D_3$  must be ON
- $D_4$  must be ON
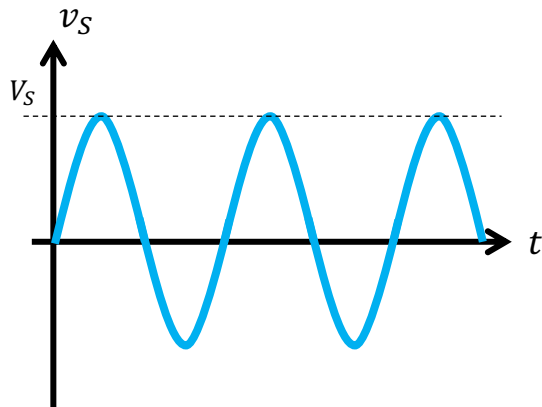
$$\begin{cases} v_3 > v_{out} > 0 \\ v_1 < 0 \end{cases} \rightarrow \text{requiring } v_s < 0$$




# Example 6: bridge rectifier

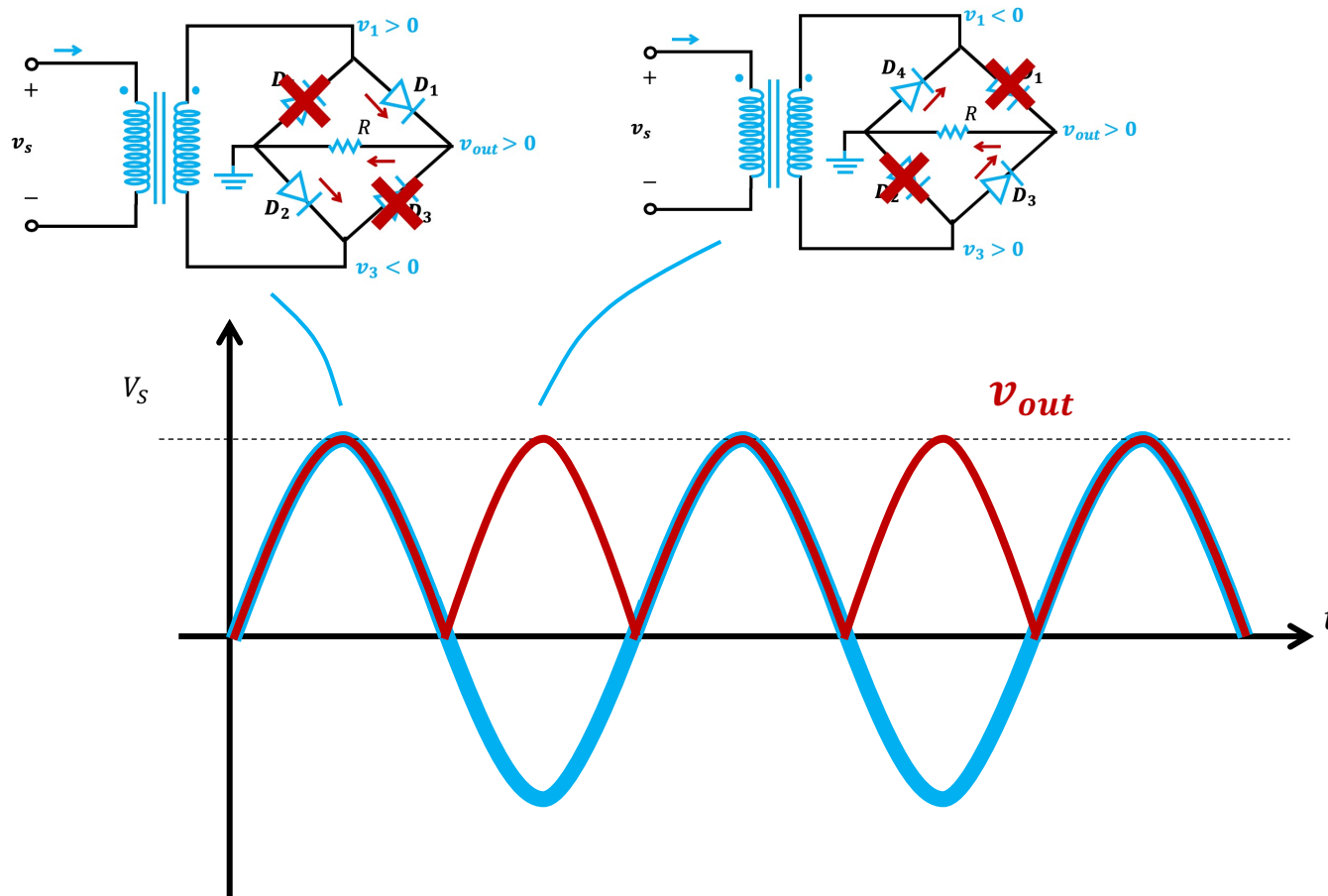**QUESTION:** Find the output voltage with the given input. The diodes are ideal.




# Example 7: peak rectifier

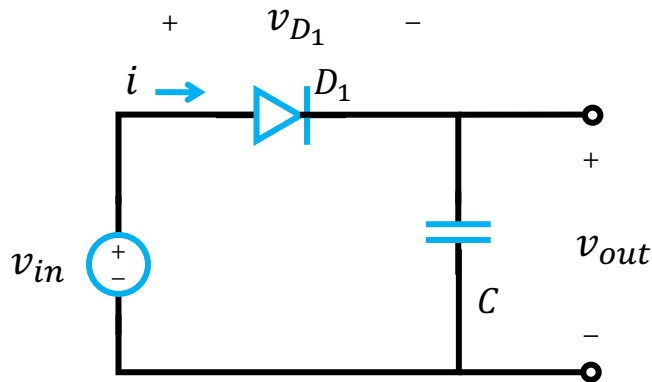**QUESTION:** Find the output voltage with the given input. Use the constant-voltage-drop model of the diode with  $v_D = 0.7V$ .  $v_{out} = 0$  at  $t = 0$ .



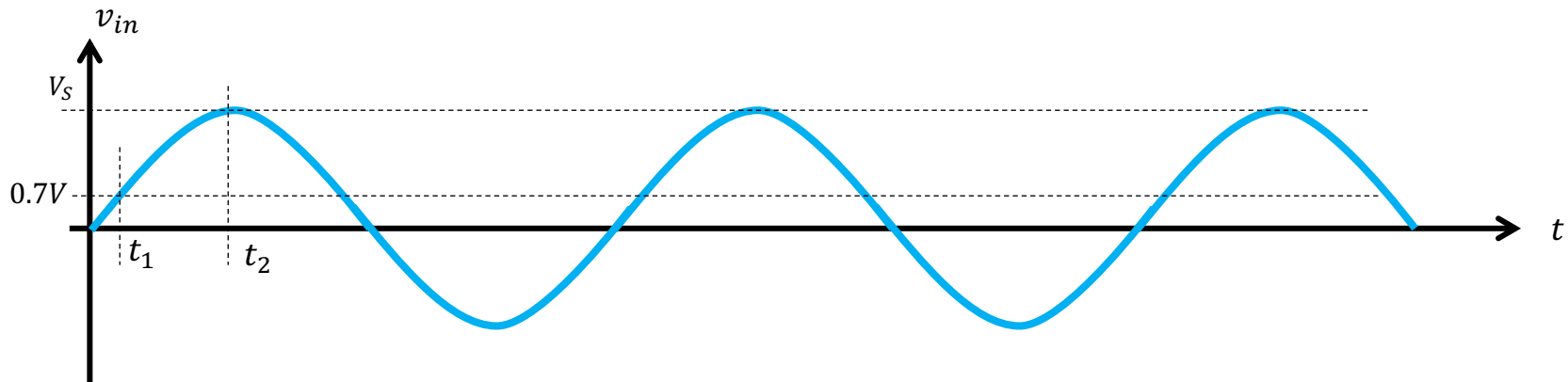
- When  $t < t_1$   
 $v_{D_1} = v_{in} - v_{out} < v_D$   
The diode is OFF  
 $\rightarrow v_{out} = 0$






# Example 7: peak rectifier

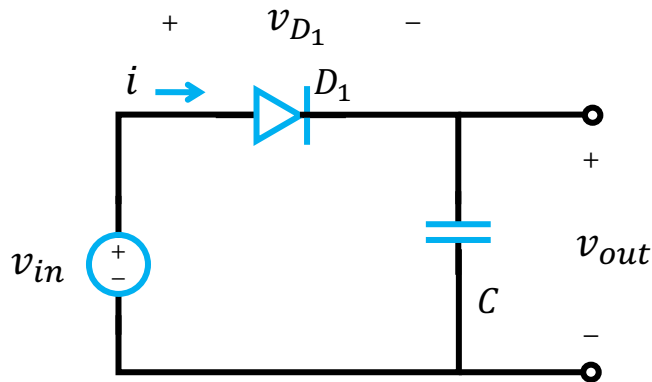**QUESTION:** Find the output voltage with the given input. Use the constant-voltage-drop model of the diode with  $v_D = 0.7V$ .  $v_{out} = 0$  at  $t = 0$ .




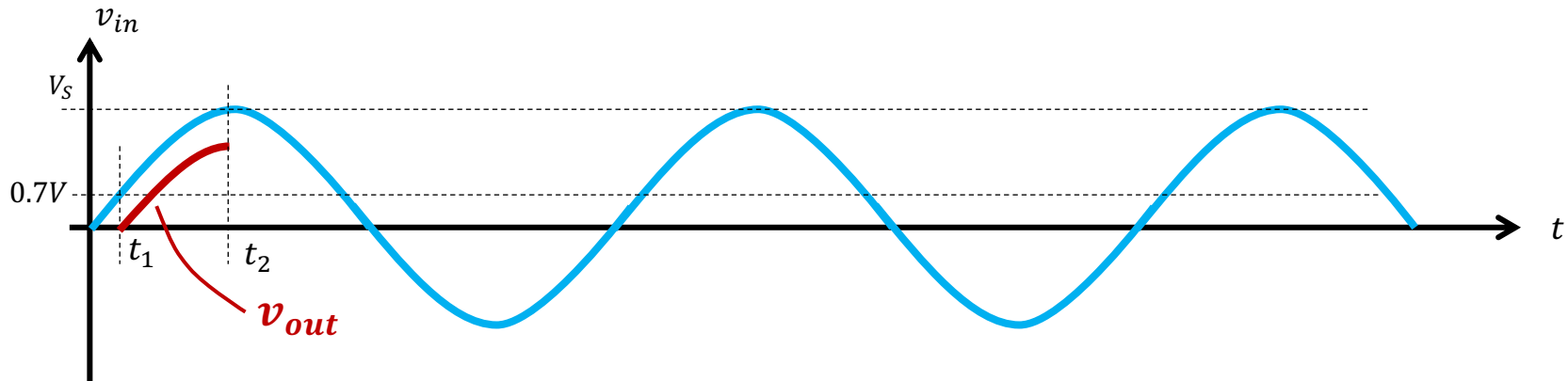- When  $t \in [t_1, t_2]$   
 $v_{D_1} = v_{in} - v_{out} > v_D$   
The diode is ON.  $C$  charged to the peak.  
 $\rightarrow v_{out} = v_{in} - v_D$




# Example 7: peak rectifier

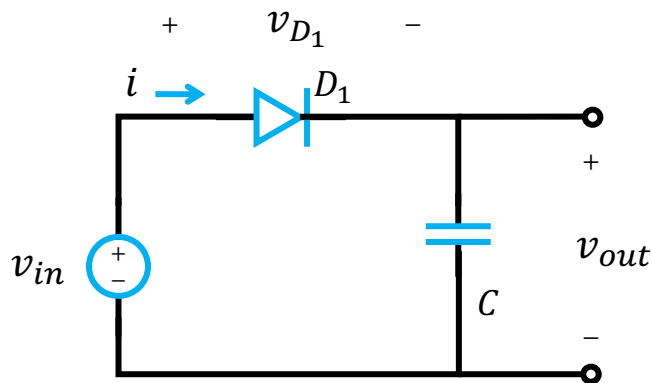**QUESTION:** Find the output voltage with the given input. Use the constant-voltage-drop model of the diode with  $v_D = 0.7V$ .  $v_{out} = 0$  at  $t = 0$ .





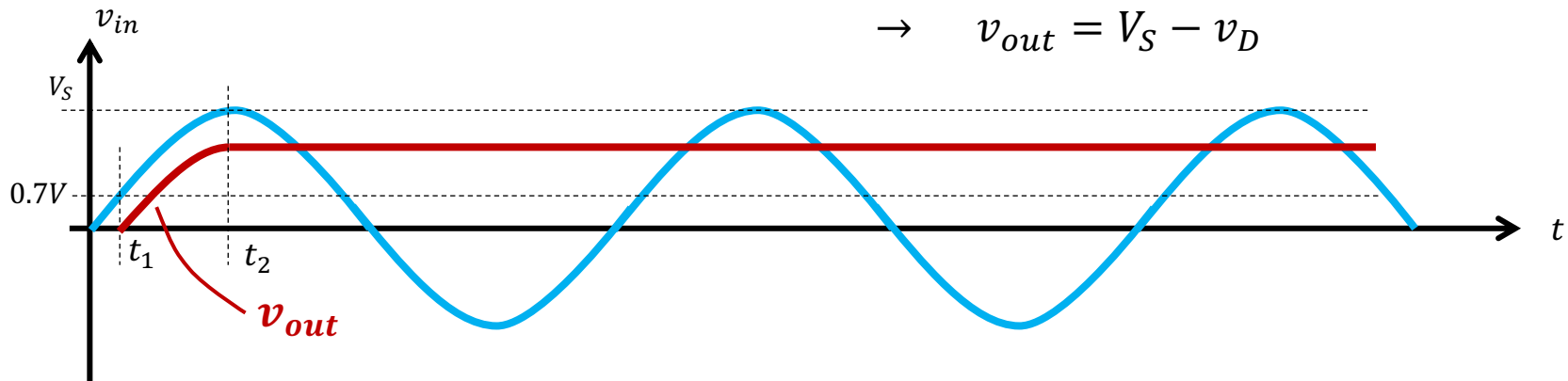- When  $t > t_2$ 
  - $v_{D_1} = v_{in} - v_{out} < v_D$
  - The diode is OFF.
  - There is no way to discharge  $C$
  - $\rightarrow v_{out} = V_S - v_D$



# Example 8: peak rectifier

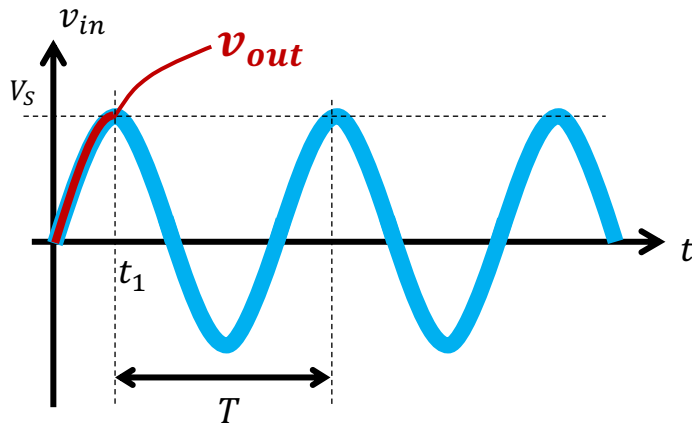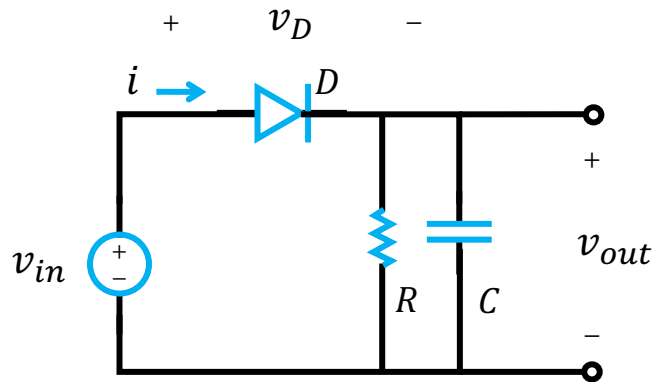
**QUESTION:** Find the output voltage with the given input. The diode is ideal.  $v_{out} = 0$  at  $t = 0$ .  $RC$  is much larger than  $T$



- When  $t < t_1$   
 $v_{D1} = v_{in} - v_{out} > 0$   
The diode is ON.  $C$  charges to the peak  $V_S$   
 $\rightarrow v_{out} = v_{in}$
- When  $t > t_1$   
 $v_{D1} = v_{in} - v_{out} < 0$   
The diode is OFF.  
 $C$  discharges through  $R$


# Example 8: peak rectifier

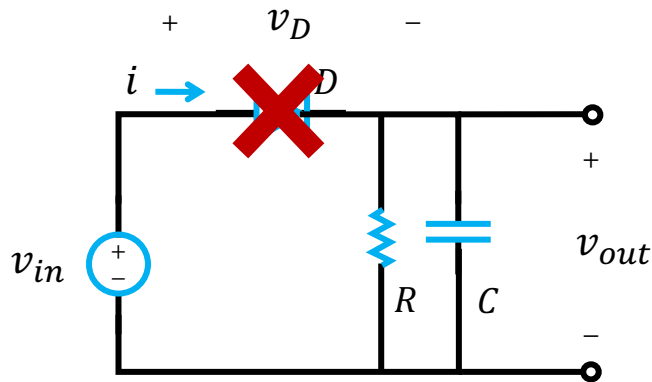**QUESTION:** Find the output voltage with the given input. The diode is ideal.  $v_{out} = 0$  at  $t = 0$ .  $RC$  is much larger than  $T$




- According to KCL
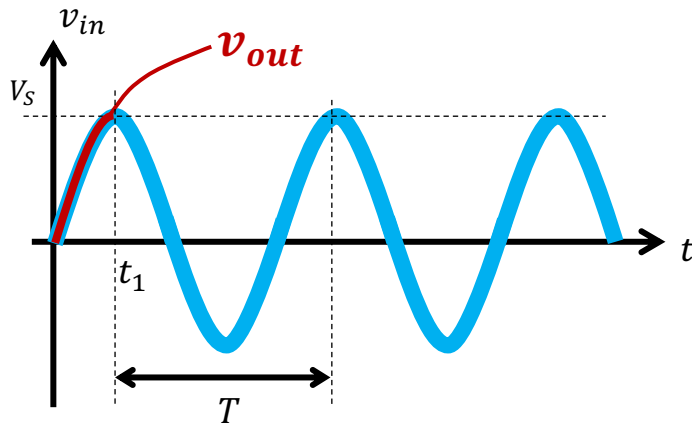
$$\frac{v_{out}}{R} + C \frac{dv_{out}}{dt} = 0$$





# Recall: Source free RC circuit

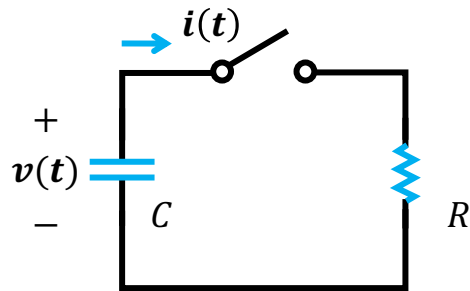**QUESTION:** Assume the capacitor  $C$  has been charged to  $V_0$  before the switch is turned on. Find the response after the switch is turned on.





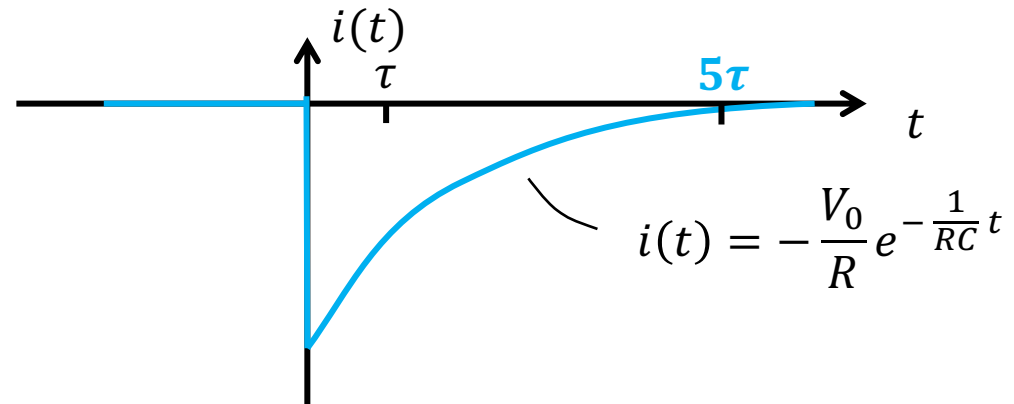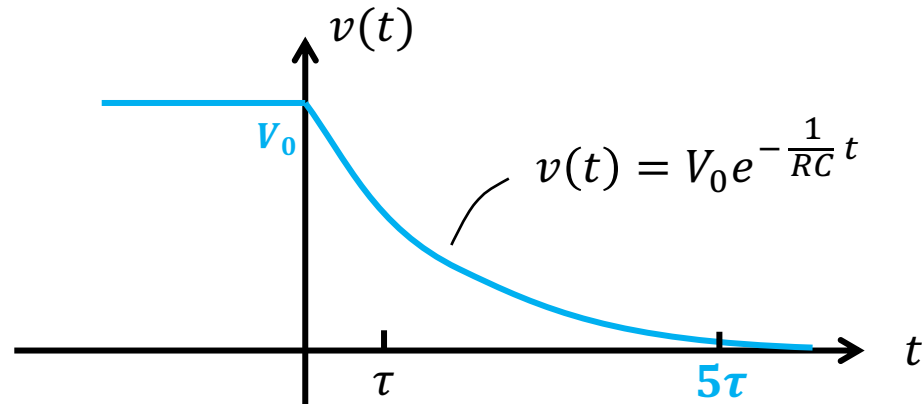Voltage on capacitor  
CANNOT change abruptly,  
but current can.



# Example 8: peak rectifier

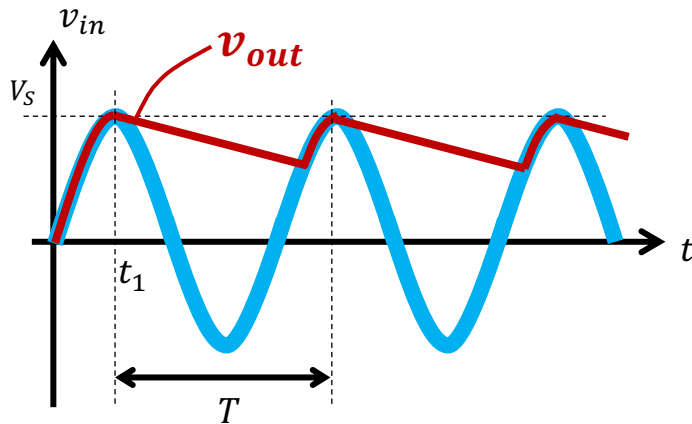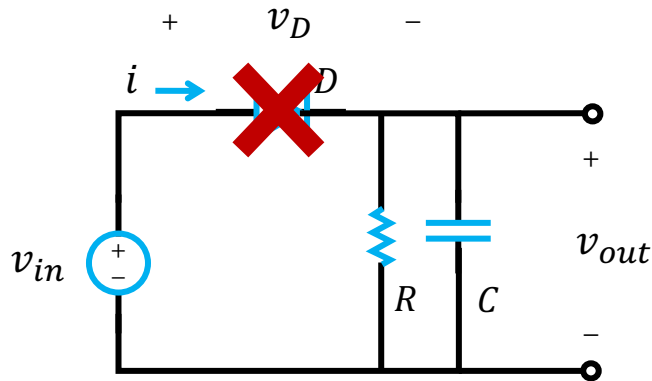**QUESTION:** Find the output voltage with the given input. The diode is ideal.  $v_{out} = 0$  at  $t = 0$ .  $RC$  is much larger than  $T$



- According to KCL

$$\frac{v_{out}}{R} + C \frac{dv_{out}}{dt} = 0$$


$$v(t) = V_S e^{-\frac{1}{RC}t}$$

- Since  $CR \gg T$


$$v(T) = V_S e^{-\frac{T}{RC}} \approx V_S \left(1 - \frac{T}{RC}\right)$$

# Example 9: precision half-wave rectifier

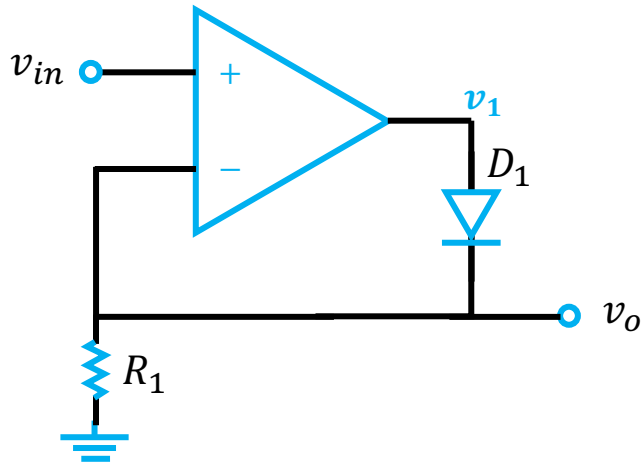**QUESTION:** Find the output voltage with the given input. The diode is not ideal.




- Assume  $D_1$  is ON

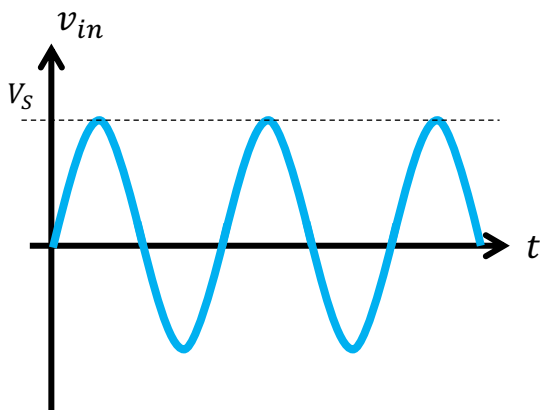

# Recall: Op-Amp & Feedback

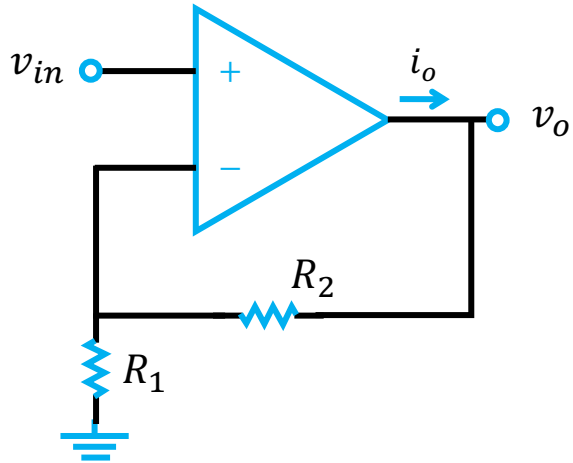**QUESTION:** Find the output of the circuit,  $v_o$ , and the relationship between  $i_o$  and  $v_{in}$ .



$$\left\{ \begin{array}{l} i_{R_1} = \frac{v_n}{R_1} = \frac{v_{in}}{R_1} \\ i_{R_2} = \frac{v_o - v_n}{R_2} = \frac{v_o - v_{in}}{R_2} \\ i_{R_1} = i_{R_2} \end{array} \right.$$


**IDEAL OP-AMP with NEGATIVE FEEDBACK enables linear region biasing**

$$\Rightarrow v_o = \frac{R_1 + R_2}{R_1} v_{in}$$



# Example 9: precision half-wave rectifier

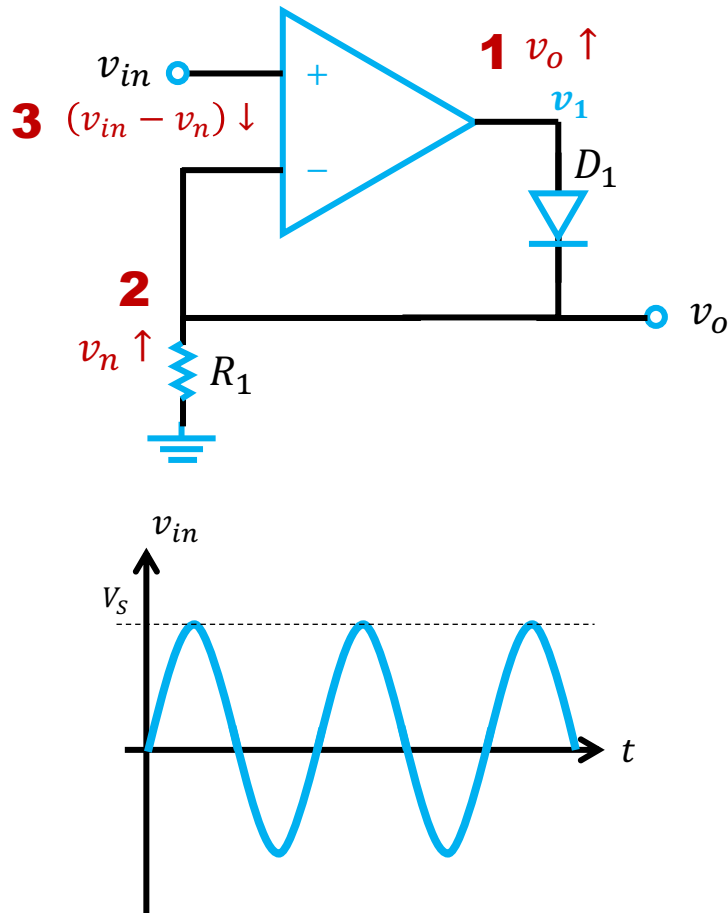**QUESTION:** Find the output voltage with the given input. The diode is not ideal.



- Step 1: Assume  $D_1$  is ON
- Step 2: check if negative feedback



- If there is an increase @  $v_o$   $v_o \uparrow$
- The inverting input  $v_n$  increases correspondingly
- If the op-amp is biased in the linear region,  $v_o = A(v_{in} - v_n)$  decreases



**NEGATIVE FEEDBACK is observed**

# Example 9: precision half-wave rectifier

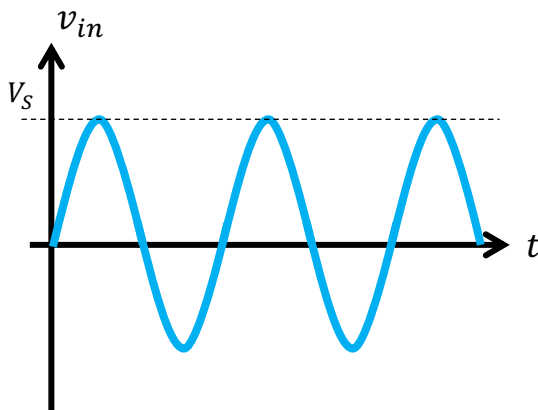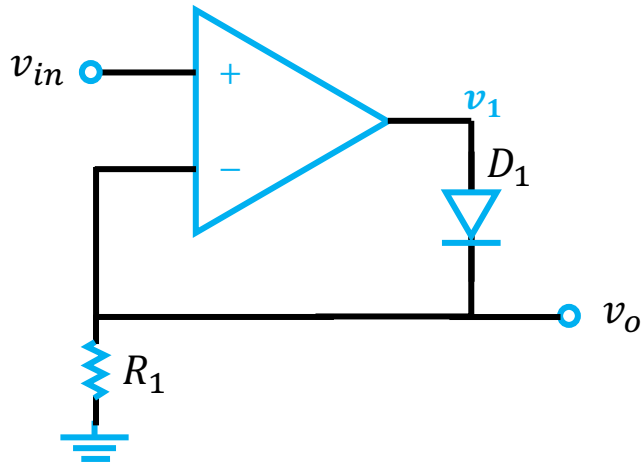**QUESTION:** Find the output voltage with the given input. The diode is not ideal.



- Step 1: Assume  $D_1$  is ON
- Step 2: check if negative feedback
- Step 3a: ideal op-amp
  - open circuit @ inputs
  - $i_p = i_n = 0$
- Step 3b: “short” the inputs



$$v_n = v_p = v_{in} = v_o$$

$$i_{R_1} = \frac{v_{in}}{R_1}$$

$$v_1 = v_o + v_{D_1} = v_{in} + v_{D_1}$$

# Example 9: precision half-wave rectifier

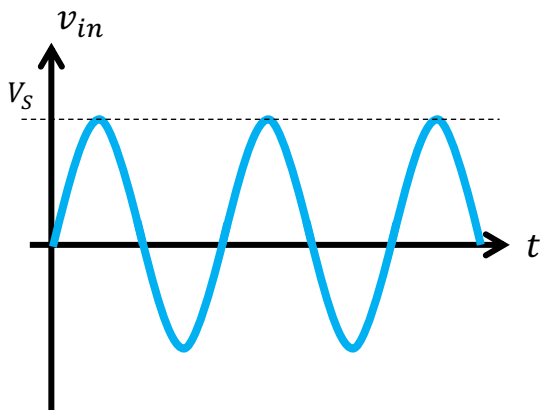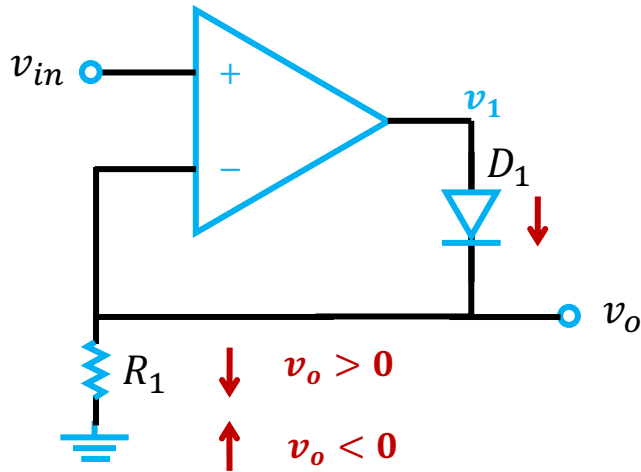**QUESTION:** Find the output voltage with the given input. The diode is not ideal.



- Step 1: Assume  $D_1$  is ON
- Step 2: check if negative feedback
- Step 3: solve the circuit

$$v_n = v_p = v_{in} = v_o$$

$$v_1 = v_{in} + v_{D_1}$$

- Step 4: check the assumption


$$\text{If } v_{in} > 0 \quad \rightarrow \quad v_o > 0$$

$$\text{If } v_{in} < 0 \quad \rightarrow \quad v_o < 0$$




# Example 9: precision half-wave rectifier

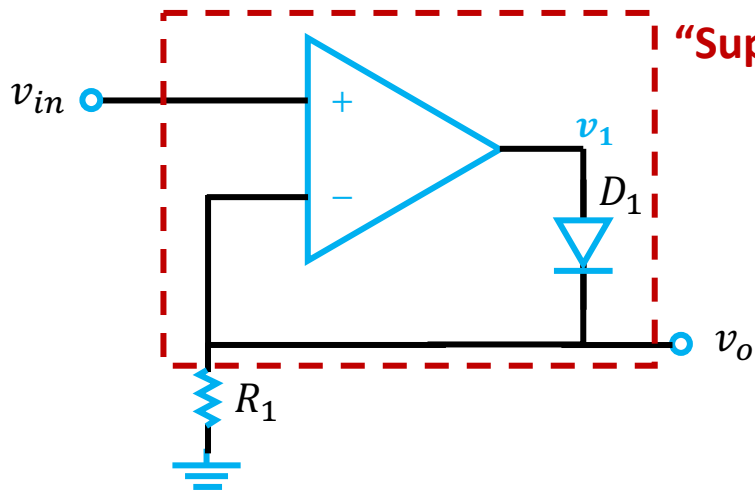**QUESTION:** Find the output voltage with the given input. The diode is not ideal.



$$v_o = \begin{cases} v_{in} & \text{If } v_{in} > 0 \\ 0 & \text{If } v_{in} < 0 \end{cases}$$

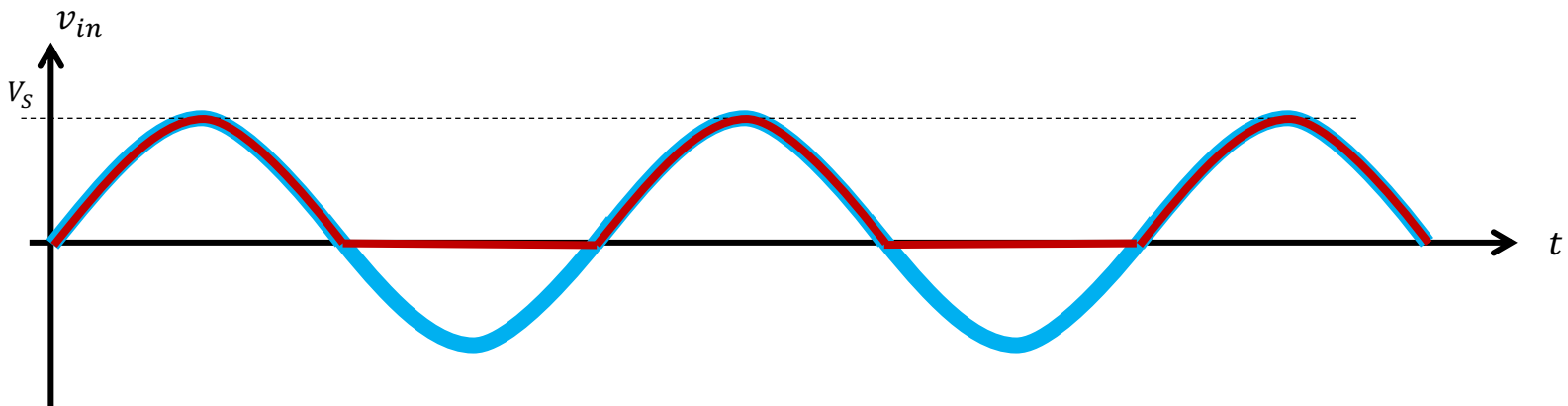
The offset voltage due to the diode is no longer present in the output



# Summary: rectifier

AC POWER

DC POWER

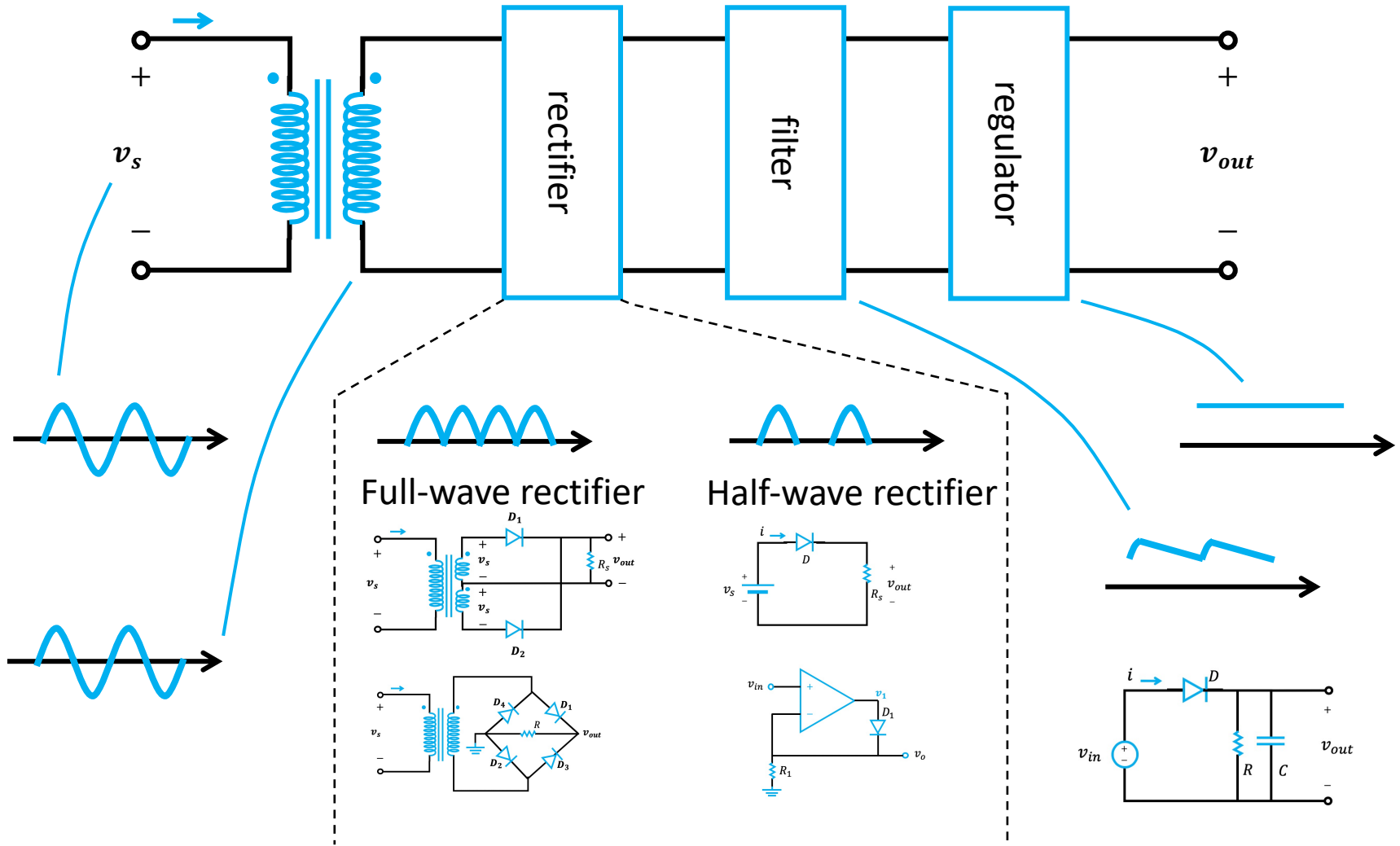

# Outline

## ■ Introduction to semiconductors


- Semiconductor material & silicon crystal
- Doped semiconductors
- Current flow in semiconductor
- The *pn* junction

## ■ Diodes

- The  $i - v$  characteristics
- The models: Constant-voltage-drop / ideal / Small-signal model
- The 3 working regions: forward / reverse / reverse breakdown
- Applications of diodes
  - Rectifiers
  - **Limiting & clamping circuits**

# Recall: Example 2: limiting circuit

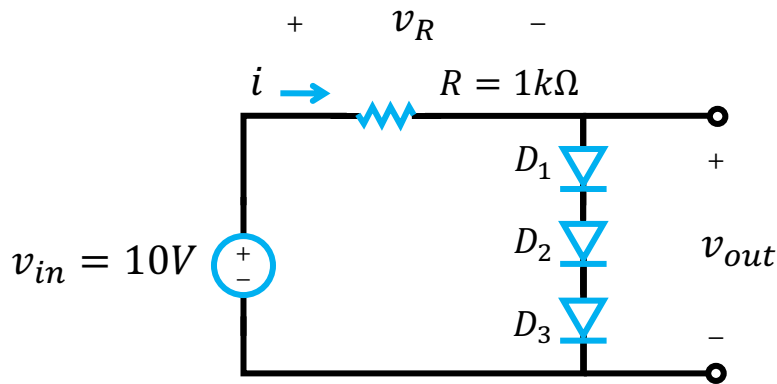**QUESTION:** Find the current through the resistor  $R$ .




- Use the constant-voltage-drop model

$$v_{out} = 0.7V \times 3 = 2.1V$$


- According to KVL
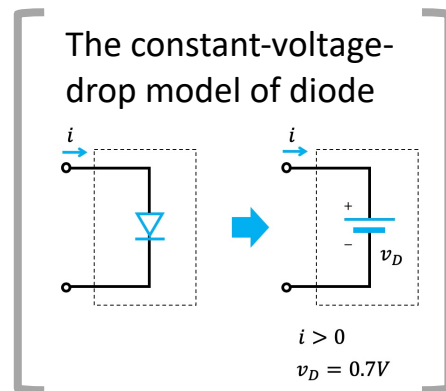
$$I_R = \frac{v_{in} - v_{out}}{R} = 7.9mA$$



# Example 10: limiting circuit

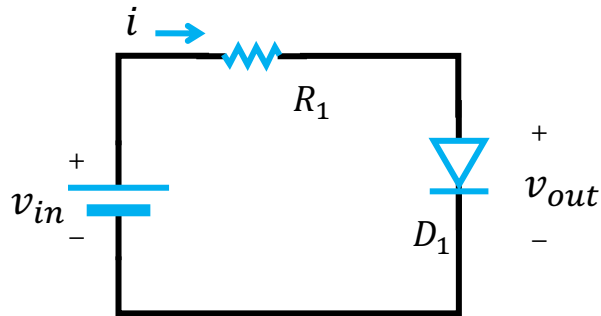**QUESTION:** Find the transfer function between the input and output voltage



- Use the constant-voltage-drop model


- If  $v_{in} > 0.7V$ , according to KVL

$$v_{out} = 0.7V$$

$$v_{R_1} = v_{in} - 0.7V$$

- If  $v_{in} < 0.7V$ ,  $D_1$  is OFF



$$v_{out} = v_{in}$$

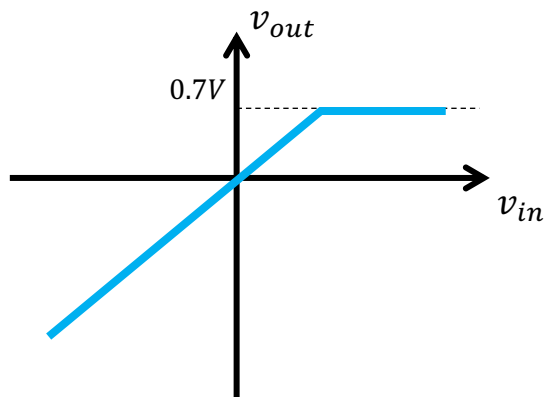



# Example 11: DC restorer

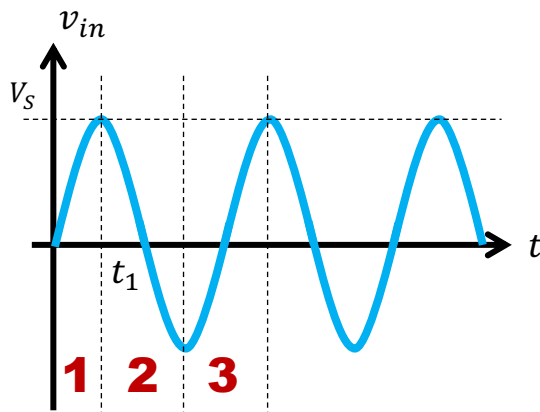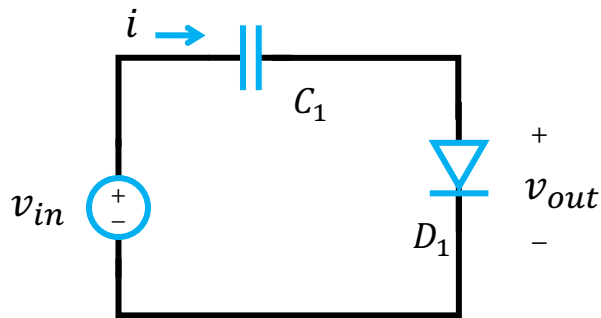**QUESTION:** Find the output voltage with the given input. The diode is ideal.  $v_{out} = 0$  at  $t = 0$ .



- In phase 1

$D_1$  is ON

According to KVL

$$v_{C_1} = v_{in} \quad v_{D_1} = 0$$

$$v_{C_1}(t = t_1) = V_S$$

- In phase 2


$D_1$  is OFF

Voltage on  $C_1$  CANNOT change abruptly

$$v_{out} = v_{in} - V_S$$

# Example 11: DC restorer

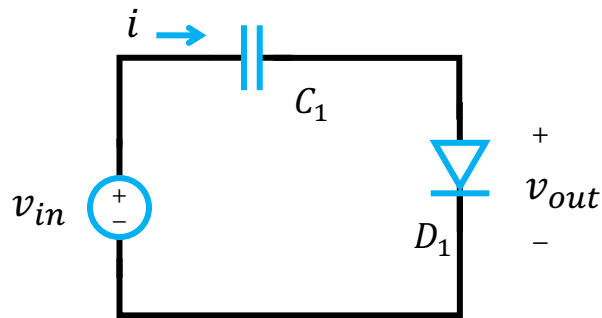
**QUESTION:** Find the output voltage with the given input. The diode is ideal.  $v_{out} = 0$  at  $t = 0$ .



▪ In phase 3

$D_1$  is OFF




$$v_{out} = v_{in} - V_S$$

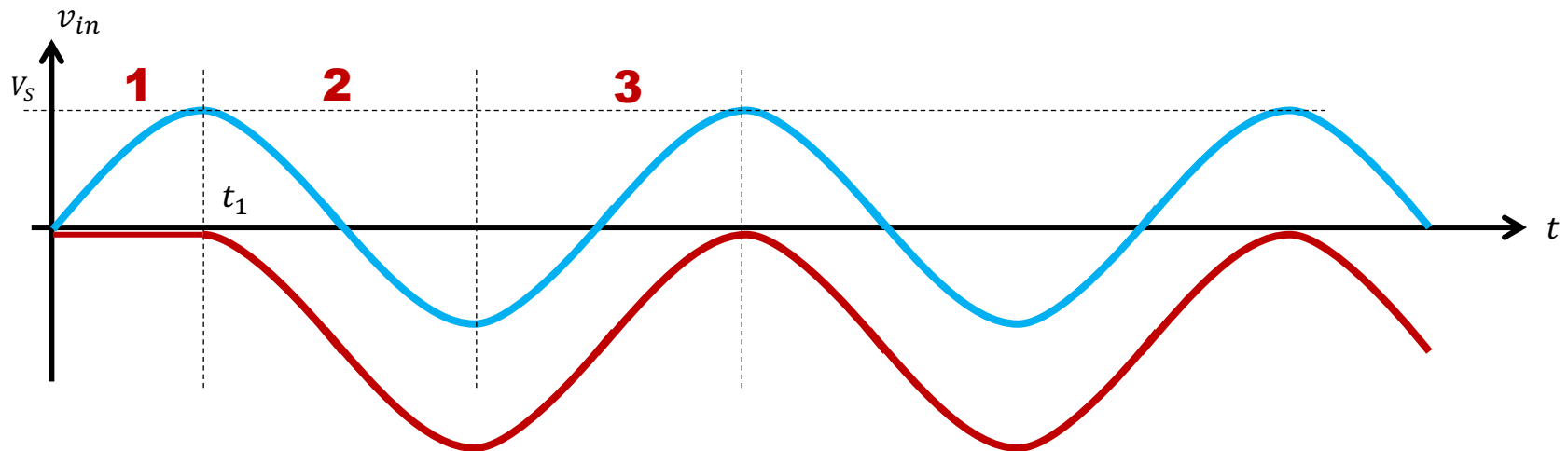

# Outline


- Introduction to semiconductors
  - Semiconductor material & silicon crystal
  - Doped semiconductors
  - Current flow in semiconductor
  - The *pn* junction
- Diodes
  - The  $i - v$  characteristics
  - The models: Constant-voltage-drop / ideal / Small-signal model
  - The 3 working regions: forward / reverse / reverse breakdown
  - Applications of diodes
    - Rectifiers
    - Limiting & clamping circuits
  - **Special diodes**

# Light-Emitting Diodes (LEDs)

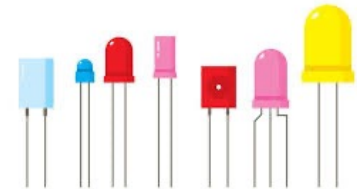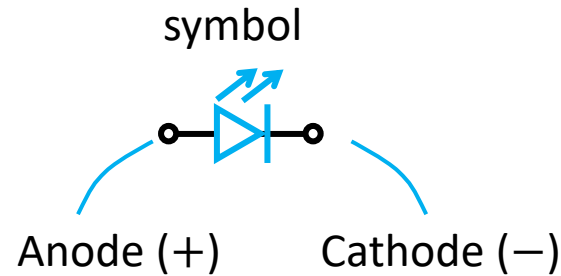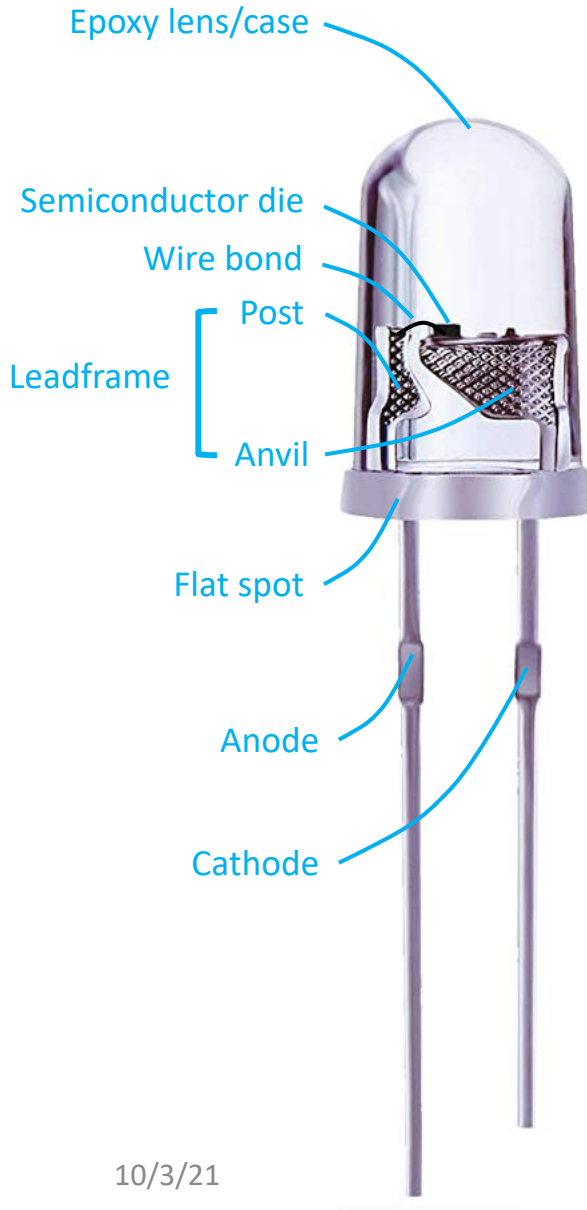

- Convert a **forward current** into **light**
- The light emitted by an LED is proportional to the forward current in the diode


# Photodiodes

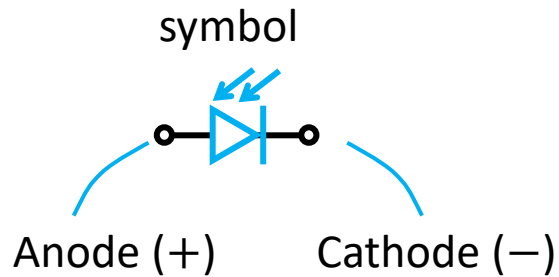

- Photodiode is a reverse-biased  $pn$  junction
- Convert incident light to a reverse current



Application 1: Fiber-optic receiver


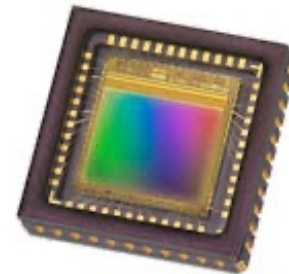


Application 2: Image sensor

# Summary
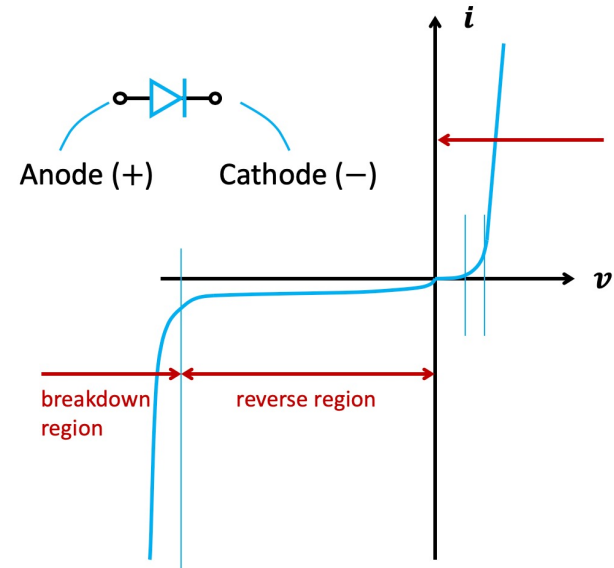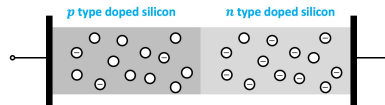
## Introduction to semiconductors


- Semiconductor material & silicon crystal
- Doped semiconductors
- Current flow in semiconductor
- The *pn* junction




## Diodes

- The  $i - v$  characteristics
- The models:


Small-signal model

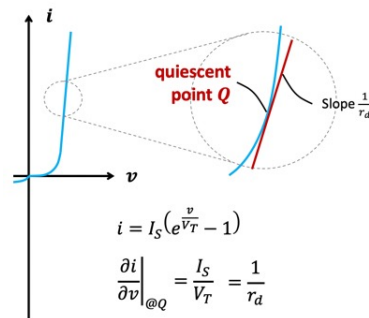

Constant-voltage drop model

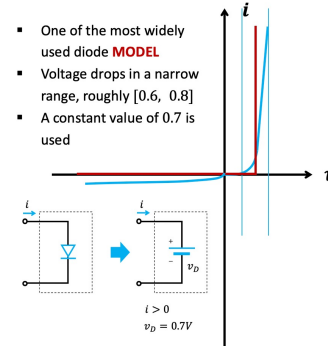

Ideal model

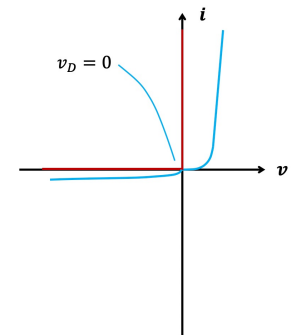

- Applications of diodes / circuit analysis with diodes
- Special diodes

# Reading tasks & learning goals

- Reading tasks
  - Microelectronic Circuits, 6<sup>th</sup> edition
    - Chapter 3-4
- Learning goals
  - Know the two types of doped semiconductors
  - Know how **pn junction** works
  - Well understand how to analyze a circuit with **diode** using different **models**