

Fundamentals of Electronic Circuits and Systems II

Oscillators & Signal Generators



Milin Zhang
Dept of EE, Tsinghua University

Outline

- HOW to generate an oscillation?
- Linear Oscillator
- Non-linear Oscillator

Recall: Dynamic Circuit

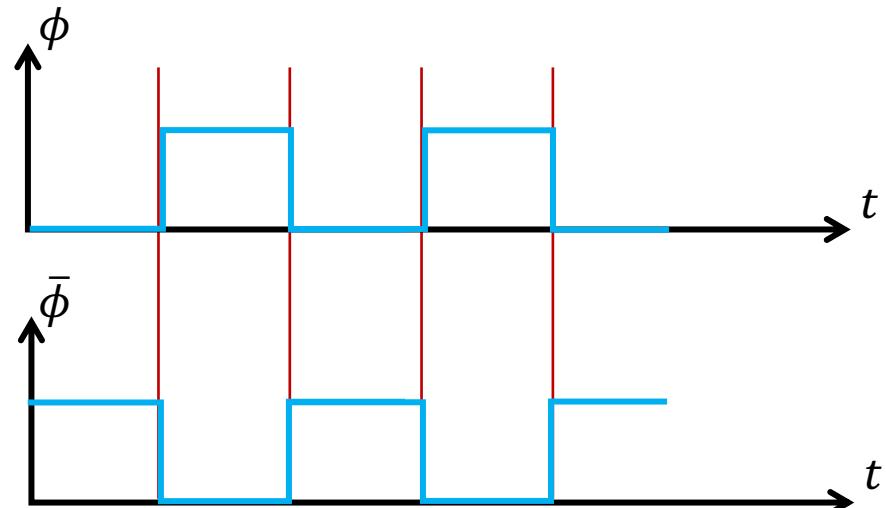
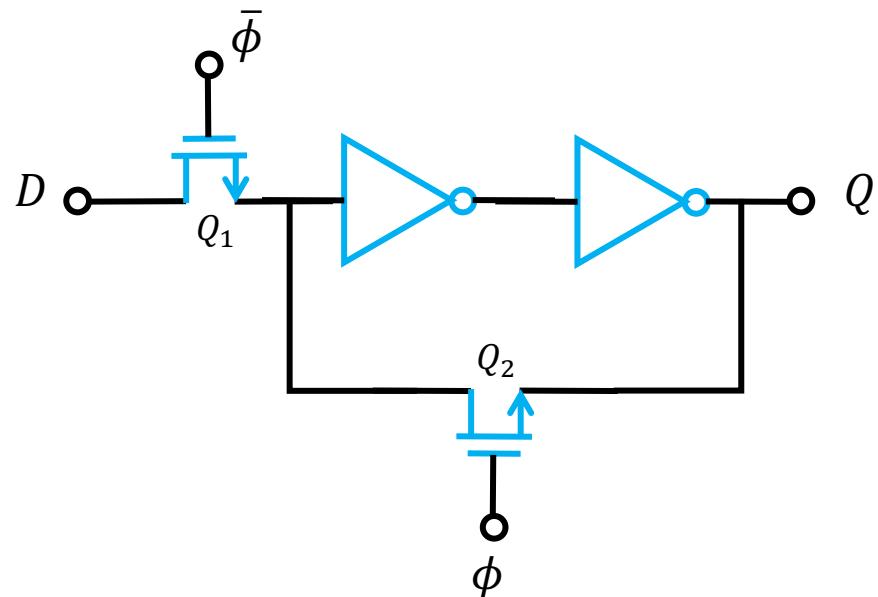
QUESTION: Find out the output Q with different input D . ϕ is a clock signal. The input switches between V_{dd} and GND




HOW to generate a CLOCK?

Recall: Source free LC circuit

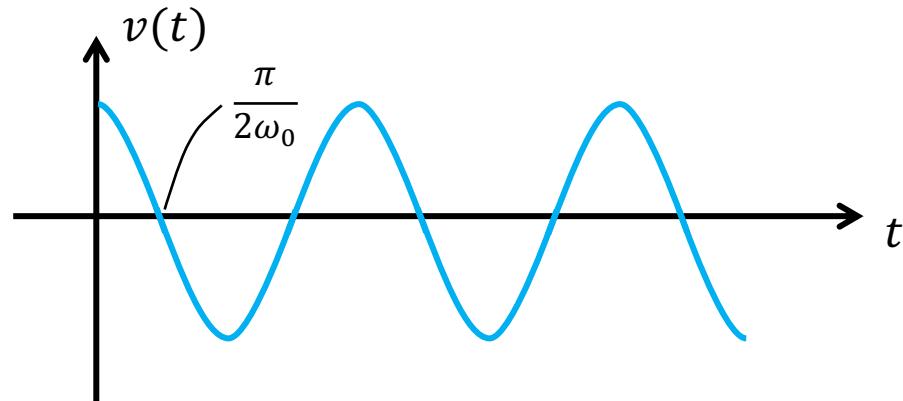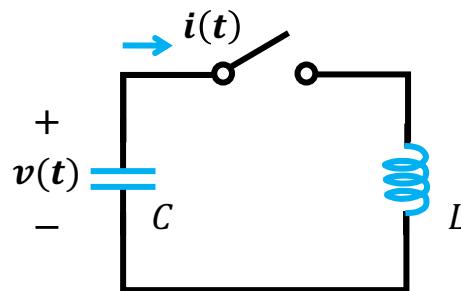QUESTION: Find how the voltage on the capacitor and the current through the inductor change after the switch is turned on.




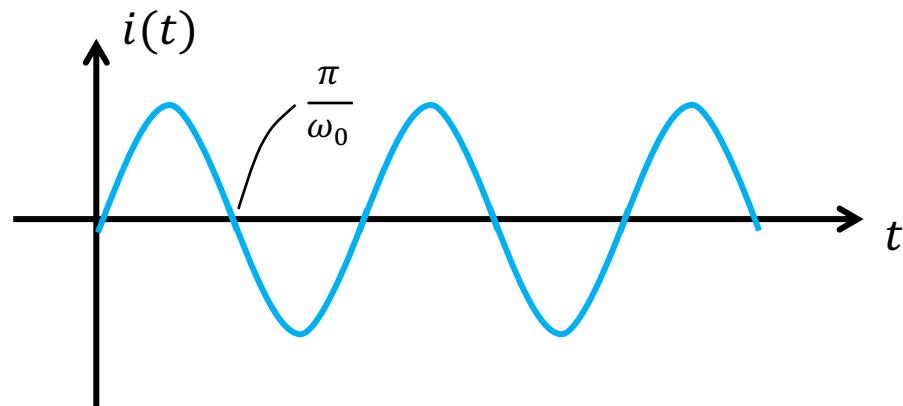
$$\begin{cases} v(t) = A \cos(\omega_0 t + \theta) \\ i(t) = \sqrt{\frac{C}{L}} A \sin(\omega_0 t + \theta) \end{cases}$$




Recall: zero-crossing detector

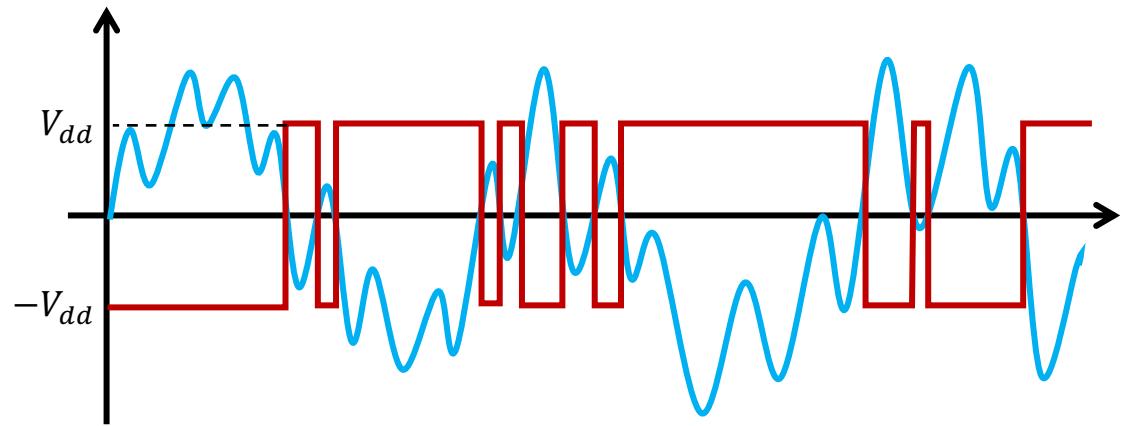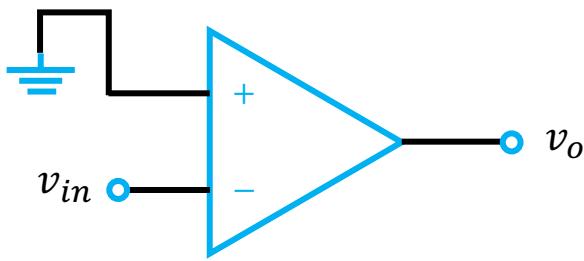QUESTION: Find the output of the circuit. The op-amp is ideal.




- If $v_{in} > 0 \rightarrow v_o = -V_{dd}$
- If $v_{in} < 0 \rightarrow v_o = V_{dd}$

How to generate a clock?

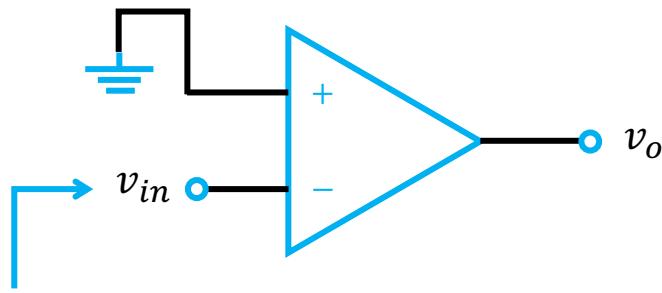


Voltage
from
free LC

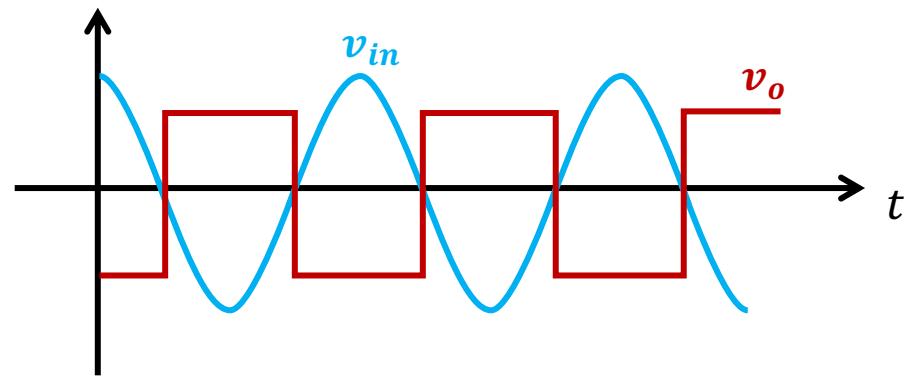

MISSION COMPLETED?

Recall: source free RLC circuit

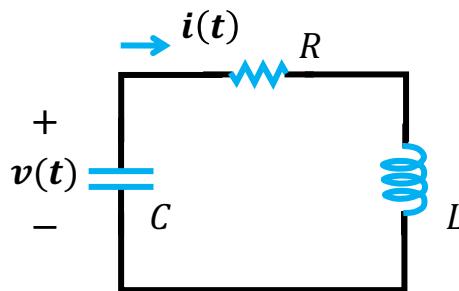QUESTION: Find how the voltage on the capacitor and the current through the inductor change.



$$v_c(t) = e^{-\zeta \omega_0 t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$

Define **DAMPING FACTOR**

$$\alpha = \frac{R}{2L}$$

Define **RESONATE FREQUENCY**

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Define **DAMPING RATIO**


$$\zeta = \frac{\alpha}{\omega_0} = \frac{R}{2\omega_0 L}$$

$$\frac{d^2v(t)}{dt^2} + \frac{R}{L} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) = 0$$



Solution: $v(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$

Where $\begin{cases} S_1 = -\zeta \omega_0 + \omega_0 \sqrt{\zeta^2 - 1} \\ S_2 = -\zeta \omega_0 - \omega_0 \sqrt{\zeta^2 - 1} \end{cases}$

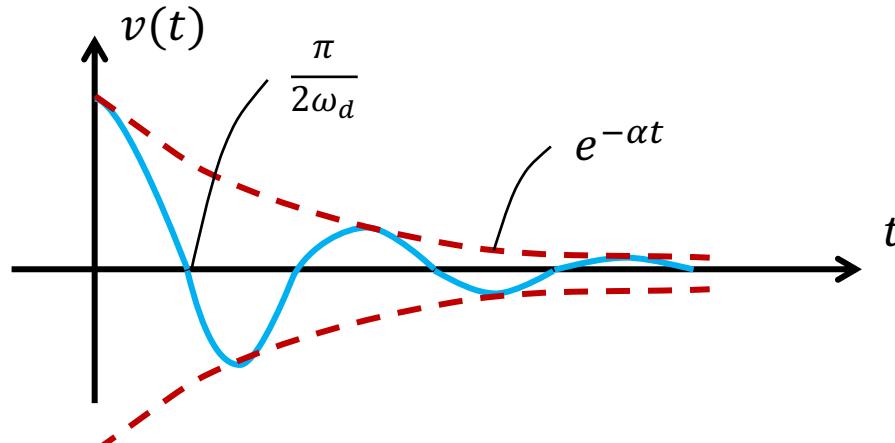and $\omega_0 = \frac{1}{\sqrt{LC}}$, $\zeta = \frac{R}{2\omega_0 L}$



Source free RLC circuit

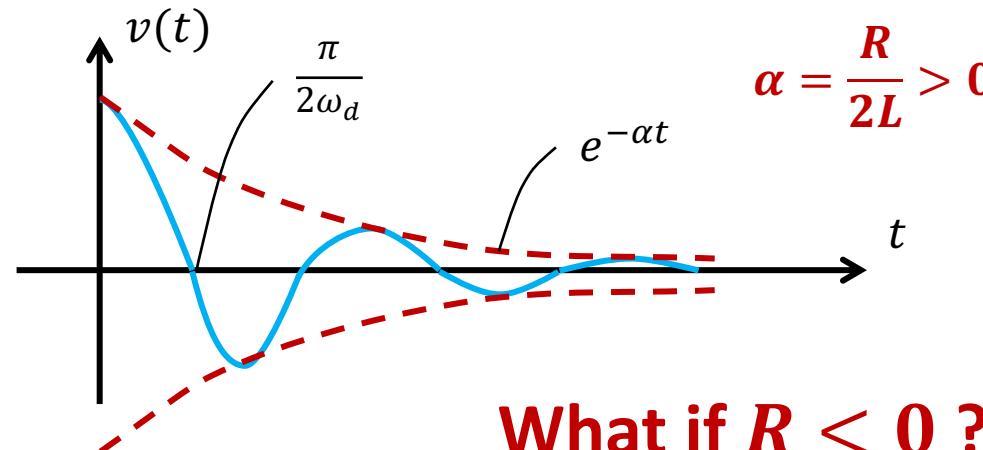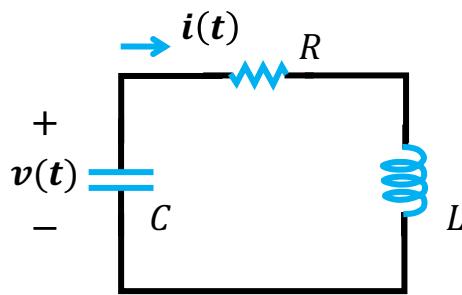


What if $R < 0$?


$$v_c(t) = K_1 e^{-\alpha t} \cos(\omega_d t + \theta_1)$$

$$K_1 = \sqrt{v_{C_1}^2(0) + \left(\frac{\alpha C_1 v_{C_1}(0) - i_{L_1}(0)}{C_1 \omega_d} \right)^2}$$
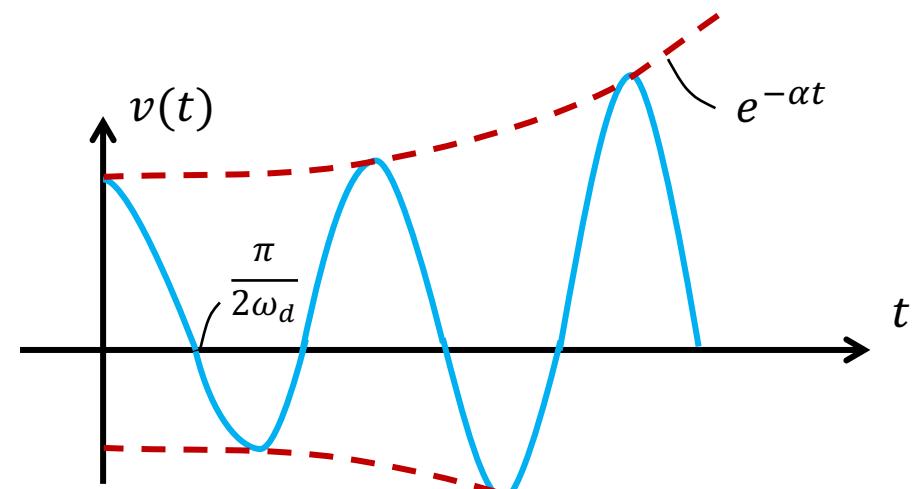
$$\theta_1 = \tan^{-1} \left(\frac{\alpha C_1 v_{C_1}(0) - i_{L_1}(0)}{C_1 \omega_d v_{C_1}(0)} \right)$$




Negative Resistance

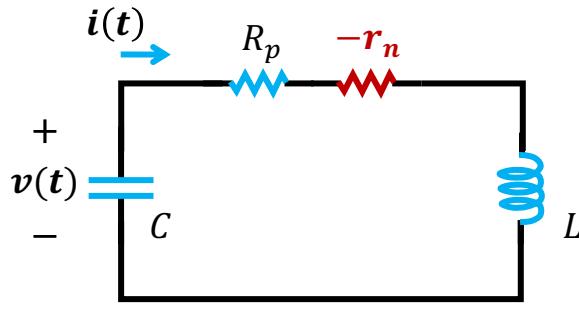


$$v_c(t) = K_1 e^{-\alpha t} \cos(\omega_d t + \theta_1)$$

Where $\alpha = \frac{R_p - r_n}{2L}$


$$R_p > r_n$$

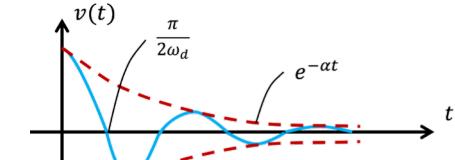

$$R_p = r_n$$

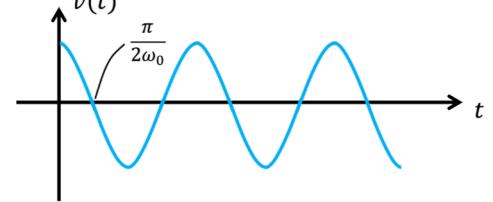


$$R_p < r_n$$

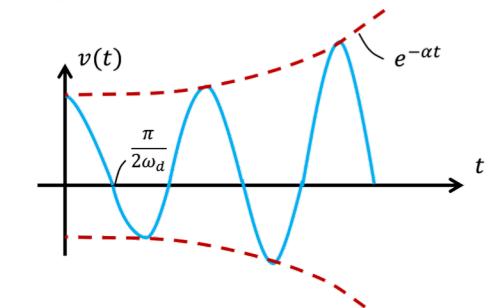


$$\left[\begin{array}{l} K_1 = \sqrt{v_{C_1}^2(0) + \left(\frac{\alpha C_1 v_{C_1}(0) - i_{L_1}(0)}{C_1 \omega_d} \right)^2} \\ \theta_1 = \tan^{-1} \left(\frac{\alpha C_1 v_{C_1}(0) - i_{L_1}(0)}{C_1 \omega_d v_{C_1}(0)} \right) \end{array} \right]$$

Devices with negative resistance



- Tunnel Diode

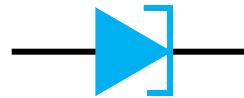

- Gunn Diode

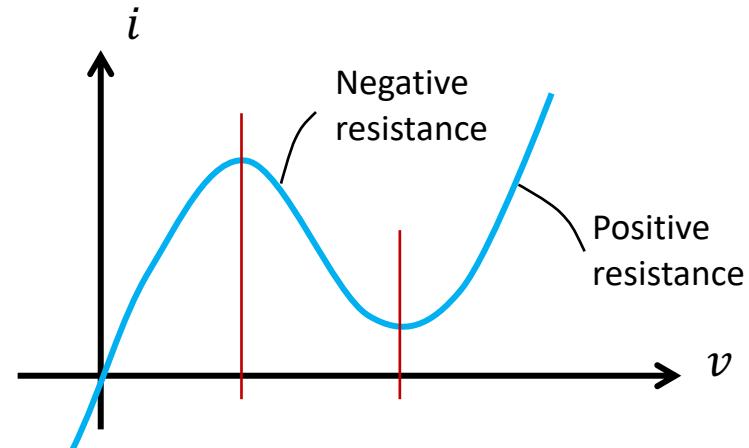


-
- Thyristor

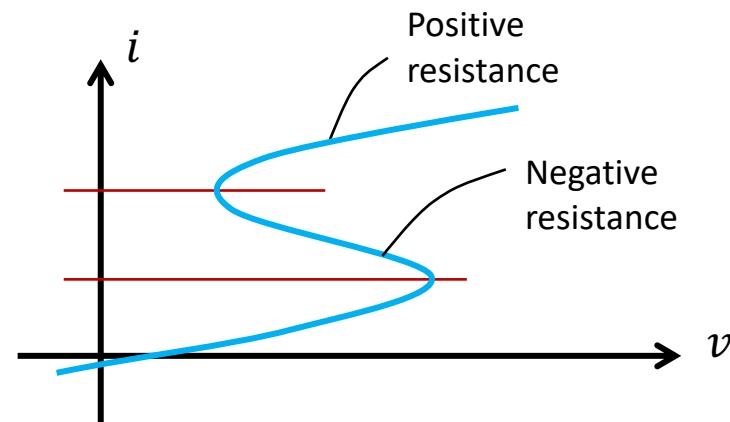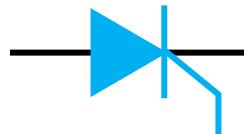


Outline

- HOW to generate an oscillation?
 - Negative resistance
 - Devices with negative resistance
 - **Circuit features negative resistance**

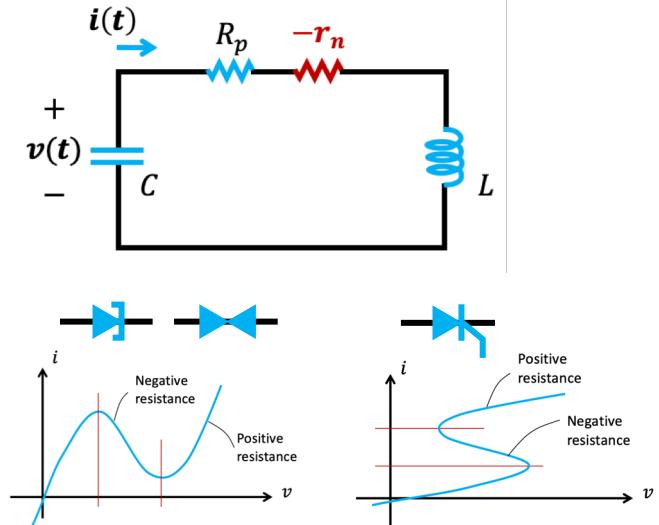

Example 1

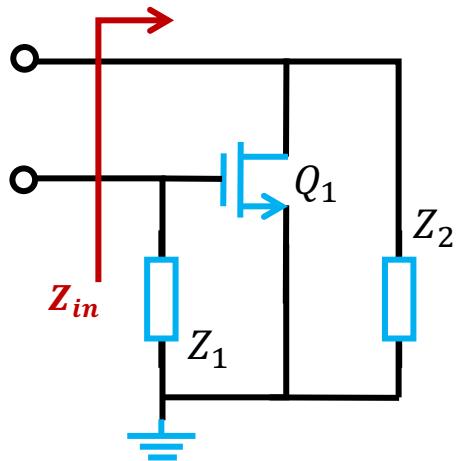QUESTION: Calculate the equivalent impedance Z_{in} of the circuit.



- **Step 1: perform DC analysis**


Assume Q_1 is biased in saturation region according to DC analysis

- **Step 2: perform AC analysis**

- **Step 2.1: replace the transistor with the small-signal model**
- **Step 2.2: turn off DC sources**
 - SHORT all voltage sources
 - OPEN all current sources
- **Step 2.3: Calculate small-signal model parameters**

Example 1

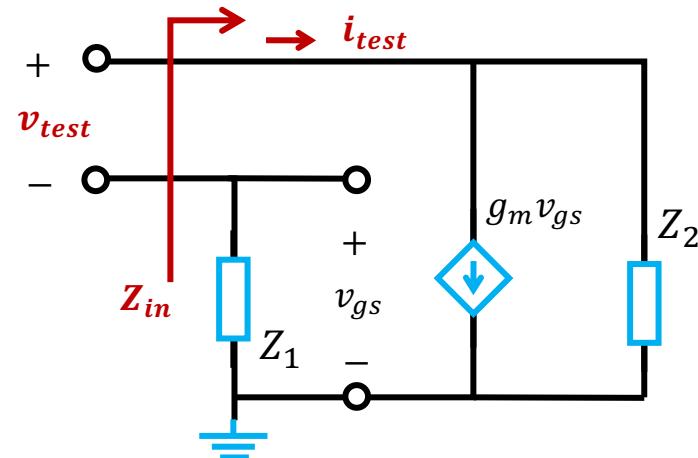QUESTION: Calculate the equivalent impedance Z_{in} of the circuit.



- According to KCL

$$i_{test} = g_m v_{gs} + i_{Z_2}$$


$$= g_m v_{gs} + \frac{v_{test} + v_{gs}}{Z_2}$$

$$= -g_m Z_1 i_{test} + \frac{v_{test} - Z_1 i_{test}}{Z_2}$$

► $Z_{in} = \frac{v_{test}}{i_{test}} = Z_1 + Z_2 + g_m Z_1 Z_2$

Example 1

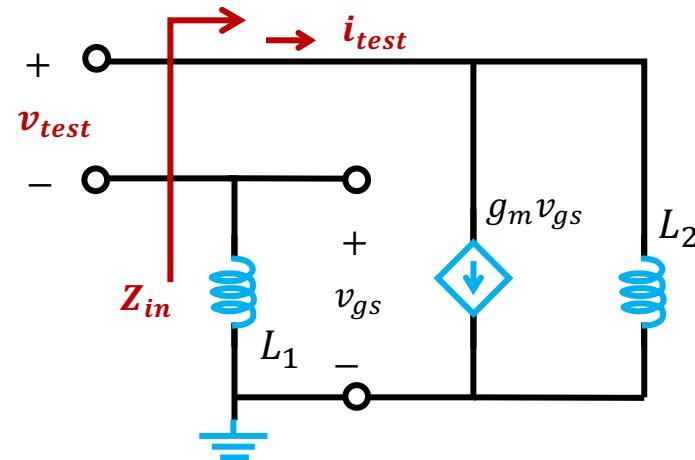QUESTION: Calculate the equivalent impedance Z_{in} of the circuit.




$$Z_{in} = \frac{v_{test}}{i_{test}} = Z_1 + Z_2 + g_m Z_1 Z_2$$

- If Z_1 and Z_2 are inductors


$$Z_{in} = \frac{v_{test}}{i_{test}} = Z_1 + Z_2 + g_m Z_1 Z_2$$

$$= j\omega L_1 + j\omega L_2 - g_m \omega^2 L_1 L_2$$

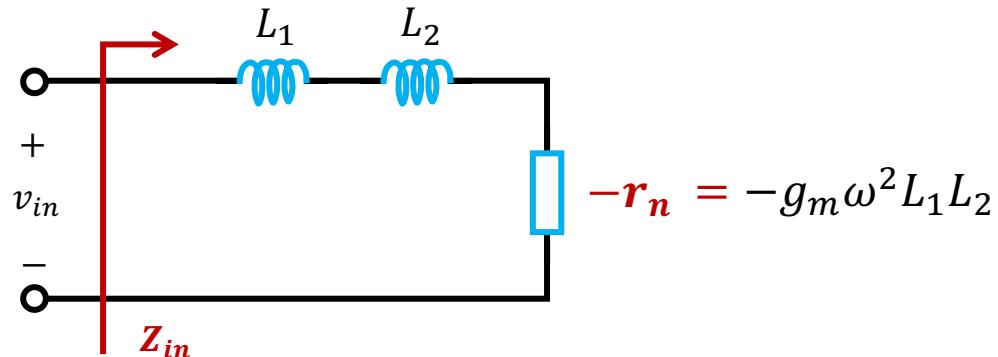

Example 1

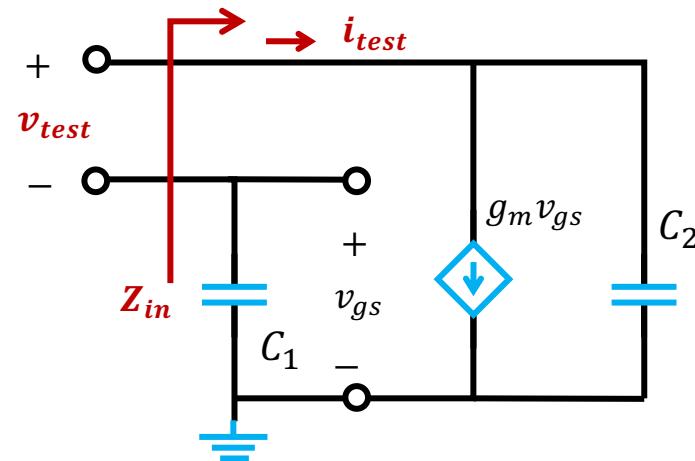
QUESTION: Calculate the equivalent impedance Z_{in} of the circuit.



$$Z_{in} = \frac{v_{test}}{i_{test}} = Z_1 + Z_2 + g_m Z_1 Z_2$$

- If Z_1 and Z_2 are capacitors
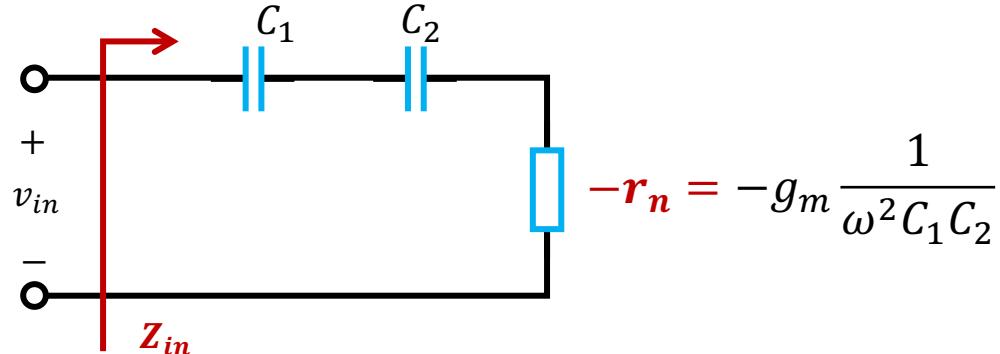
$$\begin{aligned} Z_{in} &= \frac{v_{test}}{i_{test}} = Z_1 + Z_2 + g_m Z_1 Z_2 \\ &= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} - g_m \frac{1}{\omega^2 C_1 C_2} \end{aligned}$$




Outline

- HOW to generate an oscillation?
 - Negative resistance
 - Devices with negative resistance
 - Circuit features negative resistance


■ Linear Oscillator

- LC Oscillator

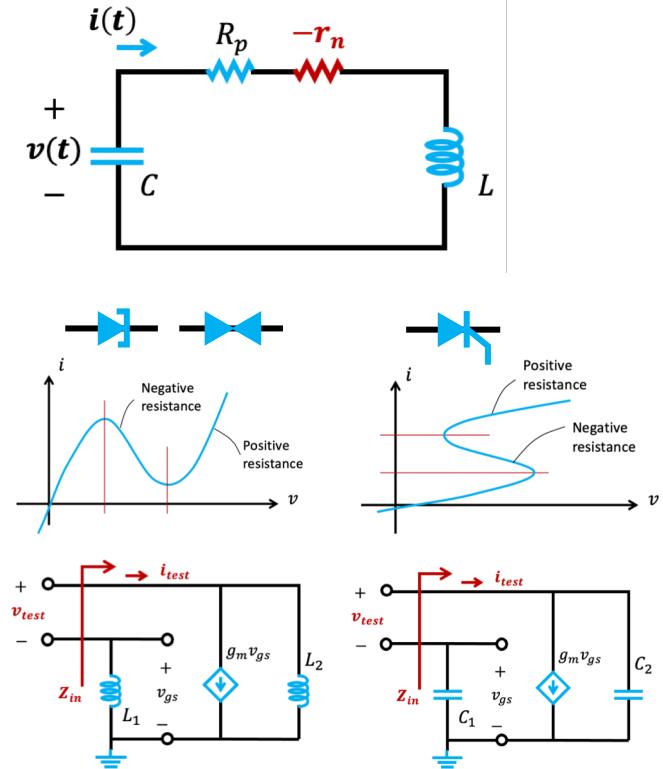

Example 2: Colpitts Oscillator

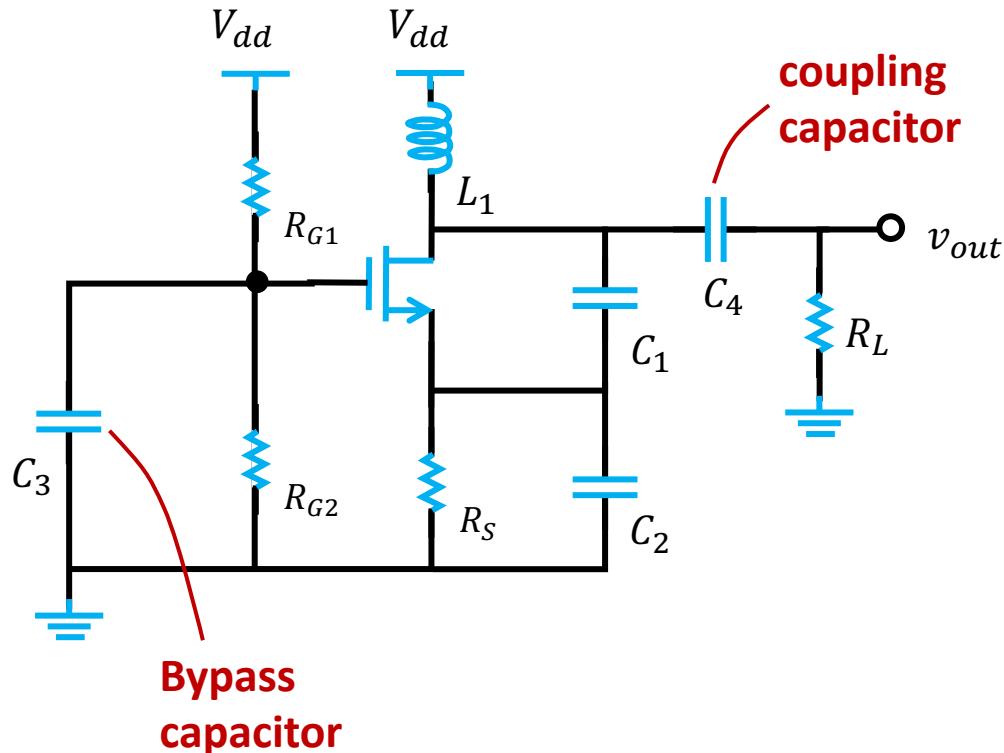
QUESTION: Find the functionality of the following circuit.



- C_4 is **coupling capacitors**
- C_3 is **bypass capacitor**
- C_3 and C_4 **IDEALLY** are short circuit @DC

Example 2: Colpitts Oscillator

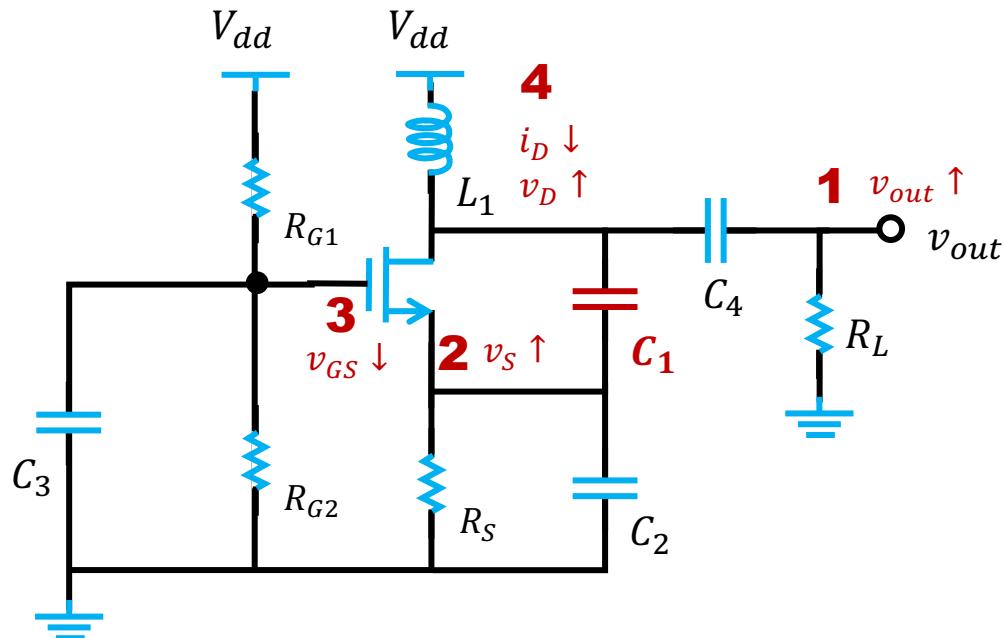QUESTION: Find the functionality of the following circuit.




What is C_1 used for?

- If there is an increase @ v_{out} $v_{out} \uparrow$
- The voltage increase @ source
- v_{GS} decrease correspondingly
- i_D decreases, causing an decreasing of v_D $v_{out} \uparrow$

POSITIVE FEEDBACK is observed

Example 2: Colpitts Oscillator

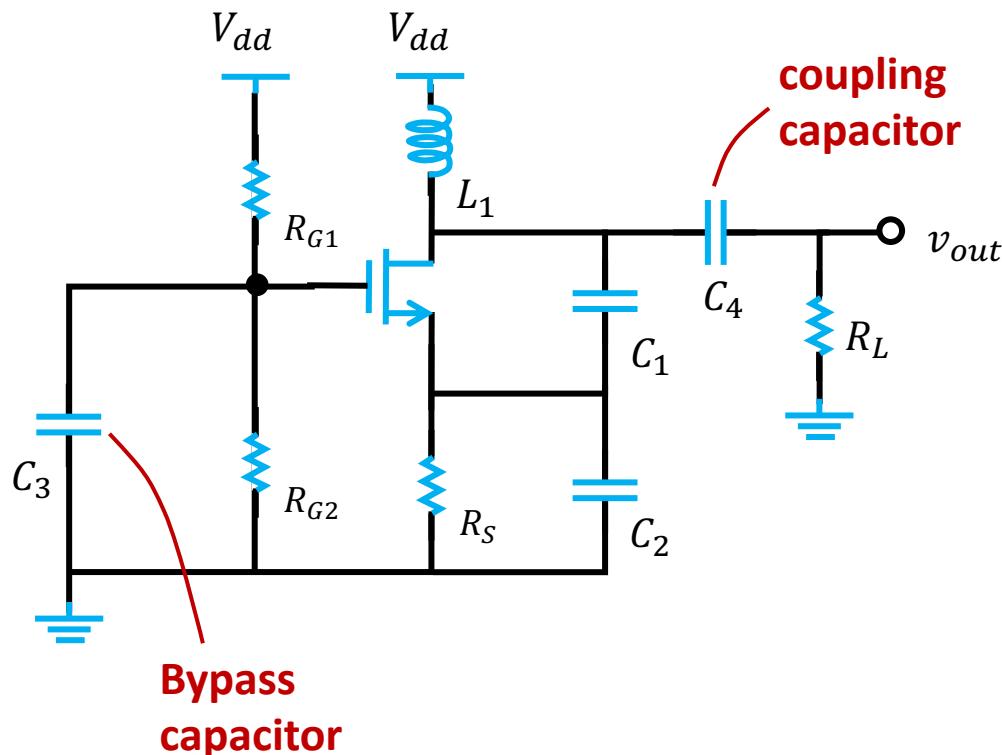
QUESTION: Find the functionality of the following circuit.



- **Step 1: perform DC analysis**
- **Step 2: perform AC analysis**
 - Step 2.1: turn off DC sources
 - Step 2.2: Calculate small-signal model parameters, g_m
 - Step 2.3: replace the transistor with the small-signal model
 - Step 2.4: Analyze the resulting circuit

Example 2: Colpitts Oscillator

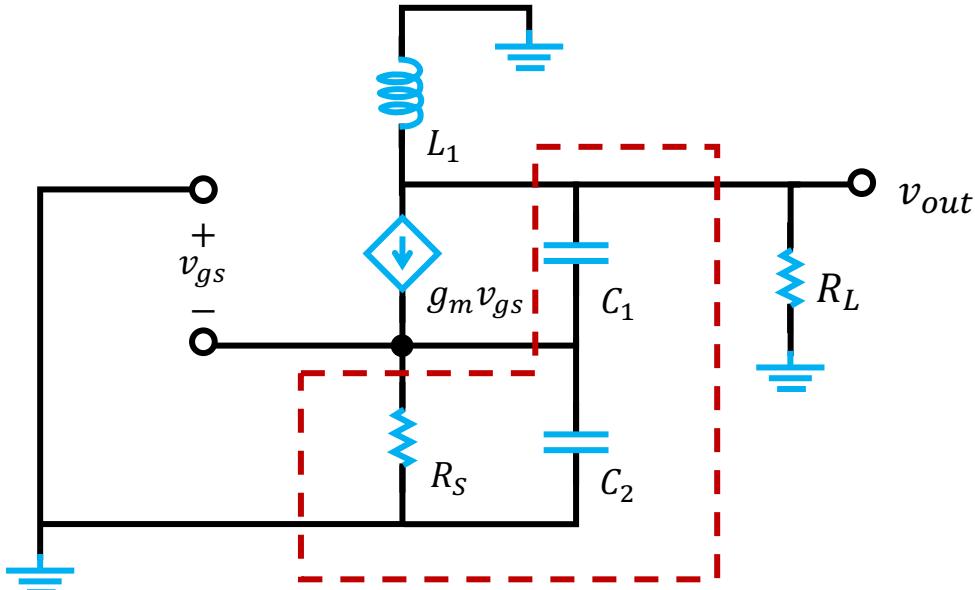QUESTION: Find the functionality of the following circuit.



$$v_{R_S} = \frac{\frac{1}{sC_2} || R_S}{\frac{1}{sC_1} + \left(\frac{1}{sC_2} || R_S \right)} v_{out}$$



↓

If $R_S \gg \frac{1}{sC_2}$

$$\approx \frac{\frac{1}{sC_2}}{\frac{1}{sC_1} + \frac{1}{sC_2}} v_{out} = \frac{C_1}{C_1 + C_2} v_{out}$$


p

$$R'_S = \frac{R_S}{p^2} \text{ to keep a same power}$$

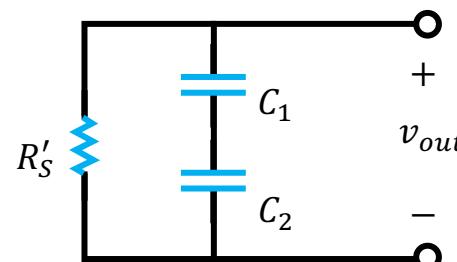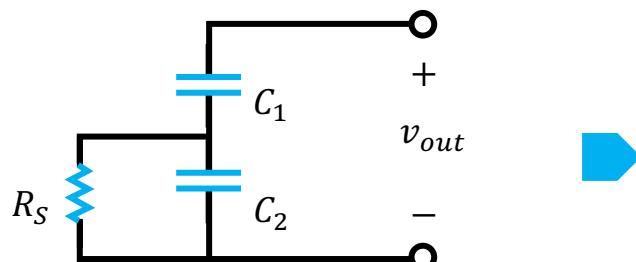


Example 2: Colpitts Oscillator

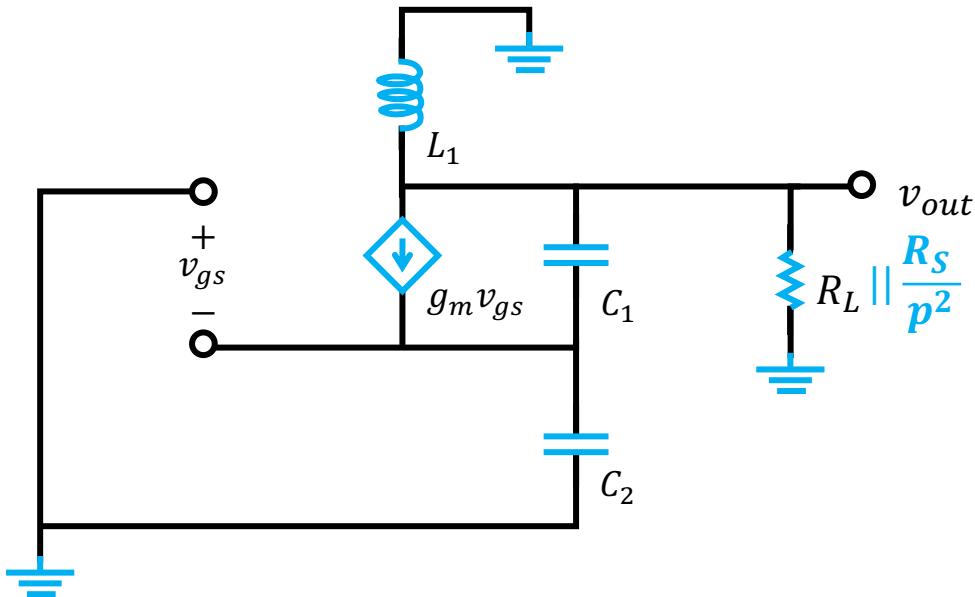QUESTION: Find the functionality of the following circuit.




Recall: MOSFET Small-Signal Model

SIMPLIFIED HYBRID- π MODEL

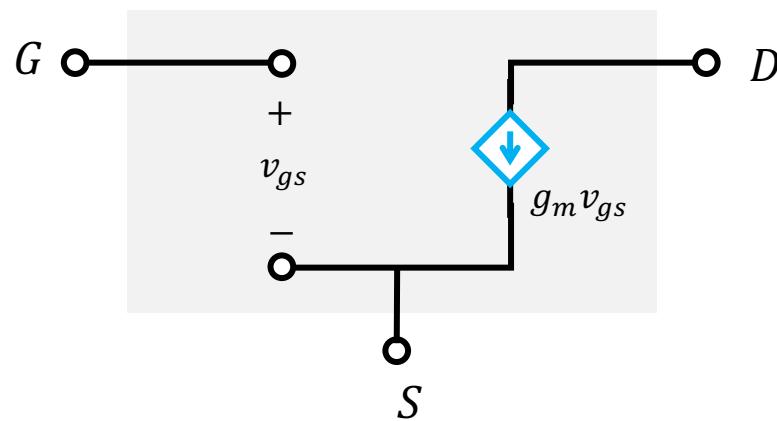



SIMPLIFIED T MODEL

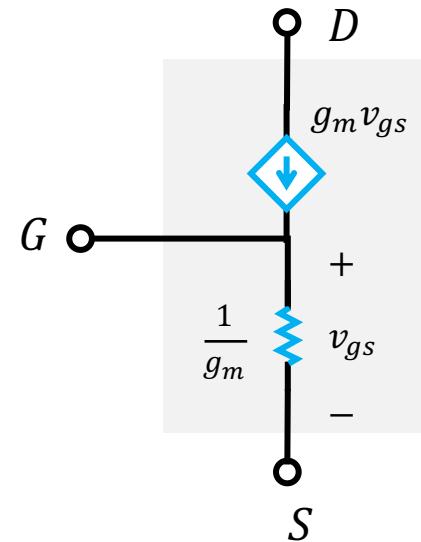


HYBRID- π MODEL and T MODEL are equivalent

Example 2: Colpitts Oscillator

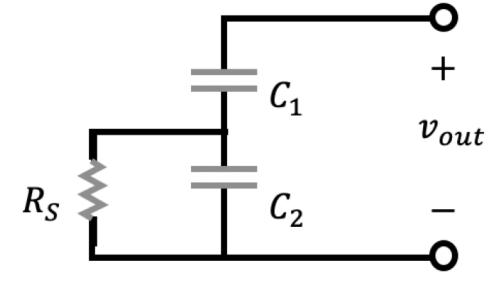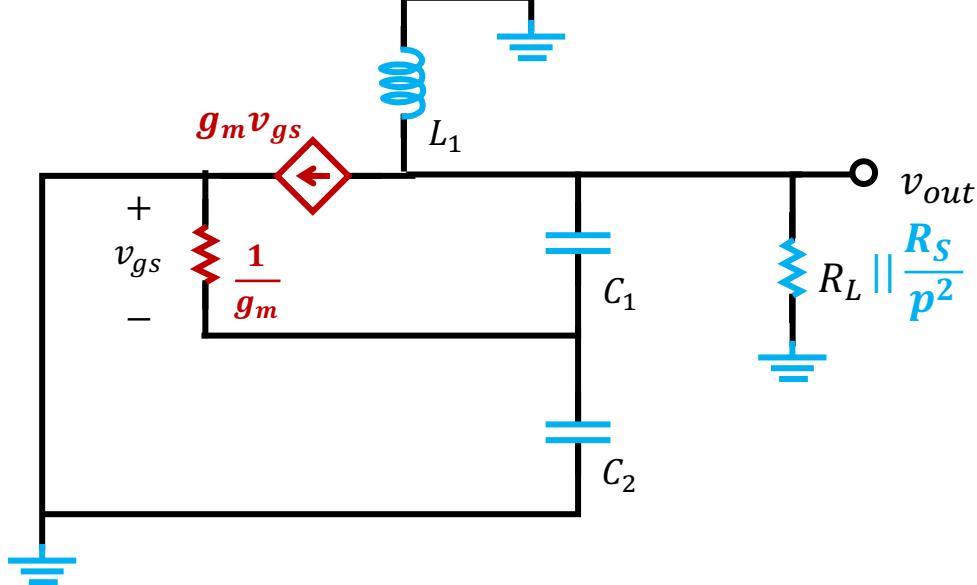QUESTION: Find the functionality of the following circuit.




$$R'_S = \frac{R_S}{p^2}$$

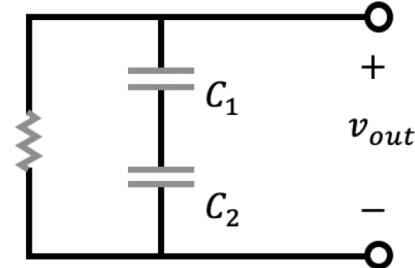

Example 2: Colpitts Oscillator

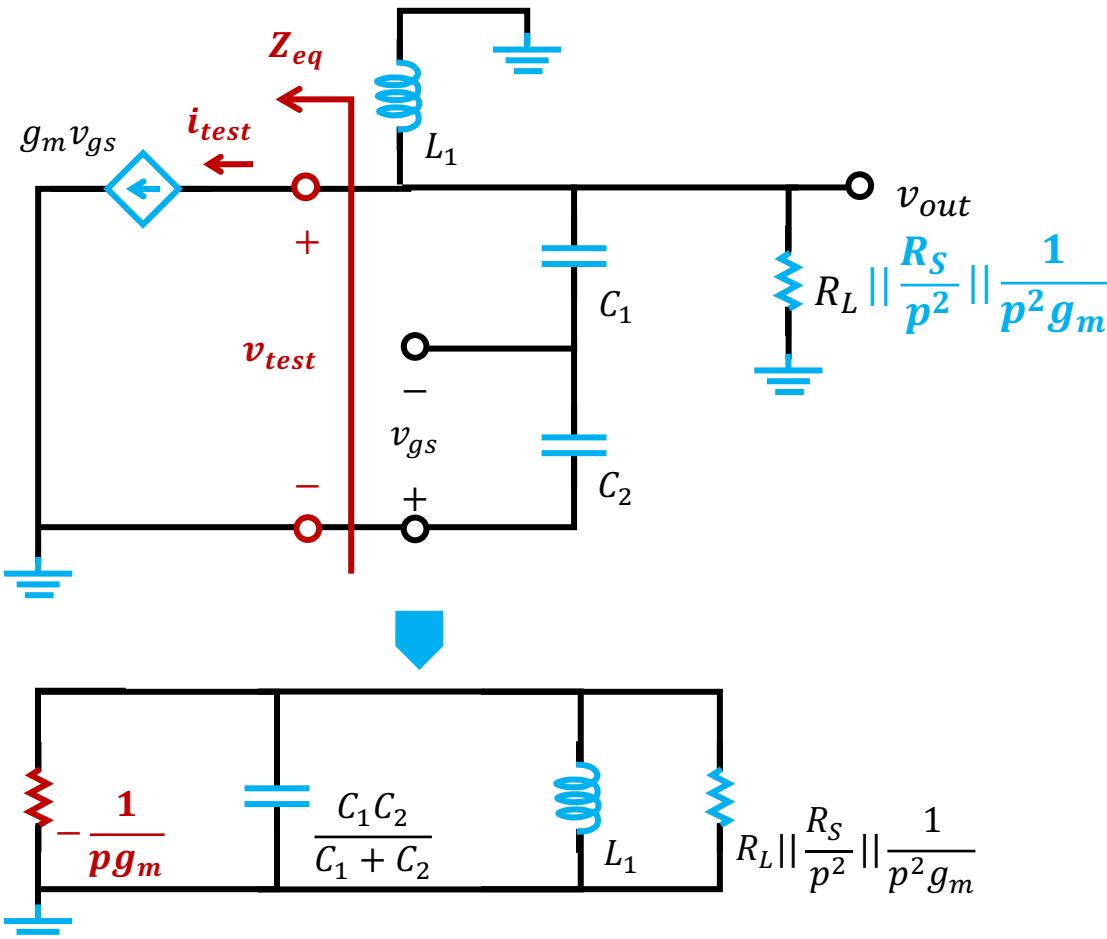QUESTION: Find the functionality of the following circuit.





- According to KVL

$$\begin{aligned}
 v_{test} &= -sC_2 v_{gs} \frac{C_1 + C_2}{sC_1 C_2} \\
 &= -\frac{C_1 + C_2}{C_1} v_{gs} \\
 &\quad \underline{\underline{1/p}}
 \end{aligned}$$

$$Z_{eq} = \frac{v_{test}}{i_{test}} = -\frac{1}{pgm}$$


Example 2: Colpitts Oscillator

QUESTION: Find the functionality of the following circuit.

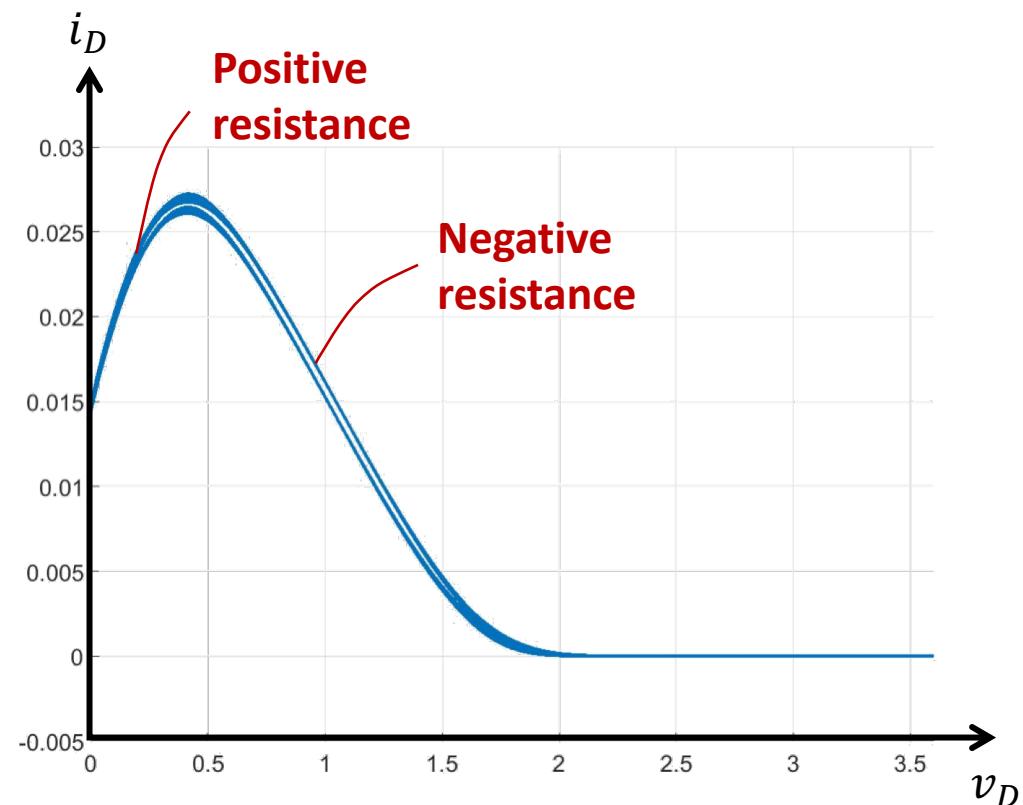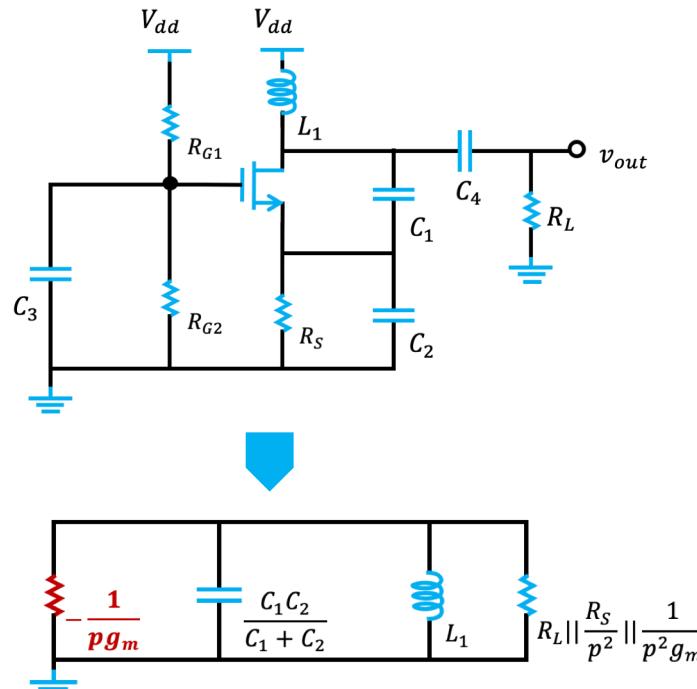


Example 2: Colpitts Oscillator

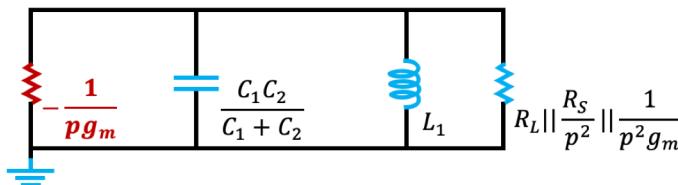QUESTION: Find the functionality of the following circuit.



- Oscillation can be expected when

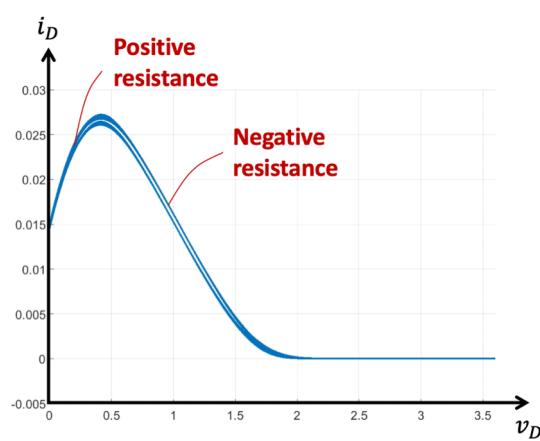
$$g_m p > p^2 g_m + \frac{p^2}{R_S} + \frac{1}{R_L}$$
$$\underline{\underline{g'_L}}$$



$$\Rightarrow g_m > \frac{g'_L}{p - p^2}$$

Example 3

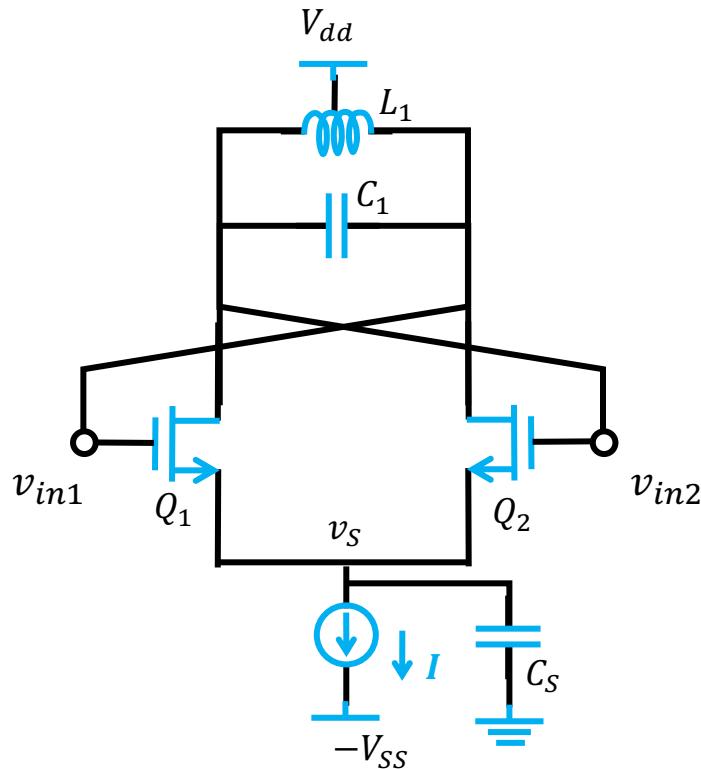
QUESTION: Find the functionality of the following circuit. Assume Q_1 and Q_2 are matched.



- **Step 1: perform DC analysis**
- **Step 2: perform AC analysis**
 - Step 2.1: turn off DC sources
 - Step 2.2: Calculate small-signal model parameters, g_m
 - Step 2.3: replace the transistor with the small-signal model
 - Step 2.4: Analyze the resulting circuit

Example 3

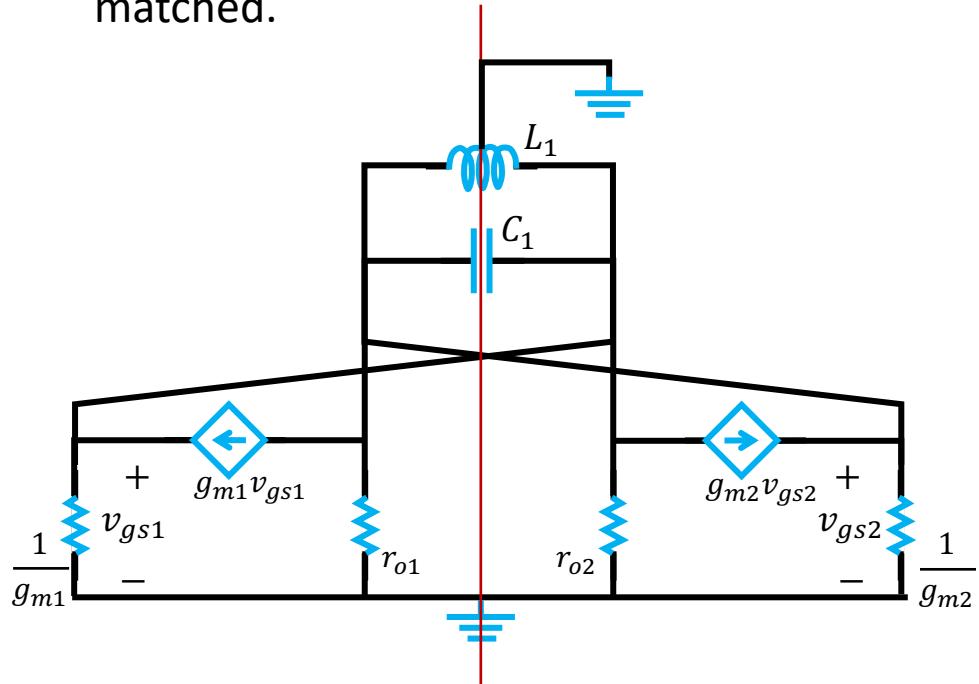QUESTION: Find the functionality of the following circuit. Assume Q_1 and Q_2 are matched.




- Since Q_1 and Q_2 are matched

$$g_{m1} = g_{m2} = g_m$$

$$r_{o1} = r_{o2} = r_o$$

Example 3

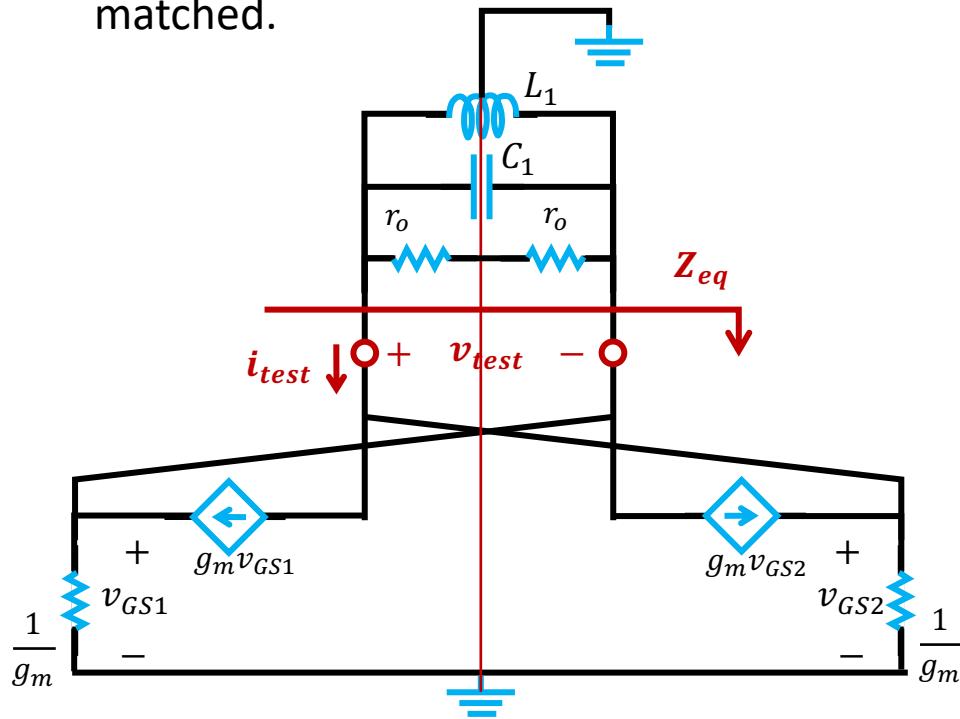QUESTION: Find the functionality of the following circuit. Assume Q_1 and Q_2 are matched.




- According to KCL & resistor characteristic

$$\left\{ \begin{array}{l} (i_{test} - g_{m1}v_{GS1} + g_{m2}v_{GS2})\frac{1}{g_{m2}} = v_{GS2} \\ (-i_{test} - g_{m2}v_{GS2} + g_{m1}v_{GS1})\frac{1}{g_{m1}} = v_{GS1} \\ v_{GS1} - v_{GS2} = v_{test} \end{array} \right.$$

$$\Rightarrow Z_{eq} = \frac{v_{test}}{i_{test}} = -\frac{2}{g_m}$$

Example 3

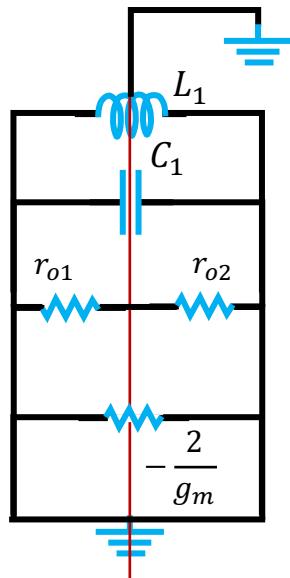QUESTION: Find the functionality of the following circuit. Assume Q_1 and Q_2 are matched.



- Oscillation can be expected when


$$\frac{g_m}{2} > \frac{1}{2r_o}$$

$$\Rightarrow g_m > \frac{1}{r_o}$$

Outline

■ HOW to generate an oscillation?

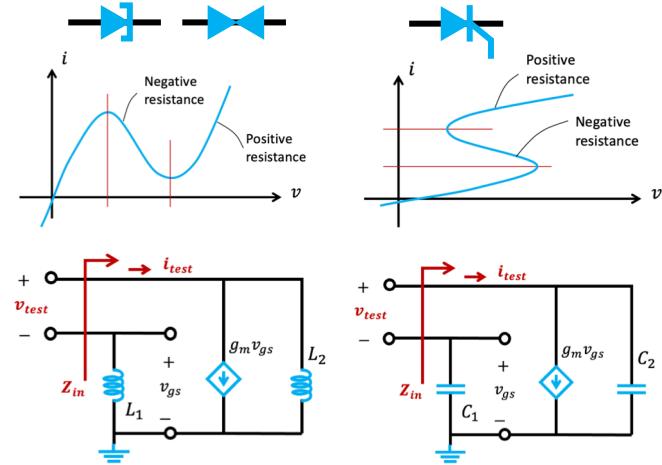
- Negative resistance
- Devices with negative resistance
- Circuit features negative resistance



■ Linear Oscillator


- LC Oscillator
- **Crystal Oscillator**

Crystal Oscillators

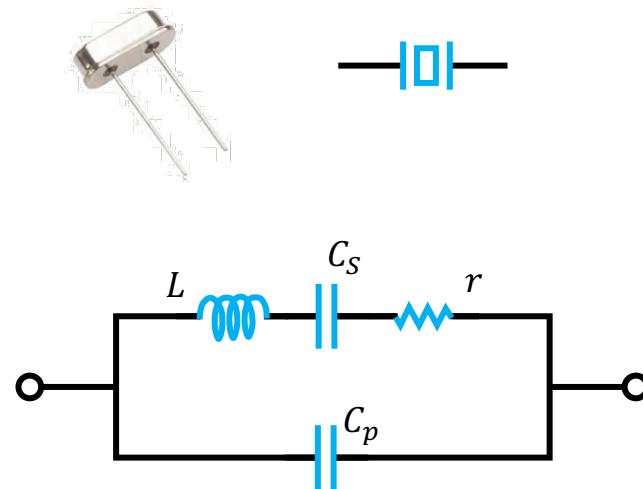

Equivalent circuit

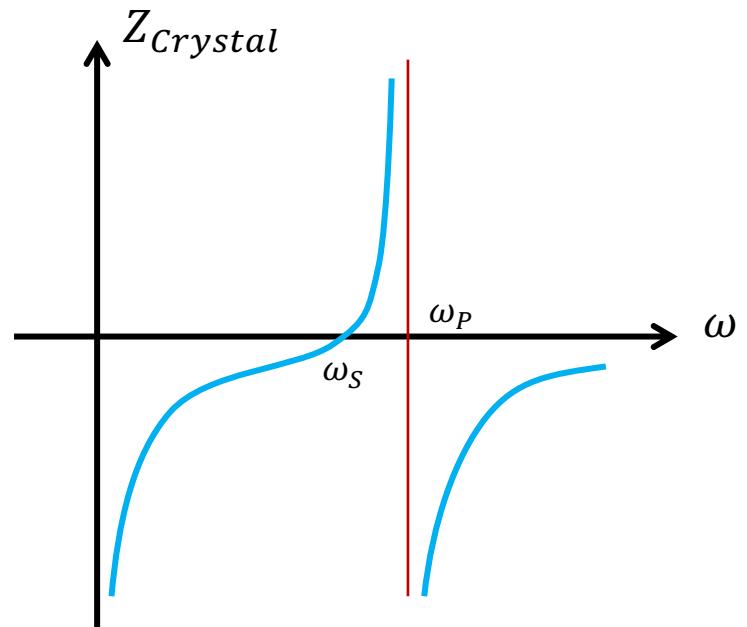
- ☺ High frequency
- ☺ High stability
- ☹ High Q factor
- ☹ Cannot integrate on chip



Outline

■ HOW to generate an oscillation?

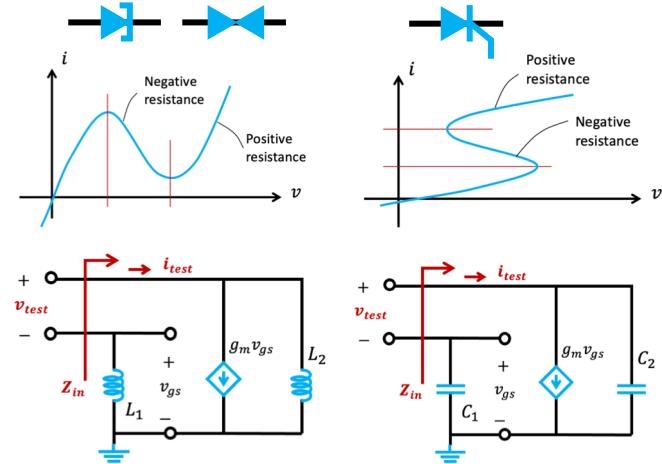- Negative resistance
- Devices with negative resistance
- Circuit features negative resistance




■ Linear Oscillator

- LC Oscillator
- Crystal Oscillator
- **Op-Amp-RC Oscillator**

Recall: Example of Positive Feedback

1

Preset temp. x_s

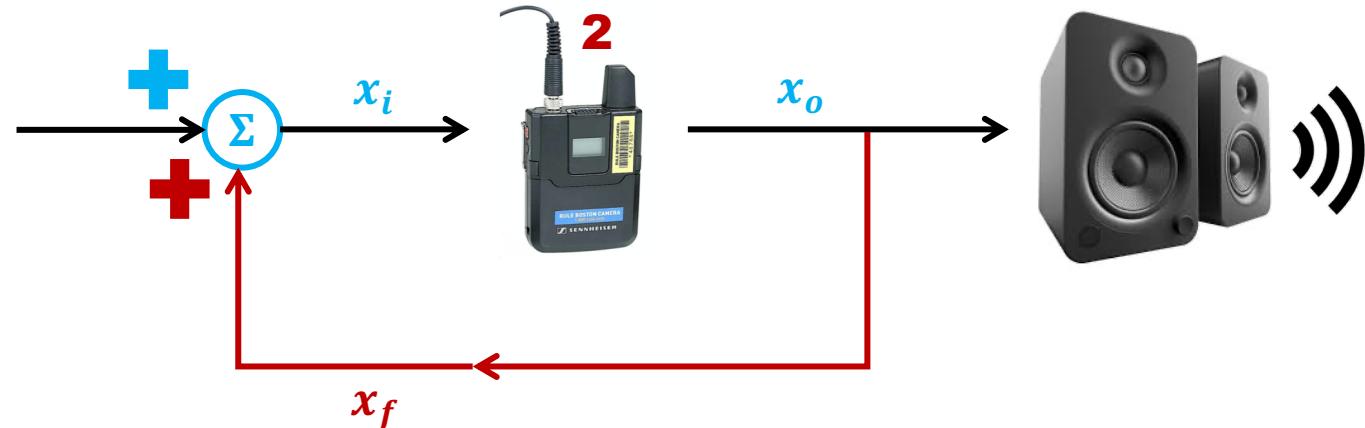


- The output x_o is related to the input x_i
- The output x_o is fed to a feedback network to generate x_f
- The input of the system turns into

$$x_i = x_s + x_f$$

THIS IS A POSITIVE FEEDBACK


The output is fed-back to input, to
INCREASE intensity of input signal

Recall: general pos. feedback structure

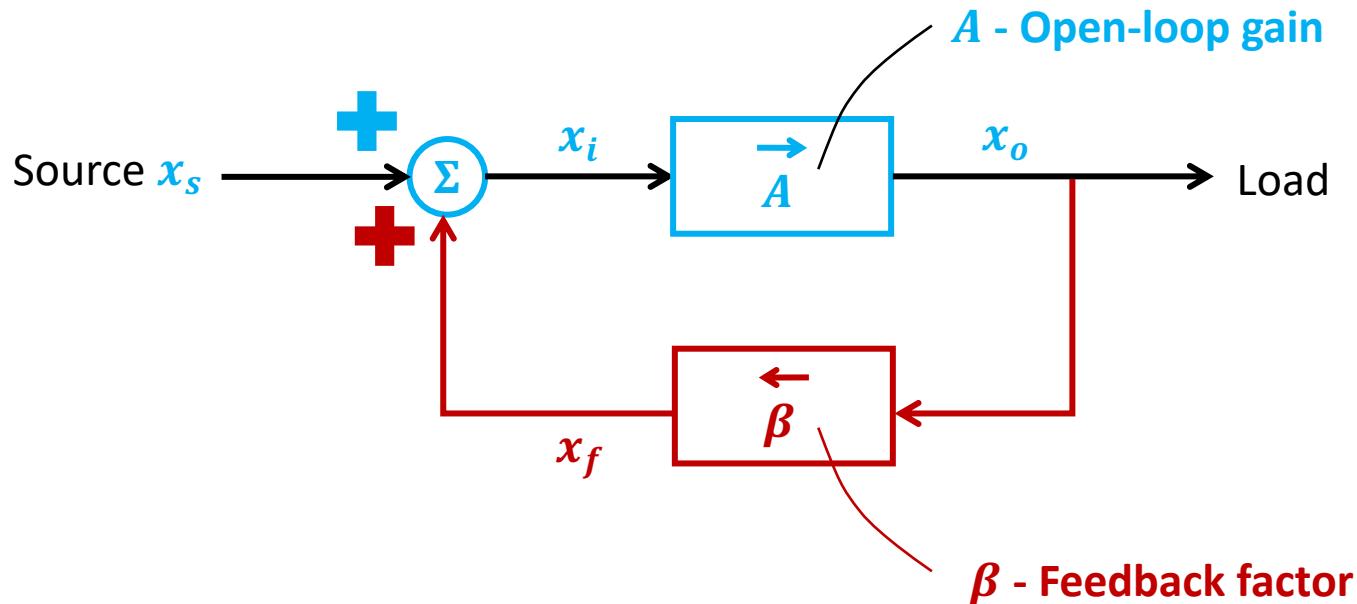

- The output x_o is related to the input x_i
$$x_o = Ax_i$$
- The output is fed to a feedback network
$$x_f = \beta x_o$$
- The input of the amplifier turns into
$$x_i = x_s + x_f$$

Recall: Op-Amp w/ positive feedback

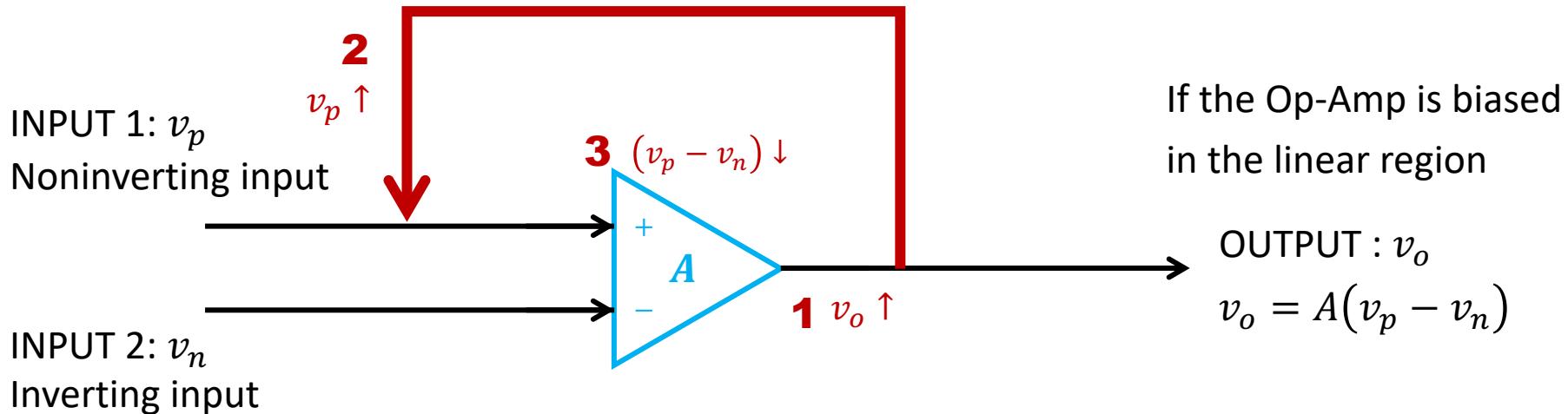

How to decide if there is a positive feedback


- If there is an increase @ v_o $v_o \uparrow \leftarrow$
 - The inverting input v_p increases correspondingly
 - If the op-amp is biased in the linear region, $v_o = A(v_p - v_n)$ increases $v_o \uparrow$
- POSITIVE FEEDBACK**

An unstable system “oscillates” between V_{dd} and $-V_{dd}$

Recall: positive feedback w/o input

WE WILL DISCUSS THIS NEXT SEMESTER

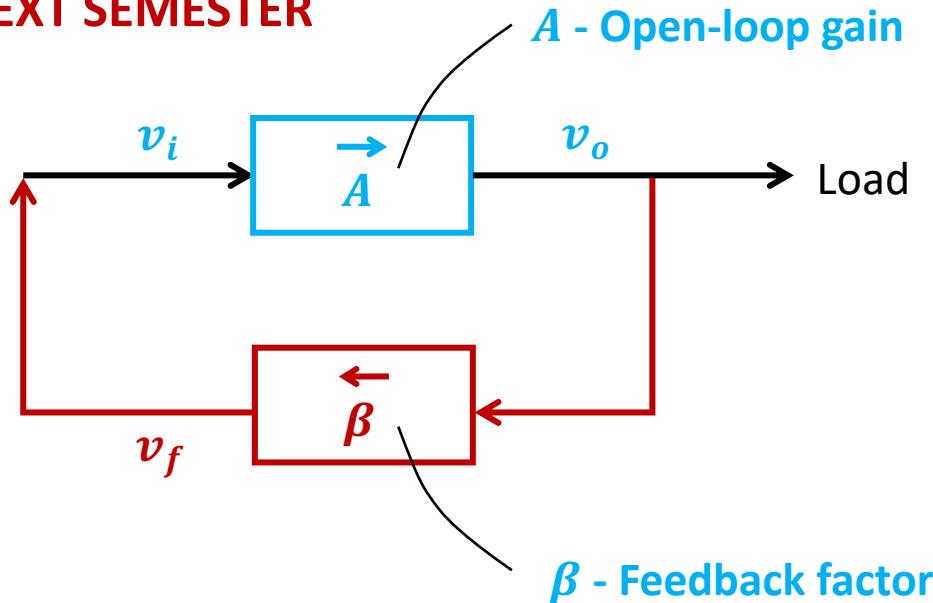
- What if there is no input in the system?
- What gonna happen if there is a disturbance?




- The output x_o is related to the input x_i $v_o = Av_i$
- The output is fed to a feedback network $v_f = \beta v_o = A\beta v_i$

What if $A\beta > 1$ at the very beginning, but decreases to $A\beta = 1$ later?


Positive feedback w/o input

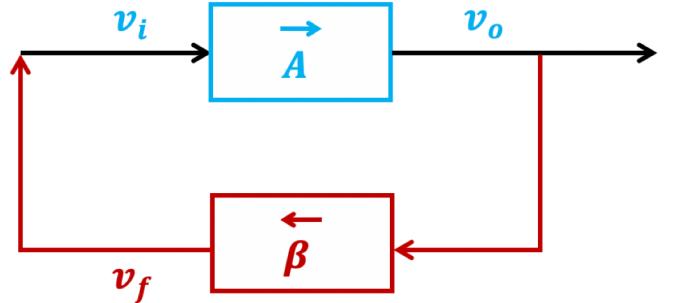

A small disturb @ x_i

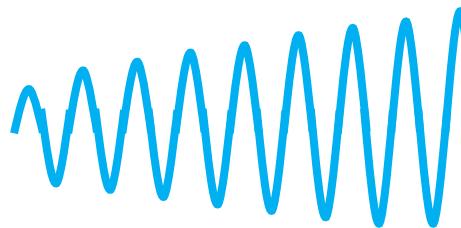


@ $A\beta > 1$
Amplitude increases

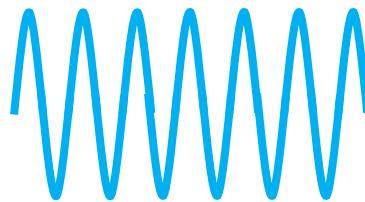

@ $A\beta = 1$
Amplitude keeps


Example 4: the Wien-Bridge Oscillator

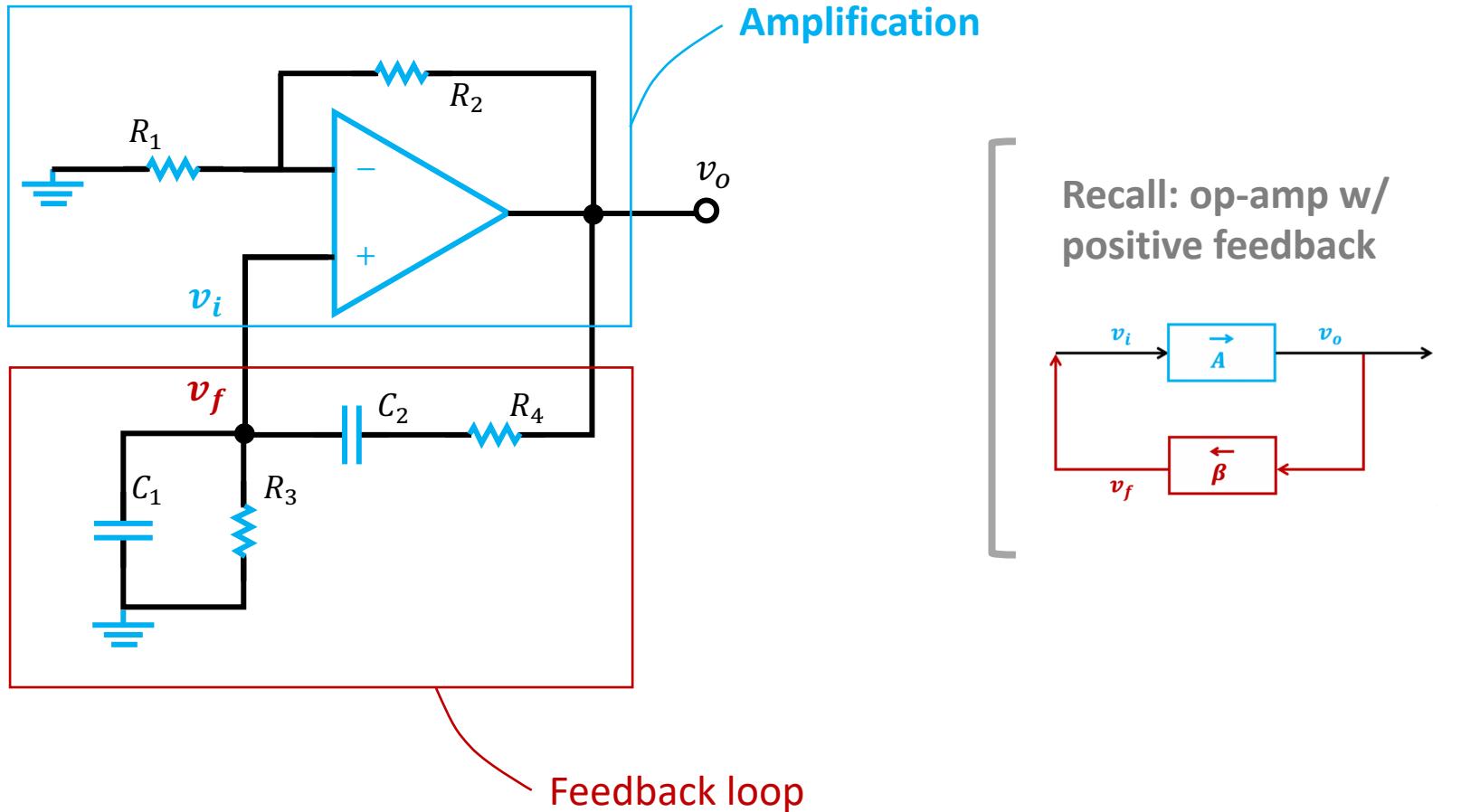QUESTION: Find the functionality of the following circuit with $R_3 = R_4 = R$, $C_1 = C_2 = C$.



Recall: The noninverting configuration

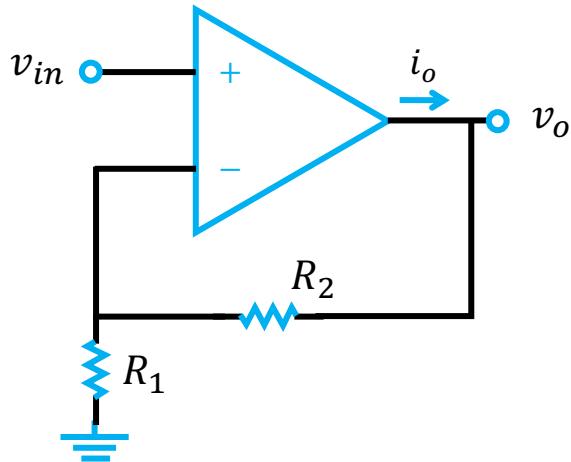QUESTION: Find the functionality of the following circuit with $R_3 = R_4 = R$, $C_1 = C_2 = C$.




$$\left. \begin{aligned} i_{R_1} &= \frac{v_n}{R_1} = \frac{v_{in}}{R_1} \\ i_{R_2} &= \frac{v_o - v_n}{R_2} = \frac{v_o - v_{in}}{R_2} \\ i_{R_1} &= i_{R_2} \end{aligned} \right\}$$

IDEAL OP-AMP with NEGATIVE FEEDBACK enables linear region biasing

$$\Rightarrow v_o = \frac{R_1 + R_2}{R_1} v_{in}$$

Example 4: the Wien-Bridge Oscillator

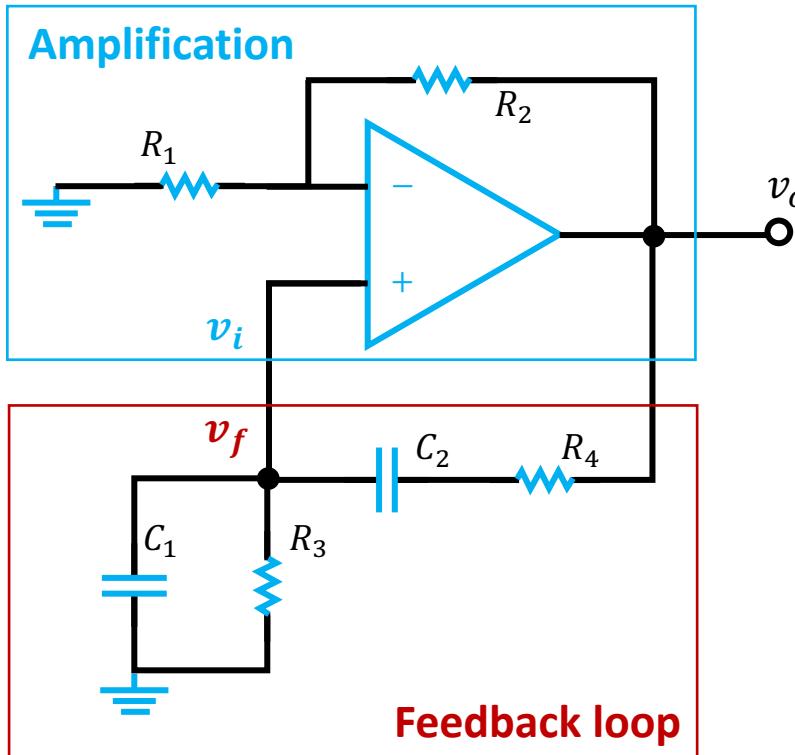QUESTION: Find the functionality of the following circuit with $R_3 = R_4 = R$, $C_1 = C_2 = C$.



- For the amplification system, the gain


$$A = \frac{v_o}{v_i} = \frac{R_2 + R_1}{R_1}$$

- For the feedback loop

$$\begin{aligned}\beta &= \frac{v_f}{v_o} = \frac{R_3 \parallel \frac{1}{sC_1}}{R_4 + \frac{1}{sC_2} + R_3 \parallel \frac{1}{sC_1}} \\ &= \frac{1}{3 + sRC + \frac{1}{sRC}}\end{aligned}$$

Example 4: the Wien-Bridge Oscillator

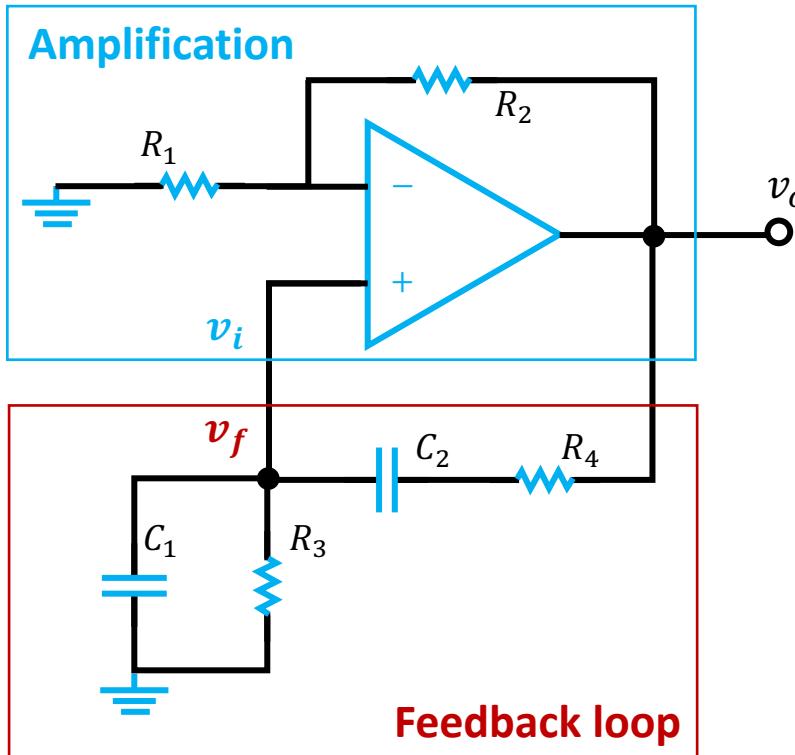QUESTION: Find the functionality of the following circuit with $R_3 = R_4 = R$, $C_1 = C_2 = C$.



- The transfer function

$$H(s) = A\beta = \frac{1 + \frac{R_2}{R_1}}{3 + sRC + \frac{1}{sRC}}$$

- $H(s)$ is a real number, when

$$sRC + \frac{1}{sRC} = 0 \quad \Rightarrow \quad \omega_0 = \frac{1}{RC}$$


The oscillation frequency ω_0 is “determined” by the feedback loop

$$\left\{ \begin{array}{l} A = \frac{v_o}{v_i} = \frac{R_2 + R_1}{R_1} \\ \beta = \frac{1}{3 + sRC + \frac{1}{sRC}} \end{array} \right.$$

12/7/20

Example 4: the Wien-Bridge Oscillator

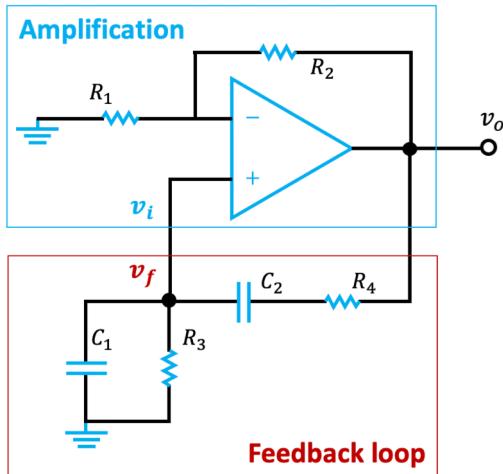QUESTION: Find the functionality of the following circuit with $R_3 = R_4 = R$, $C_1 = C_2 = C$.



- $A\beta = 1$ when $\frac{R_2}{R_1} = 2$

Positive feedback is observed

- Oscillation is triggered when $\frac{R_2}{R_1} > 2$


- The gain with feedback can be calculated as

$$A_f = \frac{A}{1 - A\beta} = \frac{A}{1 - \frac{1}{3}A} \quad @\omega = \omega_0$$

$$\left. \begin{aligned} A &= \frac{v_o}{v_i} = \frac{R_2 + R_1}{R_1} \\ \beta &= \frac{1}{3 + sRC + \frac{1}{sRC}} \\ H(s) &= A\beta \text{ is real } @ \omega_0 = \frac{1}{RC} \end{aligned} \right\}$$

Example 5: the Phase-Shift Oscillator

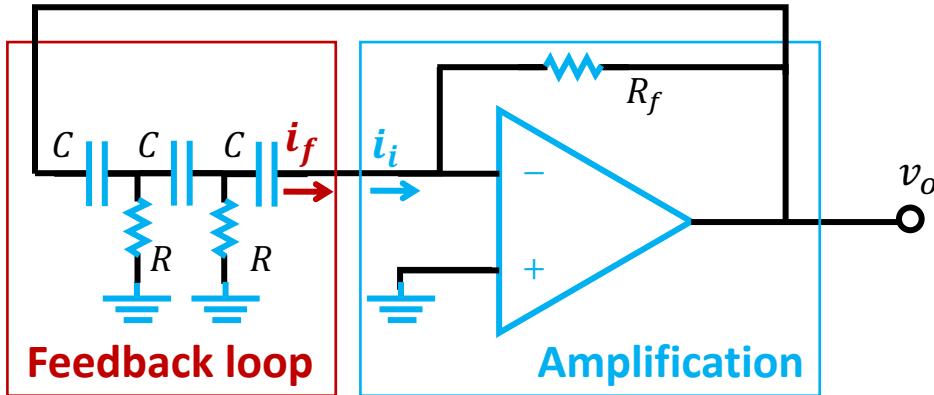QUESTION: Find the functionality of the following




- For the amplification system, the gain

$$A = \frac{v_o}{i_i} = -R_f$$

- For the feedback loop

$$\beta = \frac{i_f}{v_o}$$

Recall: T parameters

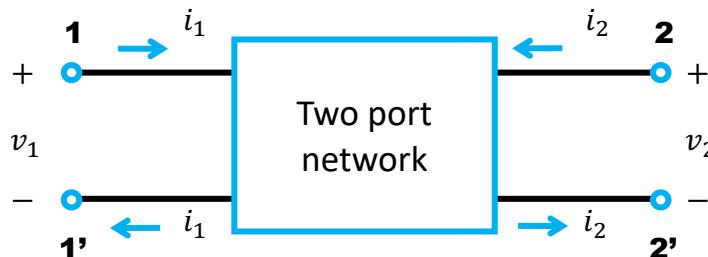

- v_1, i_1 are dependent
- v_2, i_2 are independent

→ **T parameters**

$$\begin{cases} v_1 = Av_2 - Bi_2 \\ i_1 = Cv_2 - Di_2 \end{cases}$$

or

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

$$A = \frac{v_1}{v_2} \quad \text{when } i_2 = 0$$

$$B = -\frac{v_1}{i_2} \quad \text{when } v_2 = 0$$


$$C = \frac{i_1}{v_2} \quad \text{when } i_2 = 0$$

$$D = -\frac{i_1}{i_2} \quad \text{when } v_2 = 0$$


T Parameters are also called as ABCD parameters

Recall: T parameters

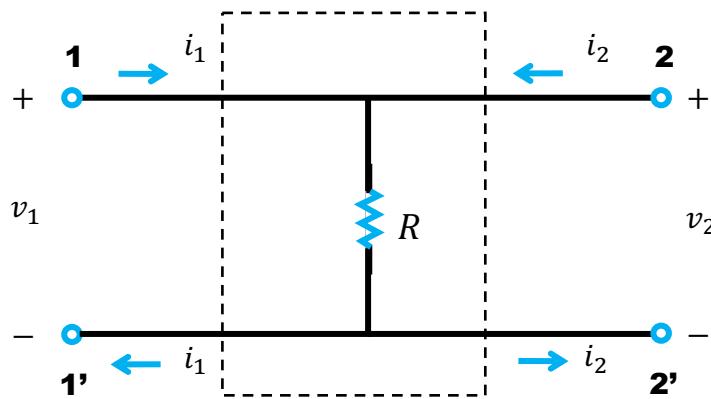QUESTION: find the T parameters of the circuit below



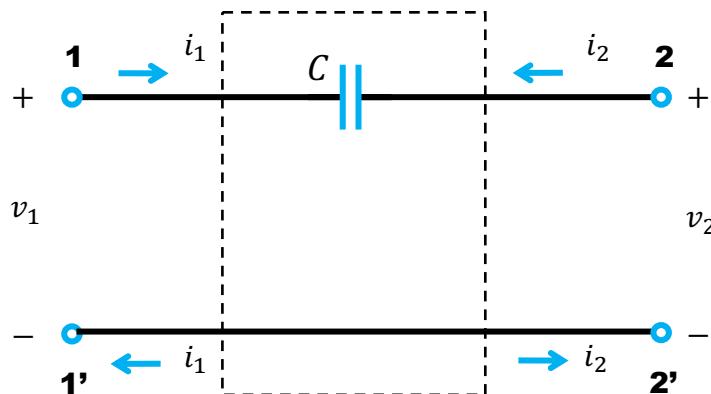
$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$



$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_2 \\ -i_2 \end{bmatrix}$$

Example 5: the Phase-Shift Oscillator

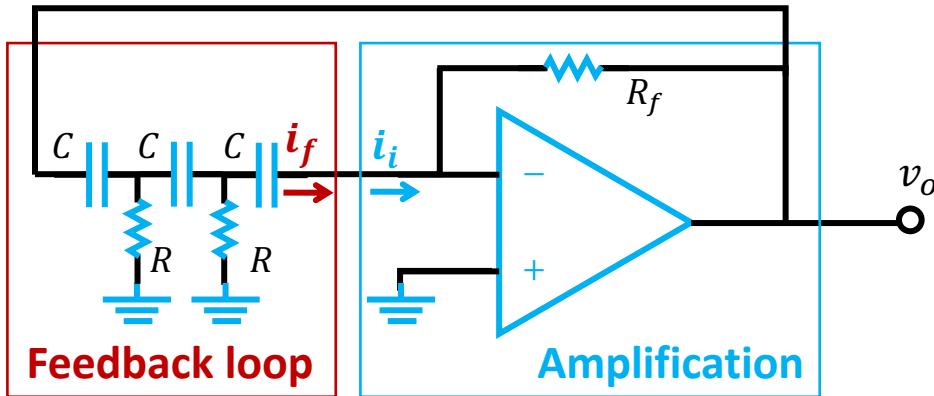QUESTION: Find the functionality of the following



- For the amplification system, the gain

$$A = \frac{v_o}{i_i} = -R_f$$


- For the feedback loop $\beta = \frac{i_f}{v_o}$

$$\begin{bmatrix} v_o \\ i_o \end{bmatrix} = \begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{R} & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{sC} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_f \\ i_f \end{bmatrix}$$

$$= \begin{bmatrix} * & \left[\left(\frac{1}{sRC} \right)^2 + \frac{4}{sRC} + 3 \right] \frac{1}{sC} \\ * & * \end{bmatrix} \begin{bmatrix} v_f \\ i_f \end{bmatrix} \quad \Rightarrow \quad \beta = \frac{i_f}{v_o} = \frac{sC}{\left(\frac{1}{sRC} \right)^2 + \frac{4}{sRC} + 3}$$

Example 5: the Phase-Shift Oscillator

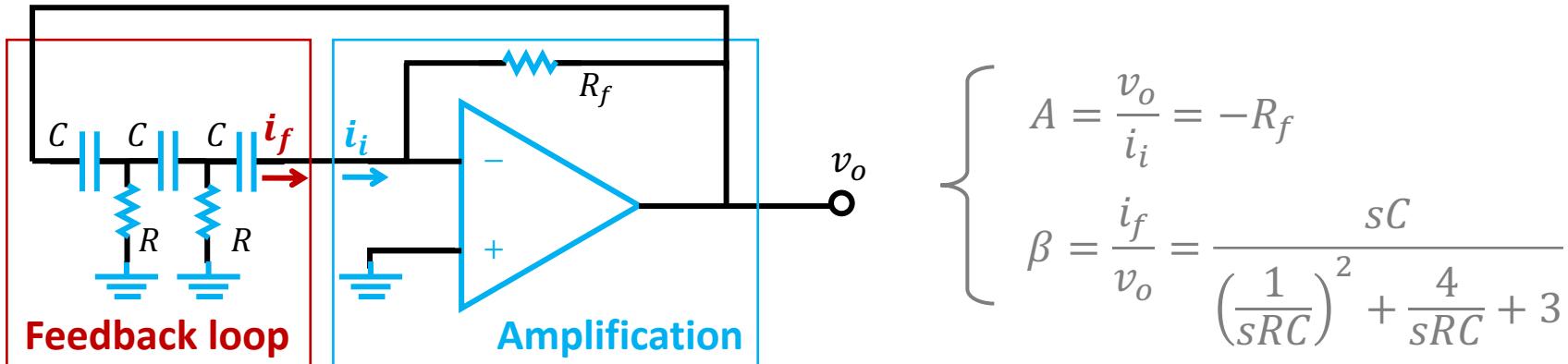QUESTION: Find the functionality of the following




- The transfer function $H(s) = A\beta = -\frac{sR_f C}{\left(\frac{1}{sRC}\right)^2 + \frac{4}{sRC} + 3} = |H(j\omega)|e^{j\varphi(\omega)}$

where $\left\{ \begin{array}{l} |H(j\omega)| = \frac{R_f (\omega RC)^3}{R \sqrt{1 + 10(\omega RC)^2 + 9(\omega RC)^4}} \\ \varphi(\omega) = \frac{\pi}{2} - \arctan \frac{4\omega RC}{1 - 3\omega^2 R^2 C^2} \end{array} \right.$

Example 5: the Phase-Shift Oscillator

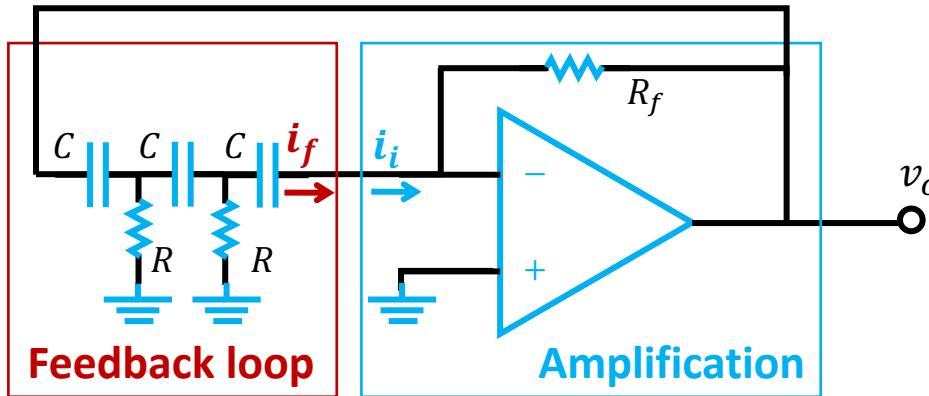QUESTION: Find the functionality of the following



$$\left\{ \begin{array}{l} A = \frac{v_o}{i_i} = -R_f \\ \beta = \frac{i_f}{v_o} = \frac{sC}{\left(\frac{1}{sRC}\right)^2 + \frac{4}{sRC} + 3} \\ H(s) = A|\beta(j\omega)|e^{j\varphi(\omega)} \end{array} \right.$$

- Positive feedback is observed when

$$\left\{ \begin{array}{l} H(s) \text{ is a real number} \\ H(s) > 1 \end{array} \right.$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{3RC}}$$

The oscillation frequency ω_0 is “determined” by the feedback loop

- Oscillation is triggered when $A\beta(j\omega_0) > 1$


$$\Rightarrow \frac{R_f}{12R} > 1$$

Outline

- HOW to generate an oscillation?
 - Negative resistance
 - Devices with negative resistance
 - Circuit features negative resistance
- Linear Oscillator
 - LC Oscillator
 - Crystal Oscillator
 - Op-Amp-RC Oscillator
- Non-linear Oscillator
 - Bistable Circuit

Example 6: Schmitt Trigger

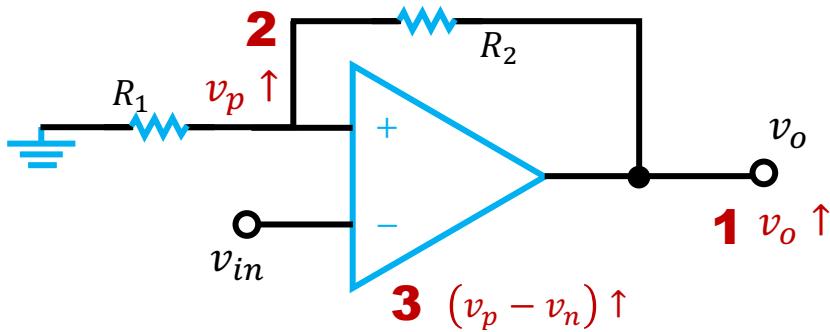QUESTION: Find the functionality of the following circuit.



THIS IS A POSITIVE FEEDBACK


The op-amp biased @ saturation region

- If there is an increase @ v_o
- The noninverting input v_p increases correspondingly
- If the op-amp is biased in the linear region, $v_o = A(v_p - v_n)$ increases



Example 6: Schmitt Trigger

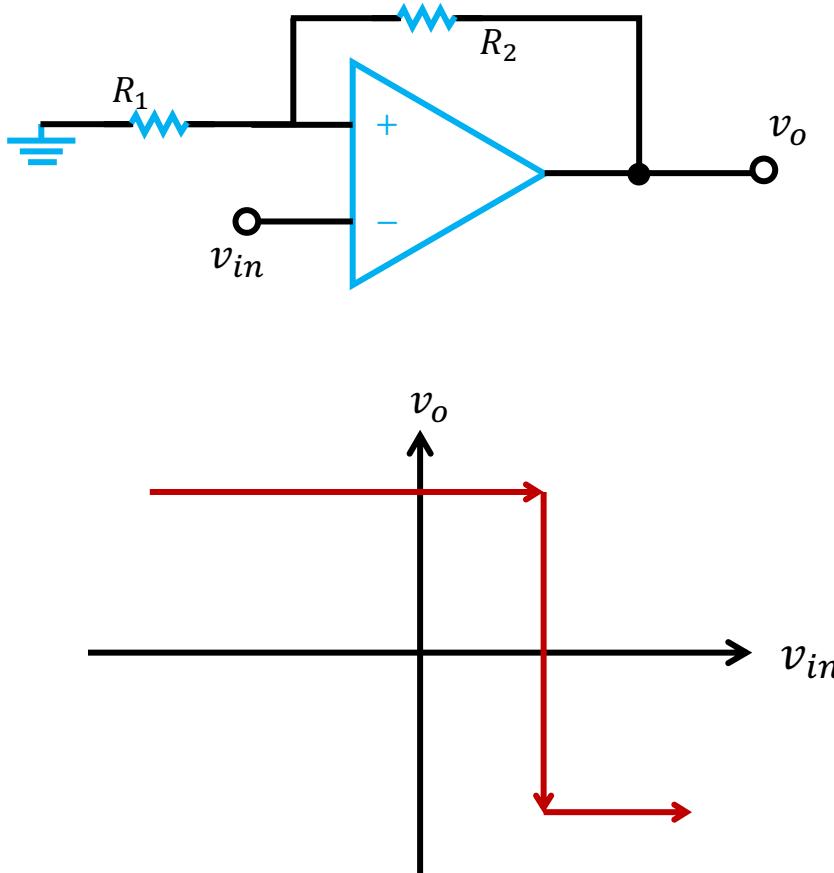QUESTION: Find the functionality of the following circuit.



- If v_{in} is very small
- The op-amp is biased in positive saturation region, $v_o = V_{sat}$
- According to KVL


$$v_+ = \frac{R_1}{R_1 + R_2} V_{sat}$$

- When $v_{in} > v_+$, the op-amp flips into the negative saturation region, $v_o = -V_{sat}$
- According to KVL

$$v_+ = -\frac{R_1}{R_1 + R_2} V_{sat}$$

Example 6: Schmitt Trigger

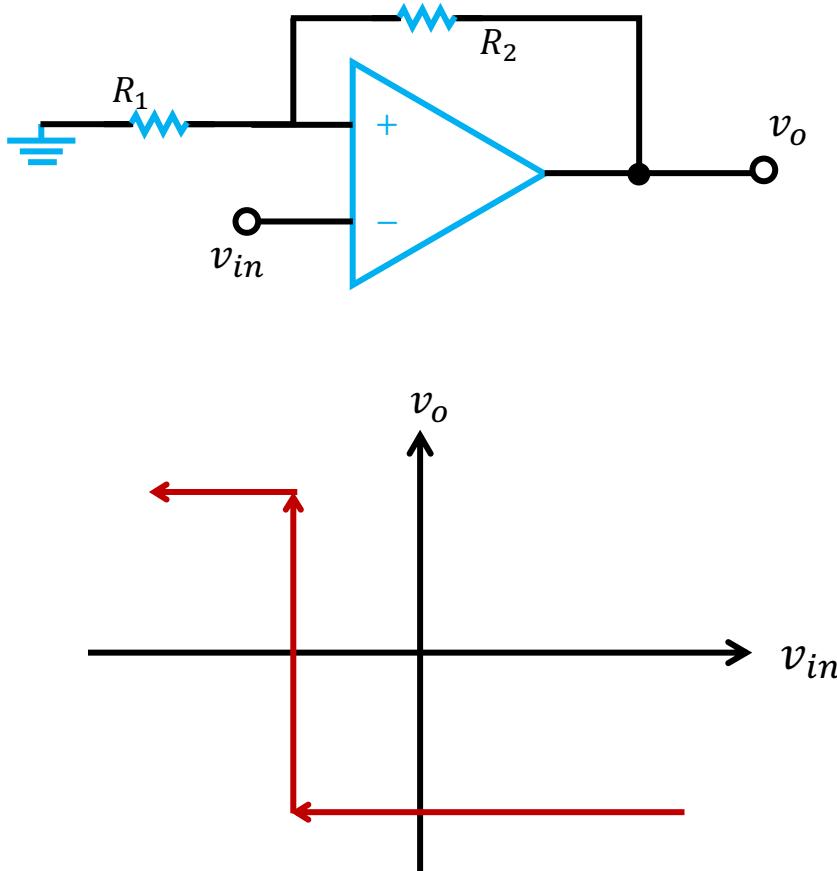QUESTION: Find the functionality of the following circuit.



- If v_{in} is very large
- The op-amp is biased in negative saturation region, $v_o = -V_{sat}$
- According to KVL


$$v_+ = -\frac{R_1}{R_1 + R_2} V_{sat}$$

- When $v_{in} < v_+$, the op-amp flips into the positive saturation region, $v_o = V_{sat}$
- According to KVL

$$v_+ = \frac{R_1}{R_1 + R_2} V_{sat}$$



Example 6: Schmitt Trigger

QUESTION: Find the functionality of the following circuit.

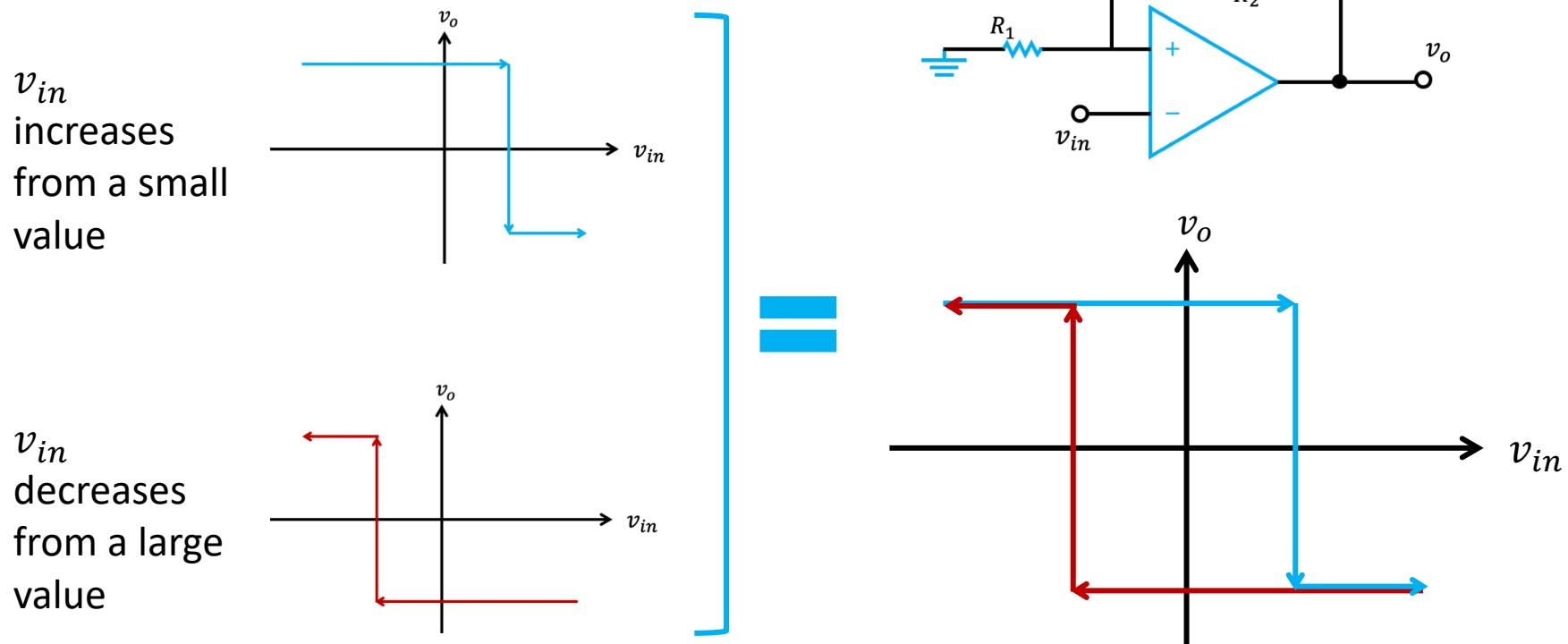


Example 6: Schmitt Trigger

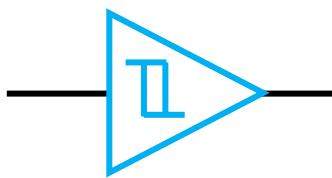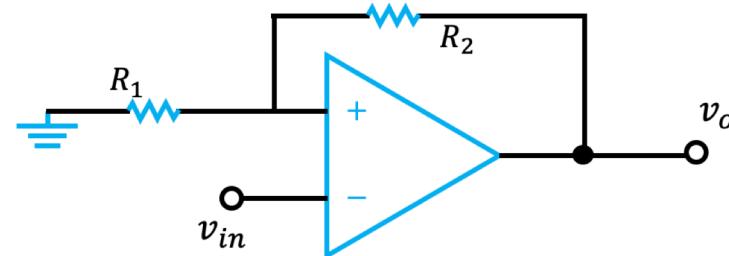QUESTION: Find the functionality of the following circuit.





Schmitt Trigger

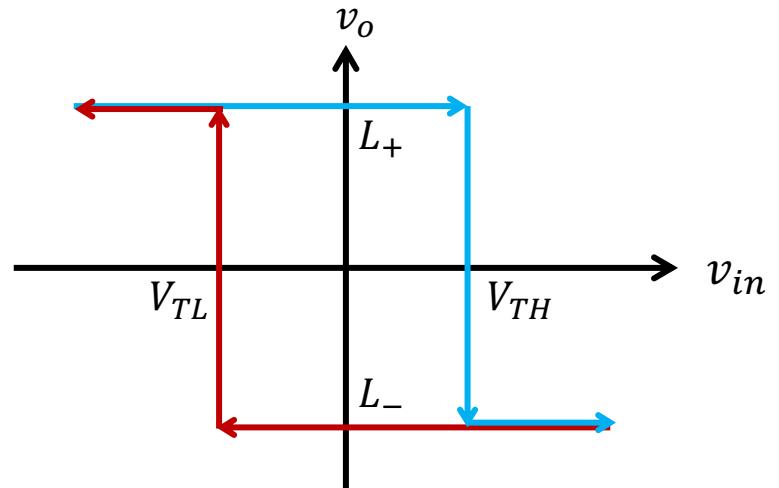

- Two possible levels: L_+ , L_-
- Two thresholds: V_{TH} , V_{TL}

Recall: zero-crossing detector

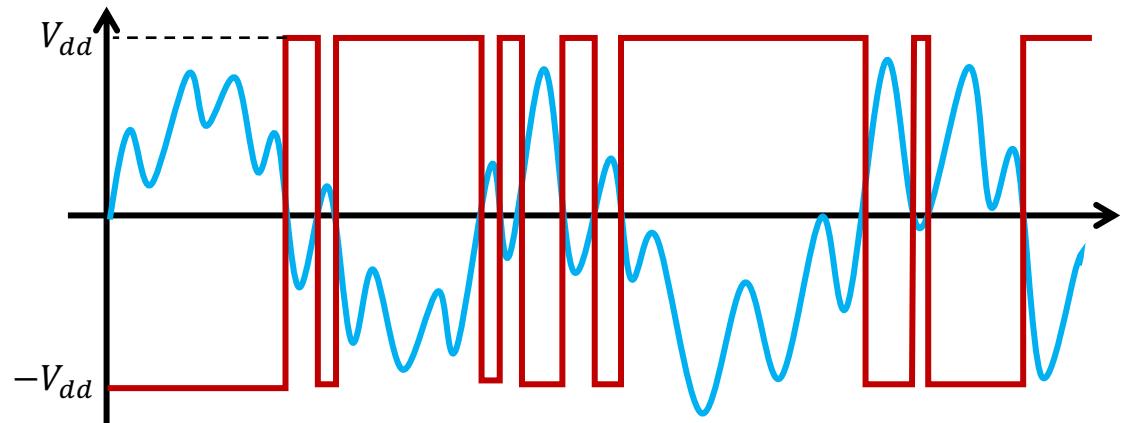
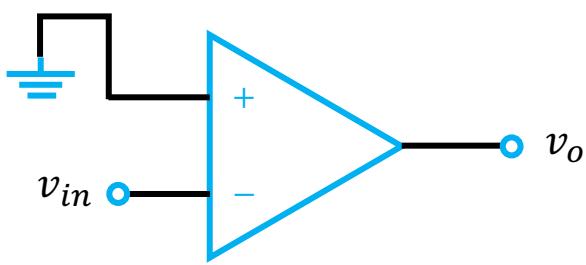
QUESTION: Find the output of the circuit. The op-amp is ideal.



- If $v_{in} > 0 \rightarrow v_o = -V_{dd}$
- If $v_{in} < 0 \rightarrow v_o = V_{dd}$

Example 6: Schmitt Trigger

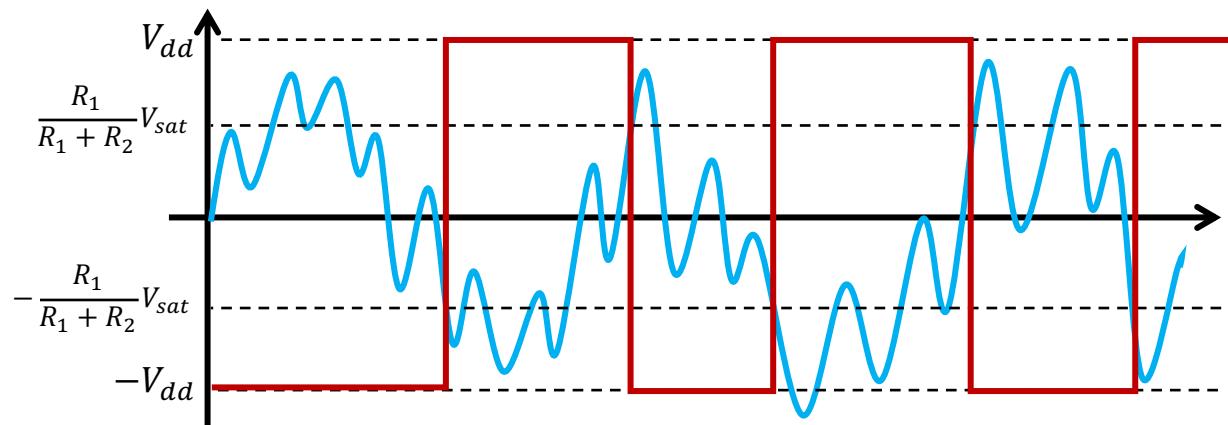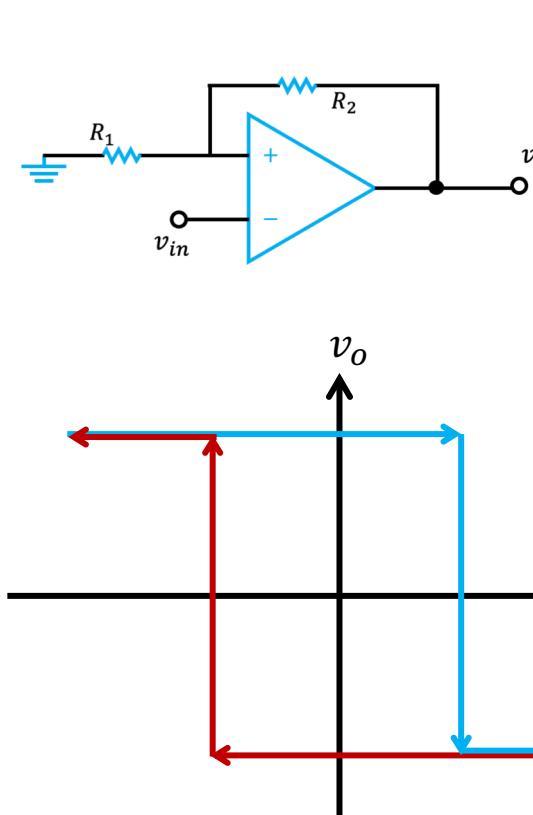QUESTION: Find the output of the circuit. The op-amp is ideal.



A better tolerance to noise

Outline

- HOW to generate an oscillation?



- Negative resistance
 - Devices with negative resistance
 - Circuit features negative resistance

- Linear Oscillator

- LC Oscillator
 - Crystal Oscillator
 - Op-Amp-RC Oscillator


- Non-linear Oscillator

- Bistable Circuit
 - **Astable Multibitators**

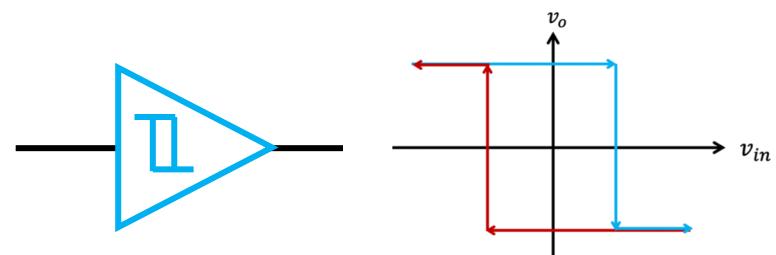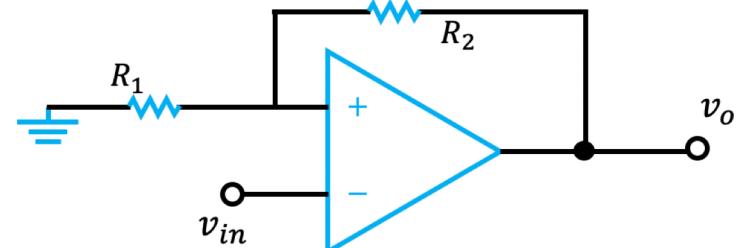

Example 7

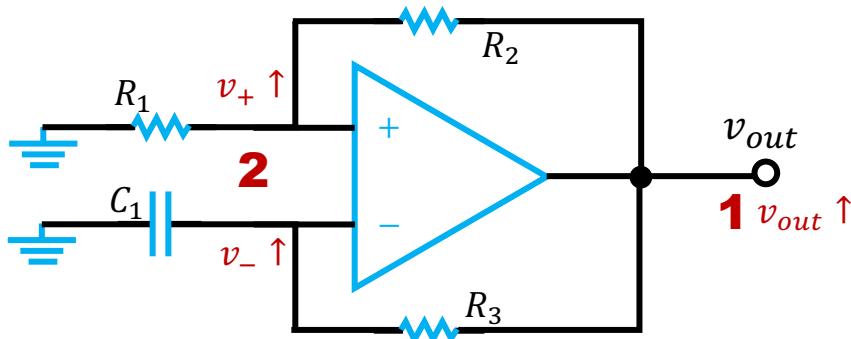QUESTION: Find the functionality of the following circuit.





What are R_2 and R_3 used for?

- If there is an increase @ v_{out}
- The input voltages v_+ and v_- increase


- If $\Delta v_+ > \Delta v_-$
 - $v_{out} \uparrow$ causing an increasing of v_{out}
POSITIVE FEEDBACK is observed
- If $\Delta v_+ < \Delta v_-$
 - $v_{out} \uparrow$ causing an decreasing of v_{out}
NEGATIVE FEEDBACK is observed

Recall: Schmitt Trigger

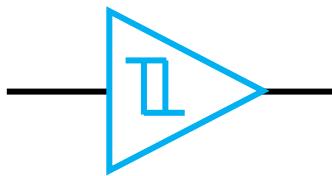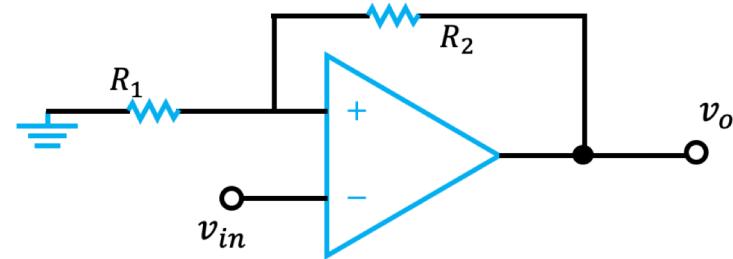QUESTION: Find the functionality of the following circuit.




Schmitt Trigger

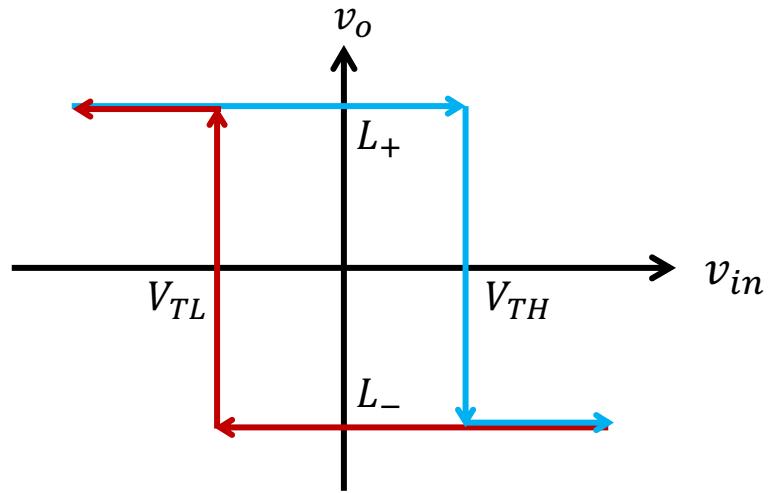

- Two possible levels: L_+ , L_-
- Two thresholds: V_{TH} , V_{TL}

Example 7

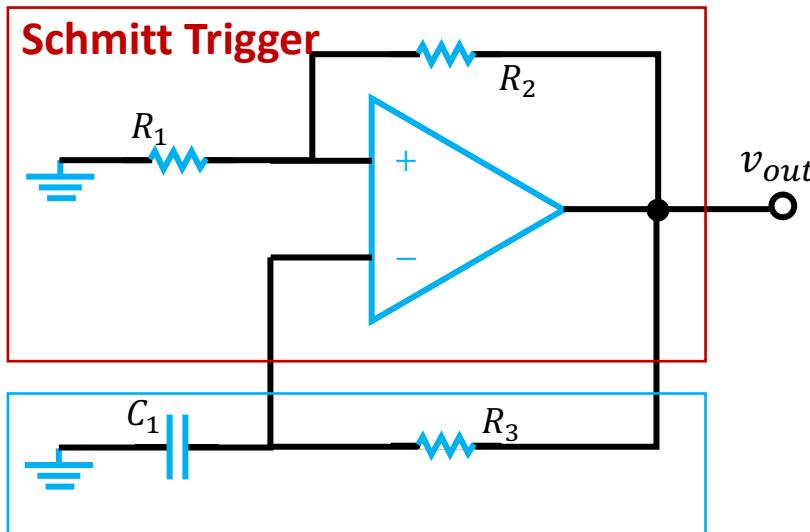
QUESTION: Find the functionality of the following circuit.



- Assume v_{out} flipped to L_+ due to unexpected disturb
- According to KVL


$$v_+ = \frac{R_1}{R_1 + R_2} L_+ = \beta L_+$$

- C_1 is charged to V_{TH}

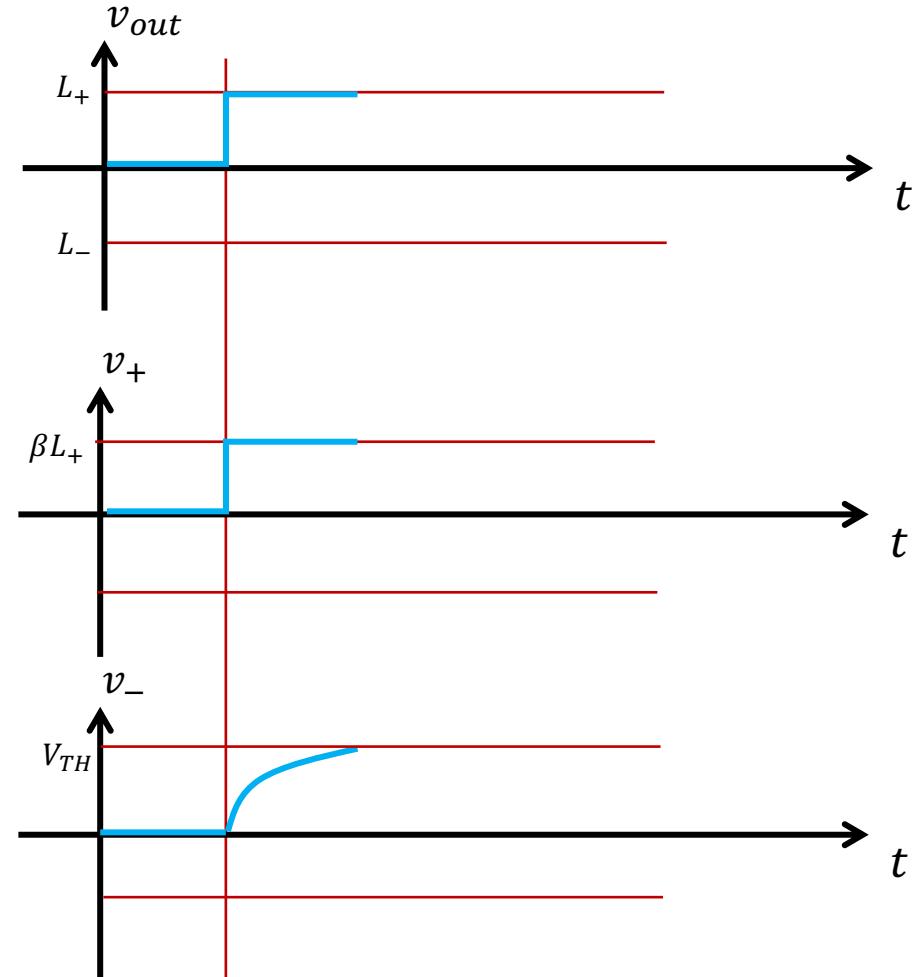

Example 7

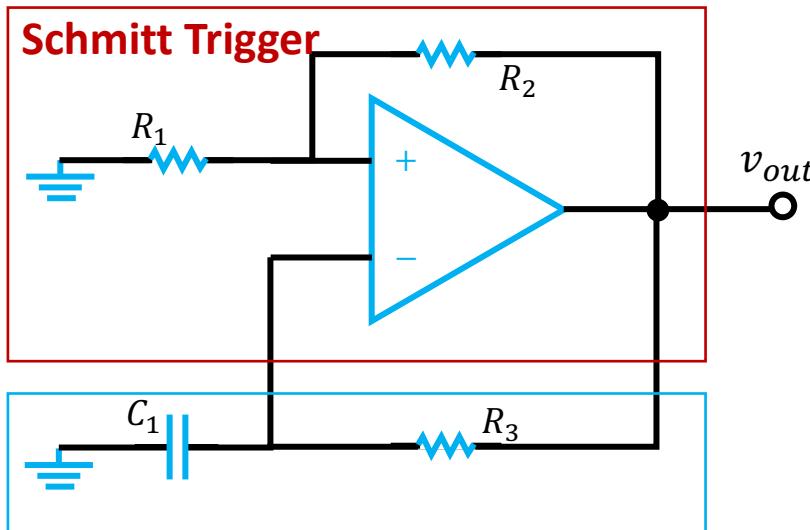
QUESTION: Find the functionality of the following circuit.



- v_{out} flipped to L_- due to the increasing of the v_-
- According to KVL


$$v_+ = \frac{R_1}{R_1 + R_2} L_- = \beta L_-$$

- C_1 is discharged to V_{TL}

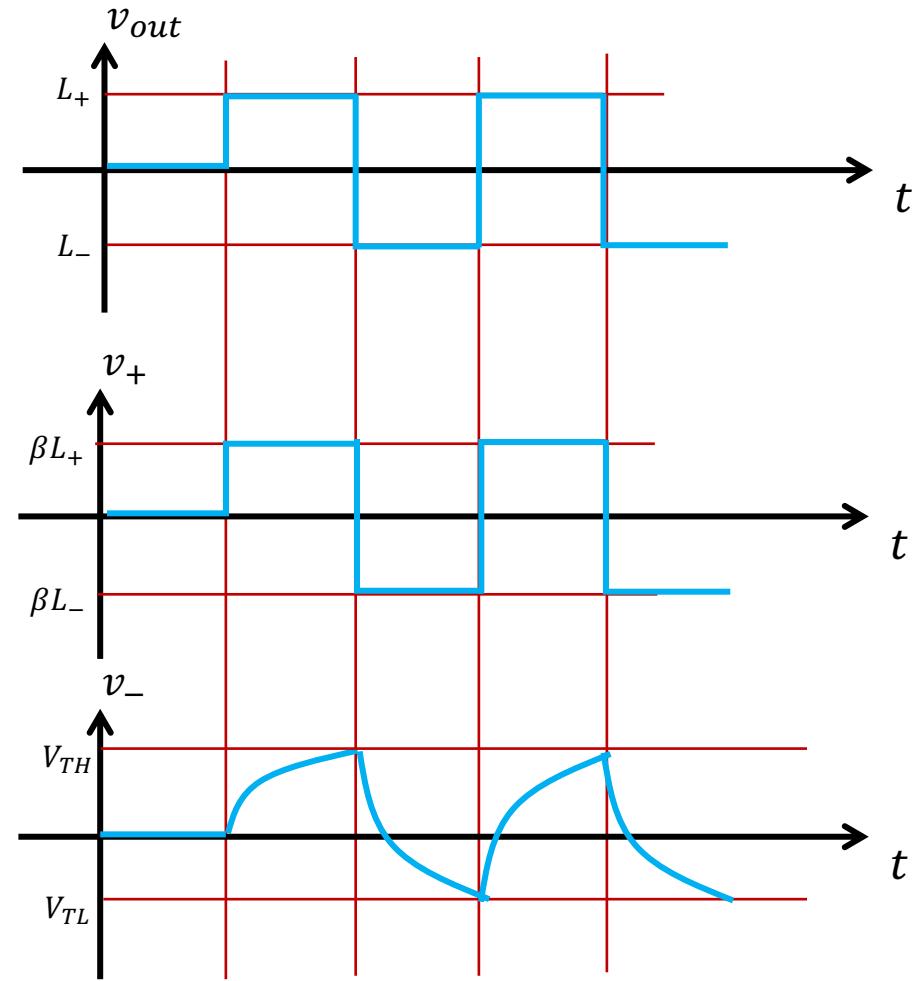


Example 7

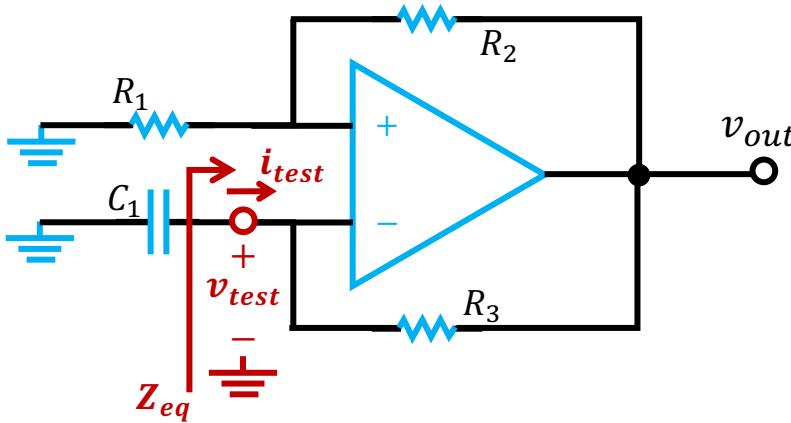QUESTION: Find the functionality of the following circuit.



Recall: Op-Amp characteristics

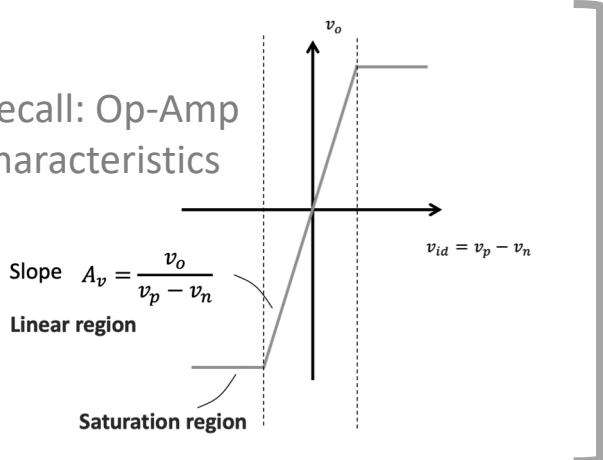

- If the op-amp is biased in **linear region**

Approximately $v_+ = v_-$

- According to KVL


$$v_+ = v_- = \frac{R_1}{R_1 + R_2} v_{out}$$

$$i_{test} = \frac{v_{test} - v_{out}}{R_3}$$


$$Z_{eq} = \frac{v_{test}}{i_{test}} = \frac{v_-}{i_{test}} = -\frac{R_1}{R_2} R_3$$

Example 7

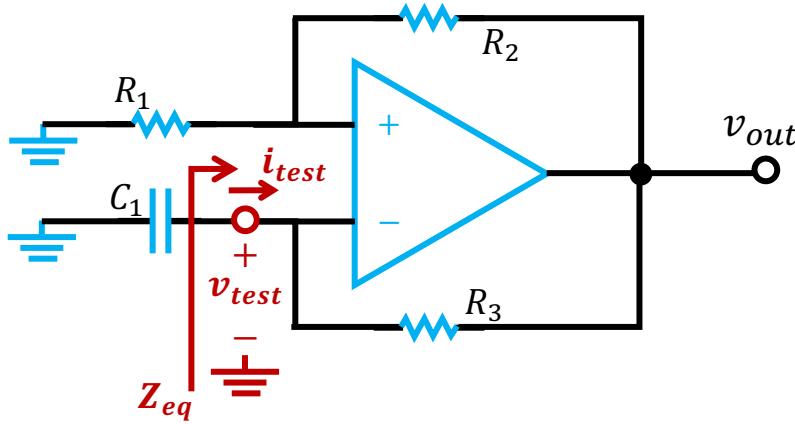QUESTION: Find the functionality of the following circuit.



Recall: Op-Amp characteristics

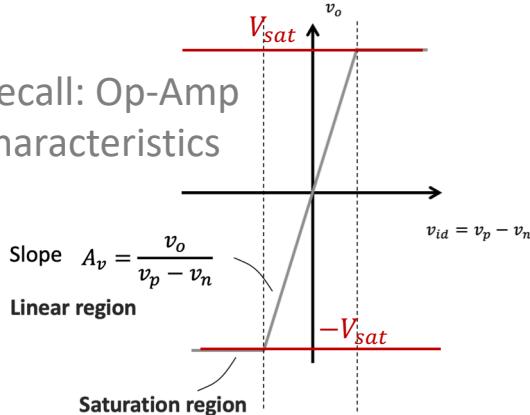

- If the op-amp is biased in **saturation region**
- If $v_{out} = -V_{sat}$ ($v_+ \ll v_-$)
- According to KVL

$$i_{test} = \frac{v_{test} - v_{out}}{R_3} = \frac{v_{test} + V_{sat}}{R_3}$$



$$Z_{eq} = \frac{v_{test}}{i_{test}} = R_3 \frac{1}{1 + \frac{V_{sat}}{v_{test}}}$$

- To keep $v_{out} = -V_{sat}$

$$v_- > v_+ = -\frac{R_1}{R_1 + R_2} V_{sat}$$

Example 7

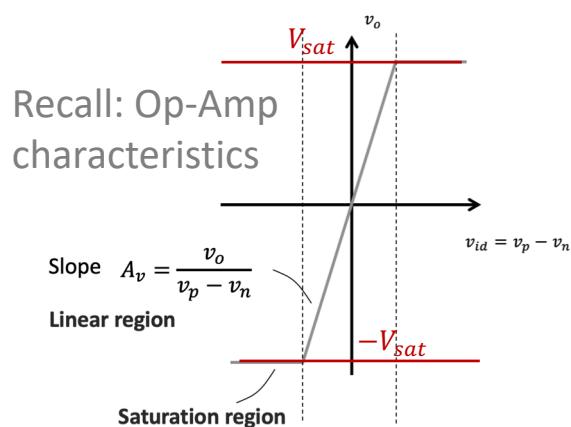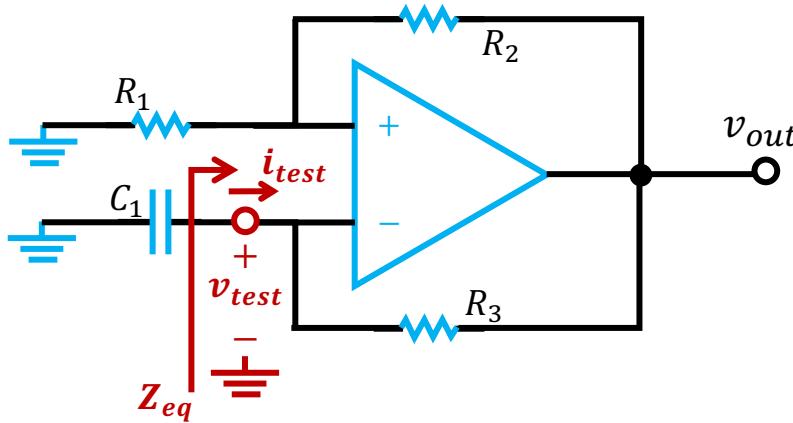QUESTION: Find the functionality of the following circuit.



- If the op-amp is biased in **saturation region**
- If $v_{out} = V_{sat}$
- According to KVL

$$i_{test} = \frac{v_{test} - v_{out}}{R_3} = \frac{v_{test} - V_{sat}}{R_3} < 0$$


$$Z_{eq} = \frac{v_{test}}{i_{test}} = R_3 \frac{1}{1 - \frac{V_{sat}}{v_{test}}}$$

- To keep $v_{out} = V_{sat}$

$$v_- < v_+ = \frac{R_1}{R_1 + R_2} V_{sat}$$

Example 7

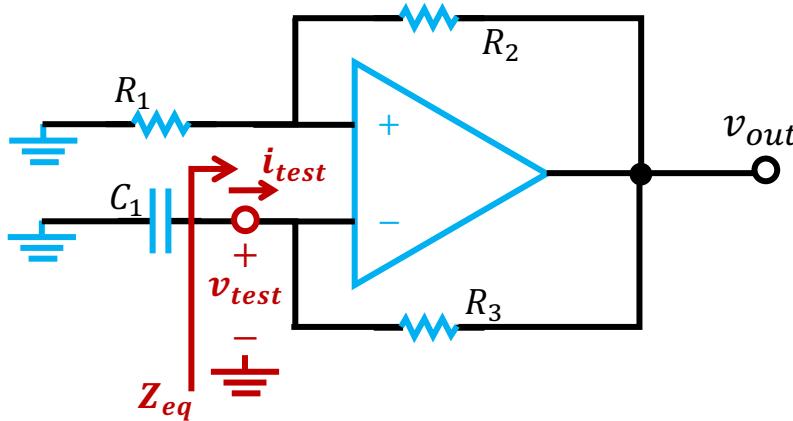QUESTION: Find the functionality of the following circuit.




Recall: Op-Amp characteristics

$$\text{Slope } A_v = \frac{v_o}{v_p - v_n}$$

Linear region

Saturation region

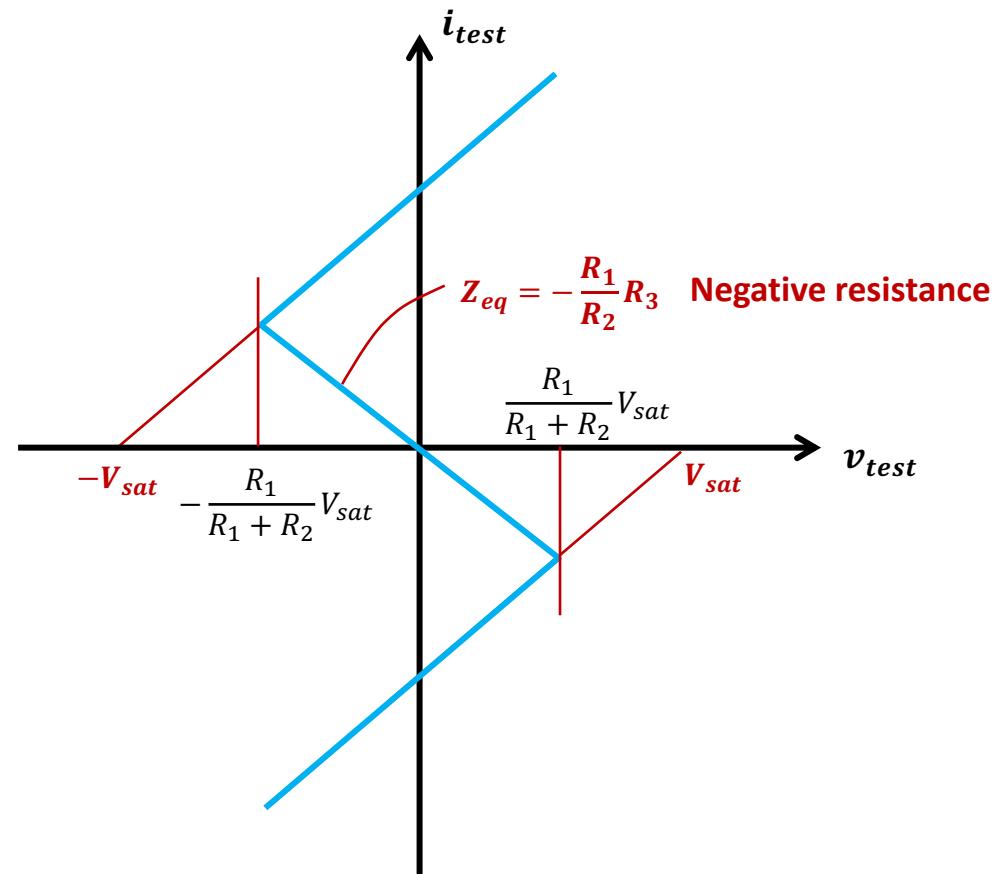

Outline

- HOW to generate an oscillation?
 - Negative resistance
 - Devices with negative resistance
 - Circuit features negative resistance
- Linear Oscillator
 - LC Oscillator
 - Crystal Oscillator
 - Op-Amp-RC Oscillator
- Non-linear Oscillator
 - Bistable Circuit
 - Astable Multibitators

Reading tasks & learning goals

- Reading tasks
 - Microelectronic Circuits, 6th edition
 - Chapter 17.1 – 17.6
- Learning goals
 - Well understand the concept of **negative resistance**
 - Well understand how to calculate the specification of a **linear oscillation circuit**
 - Well understand how to analyze a circuit consisting of **op-amp with positive feedback**
 - Well understand how to calculate the specification of a **non-linear oscillation circuit**